

Australia's Top Selling Electronics Magazine

Electronics Australia

JANUARY
1985
AUST \$2.30
NZ \$3.30

30V/1A power supply

**Multi-sector
home
burglar
alarm**

**Win a
PCB kit!**



**High-performance
stereo amplifier**

Add-ons for the VIC-20

**Solar cells:
pollution-
free power**

**Review:
National's
hifi VCR**

**32 PAGE BONUS: HOLIDAY
PROJECT BOOK**

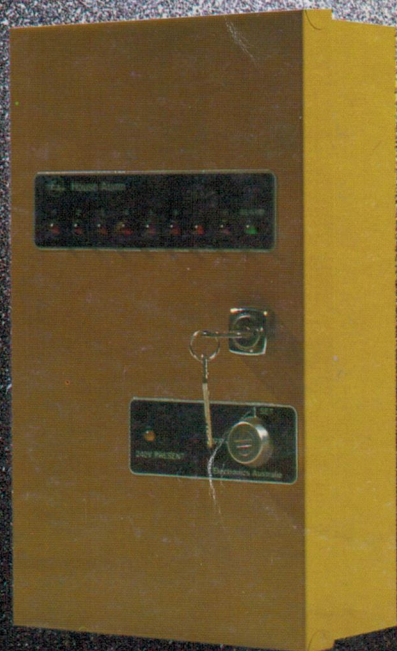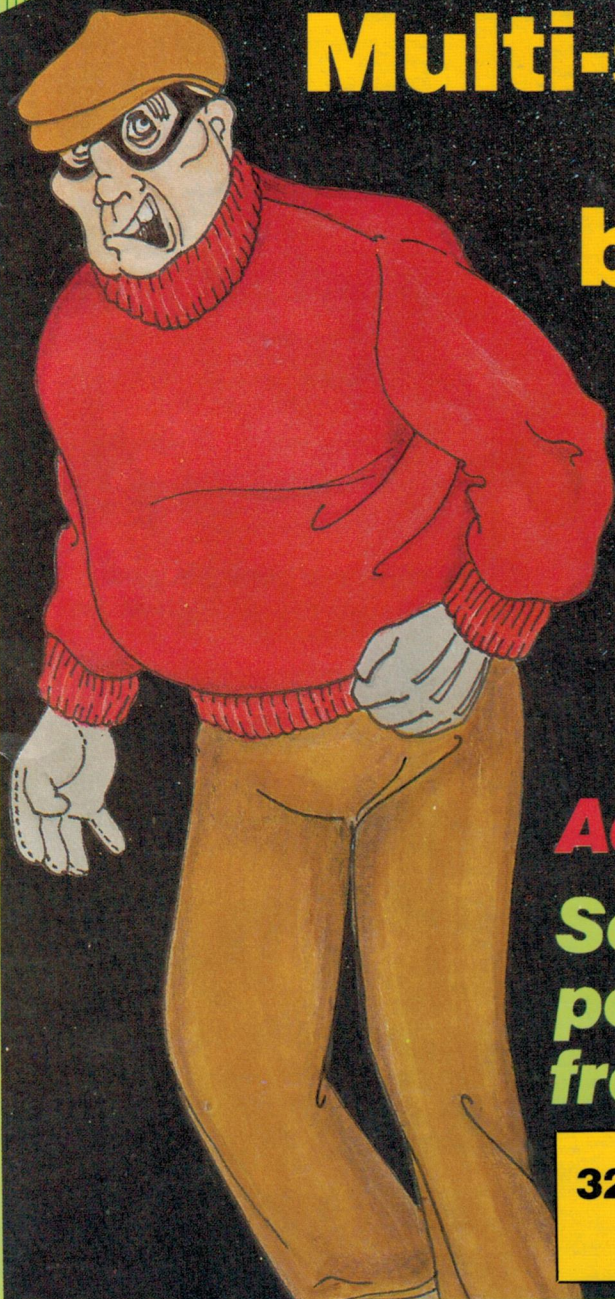

**PRICE
BREAKTHROUGH!**

Beeple: the \$99 pocket pager

At last there's a pocket radio pager that YOU can afford.

The Beeple. A small, lightweight and reliable unit that costs a tiny fraction of previous models. It's a price breakthrough!

What's a Beeple?

It's an instantly accessible automatic radio paging system activated by a simple telephone call. Just dial up the special number and a 'beep' sounds on the Beeple.

Inside the Beeple is an incredibly sensitive radio receiver capable of picking up signals in really bad locations, plus the decoding & logic circuitry necessary to analyse which signal is being received.

All Beeples share a common radio frequency, which helps keep the cost way, way down. It's up to the Beeple to decide whether the signal is for it: if so, it sounds the beep.

Clever, isn't it!

Because each Beeple can have up to four different access numbers (and four different beeps) you can have a system where you **know** by the sound of the beep who wants you. It's so simple.

Even more, it has a memory facility – in case you're in the middle of an important meeting and don't want to be disturbed. Not even to tell you you've won the lottery and you don't even need to be at work any more!

Where can you use your Beeple?

Virtually anywhere in the Sydney or Melbourne metropolitan areas – and up to about 100km outside.

That means your Beeple should work from about Newcastle to Wollongong and out to the Mountains from Sydney. Or down to Geelong, out on the bay, down the Peninsular and up as far as

Ballarat from Melbourne.

(Obviously range is limited at the extremes by topography and conditions).

Later on, it is expected that Beeple will be available in all capital cities and possibly some larger country centres too.

But that's in the future. Right now, it's Sydney and Melbourne.

Who needs a Beeple?

You do!

Businesses have recognised their value for years. Key personnel have been accessible at any time. Even staff 'on the road' have been contactable.

So why should John (or Jill) Citizen own a

beeper?

Think of the times you've been away from home and needed to be contacted.

Sometimes trivial, sometimes important – but always impossible to do anything about.

Until now... with the Beeple:

Let's imagine Dad's at the station and wants a lift home: and you've gone next door or down to the shops. With the Beeple, you could go anywhere.

Or you go out to a show and spend the whole time wondering if the babysitter has everything under control. Take the Beeple along and you know you can be contacted if something really is wrong!

Or the kids arrive home from school and you're still out. They don't know what's happened to you. With the Beeple they can find out where you are.

Or an elderly relative or neighbour is ill: and you can't go out just in case they need help. With the Beeple, you're no more than a phone call away.

Or little Johnny goes out to visit his mates a few streets away. You start to worry when he hasn't come home and ring everyone you can think of. If he had a Beeple in his pocket one call would tell him to come home!

And there are thousands of other uses!

As you can see, it's not just Dad who needs one. Mums and Housewives find them indispensable. The kids can use the Beeple.

Everyone can use the Beeple. That's why it's called the Beeple: The Beeper for People!

Where does it come from?

Beeple is manufactured by the world-famous electronics giant STC, and is serviced by Voicecall, the largest private radio common carrier in Australia.

Because of Dick Smith Electronics wide distribution network, Voicecall suggested that we should include the Beeple in our product range. And seeing the incredible potential of this product breakthrough, we readily agreed!



How much does a Beeple cost?

Unlike most previous models of pocket radio pager, you buy the Beeple outright for the amazingly low price of just \$99.

Compare this with many of the 'leased' systems still around now which cost \$40, \$50

and more **per month!** The Beeple is incredibly inexpensive!

Charges for the Beeple service vary depending on the number of telephone numbers or "tones" you want. The more you get the cheaper each line becomes! Yearly charges are: 1 line \$84, 2 lines \$104, 3 lines \$124 and 4 lines are only \$144.

This includes the telephone line rental charge from Telecom, the use of the network of Voicecall radio transmitters to get your paging message out and a service and maintenance agreement which will look after your Beeple for you!

Even in the first year of operation when you have to take into account the yearly charge PLUS the purchase price, you will still be so far ahead of leased pager rates you'll be laughing.

The following year the savings are even greater!

And remember, if you use the Beeple in any type of business, the charge and the purchase price should be tax deductible!

How do you get a Beeple?

Simple! You go in to your nearest Dick Smith Electronics store in Sydney or Melbourne.

They'll be able to demonstrate the Beeple, show you how to operate it and, best of all, sell you one. Or more!

And they'll also be able (on behalf of Voicecall) to activate your Beeple **on the spot**: you'll walk out of the store with it completely operational! No messy forms to send away and wait weeks for authorisation. It's working from day one!

ONLY \$99

**DICK SMITH
ELECTRONICS**

PTY LTD

Available in our Sydney and Melbourne area stores only (inc. Newcastle, Gosford, Wollongong and Geelong).



Electronics Australia

Volume 47, No. 1
January 1985



On the cover

Our new house burglar alarm features eight separate inputs, individual sector control, battery back up and a self-test facility. Build it and protect your home. Details page 36.

High-power Stereo Amplifier



Here is a stereo amplifier that will equal or better just about any integrated commercial amplifier, regardless of price. It is a no-compromise design capable of delivering 100W per channel at very low distortion. See page 24.

What's coming



Next month, we intend to publish a feature article on the new Philips stereo TV sets (see also page 111).

Benchtop power supply to build



This 30V/1A power supply features variable output voltage from 3 to 30V, variable current limiting over two ranges, overload protection and voltage/current metering. Construction begins on page 60.

Features

- 14 SOLAR ENERGY *Pollution-free power*
- 53 50 AND 25 YEARS AGO *Flight recorders, pedal planes*
- 111 COMING NEXT MONTH *The best amplifier ever published*
- 111 EA CROSSWORD PUZZLE *Test your knowledge*

Hifi, Video and Reviews

- 30 HIFI REVIEW *National NV-850-A hifi stereo VCR*
- 34 AUDIO/VIDEO PRODUCTS *Pioneer car stereo systems*
- 84 AMBISONICS AT THE AES CONVENTION *New life for surround sound?*

Projects and Circuits

- 24 PLAYMASTER SERIES 200 STEREO AMPLIFIER PT.1 *New high-power design*
- 36 MULTI-SECTOR BURGLAR ALARM PT.1 *Protect your home*
- 44 CIRCUIT AND DESIGN IDEAS *Digital capacitance meter*
- 60 30V/1A BENCHTOP POWER SUPPLY *Features variable current limiting*
- 68 FEEDBACK ON THE VHF/UHF TRANSCEIVERS *The common problems*
- 74 OP AMPS EXPLAINED PT.10 *High-power audio amplifiers*

Personal Computers

- 90 ADD-ONS FOR THE VIC-20 *Extra PIA, ROM/EPROM reader*
- 94 PRODUCT REVIEW *Uchida DWX-305 daisywheel printer*
- 100 COMPUTER PRODUCTS *Adam computer, high-speed printer*

Columns

- 18 FORUM *MW radio & super hifi copper!*
- 54 THE SERVICEMAN *Not so elementary, my dear Watson*
- 104 RECORD REVIEWS *Classical, popular and special interest*

Departments

- 3 EDITORIAL
- 6 NEWS HIGHLIGHTS
- 10 LETTERS TO THE EDITOR
- 46 BOOKS AND LITERATURE
- 96 NEW PRODUCTS
- 108 INFORMATION CENTRE
- 109 NOTES AND ERRATA
- 110 MARKETPLACE


BONUS! Holiday Project Book

- STEREO SIMULATOR FOR VCRs *Uses three low-cost ICs*
- SIMPLE TRANSISTOR TESTER *Checks both bipolars & FETs*
- LEDs & LADDERS GAME *Tests your patience & timing*
- WIEN BRIDGE OSCILLATOR *Delivers sine and square waves*
- SIMPLE LED METER *Add it to your amplifier*
- IGNITION KILLER FOR CARS *Simple anti-theft device*

Free in
this
issue!



IT'S BEEN WORTH WAITING FOR.

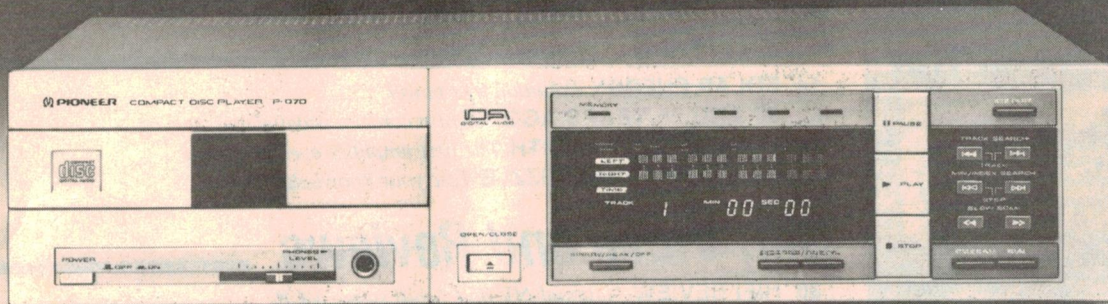

Pioneer's extraordinary second generation Compact Disc Player is here.

Time flies. Only 18 months ago, the hi-fi world was stunned by Pioneer's Compact Audio Disc player. Its laser and digital technologies introduced near-perfect stereo sound reproduction. "How will they top that?", they asked.

With the extraordinary new PD-70, Pioneer's second generation Compact Disc player.

We started by making the compact disc player more compact. The PD-70 loads horizontally (not to mention automatically), making system mounting much more practical.

The PD-70 is also an incredibly stable compact disc player. Comprehensive internal damping and robust construction means the PD-70 won't "skate" during operation.

The PD-70 is more intelligent too. Its memory can be programmed to repeat tracks up to 10 times and that programme can be interrupted or amended at any time.

The PD-70's 16-bit Digital Binary Display is the most sensitive and versatile metering system yet devised.

It breaks signal values down into 6dB increments - and switches to a "peak metering" mode at the touch of a button.

And, because all of the displayed information is both sourced and expressed digitally, the PD-70 can claim to have the most accurate metering display system available.

The PD-70's specifications speak for themselves: Dynamic range has been improved to 95dB. Signal-to-noise ratio has been improved to 95dB. T.H.D. is down to 0.004%, 1kHz.

Compact Disc has taken the next step. Pioneer's new PD-70 gives you music that is virtually distortion free, and laser technology means that your music need never deteriorate.

Pioneer's PD-70 means simply better stereo sound; a step closer to musical perfection.

In our opinion, that's always worth waiting for.

PIONEER
The power to move you.

Electronics Australia

EDITOR

Leo Simpson
B. Bus. (NSWIT)

ASSISTANT EDITOR

Greg Swain, B.Sc. (Hons. Sydney)

EDITORIAL CONSULTANT

Neville Williams
F.I.R.E.E. (Aust.) (VK2XV)

TECHNICAL STAFF

John Clarke, B. E. (Elect. NSWIT)
Franco Ubaldi B. E. (NSW)
Colin Dawson
Robert Flynn
Andrew Levido

PRODUCTION

Danny Hooper

ART DIRECTOR

Toni Henson

SECRETARIAL:

Christine Millar

ADVERTISING MANAGER

Selwyn Sayers

MANAGING EDITOR

Jamieson Rowe

PUBLISHER

Michael Hannan

Editorial and Advertising Office 140 Joynton Avenue (PO Box 227), Waterloo, NSW 2017. Phone: (02) 663 9999. Advertising Sales Manager: Sel Sayers. Representative: John Oliver.

Melbourne: 23rd Floor, 150 Lonsdale Street, Melbourne, Vic 3000. Phone (03) 662 1222. Representative: Mel Godfrey.

Adelaide: Charles F. Brown & Assoc. Phone (08) 332 7711. Representative: Sandy Shaw.

Brisbane: Media Services Pty Ltd, 4 Adelaide Terrace, Brisbane 4000. Phone (07) 229 6033. Representative: Fred Maybury.

Perth: Adrep, 62 Wickham Street, East Perth, WA 6000. Phone (09) 325 6395. Representative: Cliff R. Thomas.



Distribution: Distributed by Gordon and Gotch Limited, Sydney.

Registered by Australia Post — publication No. NBP0240. ISSN 0313-0150

Printed by Magazine Printers Pty Ltd, Regent Street, Chippendale and Masterprint Pty Ltd, Dubbo, NSW for The Federal Publishing Company Pty Ltd.

*Recommended and maximum price only.

Copyright. All rights reserved.

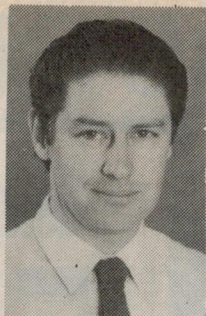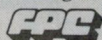

Editorial Viewpoint

The Australian hifi industry awards

Australia is to have its own hifi industry awards. Tentatively called the Grand Prix awards, they will be inaugurated in early 1985. They have been instituted mainly in the hope of promoting sales which have been in the doldrums for many years.

Many countries have their own hifi awards but Australia has been slow to move in this direction. One reason for this may be that there are very few Australian companies involved in this lucrative but very competitive market.

The idea of a hifi award brings to mind the *Car of the Year* award given by *Wheels* magazine but in this case the Hifi Industry Association, a group of Australian hifi importers and distributors, has been the prime mover. No single magazine or publishing company will have monopoly over the awards.

Several journalists who consistently write on the subject of audio will comprise the judging committee and no person involved in any aspect of marketing or selling hifi will be involved.

Eight categories have been defined for the proposed awards, although these may be modified or added to in future years. The categories are for best amplifier, receiver, tuner, cassette deck, compact disc player, loudspeaker system and a miscellaneous category called "Technological development". The judging committee will make their choice from equipment submitted by any company, whether a member of the Hifi Industry Association or not. The inaugural awards will be published in March 1985.

While the idea of hifi awards is a good one and will probably go a long way towards promoting product excellence, some aspects sound a little dubious. For a start, the idea of having the eight fixed categories is too rigid. We can easily envisage the situation where no award might be justified in one or more of those categories. What are the judges supposed to do then? Ideally, they would take the attitude that no award was deserved and act accordingly.

Another point involves the Hifi Industry Association itself. There should be no suggestion that the judges were subject to any influence from any member of the industry.

After all, if Australia is to have hifi awards, they will need to develop a reputation for excellence. We don't want the situation which obtains in some countries where the awards seem to be quite meaningless.

The delights of personal portables

Every time I see someone using a personal portable radio or cassette player, I have reason to bless the Sony Corporation for developing the Walkman in radio and cassette form. This very successful product has been imitated a hundred times over.

The result has been that Sony have performed a useful service for society at large. Sanity has returned to the streets. No longer do we have to endure the strangled sounds of improperly tuned "trannies". Instead, people are able to enjoy the music or program of their choice while not disturbing the people around them. They are a great idea. May they become mandatory for listening to music at beaches and in public places.

On that note, the staff of *Electronics Australia* wish all our readers a happy and prosperous year for 1985.

Leo Simpson

- JANUARY '85 SPECIALS

ELECTRONIC PROTECTION

At last a commercial quality single station door lock interphone system at a bargain price.

The kit of parts includes:



- ★ Outside weather proof intercom with call button and hands free operation.
- ★ An inside wall mount telephone handset with door release push button.
- ★ A heavy duty electric door lock suitable for external entry door or outside gates.
- ★ A power supply - interconnecting cable and instructions.

The electric door lock can be remotely operated from the telephone handset or by the keys supplied.

If purchased individually the component parts would cost well over \$200.

Now you can buy the whole kit with a 7 day money back satisfaction guarantee for only **\$99.00**.


This kit previously sold for **\$179.00**. Zap Electronics have made a huge scoop purchase of these quality units and are pleased to pass on the savings.

F-9700


\$99

BUY NOW AND SAVE \$80

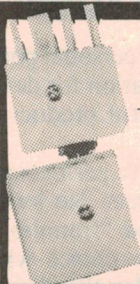Heavy duty flexible 6 conductor telephone cable suitable for many uses. Telephones, intercoms, security, control etc. Extra thick and durable outer insulation. W6010
WAS \$80/100 metres
NOW ½ PRICE \$40/m
But only while stocks last
Also available from stores per metre cut lengths.



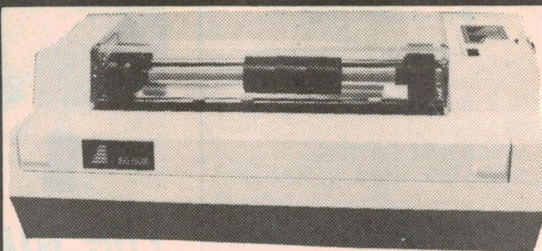TELEPHONE PLUG with grommet
T5006 **\$3.95** ea
10 up \$2.95 ea
TELEPHONE SOCKET
\$4.95 ea
10 up \$3.95 ea
T5008



GP80 PRINTER with Centronics Parallel Data Interface.

Tractor feed dot-matrix printer uses fan fold 204mm paper.

These printers are top quality, new and 100% guaranteed. C9080

AMAZING BARGAIN
SAVE \$ HEAPS \$\$\$\$\$\$

\$199

Centronics Parallel Printer Interface with graphics for the VIC-20 and Commodore 64

computers (GP80 printer compatible). C1708

\$144



3-WAY HEADPHONES

Surround your head in music with these lightweight **stereo 3 way headphones** - 7 day money back satisfaction guarantee. B0650

WAS \$39.95 SAVE \$10
JANUARY SPECIAL

\$29.95

HAITAI SEMI-AUTO BELT DRIVE STEREO TURNTABLE

Features auto return and shut-off, top quality cartridge, static balanced tone arm, 280mm die cast aluminium platter and tinted perspex cover. A2850

WAS \$97.50 SAVE \$10



JANUARY SPECIAL

\$87.50



HOME ALARM ELECTRONIC KIT

All parts supplied in this kit including micro electronics black box, key code entry/exit pad, electronic siren module and four

electro magnetic switches. S1200

SAVE \$20 - WAS \$85
NOW \$65.00

External weather proof siren S1206 **SAVE 40% \$29.50**

ZAP ELECTRONIC STORES

"TECHNOLOGICAL BREAKTHROUGH"

Zap Electronics is pleased to offer the amazing "AD-ZAPPER" to all VCR owners. The Ad Zapper is a device that connects to your VCR and automatically edits the advertisements from your recorded TV programmes (when copyright permits).


Yes, it's a technological breakthrough. The Ad Zapper detects the black space between programme and advertisement, places your VCR into pause and releases the pause on return to normal programme.

Tired of fast forwarding through those ad's in TV programmes? Now the Ad Zapper has the answer. The Ad Zapper automatically edits advertisements.

The Ad Zapper is supplied with a power supply - video cable (connect to video out) control cable with multiple plug (connect to pause or camera remote). Instructions and a video tape to explain the operation of your Ad Zapper.

An optional infra-red switch is also available for VCR's with an infra-red remote control device.

Check Stock Availability

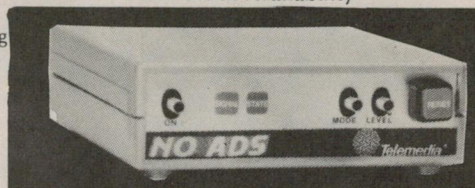

PRICES SLASHED ON TELEPHONE PRODUCTS SAVE \$2 ON WHOLESALE TELEPHONE

EXTENSION LEADS

Quality 6 conductor suitable for PABX Commander and Domestic phones.

T5010 5 metres WAS \$14.95 NOW \$12.95

T5015 10 metres WAS \$17.50 NOW \$15.50

T5020 15 metres WAS \$19.95 NOW \$17.95

TELEPHONE DOUBLE ADAPTORS

Connect two phones in parallel or a telephone answering machine permanently.

T5050 WAS \$12.50 NOW \$10.50 SAVE \$2.00

TELEPHONE EXTENSION REEL

20 metre, two conductor, telephone extension lead in a handy wind-up reel.

T5025 WAS \$24.95 NOW \$15.95 SAVE \$9.00!!



SPECIAL INTRODUCTORY

PRICE \$129

(Specify Beta or VHS instruction tape)

"Infra-Red" remote control unit \$29.00 for VCR's with infra-red remote control.

AD ZAPPER - the unit is manufactured in Australia by Pacific Automation in co-operation with the Australian Government and is unconditionally guaranteed for 90 days from date of purchase.

ZAP - NO FUSS - SECURE - MAIL ORDER SERVICE

Take advantage of ZAP's wholesale mail order service for reliability, security and guaranteed protection. When you use ZAP's mail order service you are protected three ways:- Your order is despatched within one working day. At any time you can ring our service number and check stock, prices or the progress of your order. Any product purchased can be returned within 14 days of purchase date if not absolutely satisfied, and all products sold by ZAP are fully guaranteed and covered by parts and labour warranty.

NO FUSS - SECURE - MAIL ORDER SERVICE - 3 WAYS.



"Zap's policy is to offer useful and interesting electronic products as soon as they become available at Direct Import Prices"

Pat Daly,
Manager of Zap Electronics

ZAP ELECTRONICS 5 SYDNEY STORES

CHATSWOOD 16-18 Anderson Street Ph: 411 7366

HORNSBY Shop M1 Northgate Shopping Centre Ph: 476 6122

LIVERPOOL 270 George Street Ph: 602 0777

BURWOOD 51 Burwood Road Ph: 745 3188

PARRAMATTA 60 George Street Ph: 635 5877

WHOLESALE SHOWROOM AND STORE

EASTWOOD 10A First Avenue Ph: 858 2288

For tax exempt, school, government, wholesale and dealer enquires
CONTACT MARK JORGENSEN - 858 2288

MAIL ORDERS TO: ZAP ELECTRONICS

10A First Avenue, EASTWOOD 2122 - Freight cost per order \$5
Send cheque, or Bankcard, Mastercard, American Express details or money order. - **Phone orders (02) 858 2288**

Enquires contact Julie Macdonald

YOUR ELECTRONICS STORE

ZAP

● CHATSWOOD ● PARRAMATTA ● HORNSBY
● BURWOOD ● LIVERPOOL ● EASTWOOD

News Highlights



ECHO 2000—telephone conversations for deaf

Deaf persons soon will be able to use a telephone anywhere they go — thanks to a new portable electronic device being manufactured and marketed by a South Carolina firm.

The battery-powered device, known as the Echo 2000, is easily attached to a handicapped person's telephone. Equipped with a liquid-crystal screen, it displays written messages tapped out by callers on the keys of their pushbutton phones.

At the deaf person's end of the line, the varying tones generated by the caller's pushbuttons are translated by special decoder circuits into letters that flow across the device's display window in ticker-tape fashion.

To "talk" to a deaf or hearing-impaired person, the caller must depress two

telephone buttons for each letter — the first being the key on which the letter is located, the second being the number key (either 1, 2, or 3) to indicate the position of the letter on the key initially depressed. For example, to transmit the letter A, the user taps the middle key in the top row (which contains the letters A, B, and C), followed by the "1" key to indicate it's the first letter in the series. To transmit the letter B, the user would first hit the same middle key and then the "2" key, and so on.

To transmit a number, a caller simply strikes the desired number key and then the pound (#) key. In addition, there are abbreviated, two-button, codes for some of the most frequently used words. For example, "00" denotes "hello" and "*0" indicates "goodbye."

Top priority topics for CSIRO

The CSIRO has recently formed a list of eight research topics related to manufacturing which will be given the highest priority.

Included on the list are: application of computer technology and micro-electronics to industrial processes, advanced technologies for process and

quality control, development of new materials and instruments for environmental monitoring and exploration. Communications devices — particularly those related to satellite communications — and various agricultural chemicals and pharmaceutical products are also included in the list.

Computer sales up but profits down

Sales of personal computers will grow more than 50% this year in the US, but the big US retailers who sell them are having a hard time making a profit. Price cutting and a near glut of personal computer products have battered stores' profitability.

These developments are already forcing a shakeout among the small retailers, particularly those that don't carry the International Business Machines Corp or Apple Computer Inc lines. But even the big chains that carry those brands are losing money or turning only small profits. Stung by an especially slow summer, these retailers are hoping for huge Christmas sales to bring profits back in line.

For many big retailers, the problems began last spring when IBM was able to ship all of the computers the retailers wanted. But sales began to slow at the same time the inventories began to bulge. Then, in June, IBM cut prices by as much as 23% and several retailers said IBM offered to reimburse them for price differences for only the previous 45 days instead of the customary 60.

As a result, many chains were stuck with loads of expensive equipment that could be sold only at discount prices. IBM declined to comment, saying its transactions with its retailers were confidential.


Apple dealers have had other difficulties. Apple was slow to produce software and peripherals for the Macintosh and Apple IIc computers, initially making the computers tough to sell.

Even after accessories were available, some retailers succumbed to price cutting that drove the Macintosh price down to \$US1,995 from \$US2,495 over the summer.

Even the giant Tandy Corp hasn't been immune from price cutting although, unlike the retail-only chains, it makes its own products.

Tandy, which sells its products through its Radio Shack stores, was forced to cut the price on its best-selling PC, the TRS-8 model 4, to \$US1,295 from \$US1,995.

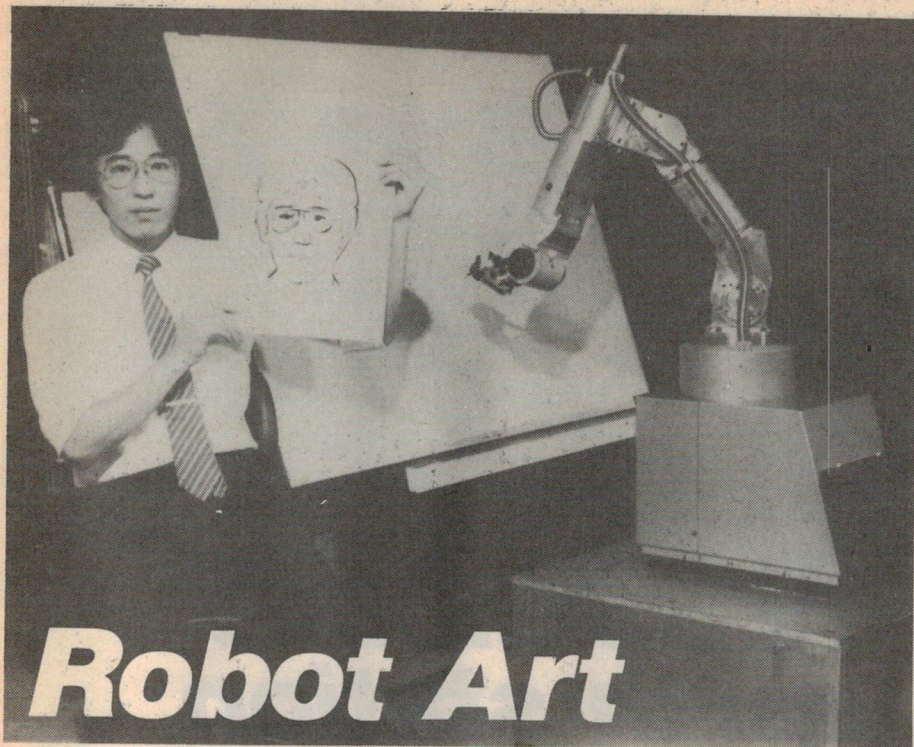The company plans to remain competitive by introducing new products at low prices.



Robot Art

Portraits painted by robots? By combining image processing and industrial robot technologies, Matsushita (National's parent company in Japan) makes it possible. Their robot system can draw a picture of a model's face with a brush in less than three minutes.

Three separate units combine to make the system work: an image processor,

which uses a video camera to obtain an image of the model's face and then processes it into line image information; a robot that holds a brush and draws an image of the model on canvas according to the line image information; and a control unit that controls the entire system.

An image of the model's face is

obtained by means of video camera, and then converted into a still picture.

The image processing unit converts this picture into line drawing information (drawing data) to control the movements of the robot. However, the time that the robot would require to complete a fully detailed drawing is beyond reasonable limits. Therefore, the large amount of information contained in the original image must be greatly simplified.

The image processing unit reads the degrees of variation between highlighted and shaded parts of the original picture, forming contours which are connected to form the line drawing. Only those lines, representing distinct features are used as basic line drawing information. Important parts such as eyes and brows are specially processed and retained as drawing data. This complicated information is processed by a high-speed arithmetic circuit in less than 10 seconds (regardless of the model's appearance!).

Guided by the drawing data, a vertical, 6-axis, articulated robot arm produces an A3 portrait, using a brush. Actual drawing time is less than 2 minutes.

These new developments are not merely art for art's sake! The high-speed image processing technology developed for this system will make it possible to advance a robot eye function that can recognise an object's shape, position and direction for use in assembly and inspection operations.

\$32M telescope for Australia

A \$32M radio telescope project which will eventually link major telescopes across Australia was recently inaugurated by the Minister for Science and Technology, Mr Barry Jones.

The telescope, to be known as the Australia Telescope, will be built at Culgoora in northern NSW. It will comprise a 6km array of six fully steerable and movable 22m antennae at Culgoora, a new fixed antenna at Siding Spring (also in northern NSW) and will incorporate the already established 64m radiotelescope at Parkes, central NSW.

By linking these antennae electronically, they can be operated as one to simulate a giant telescope 300km in diameter.


Researchers from the Division of Radiophysics at the Commonwealth Scientific and Industrial Research Organisation (CSIRO) are also looking at the possibility of linking the Australia Telescope with other radio telescopes across Australia, making it one giant

radio telescope 3500km in diameter. Such an array would be able to resolve detail down to one-thousandth of a second of arc. This is equivalent to a person in Sydney being able to see a 10-cent coin (about 24mm in diameter) in Melbourne, 720km distant.

The Australia Telescope, mooted in 1975, will give Australia the most versatile telescope in the world, with a capability of making major discoveries in the field of quasars, black holes and interstellar chemistry well into the 21st century.

To observe astronomical phenomena, the antennae are designed to operate over a wide range of frequencies — from 327MHz to an upper frequency of about 115GHz. As it is not possible to design a single feed horn to operate over such a wide frequency range, a number of horns of different sizes are necessary.

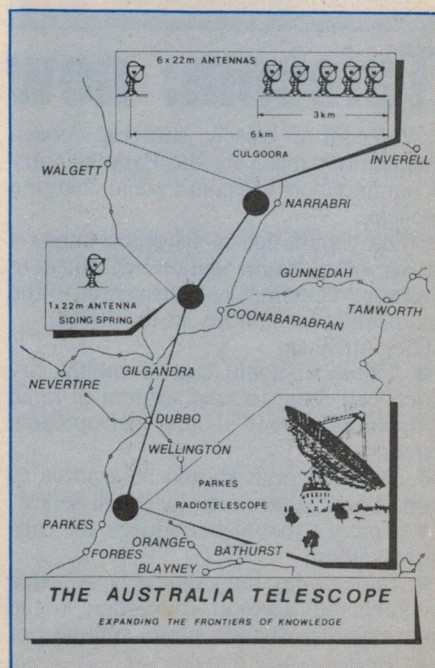The project is due for completion for the celebration of Australia's Bicentenary in 1988.



News Highlights

X-ray testing for military aircraft

A major problem involving aircraft safety, and particularly high performance military aircraft, is the down time required for regular inspections for airframe corrosion, fatigue, and other defects. The process involves removal of major aircraft sections, such as wings, tail assemblies, etc, for inspection, after which they have to be reassembled. Apart from the down time, the cost in man hours is extremely high.

As a counter to this problem the US Air Force is planning to install a giant x-ray and neutron radiography non-destructive inspection system which they hope will reduce both time and cost significantly.

The system will operate from a gantry via a remotely controlled arm, which will carry the x-ray and neutron generators and detectors, and which can be positioned to within 6mm. The neutron source is the isotope Californium-252.

Both systems will operate in conjunction with closed circuit TV systems to allow the operators to view the images. While the x-ray system will produce an instant picture, the neutron system requires time to build up an image. A feature of the neutron system is that it will detect hydrogen, resulting from corrosion, which the x-rays will not. The x-rays will detect cracks or mechanical damage.



TESS-Mobile earth station

With the commissioning of Aussat later in 1985, Australian radio and television networks will have the ability to provide live broadcasts to homes everywhere.

Soon, using a "transportable earth satellite station" (TESS), it will also be possible to bring news, as it happens, from the remotest areas.

Sam Technology, a Sydney firm which specialises in handling hi-tech systems, has gained the agreement of American Uplinks Inc, USA, to design and construct their transportable earth satellite stations in Australia to suit

Australian conditions.

The TESS is self contained within a single non-articulated truck chassis — it is as transportable as the truck.

Transmission quality is said to be undetectable from local broadcasts. An on-board uninterruptible power supply accompanying TESS virtually eliminates breaks in transmission.

Each TESS will carry all its own electronic quality control monitoring systems and test gear, plus repair, replacement and backup equipment. Its five metre antenna dish will disassemble for transport.

Telecom: new zonal charges

Telecom is closely studying recommendations made by the Parliamentary Committee on Telecom's zonal charging policies.

The Committee in its report made a series of recommendations designed to improve Telecom's responsiveness to the Australian community in the 1980s. These include:

- Telecom should extend capital city local call zones to take account of rapid population growth in outer metropolitan areas;
- Reduced rates should be granted to subscribers adjacent to local call zones;
- Charges should be reduced for calls up to 50km;
- Time of day rates should be adjusted to take into account congestion in the network at particular hours and days of the week;

- Telephone directories should be simplified and amalgamated to better reflect communities of interest;
- Charging policies for provincial cities should be reviewed. Local call zones should be extended for provincial cities with high population growth, eg Gosford/Wyong, Sunshine Coast, Gold Coast. Reduced rates should apply for provincial cities linked with adjacent capital cities, eg for calls between Wollongong and Sydney and Geelong and Melbourne.
- The committee does not favour the introduction of timed local calls;
- All costs associated with extending local call zones should be financed from Telecom's internal sources;
- STD charge steps should be reduced to reflect the declining importance of distance in telecommunications.

VHS editing facilities for ABC


The ABC expects to reduce costs and speed production of videotapes following the acquisition of half inch tape editing facilities.

One inch master tape will now be copied onto VHS, along with time and frame coding information. Editing will then be performed on the smaller tape format until a satisfactory article has been produced.

After preparation of the VHS tape the one inch version can quickly be edited by duplicating the VHS frame numbers. This will significantly reduce the amount of time spent on the larger editing machines.

KITS specially picked for the school holidays, from Rod Irving Electronics — the kit specialists!

★★ RECENT RELEASES ★★

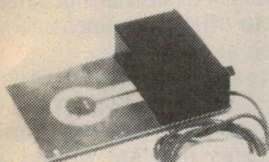

ELECTRONIC MOUSETRAP

This clever electronic mousetrap disposes of mice instantly and mercifully, without fail, and resets itself automatically. They'll never get away with the cheese again! (ETI Aug. '84).

Cat. ETI 1524


\$29.95



SOUND SIMULATOR FOR MODEL TRAINS

Fancy a diesel sound simulator for your model train layout? This circuit mounts inside the train for added realism and even varies its 'speed' according to the throttle setting. (EA Nov. '84).


\$18.00

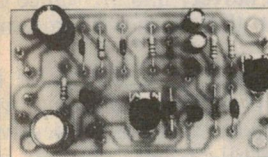

1W AUDIO AMPLIFIER

A low-cost, general-purpose, 1 watt audio amplifier, suitable for increasing your computers audio level, etc. (EA Nov. '84).

\$9.95

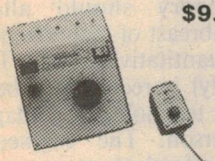

RAILMASTER PULSE POWER TRAIN CONTROLLER

Here's an up-to-the-minute train controller offering all the most desirable features including inertia, full overload protection, walk-around throttle and excellent low-speed running characteristics. Probably the best controller available, regardless of the cost! (EA Sept. '84, 84tc9)

Cat. K84091

\$79.50



COMPUTER DRIVEN RADIO-TELETYPE TRANSCIVER

Here's what you've all been asking for — a full transmit-receive system for a computer-driven radio teletype station. The software provides all the latest "whizz-bangs" like split-screen operation, automatically repeating test message, printer output and more. The hardware uses tried and proven techniques. While designed to team with the popular Microbee, tips are available on inter-facing the unit to other computers. (ETI Nov. '84, ETI-755)

Cat. K47550

\$119.00



DRUM SYNTH. MODULE

A simple, low-cost Module that will generate a wide variety of drum-like sounds from a pulse input provided from a sound pick up or electronically. (ETI Oct. '84).

ETI-610

\$24.95



SOLAR POWERED HOUSE NUMBER

Searching for a house at night in an unfamiliar street can be a frustrating business. This illuminated house-number switches itself on at dusk and switches off six hours later. (EA Sept. '84, 84MBB)

Cat. K84092




EA AM STEREO DECODER

AM stereo is now broadcast in Australia on an experimental basis. This add-on decoder works with the Motorola C-QUAM system. (EA Oct. '84, 84MS10)

Cat. K84101

\$24.95

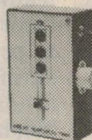

READY-SET-GO LIGHTS

A simple project for starting slot car races, etc. It provides the traditional Red/Amber/Green lights with a random delay between the amber and green. (ETI Oct. '84).

ETI-277

\$24.95




150 W BASS AMP

This guitar amp for impeccable bass players features many facilities found on expensive 'commercial' ones. It delivers 150 watts into 4 ohms, has a t-band graphic, limiter, line out and bi-amp facilities. (ETI Aug. '84, ETI-1410)

Cat. K54100

\$299.00

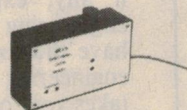

DIRECTIONAL DOOR MINDER

Most electronic door minders function by having a beam of light shining across a doorway interrupted, but are incapable of detecting whether the light beam is broken by a person entering or leaving the room. This project overcomes that problem with the aid of digital logic. (ETI Nov. '84, ETI 278).

Cat. K42780

\$29.95




EFFECTS UNIT

An "effects unit" that can create phasing, flanging, echo, reverb and vibrato effects. (EA June '83).

83GA6

\$65.00

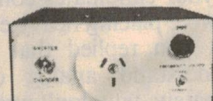


INVERTER

This 12 240V inverter can be used to power mains appliances rated up to 40W, or to vary the speed of a turntable. As a bonus, it will also work backwards as a trickle charger to top up the battery when the power is on.

(EA May '82)

\$49.50

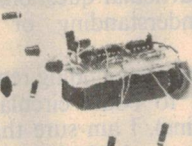

CUDLIPP CRICKET

A fascinating Electronic Cricket with just two ICs. The Cudlipp can be used to bug your home, office etc. Great fun! (EA Feb. '82).

Cat. 82EG2

\$12.00



ELECTRONIC WATT METER

This unit will measure the power consumption of any mains appliance with a rating up to 3 kilowatts. It makes use of a special op amp called an "output transconductance amplifier" or OTA, for short. (EA Sept. '83).

Cat. 83WM8

\$79.50



PH METER KIT

Build this pH meter for the swimming pool season is here again!

From swimming pools to fish tanks to gardening, this pH meter has many applications around the home. This unit features a large 3 1/2 digit liquid crystal display and resolution to 0.1 pH units, making it suitable for use in the laboratory as well. (EA Dec. '82).

Cat. 82PH12

\$139.00




ELECTRIC FENCE

Mains or battery powered, this electric fence controller is both inexpensive and versatile. Based on an automotive ignition coil, it should prove an adequate deterrent to all manner of livestock. Additionally, its operation conforms to the relevant clauses of Australian Standard 3129. (EA Sept. '82)

82EF9

\$19.50

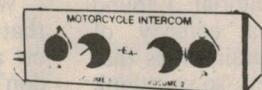


MOTORCYCLE INTERCOM

OVER 500 SOLD!

Motorcycling is fun, but the conversation between rider and passenger is usually just not possible. But build this intercom and you can converse with your passenger at any time while you are on the move. There are no "push-to-talk" buttons, adjustable volume and it's easy to build! (EA Feb. '84).

84CM5

\$45.00

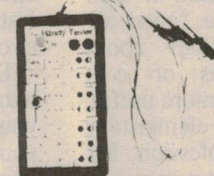


TRANSISTOR TESTER

1000's SOLD

Have you ever desoldered a suspect transistor, only to find that it checks OK? Trouble-shooting exercises are often hindered by this type of false alarm, but many of them could be avoided with an "in-circuit" component tester, such as the EA Handy Tester. (EA Sept. '83)

83TT8

\$15.00

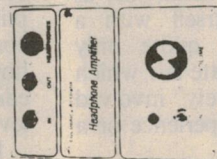


HEADPHONE AMPLIFIER

PRACTISE WITHOUT ANNOYING THE FAMILY! If you play any type of electronic instrument, this headphone amplifier will surely interest you. It will let you practise for hours without upsetting the household, or you can use it to monitor your own instrument in the midst of a rowdy jam session. (EA Feb. '84).

83MA11

\$28.00

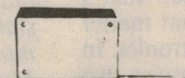

TEMP PROBE

Can measure temperature from -50 to +150 C. It simply plugs into your multimeter — great for digital multimeters. Accuracy of 0.1 C resolution of 0.1 C. (ETI June '83)

ETI-153

\$22.50

rie

Rod Irving Electronics

425 HIGH STREET,
NORTHCOTE VICTORIA.
Ph: (03) 489 8866 489 8131
48-50 A'BECKETT STREET,
MELBOURNE VICTORIA.
PH: (03) 347 9251
Mail Order and
correspondence:
P.O. Box 235
NORTHCOTE 3070

**YOU WON'T GET
BORED OVER
THE HOLIDAYS
WITH THESE
GREAT
SPECIALS!!
GREAT 'IN
STORE' BAR-
GAINS TOO!**


Call in at either 2
of our convenient
located stores:
48-50 A'Beckett
St., Melbourne
425 High St.,
Northcote.
Or take advantage of our Mail
Order Department.

Write to:

MAIL ORDER CENTRE
ROD IRVING ELECTRONICS
P.O. BOX 235
NORTHCOTE 3070

or phone ...

MAIL ORDER
HOT LINE

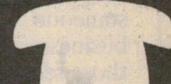

481 1436



POSTAGE RATES	
\$1-\$9.99	\$1.50
\$10-\$24.99	\$2.00
\$25-\$49.99	\$3.00
\$50-\$99.99	\$3.50
\$100-\$199	\$5.00
\$200-\$499	\$7.50
\$500 plus	\$10.00

"We wish you a
Merry Christmas
and a Happy New
Year!"

from all at Rod
Irving Electronics.



Letters to the editor

"So, you think you're a journalist, mate?"

Having graduated recently with a degree in communications engineering, it was with great interest that I read your August editorial. I found this to be such a comedy of assumptions and generalisations that I feel justified in asking "so you think you're a journalist, mate?"

In the first instance you claim to be interested in engineers with a "good grounding in the fundamentals" however your "simple knowledge test" bears no relevance to fundamental principles. Had you quizzed your candidates about tuned circuit resonance or emitter-follower configurations, you may have obtained a clearer indication of their knowledge. To test for a "good all-round engineer", questions about circuit layout practices or cost efficient design would be more useful.

Contrary to your elementary understanding of the profession, Mr Simpson, an engineer is not someone who knows how everything works, but who can analyse and understand circuits, and use them in a design to satisfy a given set of specifications with due regard to cost, environmental and human factors.

A student engineer studies hundreds of circuits while at college, and cannot be expected to remember the workings of all of them; just as someone such as yourself with a business degree could quote only those sections of corporate law which he has been extensively involved with, either through experience or a special student project.

You state in your editorial that your candidates were "considerably less informed than the typical hobbyist... who reads *EA*... avidly every month"; and later on "anyone who has been a regular reader of *Electronics Australia* over the last few years would have had little difficulty handling the questions listed above". I have been buying *EA* for 10 years now, but this does not mean that I read every article, or for that matter articles in every field of electronics. In fact, I would struggle to answer two of your questions "competently". In any case, many of your articles are

written in such a confusing manner that they fail to convey a proper picture of the circuit operation.

When your candidates complained that you were placing heavy emphasis on audio, you replied that "if you don't understand analog circuitry then ultimately, you don't understand digital circuitry either." Do you really consider that a lack of knowledge of specific audio circuits implies a total ignorance of analog circuitry? I think that what your candidates were getting at was that you advertised for an electronics engineer, and then asked questions more relevant to communications engineering. In any case, your particular questions do not test an understanding of analog circuits.

Despite your concluding remarks (a blunt effort to boost circulation of your magazine), I am sure that even you would concede that the institute journals and trade magazines provide the greatest source of up to date technical information.

In closing I would like to add that over the years I have enjoyed reading your magazine, and have gleaned much valuable information from it. I am however disappointed by the declining journalistic standard of late, as well as the quality of the technical content. I therefore challenge you to publish this letter to encourage comment from other readers, and hope that you endeavour to lift the editorial standard of *EA* back to the level set by your predecessor.

Richard Lawrence B.E. (Comms),
Blackburn, Vic.

● *Of course our knowledge test had relevance to fundamental principles. That was the problem for the applicants; they didn't know the principles.*

We do consider that a lack of knowledge of the complementary symmetry amplifier implies a serious ignorance of analog circuitry. We quizzed applicants closely on thermal stability of the output stages, Vbe multipliers, bootstrapping and so on. Many had no familiarity with the circuitry and, more seriously, had no ability to analyse them. (Ed.)

Reply to "KL"

Although I did not read the editorial which stimulated the engineers versus technicians debate, I would like to offer a comment about persons such as "KL".

The rights and wrongs of the article and the replies are not the point in dispute. Opinions are not necessarily worth the paper they are written on — a personal opinion is of no consequence.

What does matter is attitude. The fact that KL is never again to buy *EA* is, from any point of view, a threat. Perhaps only a little, insignificant threat, yet a threat none the less.

KL is not debating, he is opinionating and egotripping. His type of attitude causes stifling of free speech and often leads to violent conflict. In Australia, KL withholds

Editorial backlash

Regarding the Editorial Viewpoint "So you think you're an engineer, mate", you demonstrate a naivety and arrogance of such an order that it makes amusing reading.

You clearly have no idea of what is expected of a professional engineer. An electrical engineer takes an intensive four year (full time) course in mathematics, science and engineering theory. The engineer's career then spans a period of approximately 40 years during which time his/her grounding in fundamental theory should allow him/her to keep abreast of technological change at a quantitative level. The engineer (generally) is required to be a team leader and a technologist, manager and business person. The engineer's practical training effectively commences after graduation and continues for the rest of his/her career.

I agree that you could be unwise in employing a recent graduate with limited benchtop skills. However, you are totally out of order to claim that recent graduates who could not satisfactorily answer the quiz questions are not competent for a career in engineering. At worst, these young engineers are silly to apply for a job with your magazine.

I put it to you that you have had little, if any, experience in a professional engineering environment and do not have the competence to criticize formal engineering education. The reader who takes your comments on face value must be left wondering who in fact advances the state of the art in engineering (including electronics) — perhaps *EA*?

M.J. Flaherty,
Norman Park, Qld.

his \$2.30. If this were a banana republic, he would probably be assassinating Leo Simpson for his opinion.

It is not my intention to criticise EA or its staff. At times, I too have wondered whether a particular article might be erring towards profit motive rather than information. But that is only my opinion.

However, it was EA who threw the debate open for comment. Such courage must be admired and replied to in like spirit. Issuing threats — no matter how small — completely changes the issue.

Tolerance and humour are a man's greatest assets and may well be the only virtues safeguarding us from extinction.

M. de Botella,
Derby, WA.

Tripler replacement method not safe

In "The Serviceman", an article appeared regarding the replacement of triplers in early Rank Arena CTV receivers. This described the use of a Philips/Varo type tripler as a replacement type in conjunction with several resistors as a focus supply source. I produced such a note at RMIT, around 1979, for student use.

Unfortunately, on further investigation, this method is not a reliable or safe substitution. Without the large VDR resistor in circuit, the EHT voltage rises from the original 26kV to around 35kV at low brightness levels.

A substitute tripler is available from Skandia Electronics (Victoria) which

incorporates the original VDR, thus maintaining EHT regulation. Alternatively, if the original Rank neoprene EHT ultor cap is used, 2 EHT cables can be inserted (with Silastic added), one from the tripler and one from the VDR resistor.

The fault occurring with the original tripler is usually EHT punch-through at the casing. Sometimes this is repairable with Silastic (clear, non-acetic), but the punch-through frequently occurs again on either the front or back of the tripler, or where the EHT cables exit. The arc-over usually destroys the vertical output and drive stages as well, so with the cost of the tripler and replacement transistors the owner will be up for repair costs of around \$200.

R. Humphris, RMIT,
Carlton South.

Car batteries and resistor colour codes

Over recent months you have highlighted problems in the areas of motor car battery life and colour markings on resistors. I would like to comment on these topics.

Having purchased a brand new Ford Falcon station wagon just over two years ago I was very disappointed when the battery "packed it in" after just 15 months service. I took the car back to the Ford dealer from whom the car was purchased (and who had carried out all service since purchase) believing I would have some guarantee cover on the battery for such a short service life. I was informed that there was no guarantee or warranty on batteries in new cars produced by Ford! The same applied to tyres and other items not made by Ford.

I had to accept this situation and asked the dealer to fit a new battery. When I

collected the car that evening and inspected the new battery I was astonished to see that it was the same brand name as the battery that had packed it in after 15 months. I was on the point of refusing to accept this new battery when the service representative hastened to say that new car equipment batteries were of cheap manufacture, whereas the new battery, even though it was the same brand name was a top quality battery and equal to the best on the market.

Therein lie several matters of concern: batteries which last only 15 months and not three to four years as we are lead to believe; the claim that, in this instance at least, original new car equipment includes "cheap batteries"; and the absence of guarantee on items such as batteries (and tyres, etc) sold as an essential working part of a new car.

My next experience relates to incorrect resistor colour codes. Sometimes I purchase resistors in lots of 10 or more to take advantage of the lower cost. On this occasion I purchased 15 resistors of 1kΩ value and promptly put them in my 1kΩ drawer.

Some time later my son, who checks resistors before using them in a project, found that one of these resistors measured 10kΩ. We both looked at the colour bands and, sure enough, they were brown, black, and red — 1kΩ. I checked the other 14 resistors and they all measured 10kΩ and so were incorrectly marked during manufacture.

I wonder how many other people bought alleged 1kΩ resistors from this batch and have run into problems.

I hope these remarks may be of use to you.

B. Hunt,
Heathmont, Vic.


QUALITY FROM ENGLAND

CLIFF

AUST DIST:


PTY. LTD.
Delsound
YOUR ONE STOP ELECTRONIC SUPPLIER

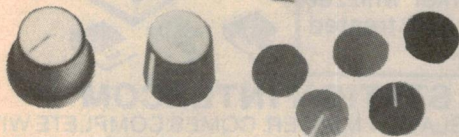1 Wickham Tce,
Brisbane 4000,
Ph: (07) 229 6155
Telex: AA 44442




K9 19 x 20mm, K11 20 x 19.7mm
K10 18.5 x 17mm, K12 19.2 x 25.3mm

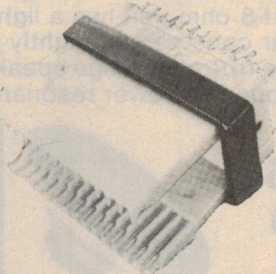K9-10-11-12 MATT BLACK FINISH
AVAILABLE IN PUSH ON OR SCREW FIX,
PUSH ON CAPS, AVAILABLE COLOURS
RED, BLACK, WHITE, BLUE, YELLOW,
ORANGE, GREY OR GREEN.



IC TEST CLIP

3 SIZES — 14-16, 26-28
AND 40 WAY.

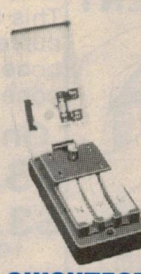

QUICKTEST

IDEAL FOR W/SHOPS AND
TEST DEPTS. PLUGLESS
LEADS, RAPIDLY CONNECTED
TO MAINS.



S2 SERIES

S2 RANGE 6.5mm
NYLON MONO AND
STEREO SOCKETS. HIGH
QUALITY BRASS, HIGH
NICKEL CONTACTS.
COLOURS AVAIL.



P2 SERIES

6.5mm PLUGS. NYLON
AND METAL COVERS.
MONO AND STEREO.
COLOURS AVAIL.


JAYCAR JANUARY SPECIALS

- WE HAVE NEVER BEEN SO DESPARATE!!!

SAVE A FORTUNE



**Ceiling Grilles
for 8" speakers**

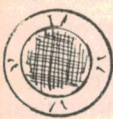

1-9 \$1.25

10 up \$1.00

Ideal for PA
installers

Cat. AX-3560

MASSIVE SAVING

**TAPE HEAD
DEMAGNETISER**

Cat. AC-1600

Works on cassette and
Reel-Reel. Special
cushion head designed
to get into tight corners

240V

NORMALLY \$5.95

JANUARY PRICE

\$3.95

SAVE

\$2

SAVE AT
JAYCAR

8" WOOFER

This superb Pioneer woofer will handle about 20 watts rms. Frequency
response is 50 - 3kHz. These are usually worth \$15 each.
Cat. CW-2112

ONLY \$7.50 each

SAVE \$7.50 each (50%!!)



EACH BAG
CONTAINS HEAPS
OF GOODIES
FOR YOUR
JUNK BOX
**AVERAGE
WEIGHT IS 1kg!**

STOCK MAY BE SCARCE FROM TIME
TO TIME AS WE ONLY MAKE THEM
WHEN WE HAVE NOTHING ELSE TO
DO (AS THEY ARE BELOW OUR COST)

SORRY! PERSONAL SHOPPERS ONLY


**SWIVEL/TILT BASES FOR
MONITORS - ARE WE CRAZY?**

**NORMALLY
\$29.95**

SAVE 1/3

**THIS MONTH
\$19.95**

Cat. XM-4540

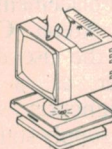

**GOING ON
HOLIDAYS?**

DON'T GO WITH-
OUT A "JETPHONE
ADAPTOR",
CONVERTS THE AIR
TYPE HEADPHONE
SOCKET IN A PLANE
TO ELECTRIC. YOU
CAN THEN PLUG
YOUR OWN PHONES
IN & LISTEN IN
COMFORT!

1st CLASS!!

WERE \$8.95 &

\$5 AT TIMES

LAST YEAR

THIS MONTH

\$3.95

ONLY A FEW
LEFT - HURRY!
SO BEFORE YOU
FLY OUT, FLY IN
& GRAB ONE!
Cat. AA-2040

**Jaycar
ELECTRONICS**

**PIONEER 10" GUITAR
SPEAKER**

Quality Pioneer brand - check the specs! Check the price!

★ Impedance 8 ohms ★ Voice coil diameter 1 1/2" ★
Power rating 60 watts rms ★ Resonant frequency 80Hz
★ Sensitivity 98dB(dB/W) ★ Response 80Hz - 7kHz
★ Total flux 61,100 Maxwell ★ Flux density 8,300
Gauss ★ Net weight 1.54kg.



ONLY \$29.95
CATALOGUE PRICE \$39.95

SAVE \$15 ON

**LOW-COST COMPUTER/
AUDIO CASSETTE RECORDERS**



- WORKS WELL • MAINS/
BATTERY OPERATED
- SPECIAL TAPE LOADING
INSTRUCTIONS • TAPE
COUNTER (a must) INBUILT
- ELECTRET MIC. • LED
RECORDING INDICATOR


WERE \$39.95

Cat. XC-4905

THIS MONTH ONLY \$24.95

**110v COMPUTER
GRADE FANS**

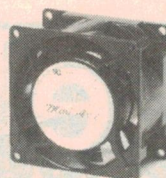- NEVER TO BE
REPEATED OFFER
- GERMAN MADE
- 'EBM' BRAND
- 80mm SQUARE (std) FITTING



**LIMIT STRICTLY 1 PAIR PER CUSTOMER
WHAT'S THE OFFER?**

THAT'S RIGHT, 2 FANS FOR THE PRICE OF 1!
THAT WAY YOU CAN USE THEM ON 240V
(WIRE IN SERIES)

\$14.95 for 2 Cat. YX-2508

**MOISTURE REPELLENT
SPRAY**

400g CAN

WERE SELLING FOR
\$6.95 WE HAD THEM
FOR \$3.95 LAST YEAR
(BARGAIN!) STILL A
FEW LEFT. ONE OF
THE BEST BARGAINS
ON THIS PAGE AT -

\$2.95 Cat. NA1020
A CAN



Beautiful Brown 6" Twincone Speaker

This 5 watt 8 ohm unit has a light brown
curvilinear cone with a slightly darker whizzer
cone. It is a true widerange speaker with treated
cone surround for lower resonance.

**Only
\$3.95 ea
\$3.50
10 up**

Cat. AS-3013



4 STATION INTERCOM

3 SLAVE, 1 MASTER. COMES COMPLETE WITH
LOTS OF WIRE, STAPLES & INSTRUCTIONS.
RELIABLE SOLID STATE IC CIRCUITRY.

NORMALLY \$29.95 JAN ONLY \$19.95

SAVE \$10.00

Cat. AI-5504



START THE YEAR OFF RIGHT, WITH BARGAINS FROM JAYCAR!!

**SAVE
UP TO 66%**

1-9 \$0.99¢
10 up \$0.50¢ ea

Cat. LA-5270

50¢

INCREDIBLE
TELEPHONE BELLS
- TWO TONES
- ADJUSTABLE LEVEL
- BRAND NEW

- AS USED IN 'GONDOLA' PHONE

WERE
\$1.50 ea

50% OFF SALE

IC INSERTERS & EXTRACTORS ETC

- CMOS SAFE
- BENT PIN STRAIGHTENER
- ONE HAND OPERATION

	WAS	NOW	SAVE
TH-1810 8-20 pin IC inserter	\$5.95	\$3.95	\$2.00
TH-1808 14-16 pin IC inserter	\$5.95	\$3.95	\$2.00
TH-1812 22 pin IC inserter	\$6.50	\$3.50	\$3.00
TH-1814 24-28 pin IC inserter	\$6.95	\$3.95	\$3.00
TH-1816 36-40 pin IC inserter	\$8.95	\$4.95	\$4.00
TH-1818 8-40 pin extraction tool	\$2.95	\$1.95	\$1.00
TH-1824 auto wire stripper/cutter	\$9.95	\$7.95	\$2.00




MICROCOMPUTER POWER SUPPLY

REGULATED. BUILT AND TESTED UNIT
INCLUDES GOLD ANODISED HEATSINK,
WIRING INSTRUCTIONS AND SCHEMATIC
DIAGRAM. TRANSFORMERS NOT SUPPLIED.
OUTPUT VOLTAGES: +12V @ 1.5A; -12V @ 0.5A;
+5V @ 6.0A; -5V @ 0.5A.
Cat. MP-3024

WAS \$39.95

NOW ONLY \$19.95

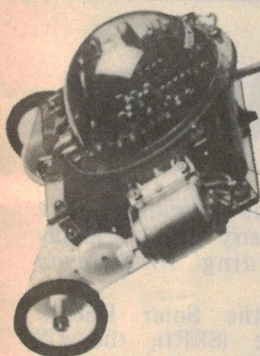NOW OPEN 144 LOGAN ROAD BURANDA QUEENSLAND



VHF/UHF ROTARY
TUNERS - see previous ads
for details.
WERE \$69.95
NOW \$39.95 Cat. DM-9004

SAVE \$30!
SAVE OVER 40%
For advanced
experimenters only!

PIPER MOUSE ROBOT
Fun KIT to assemble in the holidays
WERE \$34.95
NOW \$19.95
Cat. KJ-6680

SAVE OVER 40%

8" 3-WAY SYSTEM

Superb 8" woofer with foam surround suspension and heavy magnet assembly with sealed backmidrange and tweeter. System impedance 8 ohms. Power handling 40 watts rms. Crossover capacitors and connecting diagram and recommended 8" cabinet detail drawing supplied.
Cat. CS-2453 (2 required for stereo)

SAVE \$5.00

\$24.95

set



SAVE \$5.00

\$34.95

set



10" 3-WAY SYSTEM

Once again, a high quality 10" woofer with high power, sealed back midrange and tweeter. System impedance 8 ohms. In addition a quality Pioneer 3-way crossover is provided at no extra charge. Connection instructions are also provided as well as recommended 10" cabinet plans.
Cat. CS-2454 (2 required for stereo)

INCLUDES PIONEER 3-WAY CROSSOVER

WHAT A FLOP! SOLDERING IRON TESTER

NOW OPEN BURANDA QUEENSLAND

We thought that more people would want to know the temperature of their soldering iron - but they didn't! We imported a great little soldering iron temperature meter that was accurate. It just did not sell. It was put on the market at a very reasonable \$29.95 but all it did was stay on our shelves. We put them on special last year at \$19.95 and a few went. But not enough! So this month? An absolute bargain for the serious enthusiast.



Cat. QT-2100

THIS MONTH \$12.95

SAVE POWERTRAN KIT SPECIALS SAVE

DIGITAL DELAY LINE KIT - 400ms
SAVE \$100 WAS \$449
THIS MONTH \$349

"CORTEX" 16 BIT 16 COLOUR COMPUTER KIT


- HIGH RESOLUTION
- 24K EXTENDED BASIC
SAVE \$900 NO ROOM
ORIGINALLY \$1299, ADVERTISED AT A LOWER PRICE LAST YEAR. FOR
DEFINITELY BELOW COST AT \$399 - Cat. KJ-6630

MONEY REFUNDED FOR THOSE WHO MISS OUT DETAILS

"HEBOT" ROBOT TURTLE

- Geared DC motors
- 4 touch sensors (90° apart)
- Hefty 1.8kg
- Speed 15 feet/minute
- Independent wheel control
- Complete with 10 1/2" diameter perspex dome

SAVE \$100

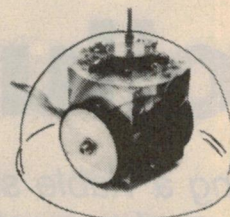

NORMALLY \$399 THIS MONTH \$299

PIEZO TWEETER - Popular PH1038 Horn. Normally \$10.95. This month \$7.50, will handle 50 watts rms and goes from 2-25kHz. Good for Hi Fi or PA. Cat. CT-1902

ONLY \$7.50



Jaycar

ELECTRONICS

Incorporating ELECTRONIC AGENCIES
NUMBER 1 FOR KITS

N.S.W.
SYDNEY: 117 York Street. Tel. (02) 267 1614
CARLINGFORD: Cnr. Carlingford & Pennant Hills Road. Tel. (02) 872 4444
CONCORD: 115/117 Parramatta Road. Tel. (02) 745 3077
HURSTVILLE: 121 Forest Road. Tel. (02) 570 7000
BURANDA: 144 Logan Road. Tel. (07) 393 0777

MAIL ORDERS: P.O. Box 480, AUBURN 2144. Tel. (02) 643 2000
HEAD OFFICE: 7/9 Rawson Street, AUBURN 2144.
Tel. (02) 643 2000 Telex: 72293

SHOP HOURS

Carlingford, Hurstville & Gore Hill
Mon-Fri 9am - 5:30pm; Thurs 8:30pm; Sat 12pm
Sydney
Mon-Fri 8:30am - 5:30pm; Thurs 8:30pm; Sat 4pm
Concord
Mon-Fri 9am - 5:30pm; Sat 4pm

POST & PACKING

\$5 - \$9.99 \$1.50
\$10 - \$24.99 \$3.20
\$25 - \$49.99 \$4.50
\$50 - \$99.99 \$6.50
\$100 - \$198 \$8.00
Over \$199 \$10.00

COMET ROAD FREIGHT ANYWHERE IN AUSTRALIA ONLY \$12



**MAIL ORDER VIA
YOUR PHONE**

SOLAR ENERGY—



At 16kW, this solar array is the largest outside of the USA. Installed at Libreville, Gabon (Africa), it's used for a microwave repeater.

Pollution-free Power

Finding a viable substitute for fossil fuels has expended a great deal of research and development effort during the last decade. The new photovoltaic cells could be the bright light on the horizon.

Solar cell efficiencies have improved to the point where, for many applications, photovoltaic panels are now a competitive energy source for consumers in areas remote from an electricity grid. Some optimistic researchers now predict that, by the turn of the century, photovoltaics will be a cheaper energy source than oil.

The last three years have seen

American manufacturers making serious commitments to photovoltaic cell production. Annual commercial production of photovoltaic cells in the USA increased 500% over the last three years. Today, most alternative energy technologies throughout the world would falter if government support of research and development were dropped. But, even without the support of

research and development, the photovoltaic industry would hardly collapse, according to leading industrialists.

Members of the Solar Energy Research Institute (SERI), the US Department of Energy, and many other leading researchers and industrial developers, all agreed at SERI's last annual meeting that photovoltaic technology is ready for commercialisation. Since the first cells were made for the US space program in 1958, they have been credited as being silent, inexhaustible, and a pollution-free source of electricity — but expensive.

Now that is all changing. Solar cells have progressively become a keen competitive energy source where

commercial power supplies are not available, especially in remote locations and in underdeveloped countries. Due to raw materials such as silicon and others being manufactured at a lower price with a higher purity rate, the efficiency of the units has risen considerably.

"Some oil companies have even made a commitment" says Roger Taylor, manager of photovoltaic research at the Electric Power Research Institute in the USA, "because they have vision and can see a viable and growing market. Other alternative energy technologies, such as wind turbines just don't have this backing."

Working solar-cell systems

From irrigation pumps to village power systems, solar cell installations are now economically producing electricity. One of the largest solar cell installations in the world is a 100kW unit at the National Bridges National Monument in Utah. Since June 1980, it has supplied energy for all the park's electrical needs.

These include water pumping, maintenance shops, a visitor's centre, motorists' trailers and service mains to several park-ranger's homes. Lead acid batteries, having 600kW.h storage capacity, are provided as back-up. So far the batteries have not discharged below 40% of their capacity.

The park's 1712 square metre solar cell layout contains 250,000 silicon cells in 4762 modules. The units provide 210 amperes at peak output.

The system also has diesel generators for back up but they are rarely needed to compensate for lack of sunlight. Instead, they are mainly used to equalize the charge between banks of batteries.

A self-sufficient billion-dollar-a-year industry is forecast for America by 1986. The timetable of user acceptance in the USA is predicted to follow this sequence: remote communities and houses, sunbelt residences already connected to the mains, remote water pumps for irrigation, houses in less sunny areas, etc.

A 3.5kW photocell system at the Papago Indian Reservation Village in Arizona is the first stand-alone unit designed specifically to supply power to a small village. Since 1978 it has delivered water for the village. The unit can send over 4000 litres an hour to the 41,600 litre storage tank. The system also provides lights for fifteen houses and keeps domestic appliances going.

The system is a success story but the Indians have developed an appetite for electricity and the system may have to be upgraded. One of the major drawbacks with a system like this is the need for "load-management". Available power

must be used effectively and this requires careful load management.

Battery storage is invariably necessary and the size must be limited to minimise the capital costs. The solar cell system therefore has controlled independent circuits and a central control unit that uses power according to specific priorities and conditions.

In most systems of this kind, functions such as water pumping and crop-grinding are permitted only during periods of high solar gain. Also, battery back-up for these functions may not be available. With the Arizona installation, the available pumping time varies from three hours per day in winter to over five hours in summer. To protect the batteries from damage and to extend their lifetime, circuits to washing and sewing machines are disconnected at 50% depth of discharge, lights at 60%, the water pump motor at 70% and refrigerators at 80%.

Types of cells

Photovoltaic cells can be fabricated from materials in a variety of ways. Generally, the materials are grouped into four categories: single-crystal silicon, polycrystalline compounds, semiconductors such as gallium arsenide, and amorphous silicon.

Single-crystal cells are approximately 19% efficient. The best commercial module efficiencies are between 11 and 12%. Most of these cells are sawn from round silicon ingots grown by the Czochralski process, then polished. This material was originally developed to form materials for semiconductors.

Polycrystalline cells are made of compound semiconductors with small crystal-grain sizes. The highest cell efficiency to date is 11%. The cells are easily and reliably produced using thin-film techniques. Their greatest attribute is that they can be mass-produced economically.

Gallium arsenide cells: the undisputed champions, where efficiency is concerned, are laboratory cells made of gallium arsenide (GaAs). Cells measuring one square centimetre have reached an efficiency of 20.34%.

No one as yet has made GaAs cells on a production line basis. However, a Californian company is developing a mass-production process and will be making them for space applications. Much of the interest in GaAs is attributed to the potential for its use in tandem cells. These are cells made from a GaAs layer deposited on top of a silicon layer. Such tandem cells potentially may reach 30% efficiency.

Amorphous silicon cells: These are the latest of the commercial cells, the first

version being fabricated in 1974. By 1982, RCA had developed a one square centimetre cell with an efficiency of 10%. Because amorphous silicon absorbs light energy more readily than single-crystal silicon, thick wafers are not needed. Of all photovoltaic cells produced in 1983, 25% were amorphous silicon cells.

Increasing cell efficiency


Until 1970, the top efficiency of any of the cells was about 14%. Today, efficiencies of up to 22% are being achieved, while tandem photovoltaic systems — groups of cells selected to utilise the wavelengths in sunlight more effectively — have produced efficiencies of over 28%. Researchers are optimistic and say that by increasing the cells in tandem, which effectively increases the light concentration, they should be able to boost efficiencies to 60%.

The goal of the US Department of Energy is to reduce photocell costs to 70 cents per watt by 1986.

Storing energy

So that electric power can be available at night and on cloudy days a storage medium is necessary with a photocell installation. Storage batteries can be too

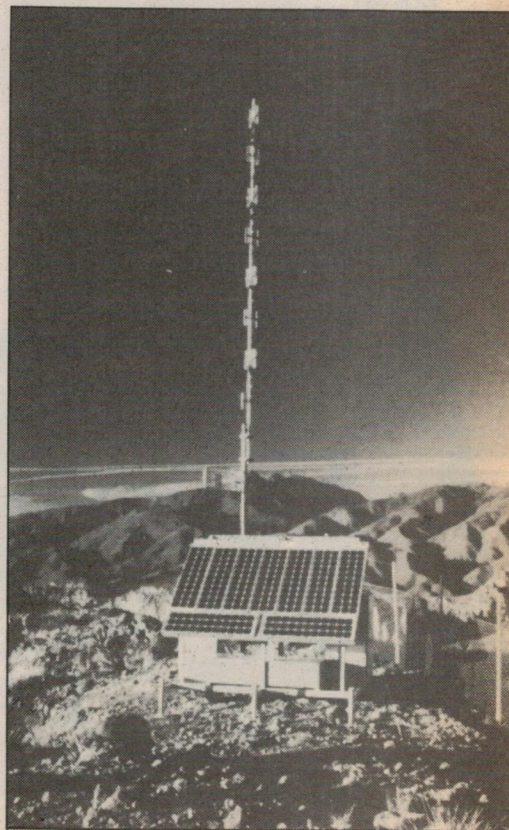This 300 watt array at Bronco Butte, Arizona, is operated by the Department of Public Safety. It powers three transmitters.



Solar Energy

expensive for larger solar installations, therefore alternative technologies have been proposed for energy storage and are receiving R&D treatment.

These technologies will also benefit conventional plants as well as solar plants because they will permit "load levelling" and improve the load factor of the system. They will allow energy to be stored during off-peak periods and therefore reduce the need for new generating capacity to meet increased peak demand.

Proposals include: rotating masses that store power as kinetic energy; hydrogen-based systems where water is electrolysed by the solar-plant output and the hydrogen product is consumed, as needed, in fuel cells; and hydropumping, where water is elevated by solar-powered pumps and then

converted into electricity by hydroelectric turbines. Regardless of solar cell advances, large scale solar power will not be really practical until an economical energy storage system is developed.

Economics

Today, solar cell power is too expensive to compete with fossil-fuel and nuclear power. If solar cell power could be reduced to around 70 cents per peak watt then it would be a viable alternative to conventional electric power generators. Impossible? Not really. The price of cells today is approximately \$10 per peak watt whereas, 10 years ago, it was \$500 per peak watt.

Sunlight varies in intensity throughout the day. Therefore, 100 10MW stations scattered throughout a region will yield more average power than a single 1000MW station. Also, this scattered arrangement would eliminate some transmission costs.

Whereas the site area, per unit power output, decreases with increasing capacity for conventional plants, the site area increases linearly with output for solar plants. A 100MW solar plant would cover approximately 2.5 square kilometres of land with solar cells. A 1000MW solar plant will need 25 square kilometres.

The economics of solar plants is strongly influenced by the cost of auxiliary equipment. The cost of mirrors or lenses in concentrating systems must be taken into account, as must the cost of a tracking system to point the concentrator towards the sun as it moves from east to west.

Some experts say that if solar cells were priced in the \$1 to \$2 range per peak watt, solar power would have an economic advantage over the diesel powered pumps presently used in irrigation schemes.

It is also likely that large-scale solar power will be exploited in the developing countries first, the main reason being the lack of grid and network distribution systems. With localised units, not involved with transmission costs, the higher cost of the solar cells will appear more acceptable. For example, for a village that is 100 kilometres from a power station or grid system, a cost of \$2 per peak watt would make the installation of a local solar power station less expensive than extending the grid.

The experts concede that no one is thinking of a total commitment to photovoltaic power at the present time. They envisage a gradual increase in the use of solar power, mainly to relieve the load on diminishing fossil-fuels and on nuclear plants.

The future

In February 1983, a 1MW solar system using single-crystal silicon panels — the largest photovoltaic central power station in the world — was commissioned in California, USA. The plant, which cost approximately \$US11 million, covers over eight hectares.


About 36MW of single-crystal-silicon modules had been installed worldwide by the end of 1983. The average selling price at the time was \$7 per peak watt. At this price, an American manufacturer says, there is a \$US100 million a year international market for panels. If costs could be brought down to \$US3 per peak watt say analysts, then the solar market could explode overnight to \$US1 billion annually. At \$US1 per peak watt, an estimated \$US10 billion solar energy market would await manufacturers.

There may not be much gold left in them thar hills — or much black gold left in some of those valleys, seas, or deserts — but the sun shines for us all: it's just a matter of catching it at the right price. ☺

NEWS RELEASE 240V AC POWER SYSTEM FROM PHOTONICS

Amtex Electronics have released three photovoltaic systems designed for domestic 240VAC use. Each system consists of solar modules, support structures, deep cycle batteries, electronic control equipment, a solid state inverter and cable assembly. Although they are designed for installation by an average handyman, professional installation can be arranged. The smallest system delivers an average of 1kWh per day in the southern parts of Australia while the largest delivers 4kWh per day. Illustrated is the Amtex small AC system consisting of 8 solar modules of 40W each, aluminium support structure, 6 deep cycle batteries, electronic control equipment and 1500 inverter.


AMTEX
ELECTRONICS

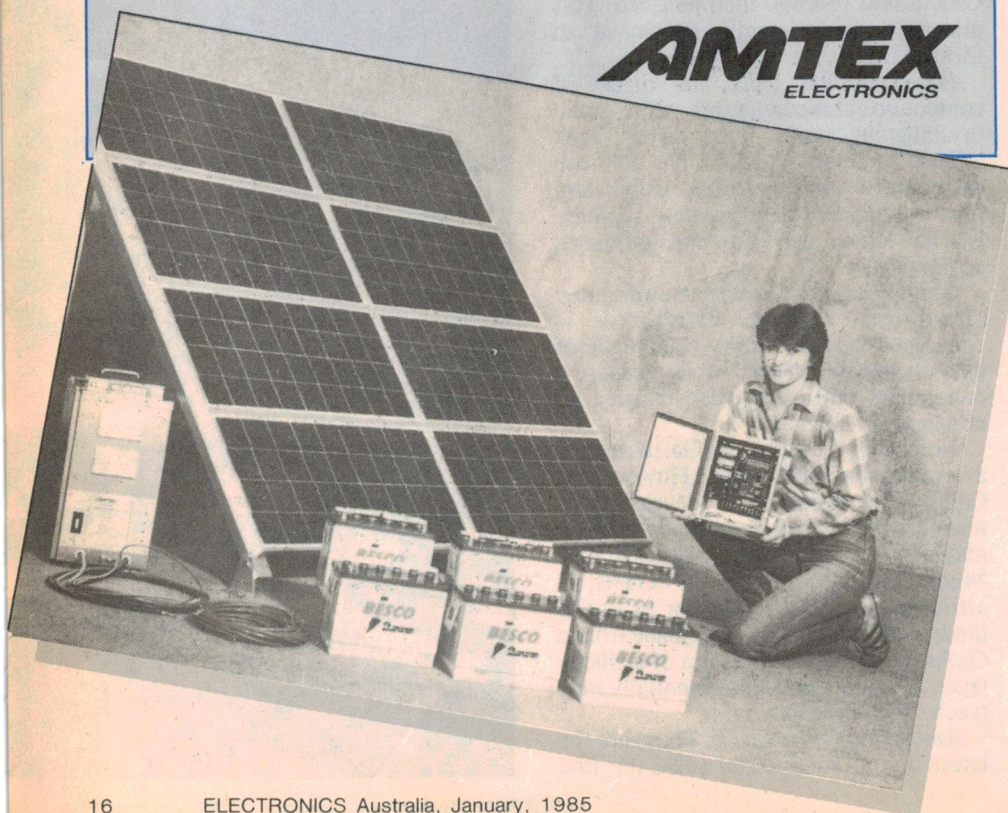


PORTABLE SOLAR GENERATOR

MODEL

NV.500M

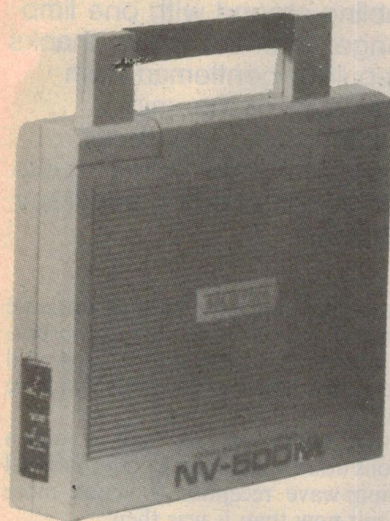

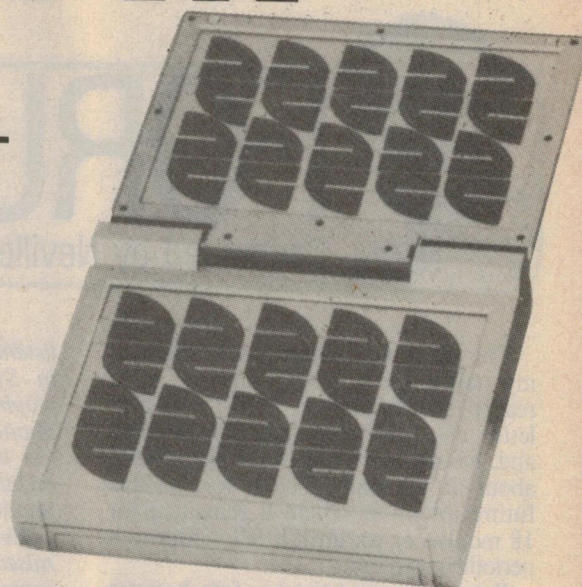NOW, FROM SOLAR-TECH COMES THE WORLD'S FIRST SOLAR POWER GENERATOR THAT RECHARGES VTR BATTERY PACKS



The new NV-500M has added features making it a more versatile portable solar generator with built-in multi-volt power outlet which can deliver power to operate your appliances in 3, 6, 9 and 12 volts.

SPECIFICATIONS	Product Name	Solar-Generated NiCd Battery Charger
	Model	NV-500M
	Solar Cell-Module	P/N Single Crystal Silicon Cell Module 0.5V/0.5A Cell \times 40 pcs., Isc 0.5A Voc 20V Condition: Sunlight 100mW/cm ² (Facing direct to the sunlight on a clear day)
	Applicable NiCd Battery	Portable VTR Battery with capacities of 12V. 0.5Ah to 2.0Ah.
	Charging Hours	$H \approx \text{Capacity of NiCd battery} \times 3.3$ (from the complete discharged level)
	Charging Method	Constant current charging with over-charging protector and circuit breaker.
	Operating Temperature Range	-10° ~ 80°C
	Dimensions	330mm W \times 350mm H \times 65mm D
	Weight	2.6kg
	Accessories	Polarities Adapter and Connector Plug

FREE

ORDERS RECEIVED BEFORE
JANUARY 31, 1985 WILL RECEIVE
AT NO EXTRA CHARGE:

NI-CAD BATTERY PACK 12V 1.2AH

NORMALLY \$59

AMTEX
ELECTRONICS

A DIVISION OF **TELCON**
AUSTRALIA PTY. LIMITED

36 Lisbon Street,
Fairfield
NSW 2165

Telephone (02) 728 2121, 727 5444
Telex AA27922 Telcon

Besides recharging various VTR battery packs with this NV-500M, you can also draw power direct through the External Outlet with the battery left inside the unit. This way you can use power longer while the solar panels keep generating power simultaneously. Through direct power supply, you can operate many other appliances such as radio cassettes, AM/FM radios, public address systems, portable fluorescent light that operate on power under 0.45A (about 5W).

FEATURES

- **PORTABILITY** — A mini-powerhouse, the size of an attache case, the NV-500M can generate enough power to recharge your VTR battery packs (12V 0.5Ah ~ 2.0Ah) anywhere whenever the sun shines.
- **VERSATILITY** — The NV-500M can house, and recharge VTR battery backs of many makers regardless of difference in size. Also NV-500M can be a handy DC power source for a variety of other appliances.
- **LIGHTWEIGHT** — The moulded cabinet is sturdy and lightweight.
- **EASY CHARGING** — The custom-designed IC assures a constant current charging either from the solar cell module under the sunlight or from AC power source. (An adapter is needed).

PRICE \$225 EA CERTIFIED POST AND PACKING \$10

ORDER FORM

To: Amtex Electronics,
36 Lisbon Street,
Fairfield, NSW 2165

Please send me NV500M @ \$225
Certified Post & Packing @ \$10

Total = \$

Enclosed is a cheque/money order.

Please charge my Bankcard:

No

Expiry

Signature

Name

Address

Leg pulling? MW radio



FORUM

Conducted by Neville Williams

Unless I am much mistaken, a number of people are hobbling around with one limb considerably longer than the other, thanks to a certain leg-pulling gentleman from New York. Either that, or the said gentleman has contrived a broadcast receiving antenna from "directional" audio cable and aimed it with unerring accuracy at Sydney, Australia!

The particular matter was brought to my notice a couple of years ago by a reader from Winmalee, NSW. I read his letter, decided it was a gag of some kind and, having more urgent things to write about at the time, filed it for possible future attention. There it remained for 18 months or so, until it fell victim to a periodic clean-out.

But that was not to be its fate, because I've just received another letter from the same correspondent on the same subject. I quote:

Dear Sir,

A couple of years ago, I brought to your attention a brief item which appeared in the Sydney "Sun" newspaper, in which it was claimed that radio 2CH in Sydney had been received loud and clear on mainland USA.

It went on to explain that an American gentleman visiting Sydney had become a devoted listener to 2CH and, prior to his departure, had rung the station and expressed his sentiments to the afternoon announcer, stating that a very sensitive receiver was on hand and that, following considerable dial twiddling, the station could be heard quite clearly.

To prove his claim, the phone was placed close to the loudspeaker, allowing the announcer to hear the music that he knew was going to air at that very moment. End of story!

In my earlier letter I posed two questions:

(1) What are the chances of a Sydney medium-wave broadcast station being received in the USA — particularly at mid-afternoon, Sydney time? In my experience it would require a near miracle to be heard in New Zealand, let alone America!

(2) "Super sensitive" receiver notwithstanding, why is 2CH not being swamped by other transmitters, many of which must surely be on or near the same frequency?

I suggested in my letter that the announcer had been the victim of a practical joke. That the American

listener had phoned a willing participant in Sydney and arranged for a radio playing 2CH to be placed close to the phone. Then our prankster had phoned the announcer, spun him the amazing reception story and simply held the two phones together, by way of proof.

Even though the matter was never raised in EA, I believed that someone, somewhere would have a quiet word in the ear of the announcer and/or the appropriate staff member of the Sydney "Sun".

But no. Two years later, an item on page 4 of "The Sun" for October 5, '84 endorses the original claim. It reads:

BARRY WINS ONE LONG RANGE FAN

Barry Spicer, 2CH arvo rating's winner, has made one fan who won't give up — even 20,000 km away, at home in New York City.

Craig Thompson, a businessman, became a Spicer convert two years ago during a visit to Sydney.

Back home, he fiddled and fine-tuned his ham radio until Barry came through loud and clear and, for the past year, he has been calling Spicer about once a month for a yarn.

Next month, Craig Thompson will be back in Sydney for a spot of business — and lunch with his Aussie hero.

Seriously, Mr Williams. Having been a regular reader of EA for over 20 years, I respect your comments. In the light of recent articles touching on the ignorance of those about to enter the electronics industry, people who may have read this "amazing reception" yarn deserve the benefit of your reaction — just to get the record straight.

Derek Hobbs (Winmalee, NSW)

Long time — but not very technical — readers of the magazine may well wonder what all the fuss is all about, remembering that, once upon a time, they used regularly to log overseas broadcast stations on their Sooper Dooper Blooperdyne receivers. They might recall that American magazines,

back in 1925, regularly used to advertise radio sets capable of picking up Europe. Yet none of those ancient models would have been a patch on receivers available today.

True, but there are half a dozen reasons (four, anyway) why international medium-wave reception is much more difficult now than it was then.

(1) There are far more stations on air, nowadays, with many of them, nationwide and worldwide, sharing each frequency channel in the broadcast band.

(2) A great many stations now operate 24 hours per day, so that DX (long distance) enthusiasts can no longer listen around the band after local stations have closed down.

(3) Most MW stations, these days, by choice or by law, use an antenna system which concentrates their signal in a designated service area. High angle transmission, which could reach further afield (and interfere with other stations) is deliberately minimised.

(4) Man-made electrical interference has increased enormously since the early days, blotting out signals which once might have been audible.

For all of these reasons, the chances of anyone in New York City — of all places — listening regularly (if at all) to 2CH in Sydney would seem to be nil. Especially to 2CH!

You see, 2CH is on 1170kHz, one of the few frequencies in the medium-wave band which are divisible by both 9 and 10. Therefore that exact frequency is going to be occupied by radio stations in countries using 9kHz separation (notably Europe and Australasia) and 10kHz (notably USA, Canada and Mexico).

Seemingly, Mr Thompson would have made things easier for himself by having an affair with any station in Sydney other than 2CH! At least he would not have had to face quite so much direct competition from within his own continent.

Unfortunately, Mr Thompson's credibility is not helped by the choice of

and super hifi copper!

words in "The Sun" news item, as quoted: "He fiddled and fine tuned his ham radio until Barry came through loud and clear". It has all the marks of a non-technical copywriter using words which he/she has picked up from somewhere and which sound appropriate.

Yes, a ham (amateur) receiver can receive signals, loud and clear, across the Pacific in either direction — but only only at certain times and in certain frequency bands. The medium-wave broadcast band is not one of them!

But even if Mr Thompson was using a modern communications type receiver covering the amateur AND broadcast bands (I have one myself, as would thousands of other readers) you don't have to "fiddle and fine tune" such a set; that sort of thing went out with blue serge suits; or rather with receivers that had unstable local oscillators and indifferently calibrated dials.

These days, if you want 1170kHz, you dial up that frequency and that's what you have; instantly, spot-on and no fiddling!

Whether what you hear is 2CH or babble from a dozen other stations on that frequency would be quite another matter.

But could that reference to a "ham" receiver be a Freudian slip? Derek Hobbis has suggested that Craig

Thompson and a fellow practical joker could be using a double trans-Pacific phone link to prove their prank. Maybe so, but it would be Telecom that was enjoying the last laugh!

How much cheaper and more practical it would be for a local amateur, on cue, to squirt 15 seconds of 2CH's program to someone on the other side of the Pacific? Illegal, of course, but I would judge that stranger things have happened, at times, on the amateur bands.

Again, might it not even be possible to simulate an international call from right here in Sydney, without letting on that you were really in the Hilton up the street?

So there you are Derek. We've dealt with your query after a mere two-year delay; we've supported accepted theory about the coverage of MW broadcast stations; we've recounted a joke, if it is a joke; and we've provided some publicity for Barry Spicer, which I'm sure he won't mind in the least!

A warning word

Incidentally, while searching for Derek Hobbis' original letter, I came across another one from the same period, which had been held over, mainly because we do, at times, have to terminate discussion on particular

subjects. But the matter raised in the letter is as relevant now as it was then. It is reproduced in the accompanying panel.

As you will note, the writer is concerned with the tendency for overseas tourists to snap up electrical or electronic "bargains", without even considering something as basic as the mains voltage on which they will have to operate.

At worst, they can end up with a 110V unit but, even if they buy something with a 220V rating, they still might not be out of the woods, for reasons which form the subject of the letter. I suggest you read it.

But now for a complete change of topic:

Hifi copper wire

An unnamed reader has sent me a photostat copy of an item in "New Scientist" for October 11, '84 entitled: "Hifi benefits from crystal-clear sound".

I quote:

"A development from Hitachi in Japan could make all existing quality sound recording and reproduction systems obsolete. The company is selling copper wire made up of long crystals which are free from oxygen."

It goes on to say that, without being able to offer reasons why, hifi

Asking for trouble: 220V equipment on 240V mains.

Without seeking to get involved in the question of the fire hazard supposedly presented by electronic equipment, I would like to draw attention to the fact that a lot of such equipment, purchased by tourists looking for duty-free bargains overseas, is unwittingly brought back into the country, without being checked to see whether it is compatible with Australian conditions.

My experience with appliances and electronic equipment brought to me, "blown up", for subsequent repair, indicates that manufacturers in Taiwan and Hong Kong, and to a lesser extent Japan, often use components which are "dead on" for the working voltage for which the particular equipment has been designed to operate.

This allows so little room for error, that the use of equipment designated as 220V AC on 240/250V AC mains is asking for trouble, especially in the case of cheap, sparingly designed apparatus.

I have measured secondary voltages from small transformers ranging between 13.7 and 16V AC instead of the required 12V RMS. My normal procedure is to replace such transformers with compatible 240/250V primary types, as well as replacing the capacitors, resistors, etc, that may have blown up.

Some mains switches are rated at 110V AC. No wonder the insulation breaks down, necessitating replacement with a more substantial type.

Capacitors seem to be the main loser in the ratings battle, having inadequate over-voltage tolerance. Diodes and bridge rectifiers also fall frequent victim to the higher peak voltages, when plugged into 240/250V mains. Strange to say, ICs seem to have some inherent protection of their own; rarely does a chip need to be replaced.

Hair dryers rated at 220V AC are prone to the loss of the rectifier diode (rated at 240V instead of 360V) which I replace with two 1000V diodes in series,

partly to alleviate the motor voltage.

I have lost count of the number of appliances, portable TV power leads, VCRs, cassette and record players, etc, which have been brought to me to have the moulded American style plugs and leads changed to the Australian equivalent. Just as well, because about a quarter of them turn out to be designed for 110/115V mains only. In such cases, the so-called savings on the duty-free articles are absorbed in the cost of the replacement transformer, lead and labour.


Presumably, a similar proportion of purchases "blow up" when non-technical buyers simply twist the American style flat pins and push them into an Australian 240V socket. EA readers would know better but non-technical friends should be warned to have their overseas "bargains" checked by a licensed electrician.

*K.B. Miranda, NSW.
(40 years a "sparks")*

Radio Despatch Service

ESTABLISHED 1934

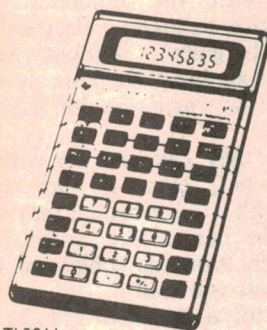1985 PROFESSIONAL & STUDENT CALCULATORS & COMPUTERS



Slimline TI-35™

The Student Calculator Math Book
• BASICS • TRIGONOMETRY
• POWERS & ROOTS • MEMORY
• STATISTICS • LOGS
• PARENTHESES

Basic to the Student math Dit is the powerful 54-function TI-35 slide rule calculator with Constant Memory® feature.


TI 3011.....	\$22.00	TI 5511.....	\$63.40
TI 30SLR.....	\$33.00	TI 57LCD.....	\$81.00
TI 35 SK.....	\$33.00	TI 166 Programmable.....	\$109.00
TI 35 Galaxy.....	\$42.00	BA 11 Executive.....	\$54.00
TI 140.....	\$36.00	BA55 Business Analysis.....	\$90.00
TI 1766.....	\$18.99	L.C.D. Programmer.....	\$75.00
TI 5020.....	\$57.00		

TI 99 4A HOME COMPUTER

(LIMITED STOCK)
ACCESSORIES INCLUDE

\$199.00

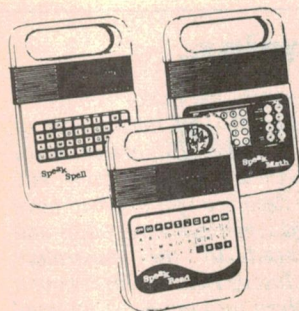Speech Synthesizer.....\$99.00
Terminal with Emulator II.....\$59.99
gives access of text to speech from user written programs
Touch Typing Tutor.....\$29.95
Educational, Entertainment and General Software
listing available on request.



SPEAK & SPELL*.....\$79.00
Brings spelling exercises to life.

SPEAK & READ*.....\$89.00
Introduces the wonderful world of words

SPEAK & MATH.....\$79.00
Correct answers praised, improvement encouraged.

* Extra modules available.....\$19.95

TOUCH & TELL \$79.00

LITTLE PROFESSOR \$25.00
Young Math students best friend


CASIO

Our vast range of products include favorites.

N.I.....	\$22.00	FX3600.....	\$52.50
MC 800.....	\$17.50	FX602P.....	\$115.00
FX39.....	\$24.95	FX702P.....	\$190.00
FX720P.....	\$133.00	FX802P.....	\$190.00

SCHOOL SPECIALS

FX 100 COLLEGE.....	\$32.50
• Scientific • LCD • 8 Digit mantissa • 2 Digit exponent	
• 42 Functions	
FX 550 48 Functions.....	\$35.00
FX 570 79 Functions.....	\$42.00
CASIO PB 410.....	\$124.50
FX 750P.....	\$208.50
PB 110.....	\$84.00

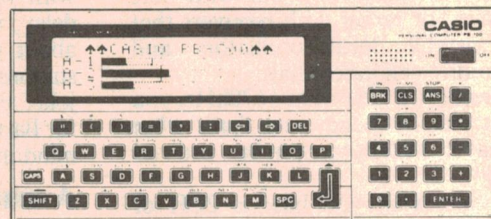

PB700—Top utility portable with big graphic display & large memory.\$250.00
(Peripheral expansion available)

FA 10-4 Colour graphic plotter printer with cassette interface\$344.50

FA4-Printer interface.....\$99.50

CM 1-Micro cassette tape recorder.....\$116.80

OR4-4KB Ram expansion pack.....\$60.00



V 212-20 mhz Dual Trace.....\$693.00
Listing of models available



Model 75.....\$160.00 Model 77.....\$200.00
Brochure available.


PLEASE CALL INTO OUR STORE AND COLLECT YOUR FREE CATALOGUE

Prices quoted include tax. We reserve the right to alter prices quoted without notice.

YES! WE HAVE MAIL AND PHONE ORDERS (PAULA JENKINS) AND USE BANKCARD, MASTERCARD AND AGC FINANCE. OR VISIT OUR STORE. We are closed on Public Holidays

Radio Despatch Service

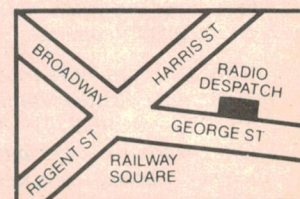869 GEORGE STREET SYDNEY 2000
TELEPHONES 211 0744 • 211 0816



FORUM — continued

enthusiasts have claimed for years that audio cabling can "colour" sound and that special cables can offer subtle improvements.

That cables introduce some electrical resistance is known and understood. It has been suggested, however, that if copper contains oxygen, oxide barriers may be present between adjacent crystals, causing partial rectification effects and modifying audio signals as a result. Cables made from oxygen-free copper would avoid this effect.

Reportedly, Hitachi has discovered that, by heating oxygen-free ingots of copper slowly, crystals are formed which are 10 times the size of those in normal copper. When drawn through a die to make cable, the crystals stretch rather than break, producing a possible 1000:1 reduction in the number of inter-crystal barriers. The item concludes:

"When this cable is wired into an audio system it is, as one audio critic put it, like lifting a veil from the sound."

At first reading, the news item might suggest that, prompted by the observations of audio zealots, Hitachi scientists have been researching the properties of copper and are now able to offer cable which actually exceeds purist expectations: not only free of oxygen but with a 1000:1 reduction in the number of inter-crystal barriers along its length.

Does this mean that the zealots have been right all along and that I, with many others, have egg on our faces? Well, not yet, anyway!

While I have frequently questioned statements and attitudes of the "golden ear" brigade, I have always left the way open for them to come up with objective support for their views. I said as much in the May '83 issue, repeated in September, p.115:

"The purveyors of deluxe and directional cable would have it made if they could only find someone from that

area (communication and cables) able to produce a rigorous engineering paper validating their claims. It would be a sensation!"

An invitation along these lines was repeated at the recent AES Melbourne Convention — without result.

But, if Hitachi has indeed succeeded in producing the "ideal" copper wire for audio cables, they should also be in an excellent position to provide the aforesaid "rigorous engineering paper", to validate any claims in respect to its performance. It would be a treatise that not even the most stubborn traditionalist could ignore.

But then I read the item again and realised that Hitachi may not have made any such claims or even had audio applications in mind. Quite possibly, their metallurgical research would have had to do with power generation and reticulation, in which the Company has a much bigger stake than in consumer audio.

Could it be that the reportedly new oxygen-free, long-crystal cable, developed for other reasons altogether, has been interpreted by an independent writer as a potential breakthrough in audio technology? From the way the original text reads, it would certainly seem to be a possibility.

Curiously, zealots have been claiming for some time that cables made from oxygen-free copper and installed with due attention to signal direction, open up a whole new world of sound; lifting a veil, as it were.

I can't help but wonder when the purists are going to run out of veils! Even Salome didn't have an unlimited supply!

In an effort to clarify the situation, I rang various outposts of the Hitachi empire in Sydney to try to track down the original news release about the long-crystal cable. No one had heard of it; no one could suggest anything other than I

write a letter to Hitachi in Japan, in the hope that it would find its way to the appropriate section.

Shades of my recent observations about our technological isolation!

In the meantime, rather than rely completely on my own intuition, I rang a friend, a university professor, who is well informed about such things. He had seen the item in "New Scientist" and did not taken it seriously — an opinion that he expressed in quite colourful terms!

Oxygen-free copper, he said, was important for its mechanical rather than its electrical properties. Oxygen atoms may combine with with hydrogen to produce water molecules, which can have a disruptive effect on the crystalline structure under certain physical conditions, producing a tendency to brittleness.

At the university, he said, they had the means to impose a signal with virtually zero distortion across a conductor and to measure extremely low levels of distortion in the resulting current. Distortion was plainly evident in a carbon resistor but they had never been able to observe it in a copper wire, despite all the talk about inter-crystalline junction effects. As far as they were concerned, in the context of audio, ordinary copper does not present a problem that requires a solution.

More than that I am not able to say, at this moment, although some other reader may possibly be able to shed light on the announcement which prompted the news item in "New Scientist".

If Hitachi have indeed come up with a new cable with objectively demonstrable advantages in audio equipment, it is important that we should know about it.

But, if its properties relate to some other application, we may have to brace ourselves for a new round of "veil lifting", no matter how irrelevant the fancy properties may be to audio. 2

ELECTRONICS AUSTRALIA
projects & circuits
\$4.50
Number 3, 1984
First printing

Transistor-assisted ignition system

Video amplifier for computers & VCRs

An easy-to-build photographic timer

Simple breath tester checks blood alcohol

MUSICOLOUR IV
10 YEAR EA PROJECT INDEX

projects & circuits

Number 3

THE CONTENTS:

Audio, Video Projects

Video Amplifier for Computers and VCRs; Video Enhancer; Vocal Canceller; Stereo Simulator for Tuners and VCRs; Guitar Booster for Stereo Amplifiers.

Power Supplies & Test Equipment Battery Saver for Personal Portables; Dual tracking $\pm 22V$ Power Supply; $3\frac{1}{2}$ -Digit LCD Capacitance Meter; In-Circuit Transistor Tester.

Mains Power Control Projects

Musicolour; Photographic Timer; Driveway Sentry; Touch-Lamp Dimmer.

Automotive Projects

Transistor-Assisted Ignition System; Breath Tester Checks Blood Alcohol Level; Low Fuel Warning Indicator; Speed Sentry for Cars; Audible Turn Signal Indicator.

Miscellaneous

Nail Finder; Portable $3\frac{1}{2}$ -Digit Heart rate Monitor; 10 Year EA Project Index.


Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017, **PRICE \$4.50** OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017, **PRICE \$5.40.**



GOODIES FOR THE HOLIDAYS...

SPECIALY SELECTED FOR YOU BY LITTLE DICK!!

ZIPPY BOX ROUND-UP TIME!

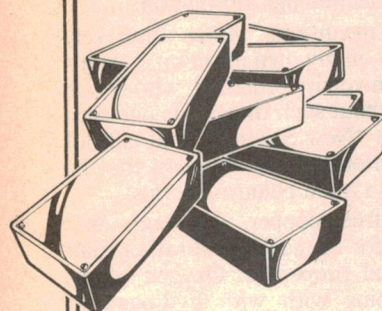

Summer projects are fun projects: but you'll need something to build them into! Your best choice is a Zippy Box: the original Zippy Boxes - and still the best, regardless of all those cheap and nasty imitations! Deep, full-length side ribbing for strength - and to let you mount PCB, etc without screws.

Dick Smith Electronics Zippy Boxes: the ones the magazines use!

Mini (29 x 54 x 83mm) Cat H-2755 **\$1.80** each
Midi (50 x 90 x 150mm) Cat H-2751 **\$2.80** each
Giant (60 x 113 x 196mm) Cat H-2752 **\$3.99** each

REMEMBER WHEN POTS DIDN'T MEAN ...

What a pot! Sliding-tap type ceramic pot with a massive 200 watt rating! A few of these and you could make a room heater ready for winter ... or audio dummy loads, etc etc. 150 ohms end to end, tap wherever you like.
Cat R-1999

\$2.95

Electronics Dickshunary

Everything you always wanted to know about electronics but were afraid to ask in case they thought you were a cretin. Now you'll be able to find out why a flip flop flips (or flops).
Cat B-3610 ONLY

\$9.95




SEE IN THE DARK WITHOUT CARROTS!

Lumi-Tabs: a great new invention helps you find that elusive power point or light switch even in the dead of night! Just stick them on or next to the p/p or switch - and they glow in the dark!!! Self-adhesive, luminescence lasts for yonks. Cat P-5350

\$1.99 pack

WANT A NEW POWER POINT TOO?

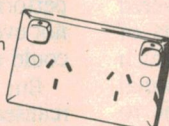Replace that single with a double: much more convenient! Then you can stick new Lumi-Tabs all around it! Standard double power point.
Cat P-5560



\$8.50


AND JUST IN CASE OF MISTAKES:

Check your power points with this fantastic little gizmo: 3-pin plug lights up to tell you if your power point is wired correctly, or if there's no earth, etc etc. Don't get fried: check that power point!
Cat P-5300



\$4.95

FABULOUS NEW BEARCAT DX-1000 RECEIVER!

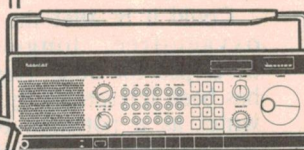

\$659.00

What a performer! What a magnificent set! And what a low, low price for today's up-to-the-minute technology! Look at what it offers for the low, low price:

- An amazing 10kHz to 30MHz range (yes, 10kHz!!!).
 - 10 memory channels INBUILT: nothing extra to buy!
 - AC or DC operation (also has DC memory back-up)
 - Better than 0.3uV sensitivity (800kHz up)
 - Push-button operation or manual tuning
 - Quality US made by Bearcat: the people who brought you Scanners!
- Call in today for a test drive. No obligation (we'll even give you a 'Little Dick' Sticker! Cat D-2830


GIVE YOUR CAR A PRESENT!

Fit a new Dick Smith top-of-the-line sound system - like this fantastic AM/FM/Stereo Cassette/Equaliser/Power Amp/Digital Clock/Etc! Yes, it's got THE LOT!

All this in a standard size unit (fits dash cut-out: throw out the junky model the manufacturers force on you and your ears will say 'thanks!') Cat A-6488



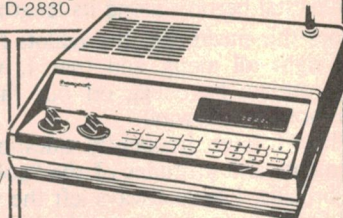\$225
BONUS!!! Choose EITHER a set of top quality co-axial speakers Cat A-7000 - value \$44.95! OR an electric car radio antenna (Cat A-7360 - value \$25.00)



A BUDGET SCANNER ... WITH DELUXE FEATURES!

Everything you could want in a scanner: 9 bands right up to 512MHz (also includes aircraft!), 16 programmable channels plus scan and search facilities ... and it operates from 12V so it's ideal for use mobile! (240V via optional adaptor). Catch all the action: with the Bearcat BC201F!
Cat D-2802

\$399

Optional AC adaptor to suit: Cat M-9530 \$22.50

HUGE SCOOP PURCHASE ... MANUFACTURER'S LOSS IS YOUR GAIN ... HURRY IN FOR THESE BARGAINS!

Save your good turntable and cartridge for your good records: let the kids use one of these! Your choice of quality magnetic or ceramic cartridge models, ready to go - motor runs off 12V. Way below manufacturer's price: just look at these!!!

Turntable with quality ADC magnetic cartridge. Cat A-3010

\$59.00

Turntable with ADC ceramic cartridge. Cat A-3015

\$27.50

HURRY! LIMITED STOCK ... IF YOU MISS OUT DON'T SAY YOU WEREN'T WARNED ... HURRY!



JUST A FEW LEFT: but hurry!

Our fantastic Strobe Flash innards bulk buy: probably about fifty bucks worth of bits: flashtube, reflector, dump capacitor, inverter, light metering circuitry, etc etc. Some work, some don't: but circuits are available for the experimenters. What a buy!

Have you ever tried to buy spares for your flash?
Cat J-1002 LIMITED STOCK

\$14.95

WIN YOUR CLUB A UHF REPEATER - AND AN AMATEUR STATION!

Buy any item of Yaesu amateur equipment from Dick Smith Electronics this month or next and you could be a winner!!! Over \$8000 worth of prizes ... details at your Dick Smith store.

SUMMER TIME IS PARTY TIME


And what's a party without the barbie, the pool and some coloured lights? We can't help you with the barbie or the pool - but if you want fantastic coloured lights, try these: PAR38 150 watt type (pressed glass construction with internal reflector), Edison Screw base floodlights in four colours.



\$7.85 EACH
(last for donkey's years)


BLUE GREEN YELLOW RED
Cat S-3854 Cat S-3856 Cat S-3850 Cat S-3852
E/S base to suit (aim where you like!) Cat P-5620 **\$6.25**

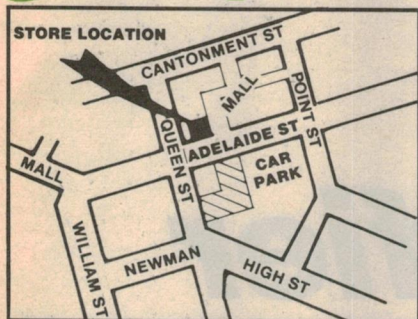More Stores to give you even better service.




FREMANTLE

66 Adelaide St
T.B.A.

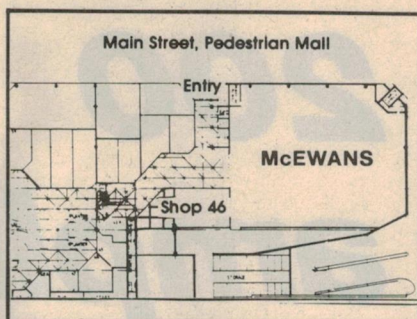

BOX HILL

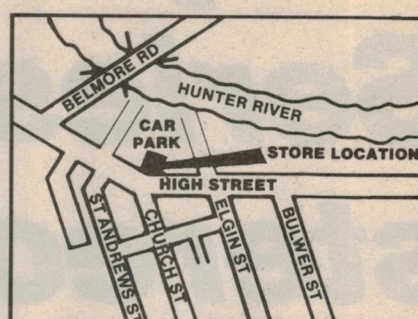Shop 46, Box Hill Central, Main St
Telephone: 890 0699



MAITLAND

450 High St
Telephone: 33 7866

STORE LOCATIONS

NSW

Cnr. Swift & Young Sts.
Parramatta Rd & Melton St
T55 Terrace Level
Shop 1, 65-75 Main St
613 Princess Hwy
Oxford & Adelaide Sts
531 Pittwater Rd
Campbelltown Mall, Queen St
Shop 3, 235 Archer St Entrance
147 Hume Hwy
162 Pacific Hwy
315 Mann St
4 Florence St
Elizabeth Dr & Bathurst St
450 High St
173 Maitland Rd, Tighes Hill
Lane Cove & Waterloo Rds
George & Smith Sts
The Gateway, High & Henry Sts
818 George St

Albury 21 8399
Auburn 648 0558
Bankstown Sq. 707 4888
Blacktown 671 7722
Blakehurst 546 7744
Bondi Junction 387 1444
Brookvale 93 0441
Campbelltown 27 2199
Chatswood Chase 411 1955
Chullora 642 8922
Gore Hill 439 5311
Gosford 25 0235
Hornsby 477 6633
Liverpool 600 9888
Maitland 33 7866
Newcastle 61 1896
North Ryde 88 3855
Parramatta 689 2188
Penrith 32 3400
Railway Sq 211 3777

6 Bridge St
125 York St
Tamworth Acde & Kable Ave
263 Keira St
ACT
96 Gladstone St
VIC
Creswick Rd & Webster St
145 McCrae St
Shop 46, Box Hill Central, Main St
Cnr Hawthorn Rd & Nepean Hwy
260 Sydney Rd
Nepean Hwy & Ross Smith Ave
205 Melbourne Rd
291-293 Elizabeth St
Bridge Rd & The Boulevarde
Springvale & Dandenong Rds
QLD
293 Adelaide St
166 Logan Rd

Sydney 27 5051
Sydney 267 9111
Tamworth 66 1961
Wellington 28 3800
Fyshwick 80 4944
Ballarat 31 5433
Bendigo 43 0388
Box Hill 890 0699
East Brighton 592 2366
Coburg 383 4455
Frankston 783 9144
Geelong 78 6766
Melbourne 67 9834
Richmond 428 1614
Springvale 547 0522
Brisbane 229 9377
Buranda 391 6233

Gympie & Hamilton Rds
Cnr Queen Elizabeth Dr & Bernard St
Cnr Gold Coast Hwy & Welch St
Bowen & Ruthven Sts
Ingham Rd & Cowley St. West End
SA
Wright & Market Sts
Main South & Flagstaff Rds
Main North Rd & Darlington St
24 Park Terrace
WA
Wharf St & Albany Hwy
66 Adelaide St
William St & Robinson Ave
Centenary Acde, Hay St
TAS
25 Barrack St
NT
17 Stuart Hwy

Chermside 359 6255
Rockhampton 27 9644
Southport 32 9863
Toowoomba 38 4300
Townsville 72 5722
Adelaide 212 1962
Darlington 298 8977
Enfield 260 6088
Salisbury 281 1593
Cannington 451 8666
Fremantle T.B.A.
Perth 328 6944
Perth 321 4357
Hobart 31 0800
Stuart Park 81 1977

Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days, or unforeseen circumstances might hold up shipments so that advertised lines are not in the stores by the time the advert appears. And very occasionally, an error might slip through our checks and appear in the advert (after all, we're human too!). Please don't blame the store manager or staff: they cannot solve a dock strike on the other side of the world, nor fix an error that's appeared in print. If you're about to drive across town to pick up an advertised line, why not play it safe and give them a call first... just in case! Thanks.

Dick Smith Electronics

MAJOR RESELLERS

These are independent businesses which stock a large range of Dick Smith Electronics products. However we cannot guarantee they will have these items or at the price advertised.

NSW — **Ballina:** A. Cummings & Co. 91-93 River St 86 2284 • **Bowral:** Barry Gash Electronics, 370 Bong Bong St 61 2577 • **Broken Hill:** Hobbies & Electronics, 37 Oxide St 88 4098 • **Charlestown:** Newtronics, 131 Pacific Hwy 43 9600 • **Coffs Harbour:** Coffs Harbour Electronics, 3 Coffs Plaza, Park Ave 52 5684 • **Deniliquin:** Deni Electronics, 220 Cressy St 81 3672 • **East Maitland:** East Maitland Electronics, 99 High St 33 7327 • **Gosford:** Tomorrows Electronics & HiFi, 68 William St 24 7246 • **Inverell:** Lyn Willing TV, 22A Evans St 22 1821 • **Lismore:** Decro Electronics, 3A/6-18 Carrington St 21 4137 • **Port Macquarie:** Hall of Electronics, Horton Centre, Horton St 83 7440 • **Orange:** M & W Electronics, 173 Summer St 62 6491 • **South Tweed Heads:** Shop 1, Inessa Court, Blundell Boulevard 36 1077 • **Swansea:** Swansea Electronics, 184 High St 71 1674 • **Wagga:** Wagga Wholesale Electronics, 89 Forsyth St • **VIC** — **Hamilton:** John Thompson & Co, 138-148 Gray St 72 2000 • **Echuca:** Webster Electronics, 220 Packenham St 82 2956 • **Mildura:** McWilliams Electronics, 110A Langtree Ave 23 6410 • **Morwell:** Morwell Electronics, 95 George St 34 6133 • **Shepparton:** G.V. Electronics Centre, 100 High St 21 8866 • **QLD** — **Atherton:** Maarten's Music Centre, 55 Main St 91 1208 • **Bundaberg:** P.M. Electronics, Takalvan St 72 8272 • **Cairns:** Electronic World Shop, 27 K-Mart, Westcourt Plaza, Mulgrave Rd 51 8555 • **Gladstone:** Purely Electronics Shop, 2 Cnr Herbert & Auckland Sts 72 4321 • **Mackay:** Stevens Electronics, 42 Victoria St 51 1723 • **Maryborough:** Keller Electronics, 218 Adelaide St 21 4559 • **Rockhampton:** Purely Electronics, 15 East St 21 058 • **SA** — **Mt Gambier:** Hutchesson's Comm. 5 Elizabeth St 25 6404 • **Whyalla:** Eyre Electronics, Shop 2 Forsythe St 45 4764 • **WA** — **Albany:** Micro Electronics, 133 Lockyer Ave 41 3432 • **TAS** — **Launceston:** Advanced Electronics, 5A The Quadrant 34 1399 • **NT** — **Darwin:** Ventrionics, 24-26 Cavanagh St 81 3491

HEAD OFFICE & DS XPRESS ORDER SERVICE

P.O. Box 321, North Ryde, N.S.W. 2113. Tel: 888 3200


SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone your order and Bankcard — it's so simple! (02) 888 2105 orders only on this number. Enquiries: (02) 888 3200

POST & PACKING CHARGES

Order Value	Charge	Order Value	Charge
\$ 5.00-\$ 9.99	\$2.00	\$50.00-\$99.99	\$6.00
\$10.00-\$24.99	\$3.50	\$100 or more	\$8.00
\$25.00-\$49.99	\$4.50		

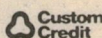Terms available to approved personal applicants



PTY LTD

(SA Credit facilities available through Custom Credit Corp. 422 King William St. Adelaide)

Introducing our new high power design **Playmaster** **Series 200** **stereo amplifier**

by LEO SIMPSON

Here is a stereo amplifier that will equal or better just about any integrated commercial amplifier, regardless of price. It is a no-compromise design capable of delivering 100 watts per channel at very low distortion.

It is with a great deal of satisfaction and some degree of relief that we at *Electronics Australia* can finally present this series of articles on our new integrated stereo amplifier. This project has been over a year in development although this has naturally been far more intense over the last few months.


And now that it has finally eventuated, we are very proud of our new amplifier. In quite a few respects, this new amplifier represents a major advance over previous Playmaster amplifiers which in themselves were very successful designs.


As well as providing high power and

very low distortion, the new Playmaster design provides much better control facilities. It is also considerably easier to build but perhaps you, the reader, will be the best judge of this last aspect.

Let us briefly consider some of the features of the new amplifier. Perhaps this should be done while looking at the accompanying block diagram which shows all the control features of the design.

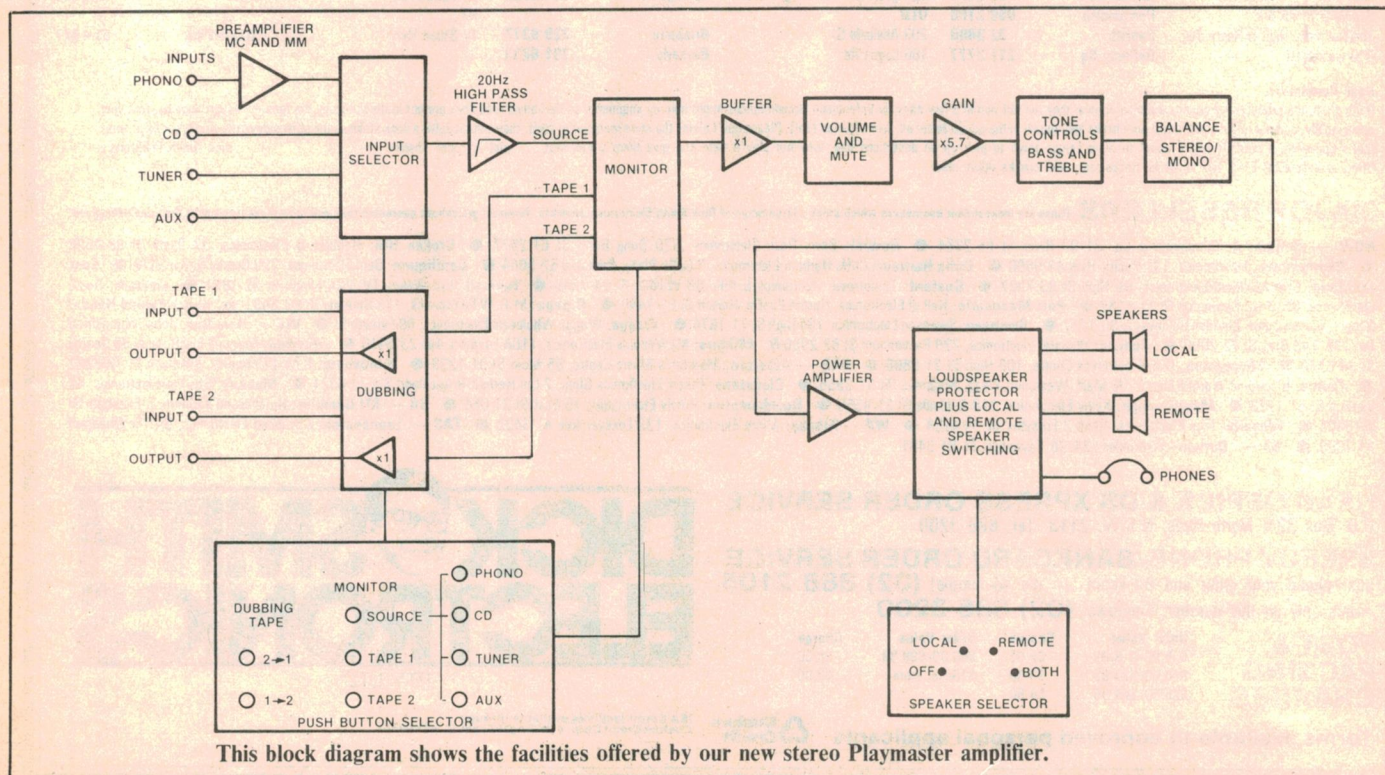As with most amplifiers these days, there are four basic stereo inputs. Both moving magnet and moving coil cartridges are catered for, by virtue of a rotary switch of the back on the amplifier which changes the gain and input impedance of the phono input.



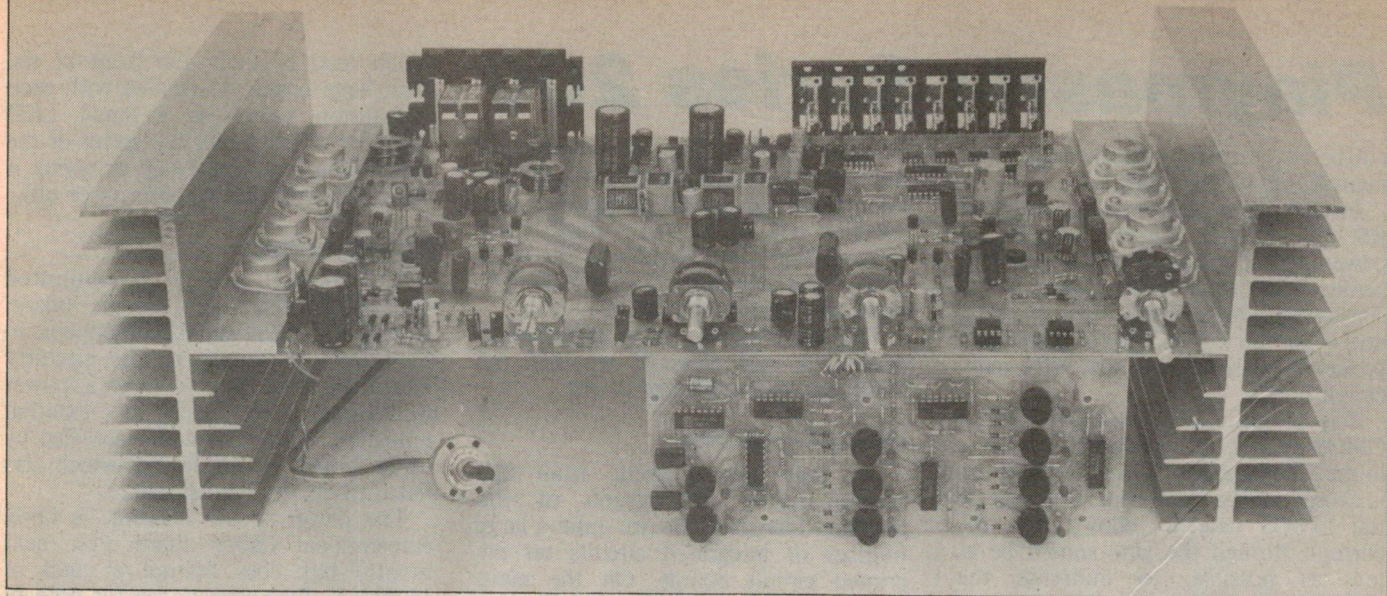

This is what the amplifier will look like before the chassis is assembled. Note the heavy duty heatsinks.

Three high level stereo inputs are provided, for compact disc (CD) player, AM/FM tuner and an auxiliary input which could be from a stereo TV tuner or hifi VCR. All three high level inputs have a degree of performance which ensures negligible degradation of the signal quality available from a compact disc player or other digital source such as laser disc player or PCM adaptor.

Input facilities are also provided for two stereo cassette decks and full monitoring facilities are available for either deck plus dubbing from deck 1 to deck 2 or from deck 2 to deck 1.

Two pairs of loudspeakers are provided for and these may be used both together or separately, or both may be switched off. Nor is there any of the funny business resorted to in some amplifier designs whereby the two pairs of speakers are connected in series or via a low value resistor. Either measure degrades the damping provided by the amplifier and is highly undesirable.

The terminals provided for the loudspeaker connections are the same as found on many commercial stereo amplifiers these days. They are a twist-type binding post which takes bared wire connections, giving a secure, low resistance connection. A particular virtue of these loudspeaker terminals is that the connections are completely shrouded by the terminal so that there is no chance of accidental shorts or shocks to the user. They look good too.

Naturally there is a 6.5mm jack socket on the front panel for connection of the pair of stereo headphones. Either high or low impedance headphones may be used.

Physically, the amplifier is quite large. Its overall dimensions are 483mm wide, 150mm high and about 290mm deep, including knobs and rear projections such as the loudspeaker terminals.

The main reason why the new amplifier is so bulky is the size of the

large heatsink on each side. These specially tooled aluminium extrusions are necessary to cope with the large amount of heat produced when the amplifier is running under "worst case dissipation" conditions. Normally of course, the heatsinks merely become warm to the touch.

While the large heatsink extrusions determine the height and depth of the new amplifier, the width was determined by the requirement that the new unit match the width of rack-mounting equipment, ie, 483mm. A look at the prototype unit will also reveal that the width was necessary to accommodate all the circuitry on the single large printed circuit board.

Design philosophy

One of the major difficulties in the presentation of a new amplifier is that it must be seen to be appreciably better than its predecessor. In a sense, this is no different from any other consumer durable product; the new model must be different and therefore better than the old.

So our problem was this: how do we produce a new amplifier which is substantially better than the previous two successful units, viz, the Playmaster Forty/Forty described in December 1976 and January 1977 and the Playmaster Mosfet stereo amplifier described in December 1980 and following months.

We decided that the Playmaster Mosfet model must represent the end of the line of development in its basic design philosophy, range of operating facilities and method of construction.

We had to come up with something considerably better. And that is easier said than done.

Logically, the best way to improve upon an existing design is to ask what is wrong with it and then see if it can be improved. Both the previous two designs

had a single large printed circuit board which accommodated all the electronic components. This was good but it still left a lot of wiring to be performed by the constructor. All the input wiring required shielded cable which is very tedious to cut, strip, solder and strap neatly into place. So that was one of our major requirements: eliminate as much wiring as possible.

When taken in conjunction with the general and very desirable requirement that the overall performance standard must be improved, a complete rethink of the design approach was needed.

Starting right at the input sockets, we decided that we had to use a moulded RCA input socket assembly which soldered directly to the printed circuit board. This eliminates the need for shielded cable but then raises the next problem: how to select the inputs and provide the fancy switching for mode selection, tape monitoring and dubbing from deck to deck.

The refined Japanese stereo amplifiers solve these problems elegantly by the use of multiple position slide switches soldered directly to the printed circuit board and operated by flat Bowden cables from the front panel controls. Plainly, we could not take that approach.

CMOS switching appeared to be the way out. CMOS analog switch ICs are cheap, readily available and can be arranged in several different configurations to suit the required facilities. Two problems presented themselves. First, CMOS switches can be a source of distortion and second, some sort of memory system was required so that switch selections would be remembered when the amplifier was turned off. The fancy way to do this would be to have a semiconductor memory or perhaps even a microprocessor to control it all. Once again, we were not going to take that

Playmaster Series 200

route although some Japanese manufacturers have done so.

Instead, we elected to use a number of RS and D-type flipflops which are powered by a couple of nickel cadmium penlite cells when the amplifier is off. This is neat and does not involve a great deal of circuitry. The dual cell holder can be seen roughly in the centre of the main circuit board.

The problem of non-linearity in the CMOS gates (read: switches) is overcome in the following way. Since the distortion is caused by the non-linear resistance of the CMOS gate it follows that the current through the gate should be as low as possible, to minimise the distortion signals generated.

This is achieved by buffering the output of each CMOS gate with a unity gain amplifier which has a high input impedance. Thus very little signal current flows and the resultant distortion due to the CMOS gates is negligible. It does mean that we have had to use a lot of op amps to do all this buffering but multiple op amp IC packages are cheap. They can also be configured in very low-noise, low distortion stages. So that was the ideal way to go for our design.

Loudspeaker switching

Having solved the problem of input wiring and switching, we then had to come up with a solution for the loudspeaker switching. Again, we did not want to have heavy loudspeaker wiring running to and from the front panel selector switch to the output terminals. We also had to face the question of current rating for the loudspeaker selector switch. When the amplifier is running at full power, the output currents are of the order of 10 amps peak (for a 4-ohm load). Rugged switches capable of reliably switching these orders of current are very expensive and not readily available.

Our solution was to use relays, one for each pair of loudspeakers. The two relays are controlled by the circuitry which

provides initial muting and protection in the event of an internal DC fault. At the same time, the actual loudspeaker pair selection (via the relays) is made via a conventional rotary switch on the front panel. This switch carries only the DC energising current for the relay coils.

The headphone socket is permanently connected, regardless of whether the loudspeakers are selected or not.

Circuit features

As may be apparent from the accompanying photograph of the amplifier chassis, there are quite a large number of integrated circuits on the printed circuit boards. On the main board, most of these ICs are low noise, operational amplifiers which, depending on the circuit application, are either FET-input types such as the TL071, or the bipolar type Signetics 5534.

We have not used discrete transistors for any of the low level input circuitry, apart from those used in conjunction with op amps in the phono preamplifiers.

A particular feature of the phono preamplifiers which should be mentioned is that they use high tolerance components in the negative feedback loop to ensure very accurate RIAA equalisation.

We will talk in more detail about the low level circuitry next month.

All the control potentiometers have a nice feature: detents. The bass, treble and balance controls have a centre detent which is desirable when you wish to centre the balance control or set the tone controls to the flat settings.

Better still, the volume control has multiple detents which make it very easy to repeat any desired volume control setting.

Another desirable feature of these pots is that they are all printed circuit mounting types which eliminates control wiring.

A similar comment can be made about the pushbutton controls. These are all momentary contact switches which are soldered directly to the vertical board,

which mounts under the front of the main large board. Associated with each pushbutton switch is a small LED indicator which shows the status of the switch (this is a fancy way of saying it shows whether the switch is on or off).

Power supply

The power supply is mounted underneath the main circuit board. Having the power supply components in such close proximity to the circuitry meant that we had to have a power transformer with a very low external hum field. This condition is satisfied by using a toroidal transformer which also has the benefit of small size.

The power supply circuitry is fairly conventional (more about that next month) but does feature a total of 16,000 μ F filter capacitance for both of the main balanced supply rails.

The power amplifiers.

Included with this article is the circuit used for the power amplifiers. Readers with long memories may conclude that it is very similar to that used in the previous Playmaster Mosfet stereo amplifier and also in the 100W subwoofer amplifier described in the July 1982 issue of *Electronics Australia*.

That impression is correct but while the circuit is very similar, the performance is not. The harmonic distortion is much improved, particularly compared with the Playmaster Mosfet design. Measured THD of the prototype design power amplifiers was less than .01%.

Our decision to use this design, which is based on Hitachi application notes, did not come easily. Indeed most of the development of this amplifier revolved around the power amplifiers.

We tried many different circuits and configurations. Some were completely symmetrical designs with double-differential input stages and so on. Cascode driver stages were tried as was source degeneration in the Mosfet output stages. Also researched was the effect of varying the driver stage currents to obtain the best overall distortion and slew rate.

After all this, we still concluded that the Hitachi design was the best overall for simplicity and performance. But one point became outstandingly clear: the performance was very dependent on the layout of the printed circuit board.

Even quite subtle changes in layout made quite dramatic reductions in the distortion performance. And as luck would have it, these changes were almost always for the worst. In other words, the design is very cranky as far as the layout is concerned.


Now let us run through the

MAIN FEATURES OF THE NEW PLAYMASTER

- Switchable phono inputs for MM and MC cartridges
- Electronic signal switching
- Full facilities for dubbing between two cassette decks
- Monitor loop for either of two cassette decks or a signal processor
- Click action pushbutton switches for selection of input sources, dubbing and tape monitor with LED status indicators
- Centre detents on bass, treble and balance controls; multiple

detents on volume control

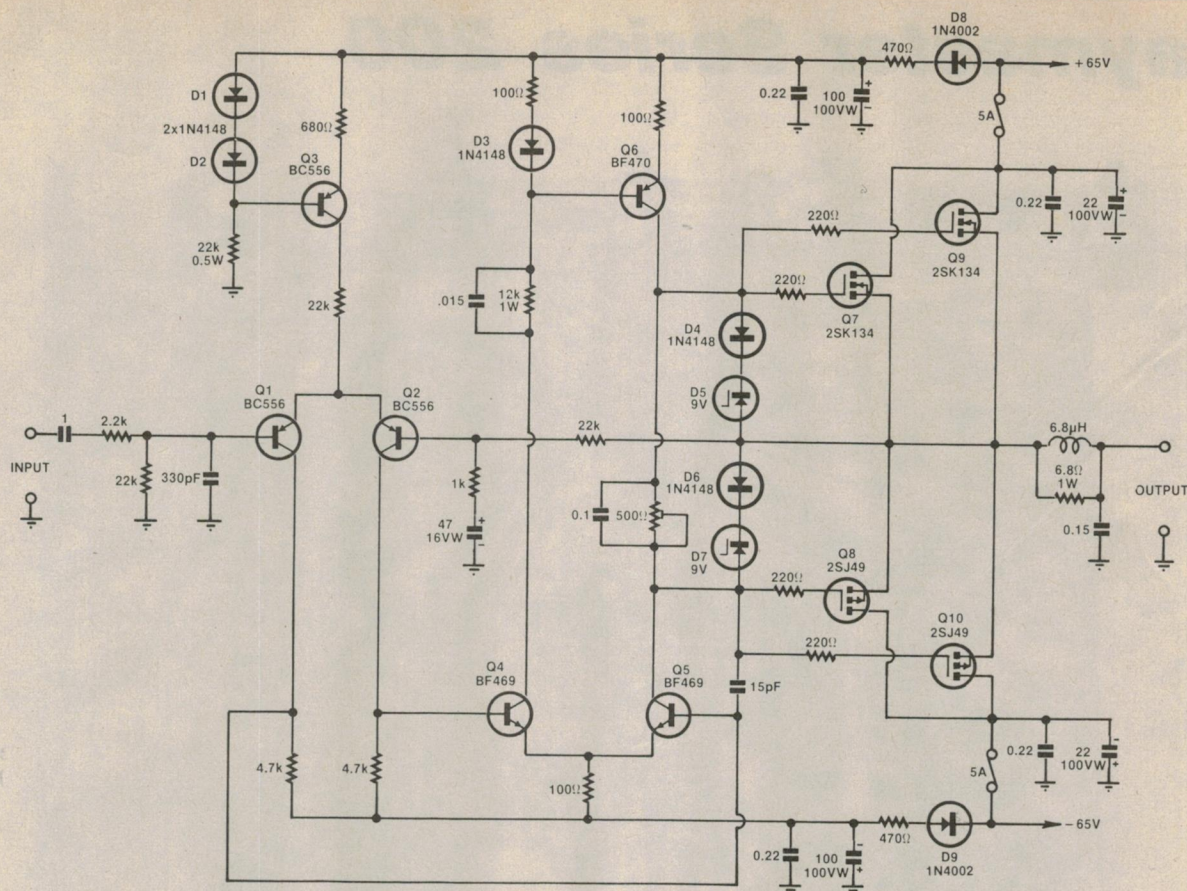- Heavy duty heatsinks
- Toroidal power transformer for low hum and noise.
- Easy to build construction — all parts except power supply mount directly on the two printed circuit boards; wiring has been kept to an absolute minimum
- 100 watts RMS per channel into 8 ohm loads
- Less than .01% total harmonic distortion.



This is the circuit of the power amplifiers used in our new Playmaster design.

description of the power amplifier circuit.

The input signal to the amplifier ranges up to about 1.5 volts RMS for full power and is coupled via a $1\mu\text{F}$ metallised polyester capacitor and a $2.2\text{k}\Omega$ resistor which, in conjunction with the 330pF shunt capacitor, acts as a low-pass filter, to remove high frequency signals in the RF region. The $2.2\text{k}\Omega$ resistor also tends to act as a "stopper", reducing the possibility of the amplifier to oscillate supersonically.

Q1 and Q2 form a differential pair with Q3 acting as a constant current "tail". By virtue of the diodes, D1 and D2, the base bias applied to Q3 is about 1.3 volts. This sets the current through Q3 at around one milliamp and this is shared equally through Q1 and Q2.

There is one major reason for the inclusion of Q3 as a constant current source. It improves the power supply rejection of the amplifier. In op amp specifications this is referred to as PSRR (power supply rejection ratio). The better the PSRR, the less likely is the amplifier to respond to variations in the power supply rails which may include large ripple signals (hum) or harmonics of the input signal (which could lead to higher harmonic distortion).

The balanced output signals from the collector load resistors ($4.7\text{k}\Omega$) of Q1 and Q2 are coupled to a second differential amplifier consisting of Q4 and Q5. These have an unconventional dynamic load in the form of a "current mirror" which is often used in integrated circuit op amps.

The current mirror (Q6) can be regarded as performing much the same function as a constant-current load for Q5 would do. That is, consider Q6 as a constant current source, with D3 applying its base bias. The mechanism is actually a little more complicated than that since there is a 100Ω resistor in series with D3. This means that signal variations at the collector of Q4 are reflected as small changes in bias at the base of Q6.

The net effect of the current mirror scheme is to give higher gain from the stage and better overall linearity over the full voltage swing. It also gives a greater voltage swing than could be obtained with a simple class-A driver stage with a boot-strapped collector load.

Q4, Q5 and Q6 have a collector voltage rating of 250V and are intended specifically for class-B video driver stages in television receivers. As such, they are ideally suited for use in low distortion driver stages as they have an excellent

gain-bandwidth product of 100MHz and good beta linearity over a wide range of operating currents.


The two differential stages provide all the voltage gain of the power amplifier with the Mosfet output stage operated in source-follower mode (which gives slightly less than unity voltage gain, similar to emitter followers).

No source degeneration resistors are used in the Mosfet output circuits. We found that we were able to dispense with these and thus gain better distortion figures. This is in line with the circuit practice adopted in the very good amplifiers produced by Perreux of New Zealand.

Nor does there appear to be any need to take measures to ensure current sharing between the parallel-connected Mosfets (by using small source resistors). In practice, if one Mosfet becomes hotter than its partner its transconductance is reduced accordingly and thus it is throttled back automatically.

The 500Ω trimpot connected between the collectors of Q5 and Q6 sets the quiescent bias applied to the Mosfet gates. The bias sets the quiescent current. The current chosen is a compromise between minimum distortion and the amount of power

Playmaster Series 200

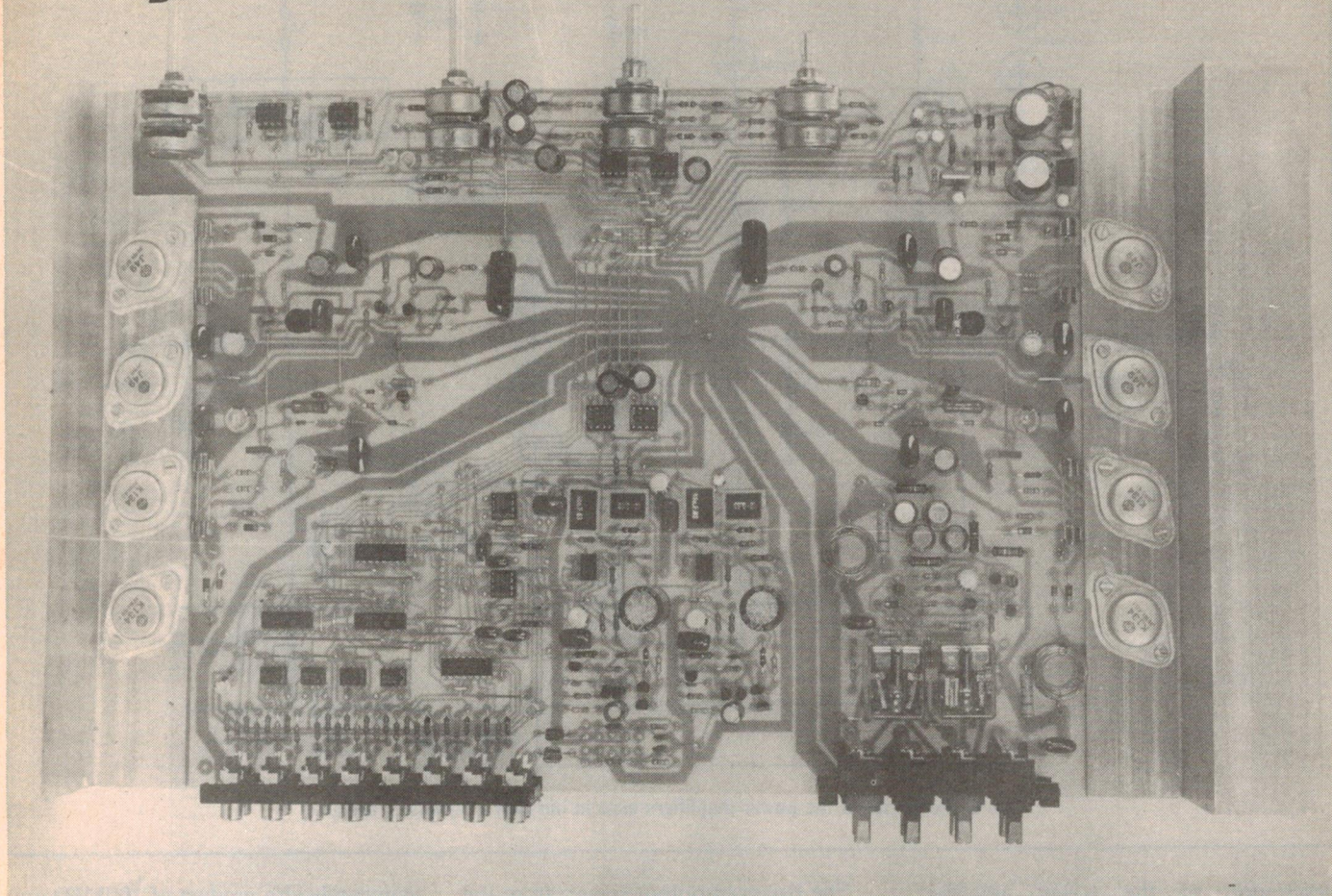

This bird's eye view shows how the printed circuit has been laid out to avoid earth loops and common impedance paths.

dissipation produced by the output stage. Since the power amplifier employs supply rails of $\pm 65\text{VDC}$, even a relatively small current results in relatively high power dissipation.

Zener diodes D5 and D7, in series with D4 and D6, set the maximum signal level which can be delivered to the Mosfet gates. Any signal in excess of $\pm 10\text{V}$ will be clipped. Thus the diodes form an effective overdrive circuit and prevent excessive power dissipation in the event of a short circuit.

220 Ω resistors are connected in series

The control pushbuttons are all soldered directly to the vertical board.

with the gate of each Mosfet to function as "stoppers" and prevent oscillation at radio frequencies.

Apart from the over-drive protection already mentioned, there is no active protection circuitry in the output stage. Fuses are included in the supply lines to protect against catastrophic device failure.

The supply fuses also provide a convenient current monitoring facility (when replaced by resistors) for troubleshooting or setting the quiescent current.

Single-pole lag frequency com-


pensation is applied from the base to the collector of Q5 via a 15pF capacitor. This renders the amplifier stable with the overall negative feedback applied.

Voltage gain of the power amplifier is determined by the ratio of the 22k Ω and 1k Ω resistors at the base of Q2. The lower cutoff frequency of the circuit is set by the 47 μF capacitor in series with the 2.2k Ω resistor.

A final refinement involves the RLC network in the output circuit. This has been a feature of Playmaster designs since 1976 and is based on a paper by A.N. Thiele in the September 1975 issue of Proceedings of the IREE. The network is incorporated to render the amplifier unconditionally stable.

The particular refinement we have made to the RLC network is to use an air-cored inductor instead of one wound on a ferrite rod. We have found that the ferrite core is a source of distortion, particularly during high power operation.

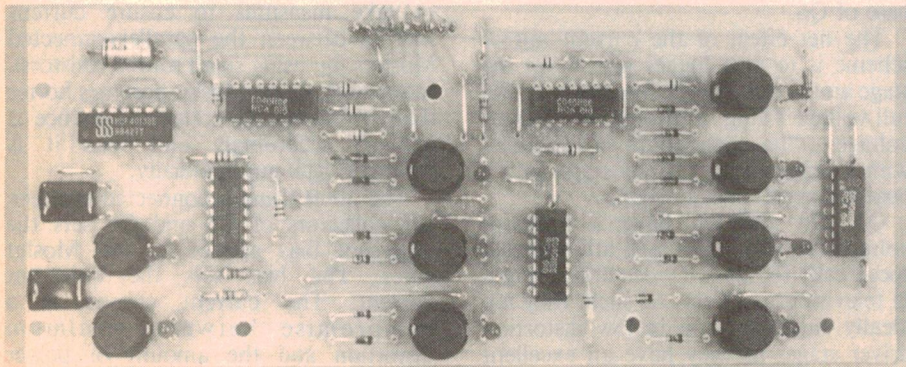In the next article we will continue with the description of the rest of the amplifier circuit and give the full specifications.






CANNON TYPE AUDIO CONNECTIONS

We've sold 1000's because of their great value!!

3 Pin line male	1-9	10+
Cat. P10960	\$1.90	\$1.80
3 Pin chassis male		
Cat. P10962	\$1.90	\$1.80
3 Pin line female		
Cat. P10964	\$2.50	\$2.10
3 pin chassis female		
Cat. P10966	\$2.90	\$2.20

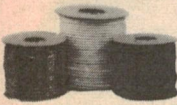

BULK CABLE 100M ROLLS

Cat. W11222	3C2V75 OHM	\$22.00
Cat. W11224	5C2V75 OHM	\$35.00
Cat. W11219	4 Core Shielded	\$49.00



MINI MODEM

300 baud full duplex
Answer originate
Plugs straight in (hardwired phone)
Superior VLSI chip performance (identical to Multi Modem)
Telecom Approval (C84/37/1173)
Incl. phone only \$199

ALUMINIUM SHEETS

CAT	SIZE	PRICE
H10770	150x150mm	\$1.75
H10771	150x300mm	\$2.50
H10772	300x300mm	\$3.95
H10773	300x600mm	\$6.90



HEX KEY PAD

19 Keys, Unencoded, 76 x 95mm
Cat. K46804 \$42.50



RECHARGEABLE 12V GELL BATTERIES

Leakproof and in 3 convenient sizes, these long service life batteries are ideal for burglar systems, emergency lighting or as a computer backup power supply. Ideal for many power needs.

Cat. S15029	12V 1.2 AH	\$17.95
Cat. S15031	12V 2.6 AH	\$34.50
Cat. S15033	12V 4.5 AH	\$44.95



INCREASE YOUR MEMORY

4116	1-9	10+
4164	1.80	1.70
2716	6.25	5.95
2732	6.25	5.95
2764	8.25	7.95
27128	27.00	25.00
6116	6.95	6.75

*** SCOOP ***



PRIME SPEC RED LEDs

We bought 100,000 so you can reap the benefits!

1-9	10-99	100+
\$0.10	\$0.09	\$0.08

Cat. Z10150




NEW SLOPING CASES

Plastic with metal front panel, available in two sizes:

Cat.H10450	190x120mm	\$9.95
Cat.H10455	265x185mm	\$17.95


(measurements are approx. only)

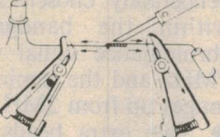

HEAT STOPPERS


For protecting parts which have little resistance against heat when soldering. Normally \$3.50.

Cat. T12440	\$2.50
-------------	--------

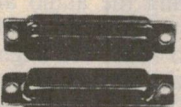

RS232 & 'D' TYPE CONNECTORS

PART	DESCRIP.	CAT. NO.
DE 9P	9 Pin Female	P10880
DE 9S	9 Pin Male	P10881
DE 9C	9 Pin Cover	P10882
DA 15P	15 Pin Male	P10894
DA 15S	15 Pin Female	P10895
DA 15C	15 Pin Cover	P10892
DB 25P	25 Pin Male	P10900
DB 25S	25 Pin Female	P10901
DB 25C	25 Pin Cover	P10902

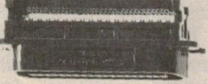

36 WAY CENTRONICS CRIMP PLUG

Cat. P12200		
1-9	10-99	100+
\$6.50	\$5.95	\$5.50



SOLDER CENTRONICS PLUGS

Unreal price for absolute top quality. Normally \$14.95 (Our opposition charge up to \$19.95)

1-9	10+	100+
\$6.95	\$5.95	\$4.95



CENTRE RETURN JOYSTICK


Features 2 x 150K pots, long shaft 40mm with 25mm control ball. Bonus adjustable offset feature on pots

Cat. X15637	1-9	10+
\$9.95	\$8.95	



PIPER MOUSE ROBOT

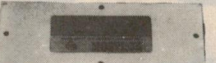This is a Super-Sonic robot, controlled by a super-sonic sound sensor and an electronic circuit. (1 channel). By using the whistle included with this Kit, Piper Mouse will obey your commands immediately turning to the left, stop, turning to the right, stop, advance and stop. Cat. K96680 \$34.95



SWITCH MODE POWER SUPPLY

DC +5V @ 5A, +12V @ 4A, DC -5V @ 5A, -12V @ 4A. Cat. M16680 \$129



JUMPER LEADS


Set of 10 high quality leads approx. 450mm long. Normally \$4.95. Cat. W12000 \$2.95



NICAD BATTERIES


Save on carbon batteries with these Appolon Nickel Cadmiums. Rechargeable up to 1000 times!

Cat. S150020	AA500 MA	
Cat. S15021	C 1.8 AH	
Cat. S15022	D 4 AH	
1-9	10+	
\$2.25	\$1.95	
\$4.95	\$3.95	
\$7.95	\$6.95	

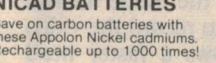

IC SOCKETS (LOW PROFILE) How cheap can they go??

1+	10+	100+	1000+
8 pin Cat	15c	14c	09c
14 pin Cat	16c	15c	10c
16 pin Cat	17c	16c	11c
18 pin Cat	18c	17c	13c
20 pin Cat	29c	28c	27c
24 pin Cat	35c	33c	28c
40 pin Cat	45c	40c	30c

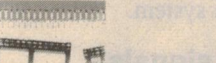


NEW JOINABLE PCB MOUNTING SCREW TERMINALS

Less than half the price of the old ones!

2 way	1-9	10+
Cat. P10542	\$0.50	\$0.40
3 way		
Cat. P10543	\$0.75	\$0.65

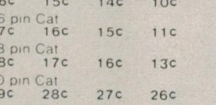(please note these are the new blue ones)



LOGIC PROBE 3800A

Features 20MHz memory TTL CMOS operation Normally \$29.50 now only \$19.50

Cat. Q11272	1-9	10+
\$19.50	\$17.50	



APPLE JOYSTICKS

Ideal for games or word processing Fits most 6502 "compatible" computers

Cat. C14200	\$19.50
-------------	---------



VERBATIM DISKS

"Lowest" price possible for "Highest" quality.

1-9	10+	100+
MD525-01	3.95	2.75
MD550-01	4.50	3.95



RELAY AND BASE

Can carry 10A at 28V DC or 5A at 240V AC. Supplied with Chassis Mounting Socket with screw terminals. Great for school projects and demonstrations, switching DC power supplies, central circuits and with contacts parallel up to 20A can be switched. Normally \$8.95

Cat. S14074	This month	\$6.95
-------------	------------	--------



ELECTRONIC CASSETTE DEMAGNETISER

Save \$2. Rec. retail \$19.95


Cat. A10006	This month	\$17.95
-------------	------------	---------



ECONOMY TOGGLE SWITCHES

Unbelievable Value!

1-9	10+	100+
S11010, SPDT	\$1.00	\$0.90
S11020, DPDT	\$1.20	\$1.00

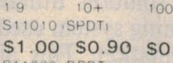


10,000uF 75V ELECTROS

25% more microFarads! Ideal for those who want a more powerful amp!

1-9	10+
\$10.50	\$9.00

Cat. R16587

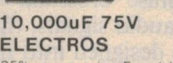

NEW JOINABLE PCB MOUNTING SCREW TERMINALS

Less than half the price of the old ones!

2 way	1-9	10+
Cat. P10542	\$0.50	\$0.40
3 way		
Cat. P10543	\$0.75	\$0.65


(please note these are the new blue ones)



LOGIC PROBE 3800A

Features 20MHz memory TTL CMOS operation Normally \$29.50 now only \$19.50

Cat. Q11272	1-9	10+
\$19.50	\$17.50	

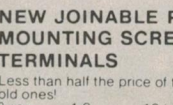

LOGIC PROBE 3800A

Features 20MHz memory TTL CMOS operation Normally \$29.50 now only \$19.50


Cat. Q11272	1-9	10+
\$19.50	\$17.50	



LOGIC PROBE 3800A

Features 20MHz memory TTL CMOS operation Normally \$29.50 now only \$19.50

Cat. Q11272	1-9	10+
\$19.50	\$17.50	

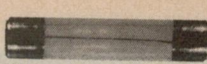

FUSE SPECIAL 3AG

Two values, 3 Amp and 1 Amp
1-99 100-999 1,000+

8¢ each	6¢ each	5¢ each
---------	---------	---------

STOCK UP NOW



PHILLIPS SPEAKER SPECIAL

Cat. C12030 AD01610 T8


Cat. C12040 AD02160 S08	\$12.95
-------------------------	---------

Cat. C12045 AD70620 M8	\$34.95
------------------------	---------

Cat. C12050 AD12550 W8	\$49.00
------------------------	---------

	\$79.00
--	---------

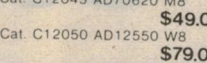You don't have to "imagine" Phillips quality at these prices!



SUPER HORN

Wide dispersion tweeter, handles up to 100W
Sensitivity: 105dB/0.5m
Frequency Response: 3kHz-30kHz
Impedance: 8 OHMS
Size: 145x54mm

Cat. C12103	\$12.95
-------------	---------



SUPER HORN TWEETER

Requires no crossover and handles up to 100W
Sensitivity: 100dB/0.5m
Frequency Response: 3kHz-30kHz
Impedance: 8 OHMS
Size: 96mm diameter

Cat. C12102	\$11.95
-------------	---------

(Rec. Retail \$12.95)




CAR ANTENNAS

We stock a wide range of car antennas including auto up/down antennas.

Cat. C12102	\$11.95
-------------	---------

(Rec. Retail \$12.95)

 


BLANK DATA CASSETTES

Brings out the best in any micro!

1-9	10-99	100
\$1.10	\$1.00	\$0.90

Cat. D11141

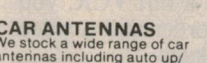

FULL STRENGTH FERRIC CHLORIDE

This month only!

250ml	1-9	10+
\$1.95	\$1.75	

500ml	\$2.95	\$2.50
-------	--------	--------

1 litre	\$4.95	\$4.50
---------	--------	--------

Cat. D11141



BULK 'IC' SPECIALS

LM 324	10+	100+	1000+
\$0.70	\$0.65	\$0.60	
LM339	\$0.70	\$0.65	\$0.60
LM555	\$0.40	\$0.39	\$0.35
LM723	\$0.60	\$0.55	\$0.53
LM741	\$0.45	\$0.40	\$0.37
LM1458	\$0.80	\$0.70	\$0.65
LM1488	\$0.60	\$0.57	\$0.55
LM1489	\$0.60	\$0.57	\$0.55



Rod Irving Electronics

425 HIGH STREET,
NORTHCOTE VICTORIA.
Ph:(03)489 8866 489 8131
48-50 A'BECKETT STREET,
MELBOURNE VICTORIA.
PH:(03)347 9251
Mail Order and
correspondence:
P.O. Box 235
NORTHCOTE 3070


YOU WON'T GET BORED OVER THE HOLIDAYS WITH THESE GREAT SPECIALS!!
GREAT 'IN STORE' BAR-GAINS TOO!
Call in at either 2 of our conveniently located stores:
48-50 A'Beckett St., Melbourne
425 High St., Northcote.
Or take advantage of our Mail Order Department.
Write to:

MAIL ORDER DEPT.
ROD IRVING ELECTRONICS
P.O. BOX 235
NORTHCOTE VIC.

or phone ...

MAIL ORDER HOT LINE

481 1436

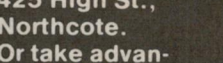

welcome here

POSTAGE RATES

\$1-\$9.99	\$1.50
------------	--------

\$10-\$24.99	\$2.00
--------------	--------

\$25-\$49.99	\$3.00
--------------	--------

\$50-\$99.99	\$3.50
--------------	--------

\$100-\$199	\$5.00
-------------	--------

\$200-\$499	\$7.50
-------------	--------

\$500 plus	\$10.00
------------	---------

PROJECT ELECTRONICS

Here are 11 great projects for the beginners from the ETI Project Electronics publication

National NV-850A hifi stereo VCR

A new era in video sound has arrived. The latest hifi video cassette recorders deliver hifi stereo sound with performance approaching that of compact discs. The NV-850-A VHS hifi VCR from National is representative of this new technology.

The biggest disadvantage of VCRs in the past has been their poor sound quality. This situation has now changed following the introduction of stereo hifi VCRs by both the VHS and Beta camps. Now, for the first time, video recorders are able to record and play in hifi stereo sound.

As an audio recorder, a hifi VCR offers much better sound quality than a conventional cassette deck. Hifi VCRs have a wider dynamic range, lower noise and distortion, improved bandwidth characteristics, and much less wow and flutter. By investing in a hifi VCR, you get a superb audio recorder and a video recorder all in one package.

Of course, to derive the benefits that a hifi VCR has to offer, a stereo amplifier and good quality speakers must be used. For the enthusiast, the new technology opens the way to a new range of pre-recorded movies with hifi sound quality.

Considerable ingenuity has gone into the development of the hifi VCRs. They

need to preserve compatibility with existing tapes and yet clearly the conventional linear track at the edge of the tape, reserved for audio, is inadequate for hifi. The combination of narrow track width and slow tape speed produce high noise, distortion and a narrow frequency response.

To obtain hifi sound, the track width needs to be wider and the relative speed of the head across the tape increased. The solution utilises the same helical scanning system used to record the video information. This allows a faster head speed by tracking transversely across the tape width.

Both audio and video information are recorded onto the same track area. To minimise crosstalk between the video and audio signals, three safeguards have been designed into the system.

Twin carrier FM signals

- In the case of VHS, the left and right channel signals are frequency modulated


on to two carriers, centred on 1MHz and 2MHz. These carrier frequencies were deliberately chosen so that they were within the bandgap between the chrominance signal which runs up to 1MHz and the luminance signal which ranges up from 2MHz.

- Two extra heads are fitted to the video drum and impose the twin sound carriers onto the tape just ahead of the video signal. Crosstalk is minimised by aligning the audio and video heads at vastly different azimuth angles. The audio heads are aligned at $\pm 30^\circ$ while the video heads remain at $\pm 6^\circ$.


- The audio FM signals are recorded deeply into the magnetic layer of the tape by using a high current and a wide-gap tape head. The video heads, however, use low currents and narrow gaps to produce a shallow recording. During recording, the video signal actually erases the preceding audio but only to the shallower depth of the video signal. The audio information thus remains at the greater recorded depth.

These three factors, reduce crosstalk between the video and audio signals to a minimum and any interference between these signals is inconsequential.

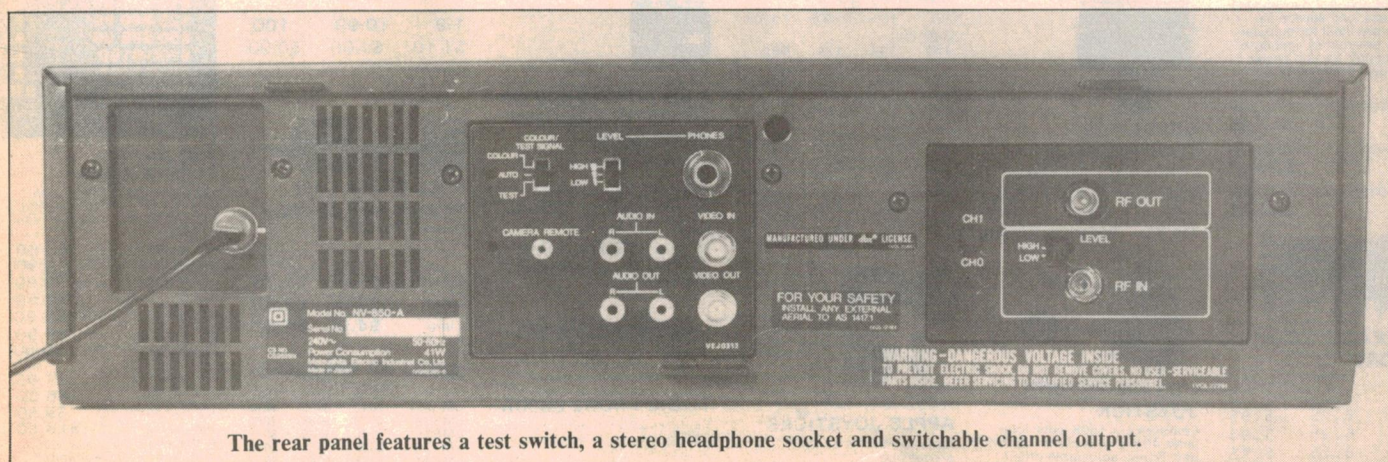The major performance specifications quoted for the twin-carrier recording system are as follows: frequency response 20Hz to 20kHz; dynamic range with noise suppression 80dB; and wow and flutter less than .005%.



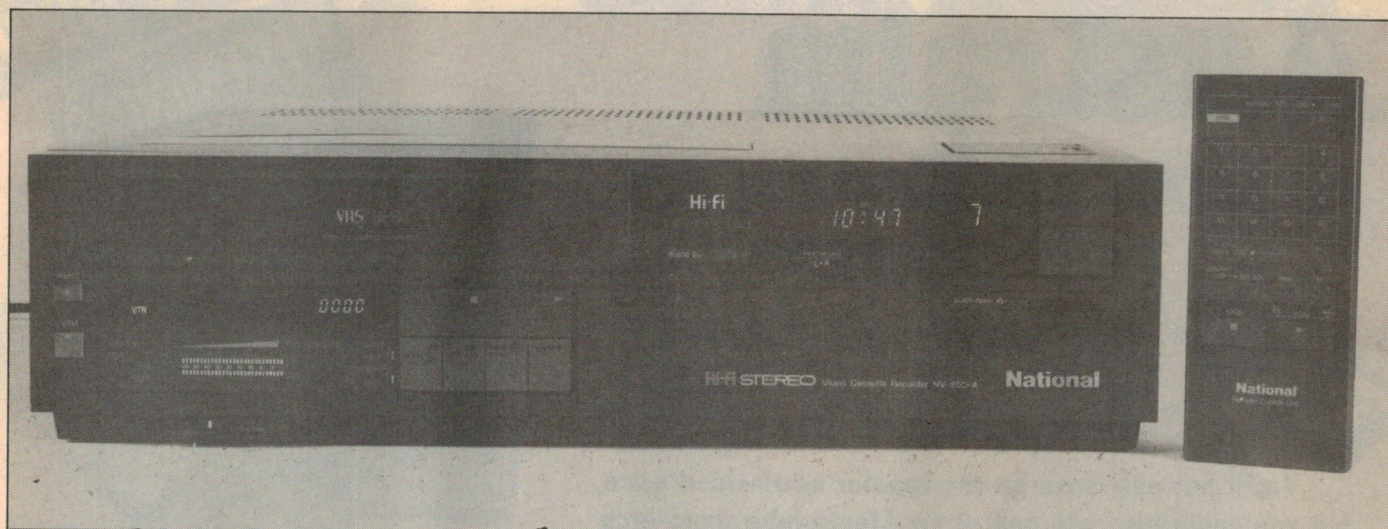The rear panel features a test switch, a stereo headphone socket and switchable channel output.



The multi-function infrared remote control duplicates most of the control features on the front panel.

National's NV-850-A

The National NV-850-A hifi VCR is a front-loading unit with overall dimensions of 430 x 370 x 115mm (W x D x H). The front panel finish is black with smoke-grey perspex used for the front cassette loading flap and as a window for the three vacuum fluorescent displays. An infrared remote control unit is supplied and duplicates most of the control features on the front panel.

Centrally located on the front panel are the controls for the tape transport mechanism: Stop, Play, Pause/Still, Still Advance, Rewind and Fast Forward. These allow the standard control features found on most VCRs, eg still frame and frame-by-frame viewing, fast frame scanning in both forward and reverse directions, and fast forward and reverse. The fast forward and reverse take five minutes to fully wind a 180 minute cassette, while the fast frame scanning increases the playback speed to five times normal.

To the left of the tape transport controls is an integrated multi-function display and audio level meter. The display indicates the status of the tape at any one time. For example, the display indicates Play, Record, Audio Dubbing and also the direction of tape travel when in Rev, Forward or Still.

A counter on the right of the display indicates tape location. The VCR can be automatically set to search for the reset (0000) tape position by using the memory search button.

Below the multifunction display is the audio level meter. This displays the relative level of audio signal from +10dB down to a useable -60dB. A switch below this can select for "display

off", for "audio level" or "hifi tracking". The hifi tracking indicator allows correct setting or the head azimuth. Being able to turn the audio level meter display off is a very useful feature as it can be very distracting if it can be seen while you are watching TV.

On the far left of the control panel is an eject button and a VTR switch. These two perform the same functions as on conventional VCRs.

An attractive feature of the National NV-850-A is One Touch Timer Recording (OTR). This controls recording for a duration of either 30, 60, 90 or 120 minutes. Recording is initiated immediately after programming or, alternatively, OTR can be set to begin recording after the elapsed times indicated above (standby OTR).

This feature is extremely useful and is more likely to be used than the full timer programming features.

A flip-down cover at the lower right of the machine reveals a multitude of less

used controls. These include the 14-day 8-program timer. This is a comprehensive timer and features a real time clock and every day and every week recording.

Other controls include the Record, Audio Dub and Audio Record Mute switches. The Audio Dub switch allows recording over the sound track of an existing video recording, while the Audio Record Mute prevents audio recording.

The NV-850-A hifi VCR can be used in any one of four recording modes:


- recording TV/FM simulcasts;
- recording TV stereo broadcasts;
- direct video plus sound recording from a camera and microphone; and
- audio recording only.

When using a TV signal as a program source, several options are available for the recording and subsequent playback of stereo and bilingual sound. When the TV signal is bilingual, you can select either channel 1, channel 2, or both channel 1 and channel 2 for recording in the hifi mode. Alternatively, channel 1 can be recorded on the normal sound track (standard mono VHS). Note that channel 2 is used for the second language in the transmission.

When the TV signal is in stereo, you can select either left, right, left and right or mono. All these selections are recorded in the hifi mode except for mono which uses the normal VHS sound track.

The above facilities are indicated by backlit lettering positioned just below the clock and timer display.

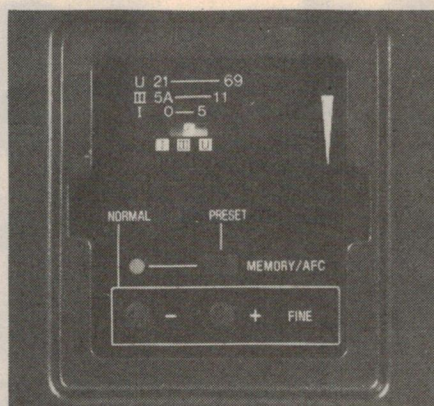The Input Select switch selects recording of either audio source, camera, tuner (TV) or simulcast audio. Hifi sound recording is available for each of these sources. The "audio" position allows the VCR to be used as an audio



These controls on the top of the VCR are used to set the TV channels.

Electronics Australia

**IS NOW CHEAPER BY
THE DOZEN**

PLUS

**YOU HAVE THE CHANCE
TO WIN AN ELECTROLUBE
CM100 CIRCUIT MAKER KIT!**

You'll not only save on the regular news-stand price,
but you could also win one of six Electrolube photo-etch
printed circuit board kits — each valued at over **\$180!**

Subscribing to **ELECTRONICS AUSTRALIA** will ensure that you get your copy of Australia's leading electronics magazine reliably every month. It's more convenient too — your copy will come straight to your mailbox, saving you a special trip to pick one up. And of course if you subscribe at the moment, you'll actually **SAVE** over TWO DOLLARS FIFTY on the regular news-stand price. In addition to this price saving, we're currently also making an exciting new offer to anyone taking out a new subscription to **ELECTRONICS AUSTRALIA**, or renewing a previous subscription before February 28th, 1985. At the end of each month, all of the subscriptions

received that month will be placed in a barrel, and TWO lucky subscribers each month will win a comprehensive, professional quality Electrolube CM100 Circuit Maker Kit for making photo-etched printed circuit boards. Each kit is valued at over \$180.

Winners will be notified by telegram and letter after each drawing of the winning subscription cards from the barrel. Simply fill in the card opposite, and send it with either a cheque or money order, or with your American Express, Bankcard or Mastercard number filled in.



YOU CAN BE A WINNER OF THE Electrolube CM100 Circuit Maker Kit

The CM100 Circuit Maker Kit is the latest addition to the well-known Electrolube range of chemicals and service aids for the electronics industry. It contains virtually everything you need to make high quality printed circuit boards using the photo-etch method, from either your own tape patterns or from same-size printed layouts. No darkroom or camera is necessary.

The kit contains the following:

- 12 sheets of autopositive film.
- 6 double-sided fibreglass blank boards, all measuring 160 x 100mm (Eurocard size).
- Universal exposure and assembly frame.
- A Photoflood lamp.

All necessary chemicals:

- developers • fixer • film clearing solution
- photoresist • copper etchant • and a combined soldering flux/protective lacquer
- A complete set of photographic dishes.
- A liquid measure.
- A retouching pen.
- A liquid-crystal thermometer.
- A couple of 1.1mm PCB drills.

And all extras like:

- Plastic gloves.
- A photoresist applicator.
- Cotton wool.
- Film clips.
- A scouring pad.
- And a full set of step by step instructions.



NOTE: The above competition does not apply to readers in Queensland or South Australia, due to the laws relating to lotteries in those states.
NSW Lottery Permit No. TC84/2457
Victoria Lottery Permit No. 84/884

hifi recorder while the simulcast position allows the user to record directly from a high-quality FM tuner during simulcasts. A microphone input records the sound when the camera selection is chosen.

Also located within the flip down cover area are three rotary controls for picture, tracking and audio record level. The picture control provides a soft to sharp range for adjusting the level of detail of the video. Tracking adjusts the azimuth of the heads for best playback response and is useful if the recording was made on a different VCR (the slight differences in azimuth between one machine and another can affect performance unless adjusted correctly).

The Audio Record Level sets the audio signal level during recording. It also has an automatic gain setting (AGC) which is the same as the ALC control found on many tape recorders.

The two large pushbutton controls to the right of the time display are used to increment and decrement the TV channel. The channel number is displayed to the right of the time display and up to 16 channels can be selected.

The TV channels are initially tuned by operating the controls beneath a small cover on the top of the VCR. These controls are easy to use and, once set, do not require further adjustment.

At the rear of the VCR is a Colour/Auto and Test switch. When in the test position, it allows adjustment of the VCR RF output frequency. Either channel 0 or 1 can be selected and two vertical bars displayed on the TV screen indicate when the TV set is correctly tuned to the VCR frequency.

Also located at the rear of the VCR are the various input and output sockets. The audio in and out sockets are RCA types while the video in and out sockets are BNC. The RF output plug and input socket are the standard "PAL" type, or

Belling Lee as they are otherwise known.

A stereo headphone socket is also located on the rear panel and a 3-position level switch selects the volume level applied to them. The remaining socket is the camera remote socket.

Removing the top cover of the NV-850-A reveals a well-constructed interior. The main support chassis is a massive precision diecasting which ensures mechanical integrity, while the tape transport mechanism is also solidly constructed. The circuitry is all accommodated on printed circuit boards, stacked one on top of the other, and includes a large number of LSI circuits.

A new noise reduction chip provides dbx noise reduction to give the 90dB dynamic range that this recorder features.

Test results

Since the video performance of the NV-850-A is equivalent to standard VHS machines, our tests were mainly concerned with audio quality. We should emphasise, however, that the hifi audio features had no effect on picture quality.

Total harmonic distortion was measured with and without the AGC and, as expected, distortion was somewhat higher (at low frequencies) when the AGC was in operation. For 0dB level we measured 0.4% THD at 100Hz, 0.5% at 1kHz and 1.6% at 6.3kHz without AGC. With the AGC in circuit, the distortion remained unchanged for the 1kHz and 6.3kHz signals, but rose to 2% at 100Hz.

Distortion at +6dB without AGC was slightly better than at 0dB, measuring 0.25% at 100Hz, 0.4% at 1kHz and 1% at 6.3kHz.

Frequency response was measured at 0dB level and resulted in -3dB points at 20Hz and 18kHz. The response was

-7dB down at 10Hz and -4dB at 20kHz.

We also ran a check on the linearity. This measurement involves recording at decreasing signal levels and noting the playback response. The NV-850-A was only 0.5dB high at the -50dB and -60dB levels and linear for signals above this level. This is an excellent result.

Signal-to-noise ratio with respect to a +6dB level was measured as 73dB unweighted, while the wow and flutter was measured at .004%. This is slightly better than the .005% claimed. However the S/N ratio does not match the claimed 80dB figure.

Crosstalk between left and right channels with respect to a +6dB level was 50dB at 100Hz, 63dB at 1kHz, and 53.5dB at 10kHz.

How it sounds

Subjectively, the audio recordings made on this VCR were superb. When making A-B comparisons directly between a compact disc source and the same material recorded on the VCR, we found it extremely difficult to distinguish between the two sources. A similar comparison using a standard audio cassette player always reveals a rise in the noise level after recording.

Although the NV-850-A VCR performs very well with regard to sound recording, several features prevent it from directly competing with a standard cassette recorder. The main problem with a VCR, when using it for sound recording, is the very slow response time of the tape mechanism. It is necessary to wait for the tape to spool itself around the tape head before play or record can begin.


Similarly, on stop, it is necessary to wait for the tape to unspool before rewind or fast forward functions operate.

The machine does, however, have a pause feature and a memory search function which quickly accesses the reset (0000) position of the tape. These features, along with the excellent timer functions, do help negate the tape transport objections. Overall the machine makes a very good audio recorder and does not require any of the bias adjustments necessary for a standard audio cassette recorder.

In summary, the National NV-850-A hifi stereo VCR is an excellent performer. The superb sound quality, excellent video reproduction and infrared remote control facilities make this a tempting package for any prospective VCR purchaser.

Recommended retail price is \$1299. ☺

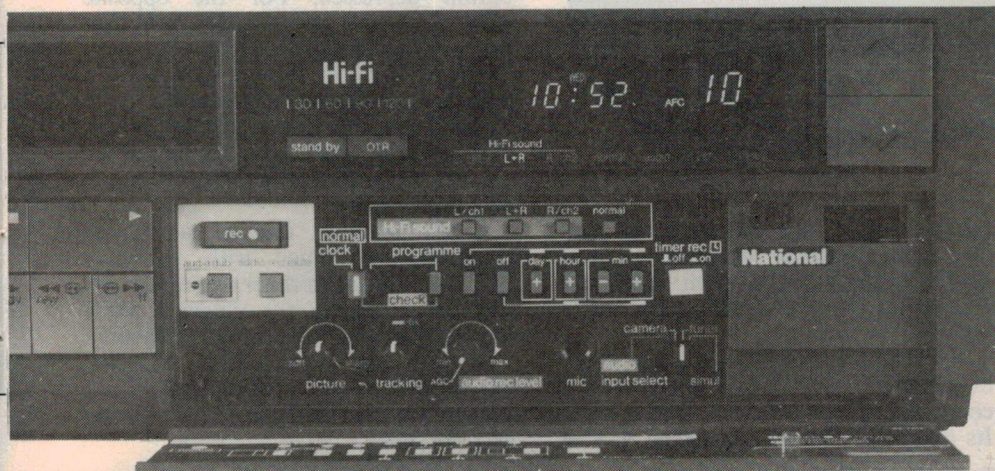This view shows the multitude of controls normally hidden by the flip-down cover.



AUDIO PRODUCTS

Pioneer car stereo systems

Pioneer has announced the release of two new 20W stereo combinations for use in cars, the KPH4000 and the KPH7000.

The KPH7000 is powerful enough to meet most people's requirements on its own. It has four separate in-built mono

amplifiers which are switchable to give 20W through each of two speakers or 6.5W through four speakers. It can also be the starting point for those seeking hifi power and flexibility in a car, van or boat, through the addition of even more powerful external power boosters or amplifiers. These can be added to the system at any stage.


The KPH7000 has a built-in preamp fader control which achieves balance

between front and rear speakers through the amplifier sections. It also has a loudness contour switch and separate bass and treble controls.

The auto reverse cassette deck section has lock-in fast forward and rewind, automatic tape tensioning, "Dolby B" noise reduction and full metal/chrome tape compatibility.

The KPH4000 is a lower priced companion model to the KPH7000. It offers 20W through two speakers utilising two separate amplifier sections. Its other features include separate bass and treble controls, loudness contour, an AM/FM stereo tuner, and a full auto-reverse cassette deck with automatic tape tensioning and key-off release and key-on play, safeguarding tape damage.

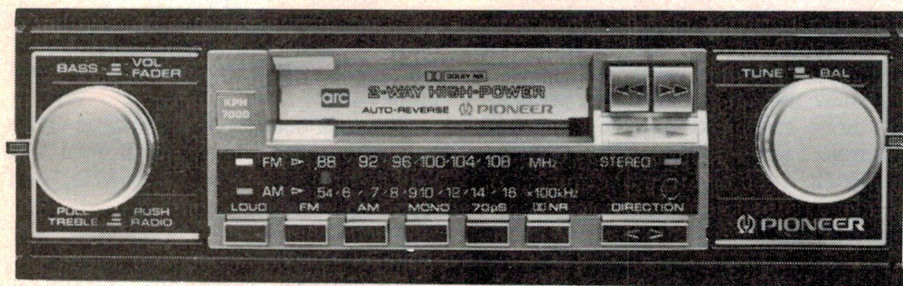Further information from Pioneer Electronics Aust Pty Ltd, PO Box 295, Mordialloc, Victoria, 3195. Phone (03) 580 9911.



Pioneer's powerful new KPH700 car stereo player.

Versatile video projection system

GEC Video Systems Division has released a new, versatile colour video projection system, the National TC-10010 PSN. Designed for front or back projection, from a ceiling or bench mounting, the unit will reproduce PAL, SECAM and NTSC VTR signals onto a range of flat or curved screen sizes from 1.3m to 2.5 metres diagonal. Each projector comes complete with a full-function

remote control unit.

The TC-10010 PSN has been designed to automatically detect PAL, SECAM or NTSC input signals and reproduce them in the correct mode. If automatic detection is not required, the unit can be preset for any one format.


The new National projector is claimed to provide a high quality picture with flat or curved screens from 1.3m to 2.5m diagonal. Three special high-brightness 180mm projection CRT's and f1.1 lenses give a resolution of 450 lines and luminous

flux of 170 lumen. A complete built-in cross hatch generator is included so that the user can make precise convergence adjustments.

Each projector comes with a remote control unit (pre-wired to 1.5m but available with optional 15m, 30m and 50m cables) for routine alignment and on-the-spot adjustment.

Further information on the National TC-10010 PSN is available from GEC Video Systems Division, 2 Giffnock Avenue North Ryde, NSW, 2113. Phone (02) 887 6222.

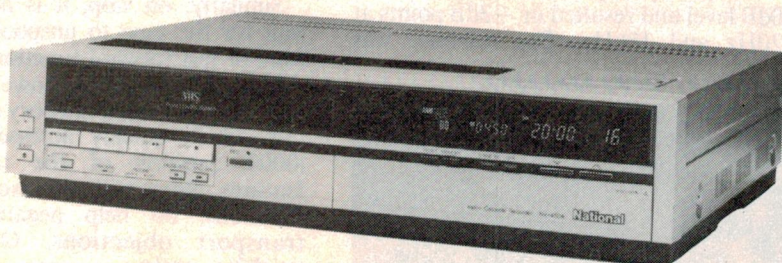Slim and streamlined ... National Panasonic's NV-450A



Slim package video recorder

National Panasonic has announced the release of a new, slimline video recorder, the NV-450A. With a height of only 9.9cm, its simple, streamlined appearance makes it a great match for

audio components and other equipment. The unit features convenient front loading operation and 43cm width and fits perfectly into a standard size audio rack.

According to National, the NV-450A combines excellent operating convenience with superb picture quality. Its 3-video-head-system provides special

playback functions such as super still playback without noise or jitter and still advance. A slow motion effect is obtainable also (1/6 normal playback speed) by keeping the still advance button depressed. For the opposite effect, cue and review operate at five times normal playback speed.

The NV-450A is equipped with a 27-function infrared remote control and has a large fluorescent multi-function display panel which gives instantaneous confirmation of every activated function at a quick glance.

Other features include a 14-day programmable timer with everyday function; one-touch timer recording with stand-by function for deferred OTR start; auto-rewind and memory function.

Further information from National Panasonic (Australia) Pty Ltd, 95-99 Epping Rd, North Ryde, 2113. Phone (02) 887 5333.



Pioneer Electronics has created a complete new range of home entertainment cabinets, based on extensive market research into the type of furniture Australians prefer in this role. The designs use a new Laminex finish called "Royal Walnut", exclusive to Pioneer. Twelve cabinets have been produced, designed to accommodate a wide range of Pioneer audio systems, including Avante systems and the Pioneer Sound Creator. Other designs make provision for Laserdisc, Compact Disc, and VCR systems. Matching speaker cabinets are also available. Pioneer Electronics Australia Pty Ltd, PO Box 295, Mordialloc, Victoria, 3195.

Broadcast monitoring stereo AM tuner

Audiosound Laboratories have just released a Motorola system stereo version of their AM 102 broadcast monitoring tuner. The new unit, titled the AMX 1, features an audio response to 12kHz (-3dB), carrier and modulation fail alarms, balanced line-output amplifiers with 40Ω source impedance, and a balanced low-noise antenna system (supplied). Two switchable 9kHz notch filters ensure

excellent filtering with minimal audio loss.

Used in conjunction with Audiosound Laboratories' PM 1 stereo program monitoring unit, the AMX 1 forms a complete AM stereo off-air receiver with modulation monitoring.


Also due for release is the AMX 1's "little brother". This domestic version lacks the alarms and balanced output amplifiers, but retains all other technical features.

Further information from Audiosound Laboratories, 148 Pitt Rd, Nth Curl Curl NSW. Phone (02) 938 2068.



The Audiosound AMX 1 AM stereo monitoring tuner features adjustable RF gain, switchable bandwidth, and modulation and carrier fail alarms.

Portable video player from Bell & Howell

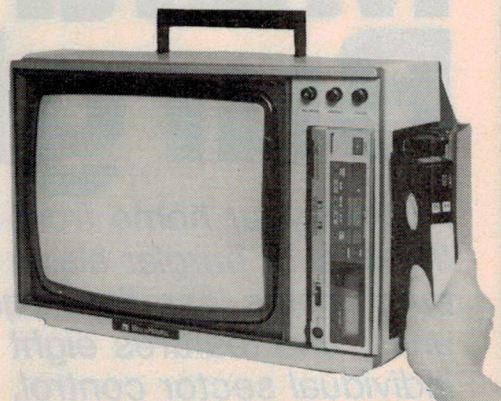

Bell & Howell has acquired the rights to manufacture an improved version of the all-in-one video presentation unit designed by Tracker Electronics. The new model, the VS-1B, is lighter and incorporates the National NV-180A, a "super lightweight" VCR recently introduced by GEC Australia Video Systems Division. The NV-180A weighs 2.3kg and measures only 215mm x 69mm x 263mm.

The compact 13kg VS-1B combines a 34cm colour monitor with the NV-180A to produce a tough, fully portable, video player suitable for sales presentations, training or educational applications.

Of particular value for use in presentation systems, the NV-180A has a double video head system for super still and super still advance playback without jitter or distortion, plus adjustable super-fine slow motion.

To produce the VS-1B, Bell & Howell strip the channel select and tuner assembly from a standard TV set and insert the NV-180A in their place. Vertically mounted, this forms one side of the modified monitor, allowing easy cassette access.

Bell & Howell estimate an annual market for the VS-1B in Australia of up to 1500 units with potential overseas sales of many thousands more. They see all kinds of applications for the unit from point-of-sale video messages to sales presentations and staff training. Several major business organisations, the police, the army, government departments and some media sales teams have already put the earlier model into use.

Further information from Bell & Howell Aust Pty Ltd, 55-59 Murray St, Pyrmont, NSW, 2009. Phone (02) 660 5366.

Keep thieves at bay— Multi Sector Burglar Alarm

by
ANDREW LEVIDO

Protect your home from intruders with this up-to-the-minute burglar alarm system. It's easy to build, costs less than equivalent commercial units, and features eight separate inputs, individual sector control, battery backup and a self-test facility.

For one reason or another, there has been a dramatic increase in the number of house break-ins over the last few years. No area is immune, although some have worse records than others as statistics released by various state police forces show.

The prime targets of thieves are the

portable, easily saleable items with which we fill our homes. Cash, jewellery and electronic equipment such as VCRs are items which immediately come to mind.

Unfortunately, the recovery rate of stolen goods is very low. This is partly because of the sheer volume of property stolen, and partly due to difficulties

associated with the identification of goods.

The financial cost of this massive increase in crime is only part of the story. Damage can be repaired and goods replaced, but the emotional effects of a robbery can often last for many years. The feelings of anger and frustration subside relatively quickly, but there is always that nagging worry that you are not safe, even in your own home.


Although the statistics paint a gloomy picture, you do not have to accept a burglary as an inevitable result of city living. There are several steps that you can take to drastically reduce the odds of your home becoming a target. The obvious things are a good start: always lock the house securely when going out, and leave a light on indoors if going out at night.

While these steps may well serve to discourage an amateur thief or passing opportunist, they present merely a minor inconvenience to a professional burglar. Against these more determined intruders, positive security measures are required. An electronic alarm system is the most common form of protection used in this role.

There is a wide range of electronic alarm systems available for protecting homes and small business premises, ranging from very cheap models to multi-thousand dollar professional installations. The very cheap models do not provide some of the features which are highly desirable, such as variable entry, exit, and alarm periods; multi-sector control; and battery back-up.

The more up-market models do provide these features, as well as others, but they can be very expensive, especially if they are professionally installed. We felt that there was a definite need for a reasonably priced, yet comprehensive alarm system for the householder who is willing to do the installation himself.

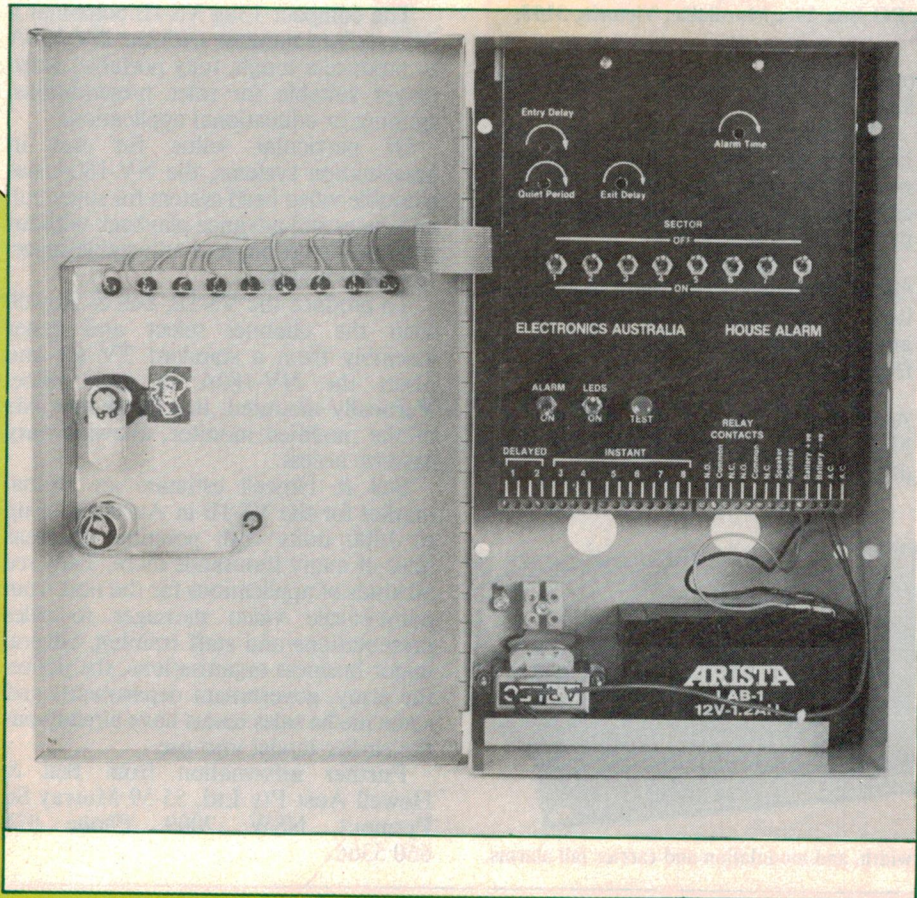The result of our endeavours is presented here — an alarm system with all the features of the better commercial models but without the price tag. It is



install this

We estimate that parts for this project will cost approximately

\$130

This includes sales tax and the cost of the 12V battery, but does not include alarm sensors.

simple to build and can be used with a variety of sensors.

Main features

At this point it would probably be a good idea to examine the features built into the alarm in some detail.

The alarm has eight separate input circuits so that eight areas (or sectors) can be monitored independently. Each circuit is provided with an indicator LED and a sector on/off switch.

This multi-sector approach has a number of practical advantages. Most importantly, it means that if one sector is triggered, and the alarm cycle has run its course, the rest of the house is still protected by the remaining active sectors.

Similarly, if one sector is not secure when the alarm is set, say because a window is left open, all areas other than that which includes the open window will be protected. This situation need not arise, however, since a check on the status of each sector can easily be made. To do this, the LEDs On/Off switch is turned on, and the LEDs checked. If a LED is lit, that sector has been activated (eg, a window has been left open) and needs to be made secure before the premises are vacated.

The LEDs switch should be turned off after this check to prolong battery life.



The sector disable switches are another convenient feature. These allow the user to isolate one or more sectors as required. In this way, some areas of the house can be used while others remain protected; eg, the internal alarm sectors can be disabled while the perimeter sectors remain active.

Each sector input stage is identical and has been designed to accept both normally open (NO) and normally closed (NC) sensors. Figs. 1-3 show how the various types of sensors should be wired. The 47k Ω resistor is necessary for correct operation of the input circuit. It should not be installed directly across the alarm terminals, but rather at some remote point in the loop. Thus if any attempt is made to cut or short circuit the wires

leading to the alarm, it will be triggered.

Many different sensors are suitable for use with this alarm. The input stage will accept any device which has normally closed or normally open switch outputs. Such things include reed switches, pressure mats, window foil, pushbutton (panic) switches, light beam relays, ultrasonic movement detectors, microwave detectors — in fact anything that you can think of which has, or can be adapted to have, switch type outputs.

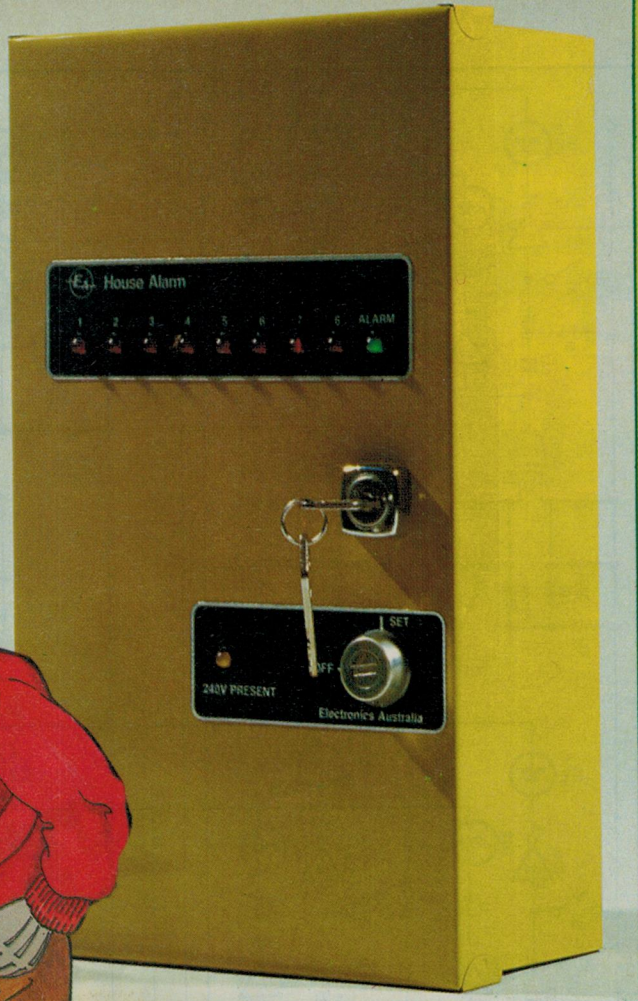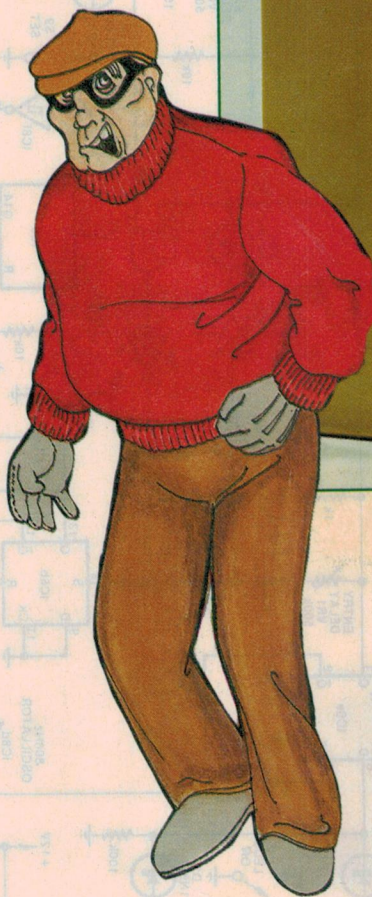Two of the inputs to the alarm are provided with an entry delay. These inputs are intended to be connected to, say, the front and the back door sensors to allow you time to enter and disable the alarm before it sounds. The delay time before the alarm sounds can be set



This is how the completed alarm will look. It is designed to be mounted on a wall.

anywhere between 10 and 75 seconds.

The alarm is set or disabled by means of a keyswitch mounted on the front panel of the case. This is the only control accessible without opening the alarm box, a job which requires a second key. The LED indicators are mounted on the front panel.

One important feature that we have not seen on commercial alarms is the warning buzzer. This buzzer, which is built into the alarm itself, sounds after a predetermined proportion of the entry delay period has elapsed. In this way, the user is provided with some warning that the alarm is about to sound. The time period before which the buzzer is activated is set by the "Quiet Period" control, and is adjustable from 5 to 55 seconds.

Thus, if you forget to turn off the alarm when you enter the house, you will receive an audible reminder before waking the whole neighbourhood. This preserves good relations with the locals and ensures that when the alarm does go off, it will be taken seriously.

For the same reason, the siren driver output is automatically muted when the alarm is tested. A pushbutton switch operates this test facility. If all is well, the siren should sound (at a reduced level)

Burglar Alarm

when the button is depressed, and cease when it is released. This will only occur if the alarm is set, and after the exit delay period has expired.

The exit delay is set by yet another timer circuit and is adjustable between 5 and 45 seconds. After setting the alarm, you have to be out of the house before this delay period expires.

When triggered, the alarm drives a separate horn-type loudspeaker for a period of between one and 15 minutes and trips a relay. The relay has two sets of contacts for connection to external devices. It could be used to turn on a bell or a closed circuit TV camera, for example.

Alternatively, you can have a silent alarm simply by opening the ALARM On/Off switch. In this case, the relay contacts would typically be used to activate an auto-dialler circuit.

The alarm is provided with battery back-up, which means that removing the mains to the house does not render the alarm inoperative. The battery, a 12V gel type, is continually charged while ever mains power is applied to the alarm circuitry.

The battery specified is a 1.2A.h model which fits nicely into the alarm case. This battery will allow the alarm to

Specifications

- Eight sectors with LED status indication.
- Two delayed entry sectors.
- Variable exit, entry and alarm time settings: entry delay variable between 10 and 75 seconds; exit delay variable between 5 and 45 seconds;

alarm time variable between 1 and 15 minutes.

- Resistive loop sensing: suits both normally open and normally closed alarm sensors.
- Battery back-up with in-built charger circuit.
- Built-in siren driver

operate for over two days if the mains is disconnected. We are aware that a 2.6A.h battery is also available (for little extra cost), and this will allow operation for over five days. The latter will not fit inside the specified case, but could be mounted externally if desired.

Quite some thought went into the selection of a suitable case to house this project. A sturdy, lockable case was required, but the purpose-built alarm boxes we investigated were far too expensive. After much head scratching, the idea of using a cheap readily available cashbox came to light.

As it turned out, the case we chose was ideally suited to this application and very little mechanical work was required to produce an attractive and functional unit.

How it works

Although the circuit of the Home Burglar Alarm is quite complex, it can easily be broken down into a number of simple sections. Each of these sections will be examined in turn and its operation explained.

The eight input stages have been designed for connection to both normally open and normally closed switches; ie, both types of switch can be connected to one input at the same time. This is made possible by having each input terminated by a resistance of 47k Ω . Normally closed switches are connected in series with this resistor while the normally open switches are connected in parallel with it (see Figs. 1-3).

Thus, when any of these switches changes state, the input will go either open or short circuit. The input stages are designed to respond to either of these conditions. As can be seen, the eight stages are identical and are built around exclusive-OR (XOR) gates IC1a-IC2d.

Let's consider input 1 which uses XOR gate IC1a, together with Schmitt trigger inverters IC3a and IC3b.

Normally, with the input terminated with a 47k Ω resistor, the junction of the two 150k Ω resistors is held at half of the supply voltage. This means that pins 1 and 2 of IC1a will be held at two thirds and one third of the supply voltage respectively. Thus, the output of the gate (pin 3) will be high.

This will hold the .047 μ F capacitor discharged, so that the input to the Schmitt inverter IC3a will be high. Thus, the output of IC3a will normally be low. IC3b is used to drive a LED indicator. Under normal conditions the LED will be off.

Note that the cathodes of all the LEDs in the input stages are connected together and switched via S12 to ground. This switch should normally be off, and should only be turned on long enough to determine the states of the sectors. If the switch is left on, with more than one or two sectors tripped, the current drain will be such that the battery will begin to discharge.

If the input now goes open circuit, pin 1 of IC1a will rise to almost the full supply voltage while pin 2 will rise to approximately two thirds of the supply voltage. This corresponds to a logic one on each input of the XOR gate. Under these conditions the output of the gate will go low.

If, on the other hand, the input is short circuited, pin 2 of IC1a will go to 0V while pin 1 will be pulled down to one third of the supply voltage. This corresponds to a logic 0 on both inputs of the gate, again resulting in the output of the gate swinging low.

In each of the above cases the 1 μ F capacitors prevent false triggering of the alarm due to spurious signals which may find their way into the input circuitry.

If, due to either an open or a short circuit on the input, the output of the XOR gate swings low, the indicator LED will light (assuming S12 is closed). As well as this, the input of inverter IC3a will go low until the .047 μ F capacitor charges via the 1M Ω resistor. This takes about 50ms. Thus, a short positive going pulse is developed at the output of the inverter if the sector input is either open or short circuited.

If switch S1 is closed, the input to the Schmitt inverter will be held high, so there can be no change at its output. This is a useful feature if it is required to disable any particular sector for some reason.

The outputs of Sectors 1 and 2 are fed to a timer circuit to provide the entry delay feature mentioned earlier. These are the two inputs that would normally

Wiring of NO & NC switches

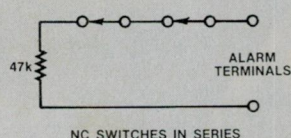


Fig. 1

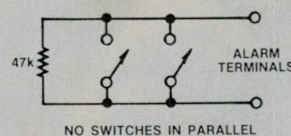


Fig. 2


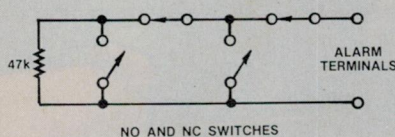


Fig. 3

These three diagrams show how normally open and normally closed switches should be wired. Note that a 47k Ω resistor is required in each case.

What would you do,

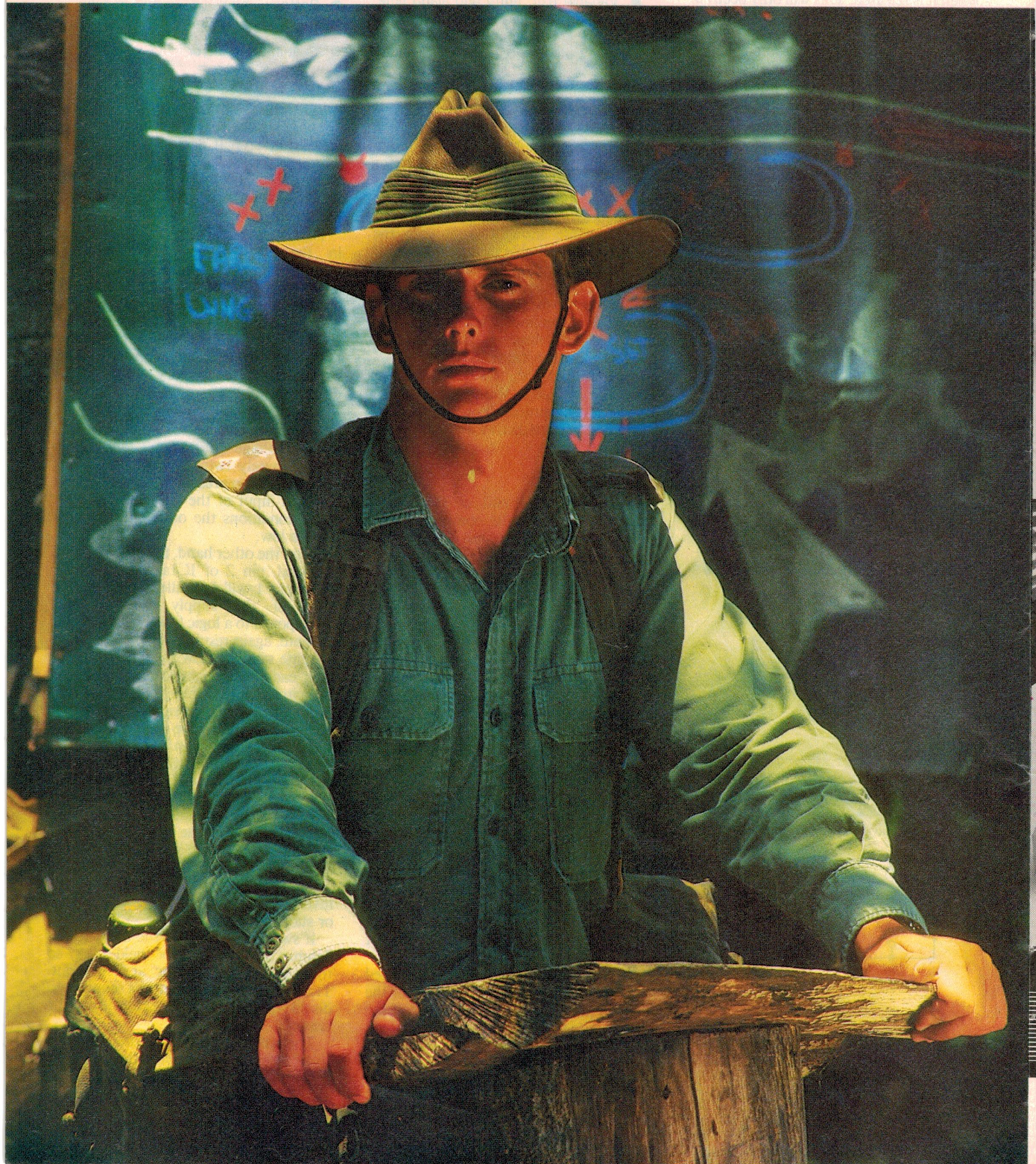

if:

IF you had to win the support and respect of thirty men and women whom you'd never met before?

IF you had to lead a platoon into unknown country for several weeks with their welfare your responsibility?

IF you had to act as a United Nations Truce Supervisor?

IF you had to handle the logistics for moving five hundred soldiers and their equipment across the continent?

IF you had to assist in directing the evacuation of a civilian population during a major civil disaster?

If you're undaunted by this kind of challenge, then you have the potential to become a professional Army Officer. It's a career in which you're regularly faced with new situations, new problems to solve and new challenges that test you both physically and mentally. But if you're equal to the task, you can achieve, at an early age, a level of executive management that few ever achieve in civilian life.

If you're a man or woman aged between 18½ and 23 on entry (or up to 25 with a degree or diploma), have your HSC or equivalent and the challenge of leadership appeals to you, contact Army Recruiting Centre or fill in this coupon.

**The 18 month
Officer Training
Course commences
each July and
January. See your
Army Careers
Adviser for
closing dates of
application.**

For more information post coupon to GPO Box XYZ,
in your Capital city.

Sydney 2195555, Newcastle 263011, Wollongong 281855,
Albury 552248, Lismore 216111, Canberra 822333,
Melbourne 6979755, Geelong 211588, Bendigo 438008,
Ballarat 311240, Brisbane 2262626, Townsville 724566,
Adelaide 2121455, Perth 3256222, Hobart 347077,
Launceston 311005.

Name _____


Address _____

Postcode _____

Phone _____

Birthdate _____

Educ. Std. _____

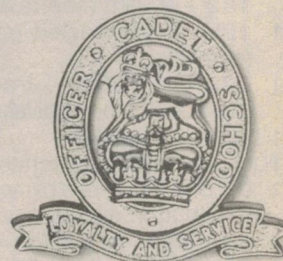

Army Officer. A leading profession.

All enquiries treated in confidence

OCS 18, DPS 1184

Burglar Alarm

be connected to the front and back door sensors. The timer circuit consists of D-type flipflop IC6a (4013) and functions in the following manner.

Normally, the flipflop IC6a is held reset, so that the Q output is low and the \bar{Q} output is high. The latter controls NAND gate IC7a. This gate is connected such that the clock signal generated by IC8d is gated through to the clock input of the flipflop.

Diodes D1, D2 and the 100k Ω resistor form an OR gate, so that if either sector 1 or sector 2 is tripped, a pulse is applied to the data input of IC6a. This pulse will be clocked through to the output on the first positive transition of the clock signal. Thus, Q will go high and \bar{Q} will go low.

Because \bar{Q} goes low, the clock input of the flipflop will be forced high via IC7a. Thus, the flipflop will latch up, with its Q output high.

Capacitor C1 now charges via trimpot VR1 and the 100k Ω resistor in series with it. When the voltage on the capacitor reaches about 70% of the supply voltage, the output of IC8a switches high, triggering the alarm via D10 and, at the same time, resetting IC6a.

The Q output of IC6a now switches low again and discharges the 100 μ F capacitor through the 1k Ω resistor and diode D11. After about 50ms, the output of IC8a switches low again, thereby ending the reset pulse and rearming

IC6a.

IC8c, Q11 and associated components provide the warning buzzer feature. During the entry delay (ie, while C1 is charging), capacitor C2 charges via VR2 and, when it reaches 70% of the supply voltage, turns on Q11 via inverter IC8c. Q11 in turn drives the warning buzzer to indicate that the entry delay is about to expire.

Trimpot VR2 sets the "quiet period" before the warning buzzer sounds. The buzzer circuit is disabled either via D9 or D12. D9 pulls pin 13 of IC8c low when S9 is opened (ie, the alarm is turned off), while D12 pulls pin 13 low at the end of entry delay period.

The outputs of the other six input stages are OR-ed with the output of the entry delay circuit via diodes D3-D8 and D10. This instant trip line is gated through to the alarm timer by IC7b and IC8e, provided pin 13 of IC7b is high.

Pin 13 of IC7b is controlled by the exit delay timer. When the alarm is off (ie, keyswitch S9 open), transistor Q1 is on, pin 13 of IC7b is low, and the alarm timer is held reset via IC8f and diode D13.

When the alarm is set (S9 closed), Q1 turns off and C3 charges via VR3 and the 100k Ω resistor. When the voltage on the capacitor reaches the upper threshold voltage of IC8f it is interpreted as a logic 1 and the alarm is triggered.

IC6b, IC7c and IC9 form the alarm timer which controls the length of time that the alarm sounds. Since this has to be a very long time delay, a simple RC time constant circuit is not practical. This timer works in the following way:

When the alarm is set, IC6b is initially held reset via IC8f and D13 until the end

of the exit delay. This means that Q is low and \bar{Q} is high and thus IC9 is also reset. At the end of the exit delay, the output of IC8f goes low and removes the reset signal from IC6b. If the output of IC8e now goes high momentarily (ie, if the alarm is triggered), Q of IC6b will go high and enable Schmitt trigger oscillator IC7c.

Trimpot VR4 sets the oscillator frequency so that the alarm time can be adjusted (1-15 minutes).

IC7c clocks IC9, a 4020 14-stage binary ripple counter. After 8192 clock pulses, Q14 of IC9 goes high and resets IC6b via D15. This, in turn, resets IC9 and disables IC7d and the siren driver circuitry.

IC11e and IC11f form a non-inverting buffer which drives indicating LED D33 and Q2, which controls the relay. Both of these devices are on when Q of IC6b is high (ie, during the alarm period). If switch S10 is closed, the siren driver is also activated for this period.

Siren driver circuit

The siren driver circuit has two inputs: an oscillator input and a gating signal input. Schmitt trigger oscillator IC8d provides the siren tone and has a nominal frequency of 800Hz. Its output is gated by NAND gates IC10a and IC10d and, via IC11d, by IC10b and IC10c.

The gating signal is connected to the remaining inputs of IC10a, b, c and d. When this signal is low, the outputs of these gates will all be high, so transistors Q3, Q5, Q8 and Q10 will be off. IC11b and IC11c invert the outputs of IC10b

PARTS LIST

- 1 PCB, code 85ha1, 150 x 191mm
- 1 cash box (SWS 74-12), 305 x 182 x 91mm (see text)
- 1 12V, 1.2Ah sealed gel battery (see text)
- 1 12.6V, 150mA transformer (type 2851 or equivalent)
- 1 8 Ω horn speaker
- 10 SPDT toggle switches
- 1 DPDT momentary action pushbutton switch
- 1 barrel-type keyswitch
- 1 12V DPDT relay, 5A contacts (DSE S-7130 or equivalent)
- 1 electronic buzzer
- 3 8-way PC-mounting terminal blocks
- 1 4-way PC-mounting terminal block
- 10 LED mounting bezels
- 3 Scotchcal panels
- 1 aluminium sheet, 150 x 190mm, 1.6mm thick

- 2 spade connectors, female
- 1 2-way mains terminal block
- 4 20mm spacers
- 2 25mm tapped spacers

Capacitors

- 1 1000 μ F 25VW axial electrolytic
- 3 100 μ F 16VW PC electrolytic
- 1 10 μ F 25VW PC electrolytic
- 1 4.7 μ F 25VW PC electrolytic
- 16 1 μ F 50VW PC electrolytic (RBLL type)
- 8 .047 μ F polyester (greencap)
- 1 .015 μ F polyester
- 2 .01 μ F polyester

Semiconductors

- 2 4030 quad exclusive-OR gates
- 4 40106 hex Schmitt inverting buffers
- 1 4013 dual D-type flipflop
- 1 4093 quad Schmitt NAND gate
- 1 4020 14-stage ripple counter
- 1 4011 quad NAND gate
- 1 4049 hex inverting buffer
- 2 TIP31 NPN transistors

- 2 TIP32 PNP transistors
- 2 BC338 NPN transistors
- 3 BC328 PNP transistors
- 1 BC548 NPN transistor
- 1 BD681 NPN Darlington transistor
- 1 15V, 1W zener diode
- 16 1N914 diodes
- 6 1N4004 diodes
- 8 5mm red LEDs
- 1 5mm green LED
- 1 5mm yellow LED

Resistors (1/4W, 5% unless stated)
 10 x 1M Ω , 16 x 300k Ω (1%), 16 x 150k Ω , 10 x 100k Ω , 17 x 47k Ω , 3 x 10k Ω , 1 x 1.8k Ω , 15 x 1k Ω , 4 x 100 Ω (1W), 2 x 47 Ω (1W), 3 x 500k Ω miniature horizontal trimpots, 1 x 100k Ω miniature horizontal trimpot.

Miscellaneous

Machine screws and nuts, 16-way ribbon cable (2 metres), solder, etc.

and IC10d, so transistors Q4, Q6, Q7 and Q9 will be also off. In this state, the circuit draws very little current.

When the gating signal is high, the 1kHz siren tone is gated through to the driver transistors by the NAND gates. The signal is inverted before being applied to IC10b and IC10c, so that the driver stage operates in the push-pull mode. This means that the signal across the speaker is about 24V peak-to-peak.

The Q output of IC6b is not used directly as the gating signal for the siren driver, since this would result in a continuous tone being emitted. Rather, the Q output is used to enable a low frequency oscillator formed by IC7d. This oscillator has a nominal frequency of 1Hz. Inverter IC11a is necessary since, when the oscillator is disabled, its output is high.

The result of all this is an ear-piercing 800Hz alarm tone, modulated at 1Hz.

Muted test facility

Note that the siren driver circuit is actually capable of driving two 8Ω horns connected in parallel. This may be useful if you own a very large house. If you do elect to use two horns, then the large 2.6Ah battery should be employed to cope with the increased current drain.

Up to this point, the 47Ω resistor and switch S11b have been ignored. These components form part of the test facility which has been incorporated into the alarm. For normal operation, the switch is normally in the position shown, so the resistor is not in circuit. When the alarm is tested, this resistor is connected in series with the horn speaker, thereby reducing its output considerably.

The other pole of this test switch (S11a) is used to provide trigger and reset pulses for the test function. The switch normally rests in the position shown and, when pressed, pulls the input of IC5f low until the .01μF capacitor charges up via the 1MΩ resistor. Thus a short (10ms) positive pulse is delivered to the instant trip line. Provided the exit delay has expired, the alarm will then sound.


When the test button is released, a reset pulse is delivered to IC6b via IC5e in exactly the same way. This pulse resets the alarm timer and so stops the siren.

The last section of this circuit worthy of comment is the power supply section. This is built around a 12V, 1.2 amp-hour, sealed gel battery. This battery provides power for the circuit at all times, and is kept recharged by the mains supply.

A standard bridge rectifier circuit is employed for the power supply and charges the 12V battery via D22 and a 47Ω 1W resistor. LED D24 and its associated 1.8kΩ current limiting resistor provides power on/off indication for the mains.

Finally, zener diode D23 prevents damage to the circuit if the battery is removed while the mains is present. If the battery is removed, then D23 clamps the supply rail to 15V, which is within the ratings of the CMOS ICs.

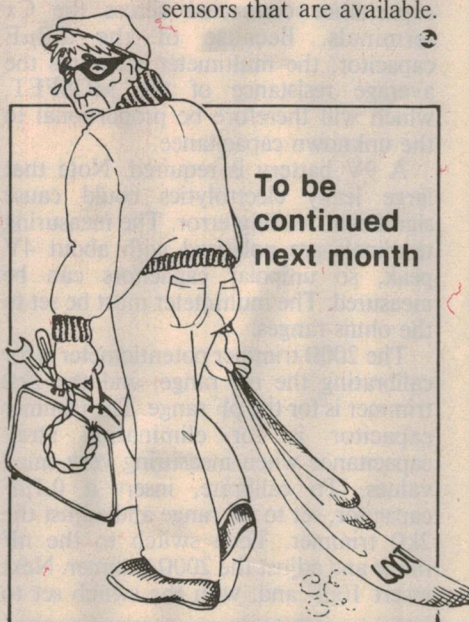Next month, we will continue with the construction details and take a look at the different types of alarm sensors that are available.



projects & circuits

Number 3

THE CONTENTS:

Audio, Video Projects

Video Amplifier for Computers and VCRs; Video Enhancer; Vocal Canceller; Stereo Simulator for Tuners and VCRs; Guitar Booster for Stereo Amplifiers.

Power Supplies & Test Equipment Battery Saver for Personal Portables; Dual tracking ±22V Power Supply; 3½-Digit LCD Capacitance Meter; In-Circuit Transistor Tester.

Mains Power Control Projects

Musicolour; Photographic Timer; Driveway Sentry; Touch-Lamp Dimmer.

Automotive Projects

Transistor-Assisted Ignition System; Breath Tester Checks Blood Alcohol Level; Low Fuel Warning Indicator; Speed Sentry for Cars; Audible Turn Signal Indicator.

Miscellaneous

Nail Finder; Portable 3½-Digit Heart-rate Monitor; 10 Year EA Project Index.

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017. **PRICE \$4.50** OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017. **PRICE \$5.40.**

ALARM

Improve the effectiveness of your alarm system by adding this revolutionary **ELECTRONIC VOICE DRIVER UNITS. \$89.00**


- Requires 12V DC/min.
- 1A power supply.
- Will say "BURGLAR" or "FIRE" with SIREN.
- Connect between alarm 12V O/P and 2x15W horn speaker.



ALARMS CONTROL PANEL

SP-1024 (4 + 1)

SP-1022 (2 + 1)

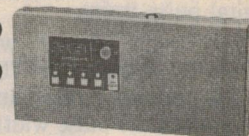

SP-1024 4 sectors + 24 hr monitor. **\$239** incl AC and 6A recharge battery.

SP-1022 2 sectors + 24 hr sector. **\$199**

GENERAL FEATURES


- 4 (or 2) independent inputs for both NO and NC circuits with selectable instant or delay on each sector.
- 24 hr monitoring on NC circuit to protect horn cover, detectors and other units.
- Built-in powerful siren output, DC 12V 600mA O/P and SPDT relay O/P (contact 1.5A).
- Alarm O/P time adjustable up to 10 min with reset option.
- 24 hr panic switch for instant alarm output.
- O/P facilities to drive telephone dialer.
- Sector report to drive telephone dialer.
- Sturdy steel casing with welded corners.

SENSORS (PHOTOBEAM, ULTRASONIC, PIR, etc) PASSIVE INFRA RED MOVEMENT DETECTORS

PIR
IR-15
IR-17



PIR
1000

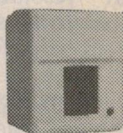

MODEL	IR-15	IR-17	PIR1000
RANGE	12M/100 deg	25M/4 deg	15M/90 deg
ZONES	14/3 planes	6/4 planes	23/3 planes
POWER	15mA/12VDC	15mA/12VDC	25mA/12VDC
FEATURES	adjust head	adjust head	highgain optic
PRICE	\$119.00	\$119.00	\$109.00

Other types (such as 360 degree) available on request.

REED SWITCHES various size and types from **\$2.80** to **\$6.00.**

PRESSURE MAT \$15.00, STAIR TREAD \$10.00.

SECURITY CABLE (WHITE, BLACK, BROWN) 4 cores **\$36.00/100M**; 6 cores **\$48.00/100M.**

WINDOWN TAPE \$6.50/33M TAPE CLIPS 40c.

SUPER QUALITY 120W/8R POWER AMP MODULE \$52.00 mono IMD 0.006% ±50V DC 2.5A, size 78x50x25mm, only 5 wires to connect, full guarantee, slew rate 15V/us, S/N 100dB, 500mV I/P.

BRIDGING UNIT for 2 modules (240W/8R !) **\$20.00**

TOROIDAL TRANSFORMERS, full range to suit the above amp and all ETI and EA MOSFET and high power amp and pre-amps.

ETI and EA CIRCUIT BOARDS

POST & PACKING \$50-\$100 ... \$5.00
Under \$25 ... \$2.00 Over \$100 ... \$6.00
\$25-\$50 ... \$3.00 Heavy items \$10.00

HI-COM UNITRONICS INT P/L

7 President Lane, Caringbah,
NSW 2229. (Next to McDonalds)
Phone (02) 524 7878

BANKCARD WELCOME

Circuit & Design Ideas

Interesting circuit ideas from readers and technical literature. While this material has been checked as far as possible for feasibility, the circuits have not been built and tested by us. As a consequence, we cannot accept responsibility, enter into correspondence or provide constructional details.

Simple pulse generator

This simple circuit is designed for use with EA's Function Generator (April '82) and delivers complementary 1 μ s digital pulse trains.

The input square wave signal is derived from pin 4 of IC7b and applied to an RC network (100pF and 10k Ω) which determines the pulse width. The signal is then buffered using the two spare inverters in the 74C14 to provide the complementary outputs.


Because the 74C14 uses +5V and

-5V supplies, each inverter output drives a single transistor stage to provide a TTL-compatible 5V output. The pulse train frequency is determined by the setting of the front panel controls as before.

Most of the extra parts can be mounted on the back of the PC board and the output run to BNC sockets on the rear panel. Note that it is necessary to isolate pins 9 and 11 from the -5V rail before mounting the extra parts.

M. Hedley,
Chatswood, NSW.

\$15

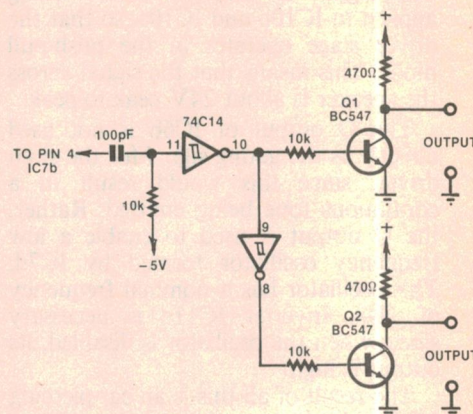

Capacitance meter

This neat little device plugs into any digital (or analog) multimeter and reads any unknown capacitance in the range 3.3pF (0.1pF resolution) up to 2000 μ F (1 μ F resolution), including polarized capacitors such as tantalum and electrolytics. There is nothing to adjust: just plug in the unknown capacitor, switch to high-range (nF) or low-range (pF), and read the capacitance value.

The unit can be made very small and can plug directly into the meter banana sockets. There is only one control switch, a three-position DPDT centre-off type. For correct readout in nF or pF, the reading on the meter must be divided by 10. That is, observe the reading in ohms and then shift the decimal place on one position to the left: it is then in nF or pF. For example an ohms reading of 1M Ω is in fact 100,000pF or 100nF.

IC1a forms an oscillator, the frequency of which is dependant on the value of the unknown capacitor. The output of this oscillator is fed to a monostable formed by IC1b and IC1c.

The resulting signal is then inverted and used to drive the MOSFET (Q1).

The result of all this is that the FET is driven by a signal which has a pulse width proportional to the value of the capacitance connected across the Cx terminals. Because of the 2.2 μ F capacitor, the multimeter measures the average resistance of the MOSFET, which will therefore be proportional to the unknown capacitance.

A 9V battery is required. Note that large leaky electrolytics could cause significant reading error. The measuring terminals are polarised with about 4V peak, so unipolar capacitors can be measured. The multimeter must be set to the ohms ranges.

The 200 Ω trimmer potentiometer is for calibrating the nF range, and the 2k Ω trimmer is for the pF range. The trimmer capacitor is for eliminating stray capacitance when measuring very small values. To calibrate, insert a 0.1 μ F capacitor, set to pF range and adjust the 2k Ω trimmer. Then switch to the nF range and adjust the 200 Ω trimmer. Next insert 10pF and, with the switch set to

pF range, adjust the trimmer capacitor to give the correct reading. Should the 2k Ω pot have insufficient adjustment range, which is unlikely, reduce the 3k Ω resistor to 2k Ω .

B. Kauler,
Collie School of Mines, WA. **\$20**

Checking transistors with a multimeter

Most readers will know how to use an ohmmeter to identify the base of a transistor, and to decide whether it is NPN or PNP. With the addition of a single resistor, one can use the same instrument to distinguish between the collector and emitter, and to estimate the current gain.


Suppose that you have an NPN transistor for which the base has been identified. First connect the base through a 20k Ω resistor to the positive terminal of your analog multimeter. Note that on most multimeters the black lead is the positive one. Now connect the two remaining pins to the two multimeter leads and note the resistance. Swap the two transistor leads around, leaving the base connected. The collector will be connected to the more positive lead (black) when the resistance is lowest.

The gain can be determined from the actual value of the resistance measured. If the resistance were, say, 500 Ω then the current gain of the transistor would be 20,000/500 = 40.

Follow the same procedure for a PNP transistor except that the base must be connected to the more negative terminal of the multimeter.

D. R. Watson,
Corio, Vic.

\$15

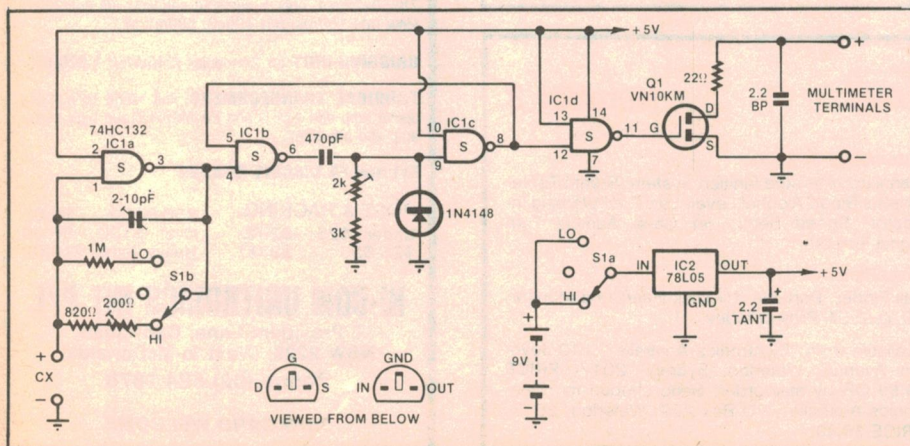

Beeper for vehicle flasher

A vehicle direction indicator which fails to reset can be a real traffic hazard. This often happens after a smooth curve or when changing lanes. If the driver has a high frequency hearing loss this problem is compounded since he cannot hear the flasher relay clicking. This circuit provides a low frequency beeping sound while ever the indicators are on, thus providing a simple solution to the problem.

The LM380 is wired as a phase shift oscillator, the values of the feedback components being chosen to produce a frequency of about 800Hz. The circuit is connected across the flasher relay terminals, and hence will


operate when the flasher contacts are open.

The circuit should be mounted in a small box, and installed near the flasher relay. Before connecting the leads to the relay terminals it is

necessary to determine the correct polarity. This can be done with a multimeter. When operating the circuit draws about 60mA.

H. L. Harvey,
Cairns, Qld.

\$20

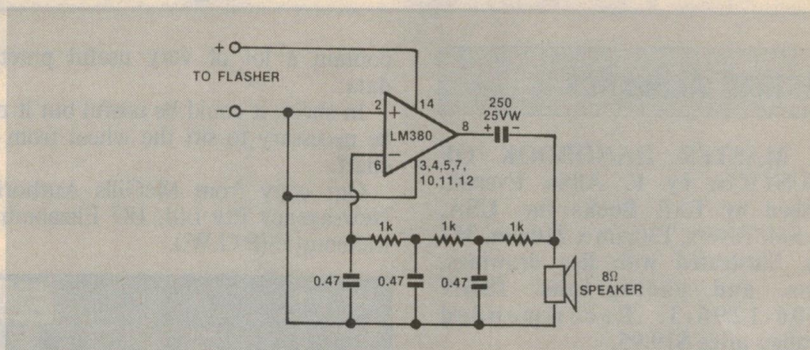

Modification to railmaster train controller

While the Railmaster train controller featured in September EA has a lot of nice features, it does have one drawback. If the controller is switched into reverse while the train is running at speed, it will try to change the direction instantaneously. Depending on the speed of the train, this usually leads to a derailment.

This circuit solves that problem. When the reverse (or forward) position is selected, it initially slows the train according to the inertia setting. Then, when the train has halted, it automatically switches the track polarity and brings the train back up to speed in the new direction, again with full inertia.

Only three ICs and a couple of SPDT relays are required for the modification. Initially, the Q and D pins of IC4 (a 4013 flipflop) are at the same logic level, pin 3

of XOR gate IC5 is low, and Q5 and relay RLA2 are off. The controller thus functions as normal with the voltage set by the speed control pot (VR1) applied to the 47 microfarad capacitor via VR2 and the NC contacts of RLA2.

Suppose that the train is initially travelling in the forward direction. If S3 is now switched to the reverse position, RLA3 will release and pull pin 5 of IC4 and pin 2 of IC5 low via its NC contacts. Thus, the output of IC5 goes high and transistor Q5 turns on and activates RLA2.

The 47 microfarad capacitor on pin 10 of IC1c now discharges via the inertia pot (VR2) and the NO contacts of RLA2 into the low output of IC1a. IC3a is wired as a voltage comparator. When pin 8 of IC1c falls below IC3a's non-inverting input, pin 1 of IC3a switches high and clocks

the low D input on IC4 through to the Q output.


The output of IC5 now goes low and Q5 turns off. At the same time, Q6 turns off and releases RLA1 which switches the track polarity. The train is then gradually brought up to speed in the new direction as the 47 microfarad capacitor charges via the NC contacts of RLA2 and the inertia pot (VR2).

VR4 sets the throttle voltage at which the train reverses direction. It should be set so that the train is almost brought to a halt. Do not set the voltage on pin 3 of IC3a below that on pin 3 of IC1a otherwise the train will never change direction.

Note that S2a (the local/remote) switch has been moved so that the inertia can be set by the pot on the main unit rather than having to wire a separate inertia control into the remote throttle.

B. Wu,
Lindfield, NSW.

\$30

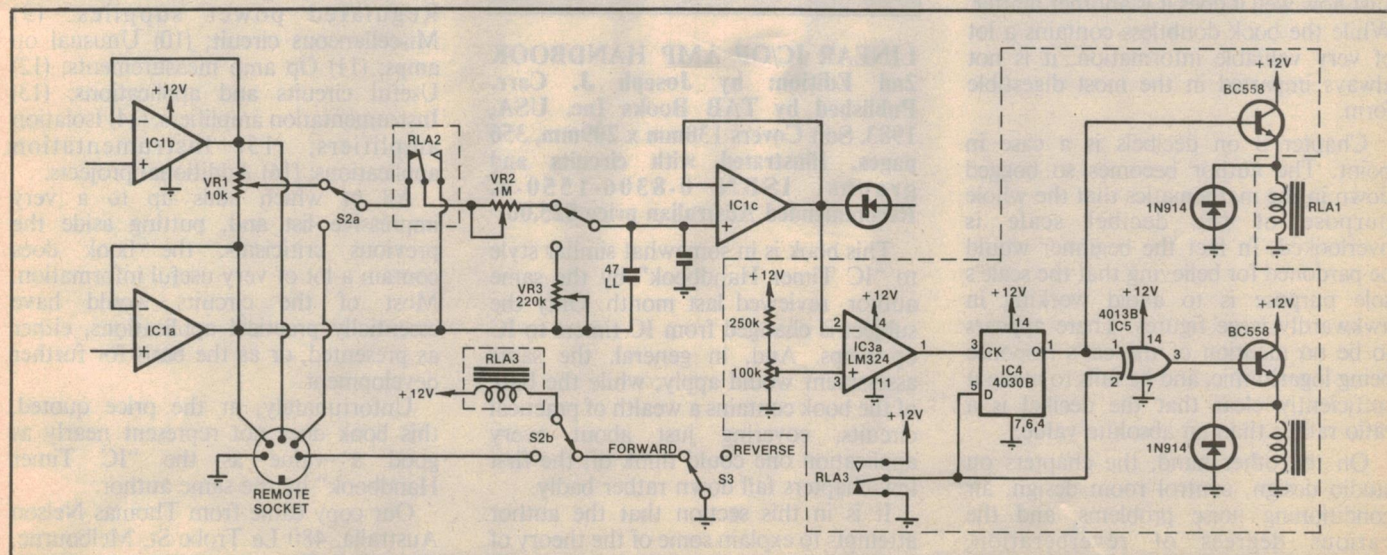

Books & Literature



Practical Acoustics

THE MASTER HANDBOOK OF ACOUSTICS: by F. Alton Everest. Published by TAB Books Inc. USA, 1981. Soft covers, 130mm x 210mm, 352 pages. Illustrated with line drawings, graphs, and photographs. ISBN 0-8306-1296-3. Recommended Australian price \$19.95.

This book is intended to cover the subject of acoustics from the fundamentals of sound and hearing to the practical problems involving control of acoustic characteristics — echo, reverberation, etc — in studios, listening rooms domestic environments, and how these may be measured, evaluated, and controlled.

The book contains 17 chapters, under the following headings (abbreviated): (1) Sound fundamentals; (2) Hearing; (3) The decibel; (4) Sound outdoors; (5) Comb filter effects; (6) Sound indoors; (7) Echoes; (8) Reverberation; (9) Noise, music and speech; (10) Absorption; (11) Diffusion; (12) Quiet studio ventilation; (13) Home listening room; (14) Building a studio; (15) Multitrack recording; (16) Control room; (17) Acoustical measurements. There is also an appendix of sound absorption coefficients.

From the above it can be seen that the book endeavours to cover a very wide range of acoustic theory and practice. Just how well it does it is another matter. While the book doubtless contains a lot of very valuable information, it is not always imparted in the most digestible form.


Chapter 3 on decibels is a case in point. The author becomes so bogged down in the mathematics that the whole purpose of the decibel scale is overlooked. In fact the beginner would be pardoned for believing that the scale's sole purpose is to avoid working in awkwardly large figures. There appears to be no mention of the ear's response being logarithmic, and he fails to make it sufficiently clear that the decibel is a ratio rather than an absolute value.

On the other hand, the chapters on studio design, control room design, air conditioning noise problems, and the various degrees of reverberation, absorption etc required, would seem to

contain a lot of very useful practical data.

In short, it could be useful but it may be necessary to sift the wheat from the chaff.

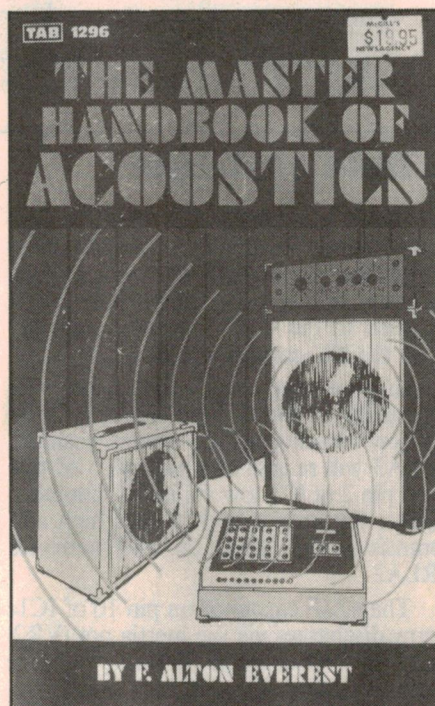Our copy from McGills Authorised Newsagency Pty Ltd, 187 Elizabeth St, Melbourne (P.G.W.).



Component data

LINEAR IC/OP AMP HANDBOOK 2nd Edition: by Joseph J. Carr. Published by TAB Books Inc. USA, 1983. Soft Covers 130mm x 209mm, 356 pages. Illustrated with circuits and graphs. ISBN 0-8306-1550-4. Recommended Australian price \$25.00.

This book is in somewhat similar style to "IC Timer Handbook" by the same author, reviewed last month. Only the subject is changed from IC timers to IC op amps. And, in general, the same assessment would apply; while the bulk of the book contains a wealth of practical circuits, covering just about every application one could think of, the first few chapters fall down rather badly.

It is in this section that the author attempts to explain some of the theory of op amps. It is not that he is lacking in his

LINEAR IC/OP AMP HANDBOOK-2ND EDITION

Packed with exciting new circuit applications for every electronics purpose!

BY JOSEPH J. CARR

own understanding of the subject, on the contrary he understands it too well to make a good teacher. As before, he pushes the reader in at the deep end on the assumption that he can already swim — or at least dog-paddle!

For the student who is really unfamiliar with the subject — and it is assumed that this is the type of person who would be attracted to the book — this approach is more likely to frighten him off, with the fear that he could never understand it.

The book has 16 chapters and four appendices and their headings (abbrev.) are as follows. (1) Inverting followers; (2) Non-inverting followers; (3) Differential amplifiers; (4) Op amp problems; (5) Op amps in computation; (6) Op amp instrument design. (7) Active filters; (8) Regulated power supplies; (9) Miscellaneous circuit; (10) Unusual op amps; (11) Op amp measurements; (12) Useful circuits and applications; (13) Instrumentation amplifiers; (14) Isolation amplifiers; (15) Instrumentation applications; (16) Additional projects.

All of which adds up to a very impressive list and, putting aside the previous criticisms, the book does contain a lot of very useful information. Most of the circuits would have essentially practical applications, either as presented, or as the basis for further development.

Unfortunately, at the price quoted, this book does not represent nearly as good a value as the "IC Timer Handbook" by the same author.

Our copy came from Thomas Nelson Australia, 480 La Trobe St, Melbourne, 3000 (P.G.W.).

ALTRONICS 1985 SUMMER SALE



Dear Electronics Enthusiasts,
Over the last 3 years we have grown enormously — Warehouse now triple in size, Mail Order/Phone Order Department Sales up several hundred percent.
All this has been made possible by the enthusiastic support of countless 1,000's of Altronics Customers throughout every Australian State and (incredibly) many more in New Zealand, PNG, Fiji, Singapore even Pakistan!

As a very special thank you I've decided to run this Sale—as you look through these pages you'll notice dozens of incredible bargains, many 1/2 price, but **don't let our low prices put you off** — All items are genuine Altronics quality products and our famous 14 day money back satisfaction guarantee applies. Like all Sales the offers are valid whilst current stocks last. As I expect many items to sell out quickly, I urge you to phone your order right now. Remember our Toll Free Line (costs you a local call fee only) Phone—008 999 007 or if this is continually engaged 09 3281599.

Our deep appreciation once again to all of you for your loyal support over the years.


JACK O'DONNELL
and STAFF

Jack O'Donnell

Incredible Price Savings Many Items 1/2 Price

Superb full 60 Key Computer Keyboard as used with Microbee Computer Brand New

"MICROBEE KEYBOARD"

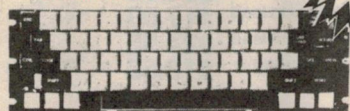


ONLY \$19.50
D1510
\$29.95

BICYCLE COMPUTER

INCREDIBLE 12 FUNCTION CAT D 2050


WHY PAY \$90
NOW \$49

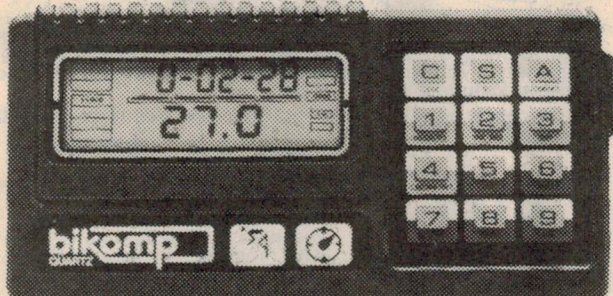The brilliant BIKOMP COMPUTER that is all the rage in USA is now available in Australia. For a few dollars more than a digital speedo this superbly accurate computer provides every activity readout the enthusiast cyclist is ever likely to require.



- * Instantaneous, Average & Peak Speed Readouts.
- * Measures Calories Used per Trip.
- * Measures Distance.
- * Clock, Stopwatch and journey time (whilst Mobile)

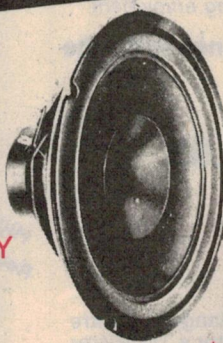- * Miles or Kilometres
- * Pacer Tone and Performance Monitor
- * Dual Display
- * Easy Removal for Security
- * Fits to Bike in minutes



DAINICHI WIDE RANGE 25 Watt

200mm (8"). This superbly smooth high power speaker comes from Dainichi, one of Japan's finest speaker manufacturers (they produce OEM Speakers for Pioneer). Max. input power 25W 8 OHM Z. Resonant fo. 60Hz.

C 2001 ... \$22.50

1 - 9 10 UP \$15 \$12 ea.

VHS 3 hr New Altronics Import


We've tested the lot Well how does ME stack up? — in a word superb

Forget all about paying a premium for BASF or TDK — Altronics positively guarantee our new ME Metallic is equal to the very best — and that goes for mechanical construction as well as picture quality!

1 - 9 10 - 19 20 + \$10 \$9 \$8

IMPORT SCOOP

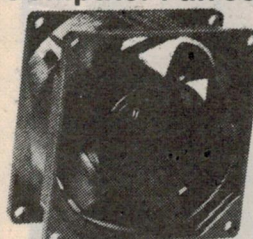Quality Commonwealth Computer Fan 80MM - 240V




CAT F 1020

\$12 4 or More \$11

Amazing Value

- * Super quiet
- * Sealed sleeve bearings for long life
- * Sturdy die cast frame
- * Operating range — 10 deg C to + 70 C

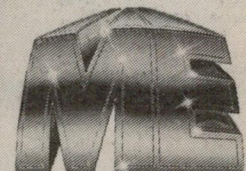HIGH OUTPUT HIGH RESOLUTION
SUPER HIGH GRADE




E-180 SUPER HG
SUPER METALLIC

Don't Forget Altronics Famous Overnight JetSERVICE Delivery

Phone Order Right Now for Delivery to your Door Tomorrow ★

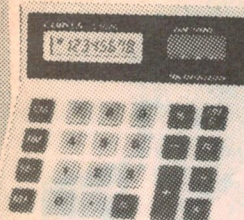★ Capital Cities and Suburbs—allow 24-48 hours additional for Country Centres.



Runs forever without Batteries! Solar Powered Desk Calculator


This superb Calculator could easily pay for itself during a lifetime without buying a single battery. Our exciting new all Solar Desk Calculator was not due for release until Feb 1985, but, with a little pleading with the maker, here it is just in time for Xmas. * Runs equally well under office or home lighting as well as sunlight * All standard calculator functions including memory function etc. A fantastic gift idea for Mum or Dad.

Cat No.X 1060 ~~\$19.95~~

Why not treat yourself? Now Just **\$15**

Get Movie Theatre Stereo Sound from your Video Recorder

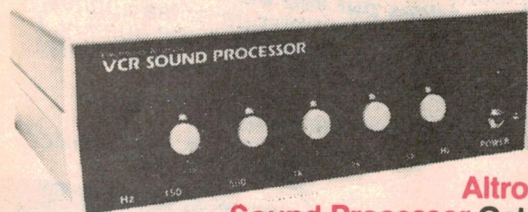Connect your VHS or Beta Video to your home Stereo System via. this superb Stereo Simulator



WHY
PAY
\$295?

Our Price
\$99

**Altronics Video
Sound Processor Cat No A 9916**

Lets face it, the mono sound you get from your typical VCR is dull, colourless and boring. This is a crying shame, as these days, movie makers invariably add outstanding stereo sound and sound effects to the movies they produce. Next time you visit a modern movie theatre you will see (hear!) what we mean. Now a quite phenomenal enhancement to your VCR audio quality and impact realism can be achieved by feeding the Video sound O/P through your home HiFi system via. EA's simply brilliant VCR Sound Processor. Not only does it give simulated stereo but the inbuilt 5 stage graphic equaliser provides tonal depth for added realism and listening enjoyment.

Got an hour or two of spare time? Why not build the Kit Version.

K 5820 only **\$55.00**

K 5821 Opt.Whistle Filter **\$19.95**

PRECISION ELECTRONIC FET MULTIMETER FOR LABORATORY OR WORKSHOP

* 10 Meg. Ohm input * 12 Amp DC and AC Current Ranges * Centre Zero Pointer Adjust for + and - readings LED indicator * Transistor Tester Inbuilt * P—P calibrated scale.

Brilliant FET Volt/Ohm Meter includes Centre Zero needle setting — allows + and - readings. Meter Scale fully calibrated for + and - readings.

DC VOLTS

Ranges
0-0.3, 1.2, 12, 30, 120, 300, 1200V
0- + 0.15, 0.6, 6, 15, 60, 150, 600V
at Centre 0.

AC VOLTS

Ranges
RMS 0-0.3, 12, 30, 120, 300, 1200V
Peak-peak, 0-8.4, 33, 84, 330, 840, 3300

DC CURRENT

Ranges
0-0.1 uA 0.3, 3, 30, 300mA, 12A
Potential Drop
300mV


AC CURRENT

Ranges

0-12A
DC RESISTANCE

Ranges

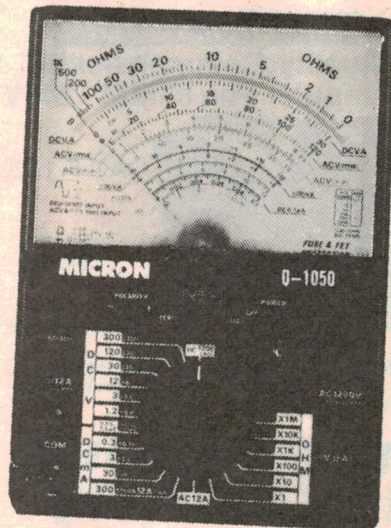Rx1 0-1K ohm (Centre 10)
Rx10 0-10K ohm (Ctr.100 ohm)
Rx100 0-100K ohm (Ctr.1K ohm)
Rx10K 0-10M ohm (C.100K ohm)
Rx1M 0-1000M ohm (C.10M ohm)



Q 1050 be quick **\$49**

**14 day Money Back
Satisfaction Guarantee**

Amazing Low Cost Smoke/Fire Detector

Never again need you or your children
risk death or injury thru house fire.

This Incredible low cost ceiling mount detector senses particles of combustion (smoke) at earliest stages of fire eg. smouldering * Deafening Alarm * Attractive ceiling Mounting type * Dead easy to fit—you only need a screw driver * Low cost 9V battery lasts approx.1 year.

Don't let the low price fool you, this is a Brilliantly designed dual chamber ionization detector.

A 0090
\$14.99

Were \$59.95
Scoop Purchase



FAMOUS VOYAGER CAR COMPUTER

Cat.No D 1000

Monitor your fuel economy as you drive in MPG & or Metric. Better than a \$700 plus unit optional in new cars. Many other features. All fitting hardware included.



FEATURES: * Instant fuel consumption in litres/100km and MPG (most others have only one of the above) just switch from one to the other as you drive along. * Instant speed, time and other fuel data. * Visual and audible excess speed alarm.

Just In! Home Telephone Extension Cords and Adaptors

Now you can have your Telephone in the backyard or just on the other side of the lounge room with these nifty telephone leads. Double Adaptor allow two phones into the one line. Ideal for cordless phones etc.

P 0990 5 Metre extn.lead **\$14.95**
P 0992 10 Metre extn lead **\$17.50**
P 0994 20 Metre extn lead **\$24.95**
P 0995 Phone Dble Adpt. **\$12.50**

Double Adaptor

Highly Recommended VideoTape RepairKit



A VHS/BETA Video Tape Repair Kit. No need to throw out your damaged tapes—this nifty splicing kit can save you a fortune (if you've got small children this kit will save you several fortunes!!)

All accessories included for joining tape and refixing leader ends etc.

A 9315 Fantastic Value **\$7.95**

At Last!
**Head Cleaners
That Really Do
A 100% Job**



Our exciting range of head cleaners are the best we've seen and more importantly they are gentle on your heads. Why risk damaging your video or audio cassette player with inferior units.

Audio Cassette

Type A 9200
Were \$5.95 Now **\$3.95**

Beta Video

Type A 9300
Were \$17.50 Now **\$9**

VHS Video

Type A 9310
Were \$17.50 Now **\$9**


DE-SOLDER BRAID



T1230 \$1

HEATSINK COMPOUND

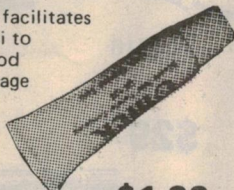Heat conducting paste facilitates heat transfer from semi to Heatsink. One tube good for up to 30 TO3 package semiconductors.



H 1600...7.5g Pack. \$1.20
New trade pack

H 1610...150g Pack. \$7.50
SAVE UP TO 33%

SUPER TYPE GLUE

New patented easy flow Dispenser and carry tube dispenses only when tube body is depressed—ensures no leaks. Many times the number of bonds over conventional tubes.

Sticks in seconds—1000' of uses



T 3010

~~\$2.95~~

\$2

PROFESSIONAL QUALITY

SOLDER SUCKERS

Not to be compared with Inferior 'Hobby types'. Saves countless hours in fault finding and repair of complex PCB's.

SINGLE HANDED OPERATION
SELF CLEANING PLUNGER
LONG LIFE TEFLON TIP
DOUBLE DIAPHRAGM,
DUAL O-RING SEAL
225mm x 20mm(d)
50mm STROKE
POWERFUL SUCTION



T1240. only ~~\$11.95~~

T1241. Replac tip. \$1.95

Professional Nicad Rechargeable Batteries

From \$1.69



S 5020 "AA" Penlight 1.95 10+
S 5022 "C" Size 4.95 3.99
1.65 AH

VINYL BINDER


Holds 12 magazines, each on a spring out wire rod. Just the shot for each year's set of Electronics Australia, ETI or any of your favourite magazine.

Suits all A4 size publications (275 x 210). Very smart Royal Blue colour with beautiful gold embossing.

B 9999.....\$5.50

THIS MONTH \$5.00

4 or more \$4.50 ea.

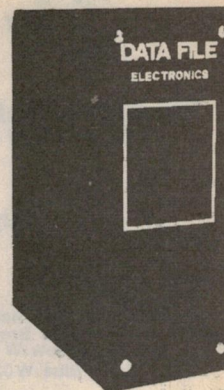

PROFESSIONAL AUTOMATIC WIRE STRIPPER

Automatically adjusts to insulation / wire diameter. This absolutely brilliant stripper is the finest we've ever used.



\$5

T 1520

~~\$9.50~~


All quality Altronics Imports — Not "Hobbyist" Seconds

LOOK

Hardware Prices from less than 1 cent per piece

DIL SWITCHES

GOLD PLATE SELF WIPING CONTACTS

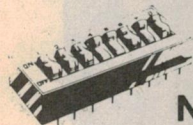

From 80¢
Near 1/2 Price

		ea.	25 Up
S 3050	4 way	90¢	80¢
S 3060	8 way	1.25	1.00
S 3065	10 way	1.50	1.35

ULTRASONIC TRANSDUCERS



D=16mm H=12mm

Ultrasonic transmitter and receiver transducers operating at 40KHz + or - 1KHz. Perfect for security applications etc. i.e. alarm sensors, counting sensors, remote control sensors and many other uses.

Sensitivity S 5115 TX 106db S 5110 RX 65db
Dispersion angle 20 deg. Max input voltage 20V
RMS Impedance S 5115 500 Ohms S 5110 30K Ohm. Operating range up to 9M.

S 5110 Receiver \$4.95 10 up \$4.50
S 5115 Trans \$4.95 10 up \$4.50

RUBBER FEET

H 0913 STD 13mm \$6
H 0942 Stickon 12mm \$8
H 0952 Stickon 20mm \$9

Packs 100



H 0800

NOW \$1.50



Rubber Grommets

Chassis Hole 9.5mm
Cable Size 5-7mm
H 1450.... 60¢

Nylon Cable Clamps

Cat. No.	Pack	Size	Price
H 1480	6	6mm	.55
H 1481	100	6mm	5.00
H 1485	6	9mm	.60
H 1486	100	9mm	6.00



Cordgrip Clamps

Packs 100



H 1476 Cables to 9mm \$9

H 1471 Cables to 6.3mm \$8

Quality Plated Screws at less than Wholesale Prices

Whitworth — Steel Nuts and bolts (Roundhead) Zinc Plated

	Length	Pack Qty	Price
H 1002	9mm	500	\$4.50
H 1007	12mm	500	\$4.50
H 1011	25mm	500	\$6.00
H 1022	Hex Nut	500	\$5.00
H 1032	S/Proof Washer	500	\$6.00

BA Bolts Cheesehead Steel, Nuts Brass

	Length	Pack Qty	Price
H 1050	4BA/12mm	25	50¢
H 1060	6BA/12mm	25	50¢
H 1070	Nuts 4BA	25	90¢
H 1080	Nuts 6BA	25	90¢

Nickel Plated Brass Spacers

Packs 100



TAPPED 4BA
H 1380 Length 9mm \$8
H 1384 Length 12mm \$10
H 1388 Length 25mm \$15

UNTAPPED 4BA or 1/8" Clearance

H 1359 Length 6mm \$7
H 1365 Length 9mm \$8
H 1374 Length 12mm \$9
H 1376 Length 25mm \$12



Pro Grade Hook Up Wire All on 100M Reels

Light Duty
Tinned
13/.012

\$5

**Buy Eight Reels
For Only \$30**

W 0250 Red W 0251 Black
W 0252 Brown W 0253 Orange
W 0254 Yellow W 0255 Green W 0256
Blue W 0257 White

Medium Duty
Tinned
14/.20

\$8

**Buy Four Reels
For Only \$28**

W 0260 Red W 0261 Black
W 0268 White W 0265 Blue

Heavy Duty
24/.20

\$10

**Buy Four Reels
For Only \$30**

W 0270 Red W 0272 Black
W 0274 Green W 0276 Brown
W 0278 Blue

Extra H/Duty
32/.20

\$15

**Buy Two Reels
For Only \$25**

W 0280 Brown W 0282 Blue

PRICE SENSATION Wire and Cable Sellout!!!

All Supplied on Sturdy
Reels—Not those
tanglesome Rolls!!

SHIELDED AUDIO CABLES

Supplied on 100m reels (not Hanks). Eminently Suitable for microphone cables,
chassis wiring, building wiring.



W 0211

SINGLE CORE

\$18



W 0214

TWIN CORE

\$29



W 0216

TWIN CORE

Fig "8"

\$29



W 0219

4 CORE

\$49



TV Feeder 300 Ohm
W 0220 Flat Ribbon **\$15**

COAXIAL

W 0222 TV 75 Ohm STD **\$25**
W 0224 TV 75 Ohm Low Loss **\$35**
W 0226 RG 58 AU 52 Ohm **\$29**



FIGURE "8" CABLE

For Speaker Wiring, Security Systems, PA
Systems, Low Voltage Wiring etc. All
include polarity trace.

W 0200 2X 14/.14
100m **\$6**

W 0201 2X 14/.19
100M **\$8**

W 0204 2X 19/.193
Red Trace Band
200M **\$25**

W 0205 2X 19/.193
Black Trace Band
200M **\$25**

W 0208 2X 24/.20
Red/Black
200m **\$30**

FROM \$6

**Phone your Order Toll Free
On 008 999 007**


PHOTOGRAPHIC XENON TUBE



Great For Strobe
Light Projects

S 4050 ~~\$2.95~~
Now \$2.00

VELOSTAT

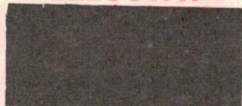


Non-Static sheeting for storing CMOS
IC's, LSI's etc. 1000 times better than
aluminium foil. Will store up to 150 IC's on
one 225 x 150mm sheet.

H 0500 ~~\$3.50~~ **\$2.00**

2N3055'S SLASHED

Z1174

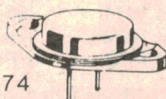

PRIME SPEC S.G.S.

1 - 9 10 - 24 25 - 99 100+
95¢ 90¢ 80¢ 70¢

FUZES 3AG



S 5940 100MA	S 5950 1A	S 5960 7.5A
S 5942 150MA	S 5952 1.5A	S 5962 10A
S 5944 250MA	S 5954 2A	S 5964 15A
S 5946 500MA	S 5956 3A	S 5966 20A
S 5948 800MA	S 5958 5A	S 5968 25A
		S 5970 30A

1 - 9 .20
10 - 99 .15
100 plus .10
Mixed 500 .08

FUSES M205

20 x 5mm

S 5910 250MA	1 - 9 .20
S 5912 500MA	10 - 99 .15
S 5914 1A	100 plus .10
S 5916 2A	Mixed 500 .08
S 5918 5A	

MINI PCB RELAYS

Low Profile 14H x 20W x 12D

12V DC Bobbin
1 AMP Contact Rating

S 4060 SPDT **\$2.00**

Now \$1.80 10+ \$1.50

S 4061 DPDT **\$2.50**

Now \$2.00 10+ \$1.70



MINI PCB RELAY H/D

Low Profile 15mm (H)

12V DC Bobbin 3 AMP
Contact Rating


S 4066 SPDT **\$2.75**

10 Up **\$2.25**

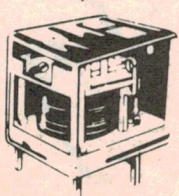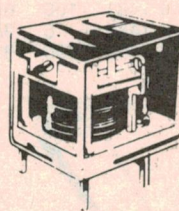

"Save up to 60%
on these prices"

IDC COMPUTER CABLE

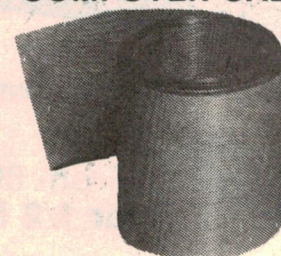

	Per Metre	Per M
W 0610 10 wire	.99	.89
W 0616 16 wire	1.59	1.39
W 0626 26 wire	2.59	2.29
W 0634 34 wire	2.99	2.69
W 0650 50 wire	5.99	4.99

HEAVY DUTY RELAY

S 4074 ~~\$9.95~~

**NOW
\$7.00**



12V coil 10 AMP DPDT contacts
OEM Quality. Heavy Duty Relay. Ideal for
power supply and control circuit switch.
Socket allows easy chassis mounting and
quick cable connection to screw
terminals.

SCREW TERMINAL

OCTAL SOCKET TO SUIT

S 4075 **\$3.95** 10 up **\$3.50**

COMPONENT JOYSTICKS

Standard type
(non-centering)

- Resistance 100K ohm
- Lever movement 60°
- Metallic knob
- For TV games, RC units
- Life 300,000 cycles

K 9680
~~\$4.95~~



Self Centering Type


Resistance 5K ohm suit ETI project for microbee
Proportional Analogue Joystick Dec 1983

K 9689 ~~\$17.50~~ **NOW \$7.50**

Micro Switch Bargains


250V 3A

Single Pole c/over Contacts

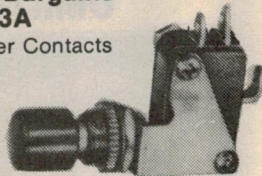

Push Button Type

S 3255 **\$2.00**
10 Up **\$1.70**

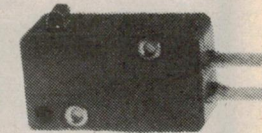

S 3250 **\$1.25**
10 Up **95¢**

MINI TOGGLE SWITCHES

OEM QUALITY 250V 2 AMP RATED

6mm mounting hole
12mm x 12.7mm x 20mm (D)



SAVE 30%

ea. 10 Up
S 1010 SPDT **\$1.00 .90**
S 1025 SPDT Centre off **1.10 .90**
S 1020 DPDT **1.10 .99**
S 1030 DPDT Centre off **1.50 1.20**

STANDARD TOGGLE

Sturdy Reliable 125V/3 AMP Rating



S 1040 SPST **\$1.00**
10 up **.90**
S 1050 DPDT **1.30**
10 up **1.10**

HEAVY DUTY TOGGLE

DPDT CENTRE OFF
125V/10A (250V AC/5A)
Ideal for car antenna switch,
automotive and marine
electrical use.



S 1055 **\$1.95**

SEALED PCB MOUNT ROTARY SWITCHES

Why Pay Over \$3 ?

1 - 9 **\$2.00**
10-24 **\$1.80**
25-99 **\$1.60**
100 + **\$1.40**



"Lorlin Style"


A real plus feature is the ability to set the number of stops to suit your own distinct requirements, e.g. A 1 pole 9 position is easily implemented using our S 3021.

S 3021 1 Pole
Configure from 1 pole 2 position through to 1 pole 12 position
S 3022 2 Pole
From 2 pole 2 position to 2 pole 6 position
S 3025 3 Pole
From 3 pole 2 position to 3 pole 4 position
S 3024 4 Pole
From 4 pole 2 position to 4 pole 3 position

**Remember Altronics deliver Next Day via JetService
Courier to all Capital Cities and suburbs—Country Areas
please allow extra 24—48 hours.**

Insulation Displacement Connectors

PCB Male Headers
with Lock Levers

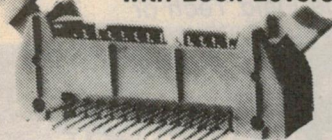

90 Degree Type		Were	Now	10 Up
P 0926	26 pin	3.95	2.50	2.00
P 0926	34 pin	4.95	3.20	2.95
P 0932	50 pin	6.50	3.90	3.40


Straight Type		Were	Now	10 Up
P 0939	26 pin	3.95	2.50	2.00
P 0941	34 pin	4.95	3.20	2.95
P 0945	50 pin	6.50	3.90	3.40

Cable Mounting Socket (Female)

		WERE	NOW	10 UP
P 0952	26 pin	3.95	2.50	2.00
P 0954	34 pin	5.90	3.90	3.40
P 0958	50 pin	6.90	4.00	3.50

**Amazing
Value**

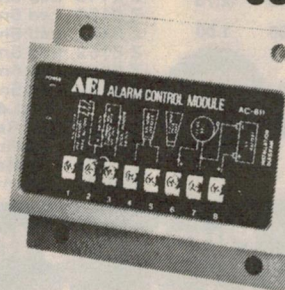EASY TO INSTALL ★ BUILT IN
SIREN DRIVER—DIRECTLY
DRIVES LOW COST 8 OHM
HORN SPEAKERS, SIREN
HORNS AND MECHANICAL
BELLS ★ LOW POWER 12V DC
OPERATION.



S5042
Only ~~\$39.50~~

Now \$32.50


ALARM CONTROL MODULE

The AC-811 is a low cost professional burglary protection system which detects the presence of an intruder who breaks into your home, office or business. The system also allows connection of emergency panic buttons, wall vibration switches, smoke and heat sensors, as well as freezing or flooding detectors to form a complete protection system.

EXIT/ENTRY DELAY
BOTH N/C AND N/O CONTACTS
**Ideal for homes,
offices, factories,
shops, caravans, any
area requiring
protection.**


MINI BUZZER 1.5-5V DC

SENSATIONAL LOW PRICE

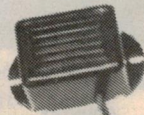

Handy little solid-state audio "Buzzer" or signalling device. Just the shot for communicator panels, or for timer alarms or in the car. Polarity conscious.

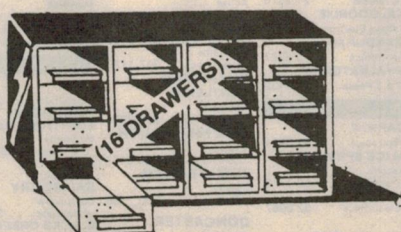S5062 ~~\$1.95~~ **Now \$1**
16 WAY PARTS DRAWER SET



See through acrylic parts drawer. Slide-in ident. card fronted drawers. Ident. cards supplied.
VALUE PLUS!

H 0440 ~~\$17.50~~ **Now \$15.00**

WEATHERPROOF SIREN HORN

12V DC operated — Deafening Siren
Wail. Super handy for audio signalling, security systems etc. Current drain 500MA approx. Completely weatherproof. Attractive off-white PVC finish.



S 5058 ~~\$19.50~~ **NOW \$15.00 ea.**
STRENGTH!

PIEZO ALARMS

Similar to "Sonalert" type. Absolutely ear piercing sound. Recommended voltage 5-15V DC. Ideal for almost all audio signalling applications. i.e. fire, water and gas signalling, computer alarms, etc.




S 5066 **\$4.95 Now \$3.50**
Dual Function Type
Pulsed or Continuous output
S 5070 **\$5.95 Now \$4.50**

IDC DIL PLUG HEADERS

		Were	Now
P 0917	14 pin	1.50	1.10
P 0918	16 pin	1.80	1.50
P 0920	24 pin	2.50	2.10
P 0921	40 pin	3.50	2.95

EGAD!!

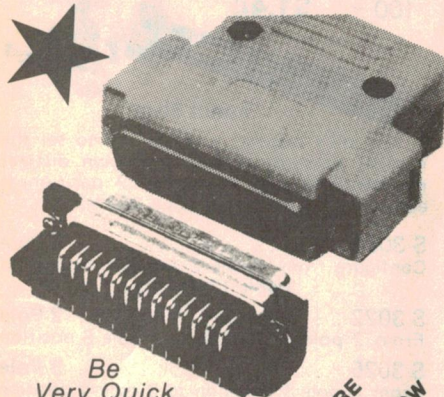Popular D Range
Computer
Connectors all
1/2 Price



Be
Very Quick
This Month Only

	WERE	NOW
P 0880 DB 9 Male 9 Pin	2.50	1.25
P 0881 DB 9 Female 9 Pin	2.95	1.50
P 0882 DB 9 Male PCB Mnt	3.25	1.60
P 0883 DB 9 Female PCB	3.95	2.00
Mount		
P 0885 DB 9 Backshell Cvr	1.80	.90
P 0890 DB15 Male 15 Pin	2.95	1.50
P 0891 DB15 Female 15 Pin	3.50	1.75
P 0892 DB15 Male PCB Mnt	3.95	2.00
P 0893 DB15 Female PCB	4.95	2.50
Mount		
P 0895 DB15 Backshell Cvr	2.00	1.00
P 0900 DB25 Male 25 Pin	4.50	2.25
P 0901 DB25 Female 25 Pin	4.95	2.50
P 0902 DB25 Male PCB Mnt	4.50	2.25
P 0903 DB25 Female PCB	5.50	2.75
Mount		
P 0905 DB25 Backshell Cvr	2.00	1.00


Stock Up Now
and Save
a Bundle



SPEAKER 8 OHM
2 1/4 INCH
From 69¢

C 0610
1 - 9 \$1
10 - 99 90¢
100 up 69¢

ECONOMY RACK CABINET

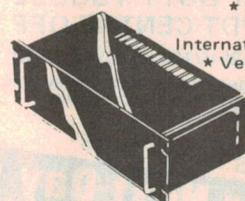

- * Solid steel construction
- * Black anodised front panel
- * 3 unit (132mm)
- * Conforms to International Standards
- * Ventilated top and side panels


H 0400 ONLY
~~\$45.00~~
\$40

LEDs

	ea	10 Up
Z 0140 Led 3mm Red	.14	.10
Z 0141 Led 3mm Green	.20	.18
Z 0143 Led 3mm Yellow	.22	.20
Z 0150 Led 5mm Red	.14	.10
Z 0151 Led 5mm Green	.20	.18
Z 0152 Led 5mm Yellow	.22	.20
Z 0154 Led 5mm Orange	.25	.22
Z 0159 Led 5mm Flashing FRL4403	.49	.45
Z 0160 Led Rectangular Red	.22	.19
Z 0162 Led Rectangular Green	.25	.22
Z 0164 Led Rectangular Yellow	.25	.22
Z 1072 Led Infra Red CQY89A	.55	.52

DIODES SLASHED DIODES SLASHED

MASSIVE
SAVINGS

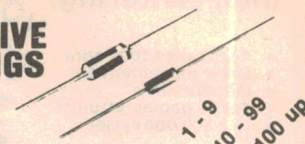

Z 0101	1N914/1N4148 Diode	.05	.04	.03
Z 0105	1N4002 100V 1 Amp	.06	.05	.04
Z 0109	1N4004 400V 1 Amp	.07	.06	.05
Z 0112	1N4007 1000 1 Amp	.08	.07	.06
Z 0115	1N5404 400V 3 Amp	.15	.12	.11
Z 0118	1N5408 1000V 3 Amp	.16	.13	.12
Z 0120	R250 A 400V 6 Amp	.60	.50	.45

Technician's
Multimeters 10K
Ohm/Volt



Robust
Meter
Movement

NOW
JUST
HALF
PRICE

Q 1015

\$9.90

Limited Stocks at This Price

DC Volts	5 ranges	.25	to	1000V
AC Volts	4 ranges	10	to	1000V
DC Current	3 ranges	100 MA	to	.5A
Resistance	3 ranges	100 Ohm to 10K	centre scale	

Positively 1st Class For
the Field Tech or
Bench Enthusiast

Purchasing from Altronics Resellers

Please note that dealers have additional costs such as freight etc. and in most cases dealer prices will be somewhat higher than offered here. Dealer prices will, however, represent a considerable saving on our competitors prices

ALTRONICS

105 STIRLING ST. PERTH — FOR INSTANT SERVICE

008 999 007 TOLL FREE
(09) 328 1599 PERTH METRO AREA & AFTER HOURS RECORDED SERVICE
All Mail Orders: Box 8280, Stirling St. Perth, WA 6000

PACKING AND DELIVERY CHARGES

\$3.00 Delivery Australia Wide - We process your order the day received and despatch via Australia Post. Allow approx. 7 days from day you post order to when you receive goods. Weight limited 10kgs

\$5.00 Overnight Jetservice - We process your order the day received and despatch via overnight Jetservice Courier for delivery next day. Country areas please allow additional 24-48 hours. Weight limit 3kgs

\$10.00 Heavy Heavy Service - All orders of 10kgs or more must travel express Road - Please allow 7 days for delivery

Insurance - As with virtually every other Australian supplier, we send goods at consignee risk. Should you require comprehensive insurance cover against loss or damage please add 1% to order value minimum charge \$1. When phone ordering please request Insurance

Toll Free Phone Order - Bankcard Holders can phone order toll free up to 6pm Eastern Standard Time. Remember with our Overnight Jetservice we deliver next day.

WA

COUNTRY

ALBANY BP Electronics 41 2681

ESPERANCE

Esperance Communications 71 3344

GERALDTON

K & B Electronics & Marine 21 2176

KALGOORLIE

Today's Electronics 21 2777

MANDURAH

Kentronics 35 3227

WYALKATCHAM

D & J Pease 81 1132

NT

DARWIN

Ventronics 81 3491

ALICE SPRINGS

Ascom Electronics 52 1713

Farmar Electronics 52 2967

ACT

CITY

Electronic Components 80 4654

Scientronics 54 8334

Australia 47 5172

VICTORIA

CITY

Active Electronics 602 3499

All Electronics Components 662 3506

McGraths Electronics 347 1122

SUBURBAN

BENTLEIGH

Absolute Electronics 557 3971

BOX HILL SOUTH

Eastern Communications 288 3107

CHELTENHAM

Talking Electronics 550 2386

DONCASTER

Clipstone Electronics 84 2868

FOOTSCRAY

Acron Electronics 889 1911

SOUTH CROYDON

Truscott Electronics 723 3860

COUNTRY

BENDIGO

K & C Johnson 41 1411

MILDURA

Electronic and Digital Services 23 3380

MOREWELL

Morewell Electronics 34 6133

SHEPPARTON

GV Electronics 21 8866

QUEENSLAND

CITY

Delouand P/L 2296155

SUBURBAN

FORTITUDE VALLEY Electronics 832 3944

St Lucia Electronics 523547

SALISBURY

Colourview Wholesale 2753188

SLACKS CREEK

David Hall Electronics 2088808

TOWONG

ECQ Technics 3710879

COUNTRY

CAIRNS

Thompson Instrument Services 512404

BUNDABERG

PM Electronics 728 272

GLADSTONE

Purely Electronics 724321

NAMBOUR

Nambour Electronics 411604

PALM BEACH

The Electronic Centre 341248

ROCKHAMPTON

Purely Electronics 21058

TRIDENT

Hunts Electronics 329677

TOWNSVILLE

Solex 722015

SA

CITY

Force Electronic 212 2672

Protronics 2123111

Gerard & Goodman 223222

SUBURBAN

DAVID RYAN Electronics 982 7500

BRIGHTON

Brighton Electronics 296 3531

CHRISTIES BEACH

Force Electronics 382 3366

KESWICK

Freeway Electric Wholesalers 297 2033

PROSPECT

Jensen Electronics 269 4744

REYNELLA

Force Electronics 381 2824

COUNTRY

MT. GAMBIER

South East Electronics 250 034

PT. LINCOLN

West Coast Elect Supplies 824 346

TASMANIA

CITY

D & I Agencies 34 7877

GEORGE HARVEY

Hobart 34 2233

Launceston 31 6533

NSW

CITY

David Reid Electronics 267 1385

Jaycar 264 6688

Radio Dispatch 211 0191

SUBURBAN

CARLINGFORD Jaycar 745 3077

DEE WHY David Ryall Electronics 982 7500

HURSTVILLE

Jaycar 570 7000

LEWISHAM

PrePak Electronics 569 9770

MATTRAVILLE

Creative Electronics 666 4000

COUNTRY

ALBURY

Webb's Electronics 25 4066

BATHURST

The Electronics Shop 31 4421

BROKEN HILL

Crystal TV 4803

COFFS HARBOUR

Coffs Harbour Electronics 52 5684

GOSFORD

Tomorrow's Electronics 24 7246

KURRI KURRI

Kurri Electronics 37 2141

NEWCASTLE

D & E Systems 69 1625

George Brown & Company 69 6399

NOWRA

Vimcom Electronics 21 4011

ORANGE

MW Electronics 626 491

PENRITH

Acorn Electronics 21 2409

PORT MACQUARIE

Hall of Electronics 83 7440

RAYMOND TERRACE

Albion Electronics 87 3419

RICHMOND

Vector Electronics 78 4277

TAMWORTH

Landlink Communications 65 4622

TOUKLEY

TES Electronics 96 4144

WINDANG

Medgen Electronics 96 5066

WINDSOR

M & E Electronics Communications 77 5935

Altronics Resellers wanted in all States of Australia (inc. WA) Phone Steve Wroblewski 09 3817233 for Details. OEM's for bulk rates Ph: 09 3817233 for super competitive rates.

50 and 25 years ago...

"Electronics Australia" is one of the longest running technical publications in the world. We started as "Wireless Weekly" in August 1922 and became "Radio and Hobbies in Australia" in April 1939. The title was changed to "Radio, Television and Hobbies" in February 1955 and finally, to "Electronics Australia" in April 1965. Below we feature some items from past issues.



January 1935

Report from USA: Mr A. Scott, chief engineer for Stromberg-Carlson, returned from an overseas tour and reported on developments in the USA.

"Plenty of experiment is going on at present with the ultra-short waves, or wavelengths from five to seven metres.

"There are several reasons for this. One of the biggest is television, which, it is generally accepted, is likely to come on the short waves.

"Television," said Mr Scott, "is proceeding mainly along cathode-ray lines, and I saw some very good stuff being put over. It is not yet ready for release on a big scale, however, and with some engineers talking about 600 lines per inch pictures it looks as though there is a long way to go before it will be.

Automatic distress signal: The first vessel in Australia to be fitted with an automatic distress signal wireless transmitter is the steamer Birchgrove Park, a small vessel trading between Sydney and Newcastle and the South Coast of New South Wales.

Only three years have elapsed since this type of wireless equipment was invented and developed by Amalgamated Wireless for the purpose of meeting the needs of small ships.

Amalgamated Wireless had to keep in mind the developing of a wireless set that would be rugged, dependable, and efficient, but occupy very little space, and also send out a call for help without necessarily having on board anyone who knew the slightest thing about the Morse telegraph code.

Associated with a very robust spark transmitter, the automatic sending mechanism takes the shape substantially of two discs, on the peripheries of which are fixed small raised pieces of metal in the proper order of dots and dashes, so that when the disc rotates and the

transmitter has the power switched on, a succession of dots and dashes are radiated as well as can be done by the most expert operator.

Don't laugh; this was serious: Surely one of the snappiest ideas ever put forth in the Sydney radio trade must be the special self-baking intermediates for the new Kriesler models, a patent for which has been secured by Mr Ray Weingott, of that firm.

Difficulty has been experienced through the effects of humidity on intermediate transformers and so in the new Kriesler intermediates there is a miniature radiator built inside the can. A nichrome winding on an asbestos former is placed in the can and is heated from a special winding on the power transformer.

Possibly in later models it will be found possible to utilise the resistance of the nichrome windings to act as bias resistors in the circuit.



January 1960

Flight recorder: A new British device called a flight and crash recorder was described by its inventor, Kenneth Dobson, in a recent BBC broadcast. During a flight the device records all important facts, such as instrument readings, engine performance and all the stresses and strains on wings and landing gear.

Should there be a crash, it will give the investigators something to work on; if the flight is perfectly normal, it will provide maintenance engineers with a record of the plane's performance that may result in not having to replace parts as often as at present.

In the event of a crash, Mr Dobson said, 99 times out of a 100 it should be possible to recover the record, which would show everything that had happened in the aircraft.

Flying TV station: A Dutch firm is preparing to transmit television programs from the air. Its transmitter will operate from a plane circling Holland and West Germany.

The transmission is expected to reach Britain, though few receivers would be able to reproduce the pictures because of the difference between British and Continental standards.

A spokesman of the firm formed to operate the service said in Amsterdam transmission probably would start early in 1960.

The plane would circle at a height of about 26,000ft, transmitting telerecorded programs.

Pushbutton telephone: Designed on the basis of many months of "human factor" study, a pushbutton type phone is said to give greater accuracy in dialling than the conventional method. This and other advances are made feasible by various electronic developments, including the transistor. Authorities say it is only a matter of time — and money — before subscribers will have available loudspeaker telephones, "television" systems, automatic transcription from teletype to words, and "personal" phones. These latter will be styled and worn like a wrist-watch and will operate into the wired system without the need for connecting leads. The pushbutton phone has been developed by Bell Laboratories.


Pedal plane: Britain is planning to build a man-powered plane. It will be powered by a propeller driven by a chain from pedals operated by the pilot. Some of Britain's leading aeronautical engineers are among a group to meet in London to raise the £10,000 needed for the project.

Most of the information needed to start work is already at hand, according to the chief engineer of British European Airways, Mr B. S. Shenstone. However, the project would not begin until the money has been found.

Britain's attempt was likely to be a fixed-wing aircraft with a propeller, which would be rotated by one or more men using bicycle pedals.

One of the main difficulties was to make the frame light enough for a man to lift. This would be overcome by using wood.

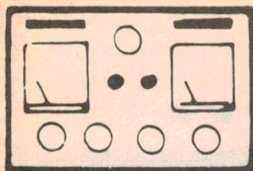Engineers say drive would be by a flexible bicycle chain, allowing a direct drive from pedals to propeller shaft.



Not so elementary, my dear Watson!

In all the best detective stories, from Sherlock Holmes to the present day, it is customary to tidy up all the loose ends with the unmasking of the villain in the last few paragraphs — the “apples bit” as one of my colleagues calls it (from “she’s apples, mate”). In real life, unfortunately, not all crimes — or TV problems — can be as successfully concluded.

The story I am about to relate is a typical example. While the various technical villains were eventually unmasked and the situation brought to a technically satisfactory solution, there were a number of questions left unanswered. So don’t expect too much of the “apples bit”.

The set involved was a Kriesler 660/3, one of the deluxe Kriesler colour TV sets in a beautiful double ended console cabinet; a most impressive piece of furniture in its own right. In fact, this is an important aspect of the story because it was a major factor in justifying the amount of work the owner, and particularly his wife, were prepared to authorise.

At a more technical level the chassis is our old friend the 59-1; a very popular one in its day and, in spite of its age, still able to hold its own alongside most modern sets. Properly adjusted it can produce a most impressive picture. The particular set was one I had known and serviced since new, mainly for quite minor problems.

At least, that was the situation until about four years ago when the owner moved to the other side of the city, well out of my territory, and rather too far for me to travel on a routine basis. So I more or less lost touch with the family, apart from an odd report from other customers who knew them.

Then one day the owner was on the phone with a real tale of woe. The basis of his call was to enquire whether I would have a look at the set and, appreciating the distance involved, he was quite prepared to bring it to me. On that basis I readily agreed but I was naturally curious as to why he should go to all that trouble when there were

almost certainly plenty of service organisations in his area just as able to help him.

It was then that the tale of woe emerged; most of it right there on the phone, and some of it later when I began asking questions. But, pieced together, it went something like this. The failure was quite sudden. The set had been performing normally when, as the owner put it, “... it suddenly stopped with a loud bang.”

Not expecting that it would be anything more than a routine repair job he called in a local serviceman. The serviceman called at the home and spent some time working on the set, but without, apparently, making any real progress. Eventually he decided that it was a job for the workshop and took the set away.

He kept the set for about two months, then returned it with the pronouncement that it could not be repaired. He went on to explain that the line output transformer had failed, that he had bought and fitted a new one, but that “voltages were excessive” and that the set was a write-off. The “voltages were excessive” bit seemed to be a rather strange remark, even to the owner, and it meant no more to me than it did to him. (I did find out what it meant later.)

But the family’s affection for the set wouldn’t allow them to accept that verdict, at least without a second opinion. They valued the set highly, both as a source of entertainment and as an important part of their lounge room decor. They weren’t going to give up without a fight. Which, of course, was where I came in.

Thus it was that the owner duly appeared, in a borrowed utility, with the

set having been manhandled on board by himself and a neighbour. Together we manhandled it off and into the workshop. To be honest, I had some misgivings about the job. In fact, I had warned the owner that it might, in truth, be a write-off and that any undertaking to tackle the job would be subject to preliminary examination, and at his risk.

While he was still there I pulled the back off the cabinet and took a quick look. What I saw didn’t reassure me. The deflection board, particularly around the line section, was a mess; whoever had been working on it would have qualified for the striped apron award of the year.


I plugged the set in and switched it on, keeping my finger on the switch. The power supply immediately hiccuped and I switched off. Next I slid the yoke back along the neck of the picture tube and examined the glass. If my predecessor had been mucking about with vital parts in the line output stage, particularly involving C747 or 746, it was quite possible that the picture tube might have been punctured by excessive EHT.

In fact I could find no such evidence, which was a relief, but this was no guarantee that the tube might not be faulty in some other way, and I pointed this out to the owner. So I thought about it for a while, and we talked it over, and I finally agreed to have a go at it — but with certain provisos.

As I put it to him, “You’re obviously going to be up for quite a lot of money. You might be looking at a couple of hundred dollars. And that’s assuming that the picture tube is OK. If it isn’t, well, it might be hard to justify the cost.”

He didn’t hesitate long. “Well, my wife really wants the set fixed, it’s her pride and joy, and I like it too. It’s gone well over all these years and if you think you can fix it within that figure, go ahead.” And so it was agreed.

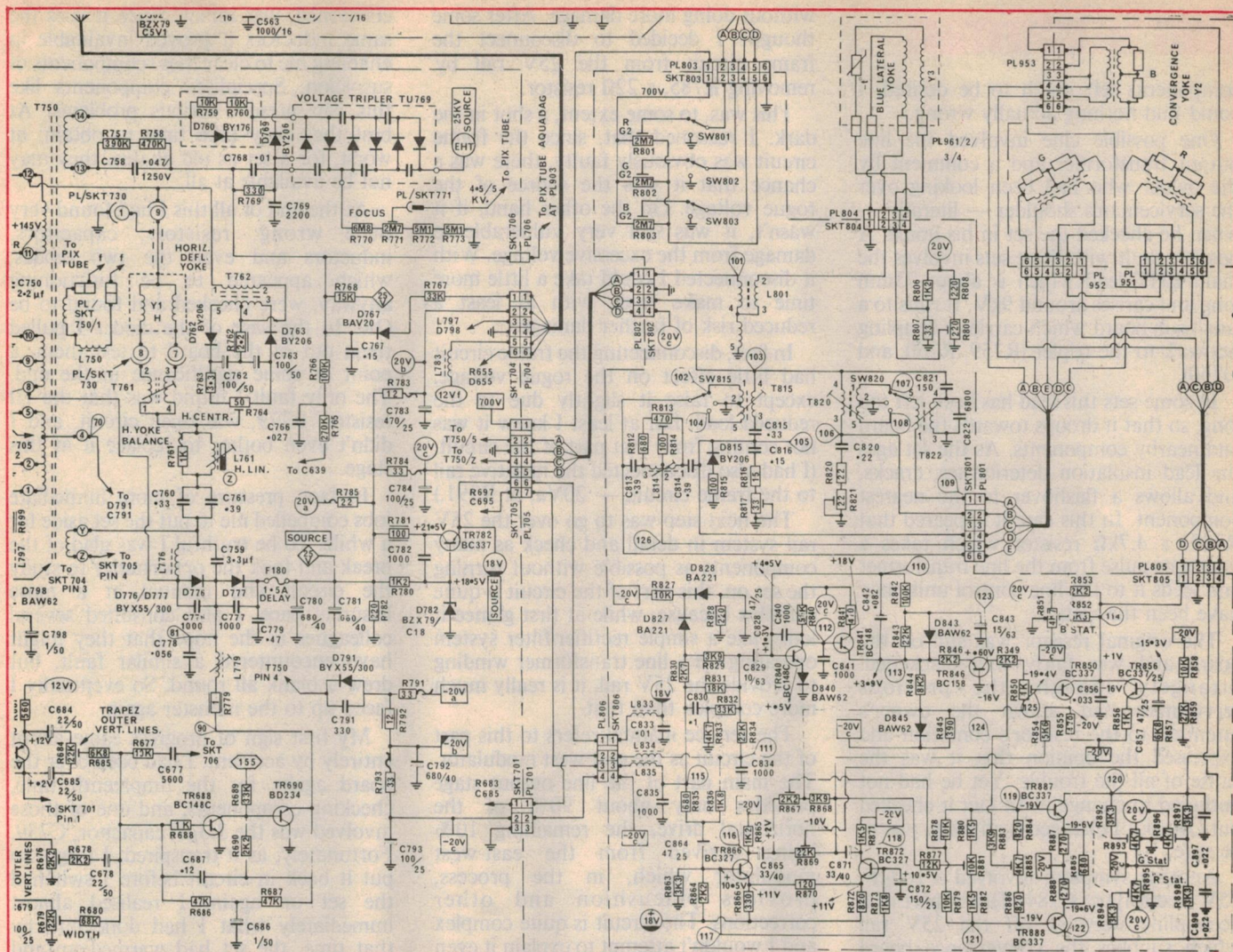Technically, the first question was why was the power supply hiccuping. It could be an overload anywhere in the set, particularly on the butchered line board, or it could even be in the power



Faulty circuit section of the butchered Kriesler 660/3 colour TV set.

supply itself. The last possibility was easily checked; I had a spare power supply board on hand and it was a simple matter to substitute it.

The result was quite conclusive; the known good board hiccuped just as did the old one, which fairly definitely cleared the latter. However I did take the opportunity to check the main supply rail voltage from both boards. This is normally 155V and is most easily checked at plug and socket 703 on the deflection board. In fact it was around 90V on the original board and slightly less again on the replacement board.

I refitted the original board and began looking for the likely cause of the overload. One of the first checks was to disconnect the tripler, but this proved negative. Progressive disconnection of other sections followed and it didn't take long to track it down. It was TR746, one of a pair of BU108 transistors (BU208 on the circuit) connected in parallel as the line output stage. It was short circuit.

This cured the hiccuping and the set showed signs of life. We had sound and something on the screen, the

"something" being a not too sharply focused white

Serviceman

components left much to be desired, I could find nothing actually wrong.

One possible clue involved the line output transformer and a comment by the owner who had been looking over the serviceman's shoulder — literally — when he checked the set in his home. A possible fault with these sets involves the main EHT lead which is about 75mm long and carries around 9kV. It runs to a small sub-board which carries a coupling network to the tripler (R759, R760, and D760).

In some sets this lead has been left too long, so that it droops towards the board and nearby components. As the set ages the lead insulation deteriorates, cracks, and allows a flashover to the nearest component. In this case it appeared that R729, a 4.7k Ω resistor which takes a reference pulse from the line transformer and feeds it to the line control unit, may have been the victim.

The original resistor was still on the board and was fairly well blackened. Strangely enough, the previous serviceman had drawn the owner's attention to the resistor's condition and expressed the opinion that it was the cause of all the trouble. Yet he had not bothered to change it! In fact it checked out OK, but I changed it anyway, just to be sure.

Another symptom involved a 100 μ F, 25V electrolytic, C784. This is part of a decoupling network off the 25V rail which supplies the convergence board via plug and socket 705, pin 5. This had been replaced and, quite obviously, the previous one had exploded, because there were still scraps of aluminium foil and insulating material scattered around the component side of the board when I checked it. I imagine this was the "bang" the owner had heard when the set failed.

Considering the voltage now on the 25V rail it was little wonder that this capacitor had failed; the real wonder was that it was the only one, several other similarly rated electrolytics being in a similarly vulnerable position. I checked the replaced C784 and it appeared to be OK. Its near neighbour, C783, a 470 μ F electrolytic was also checked and found to have virtually no capacitance, so I replaced it.

One of the main 25V rail filter capacitors, C781 already mentioned, had been replaced. I checked both and found that the replacement was OK but that the original had little capacitance and had to be replaced.

But none of these observations or repairs had any significant effect on the gross overvoltage on the 25V rail, nor did they provide any inspiration as to the best means to track down the fault

without doing more damage. After some thought I decided to disconnect the frame circuit from the 25V rail by removing R785, a 22 Ω resistor.

This was, to some extent, a shot in the dark. I reasoned that, since the frame circuit was obviously faulty, there was a chance that it was the source of the rogue voltage. On the other hand, if it wasn't, it was still very vulnerable to damage from the excessive voltage. With it disconnected I could take a little more time to make tests, with at least a reduced risk of further damage.

In fact, disconnecting the frame circuit had little effect on the rogue voltage, except to raise it slightly due to the reduced load. But at least I knew it was not coming from that part of the circuit. (I had also disconnected the negative rail to the frame circuit, — 20Va, at R791.)

The next step was to go over the 25V rail system in detail and check as many components as possible without turning the set on. This part of the circuit is quite complex because, while at first glance it looks like a simple rectifier/filter system operating off a line transformer winding to provide the 25V rail, it is really much more complex than that.

The service manual refers to this part of the circuit as the east-west modulator. The main part of the line output stage provides only about 90% of the horizontal drive, the remaining 10% being derived from the east-west modulator which, in the process, provides pincushion and other corrections. The circuit is quite complex and I wouldn't attempt to explain it even if I understood it in detail, which I don't.

Suffice it to say that the vital signals for this function are derived from the junction of D776 and D777, the latter providing the final rectification for the 25V rail, which is filtered by C780/781. From the junction of the diodes modified line energy is fed into the deflection system via inductor L776, together with a 3.3 μ F capacitor (C759), capacitors C760/761, inductor L761, resistor R761, and transformer T761, to name the major components.

The other major section of the east-west modulator (moving downwards from the D776/777 junction) involves the variable inductor L779, a 1 Ω (protective) resistor, and the network involving transistors TR688/690. This latter is fed from the vertical deflection system and TR690 acts as a variable load to vary the amplitude of the horizontal (east-west) deflection at the frame rate.

I went over all these components, and a few others as well, and checked each one either by substitution or measurement. In this respect I was fortunate. I happened to have on hand a junked Philips K9 chassis which, at least as far as this part of the circuit was

concerned, was intact. Since it uses the same inductors it proved invaluable in enabling me to clear these components of suspicion. Specialised components like this can present serious problems. At best they may take time to obtain; at worst, for a set as old as this, they may not be available at all.


At the end of all this I had found very little wrong; resistors, capacitors, inductors and even the two diodes, which appeared to be functioning anyway, were checked and found to be OK. In the case of the diodes I pulled them out of the board to test them, a point of some significance in the end. The only fault I found was that the 1 Ω resistor, R779, was open circuit, and I didn't even bother to replace it at this stage.

In fact, pressure of more immediate jobs compelled me to put the set aside for a while. To be truthful I was glad of the break and took the opportunity to study the circuit and manual at a more leisurely pace. I also consulted several colleagues in the hope that they might have encountered a similar fault, but drew a blank all round. So eventually I faced up to the monster again.


My first sign of progress came about entirely by accident. I had been over the board again, for the umpteenth time, checking components, and one of those involved was the 3.3 μ F capacitor, C759. Fortunately, as it transpired, I forgot to put it back in circuit before I switched the set on again. I realised almost immediately what I had done but, by that time, the set had warmed up and was displaying a much wider line scan; about nine tenths of the total width, which is what it should be without the east-west modulator (R779 was still open).

Just as important was the fact that the rogue voltage on the 25V rail had dropped from around 70 to under 40; still much too high, but a lot easier to tolerate. Suspecting something funny about the 3.3 μ F I had taken out I replaced it with another one, but that put things back where they were before. So I left this capacitor out for the moment.


Continued on page 57

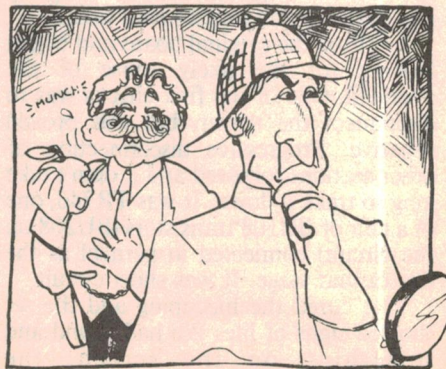


TRANSISTOR-FET TESTER

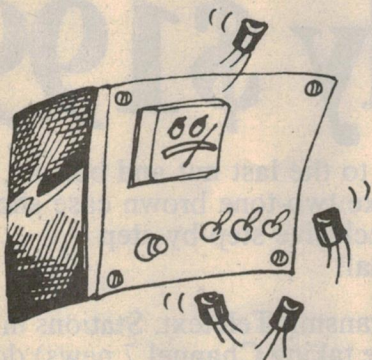

LEDS & LADDERS GAME

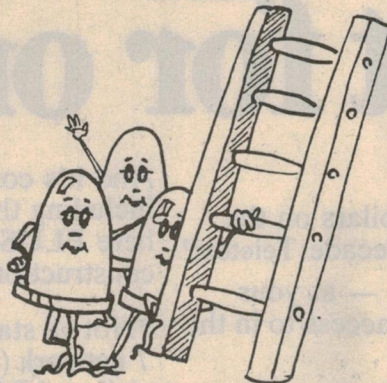


STEREO SOUND SIMULATOR

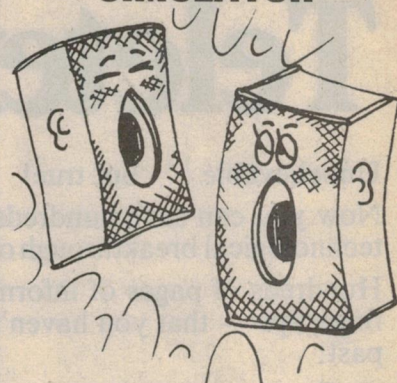


Electronics Australia Presents:

HOLIDAY PROJECTS

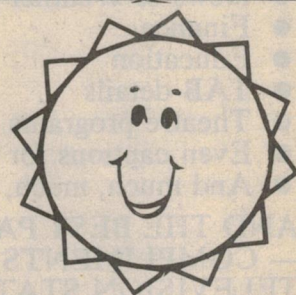


JANUARY, 1985


AUDIO OSCILLATOR

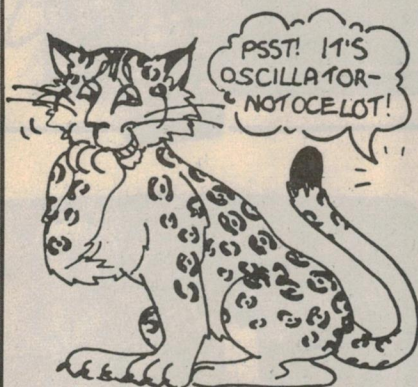

CAR IGNITION KILLER

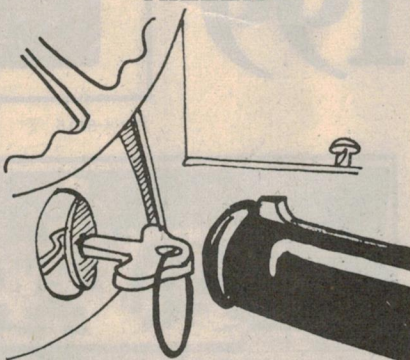

LED SOUND LEVEL METER

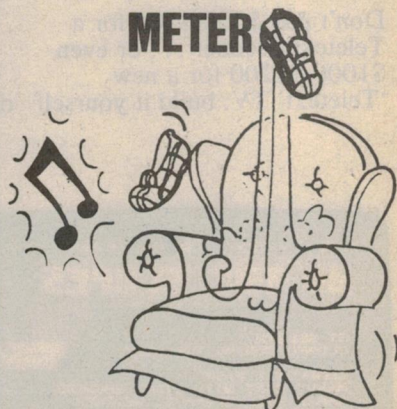

Sponsored by Dick Smith Electronics

It had to happen!

Teletext for only \$199

Unbelievable . . . but true!

Now you can save hundreds of dollars on the technological breakthrough of the decade: Teletext!

Hundreds of pages of information — at your fingertips — that you haven't had access to in the past:

- Sport
- News & Weather
- Finance
- Education
- TAB details
- Theatre programs
- Even captions for the deaf . . .
- And much, much, much more!

AND THE BEST PART OF ALL: IT'S FREE — COMPLIMENTS OF YOUR LOCAL TELEVISION STATION!*

At last, a low cost, easy-to-build kit that you can use with your VCR to give sharp, clear Teletext pictures on any TV set.




Don't pay \$500-\$700 for a Teletext decoder . . . or even \$1000-\$1200 for a new 'Teletext' TV: build it yourself only




\$199


And it's complete to the last nut and bolt — including the deluxe two-tone brown case shown here **PLUS** our exclusive step-by-step construction manual!

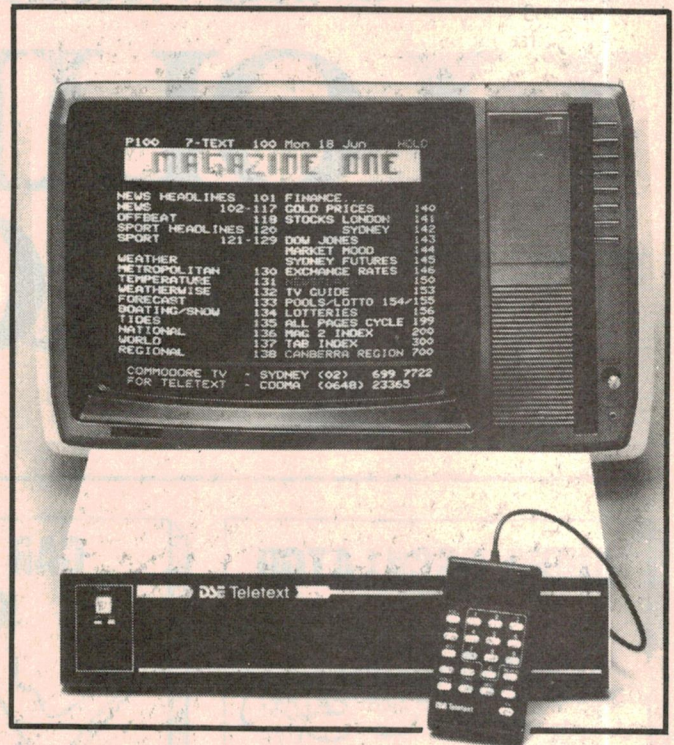*Not all stations transmit Teletext. Stations in the 7 network (ie those taking Channel 7 news) do as well as ABC stations, and many others have some Teletext transmissions. Most stations transmit Teletext subtitles for deaf people. If in doubt, ring your local station.



Cat K-6315

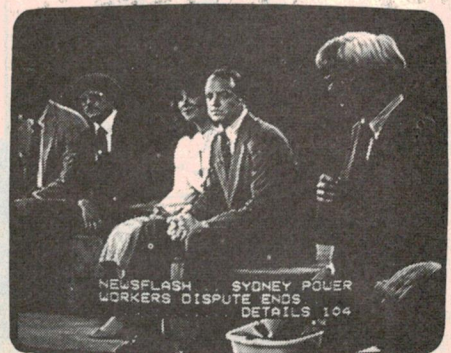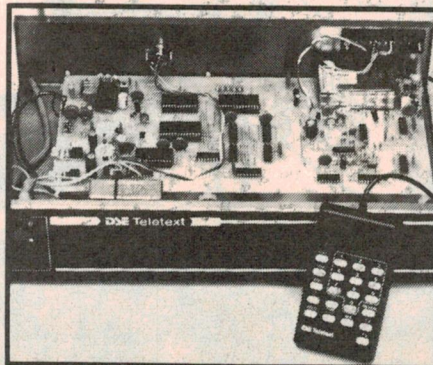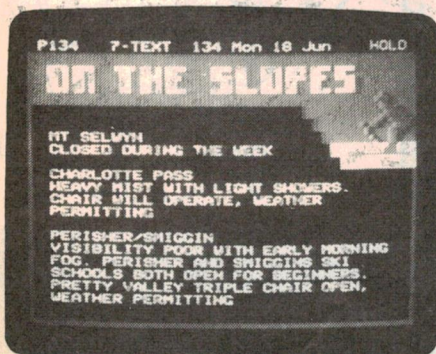

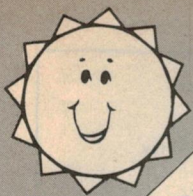

Simple circuit uses low-cost ICs

Stereo Simulator

for tuners & VCRs

Built around three low-cost op amp ICs, this simple circuit can produce simulated stereo sound from virtually any monophonic source. It can be built as a self-contained unit or installed inside an existing piece of equipment.

by COLIN DAWSON

Anyone who has built the Playmaster wide-band AM tuner (Dec, 1982 — March, 1983) will be aware that the quality of transmitted AM programs is much higher than generally accepted. In fact, it quite often approaches that of FM transmissions. But, after the initial euphoria of this discovery has subsided, the listener's satisfaction may be dampened by the inherent limitations of mono sound which, by comparison with stereo, can sound a little dull.

Our new Stereo Simulator was designed expressly to overcome this limitation, although it can also be used with other monophonic signal sources such as VCRs and TV sets. In fact, we made up two versions of the unit, and installed one permanently in the chassis of the AM

tuner. The other version was fitted inside a small plastic case to serve as a self-contained unit, and features optional mono/stereo switching.

Actually it was only last September that we presented a stereo synthesizer using a bucket brigade device. Is this previous design superseded already? No. The new design has the attraction of much lower cost but it does not offer quite the same even stereo spread of the September 1982 BBD design. Even so, the effect is very worthwhile and certainly should contribute to your listening pleasure.

Another advantage of this particular unit is its small size which generally allows it to fit inside existing equipment (including the Playmaster AM Tuner).

The accompanying specifications panel


shows the performance of our prototype unit. Note that these figures were obtained with the unit powered from an unregulated 9V plugpack supply. Both the signal-to-noise ratio and distortion figures are improved slightly when a regulated supply is used. Even so, the performance is quite satisfactory and the distortion figure of 0.1% can generally be regarded as conservative — at most frequencies it is only about .05%

Some readers may think it strange that the signal-to-noise ratio is different in the left and right channels, but this is simply a result of our having taken the measurements with respect to a 1kHz signal. At this frequency (and in fact at most frequencies), the left and right channels have different gain and hence different noise levels.

We can't claim to have derived genuine stereo from a mono recording — it is simply not possible to recover spatial information that was not recorded in the first place. In this respect, the term "stereo" is something of a misnomer since the simulator does not provide a signal with any directional information.



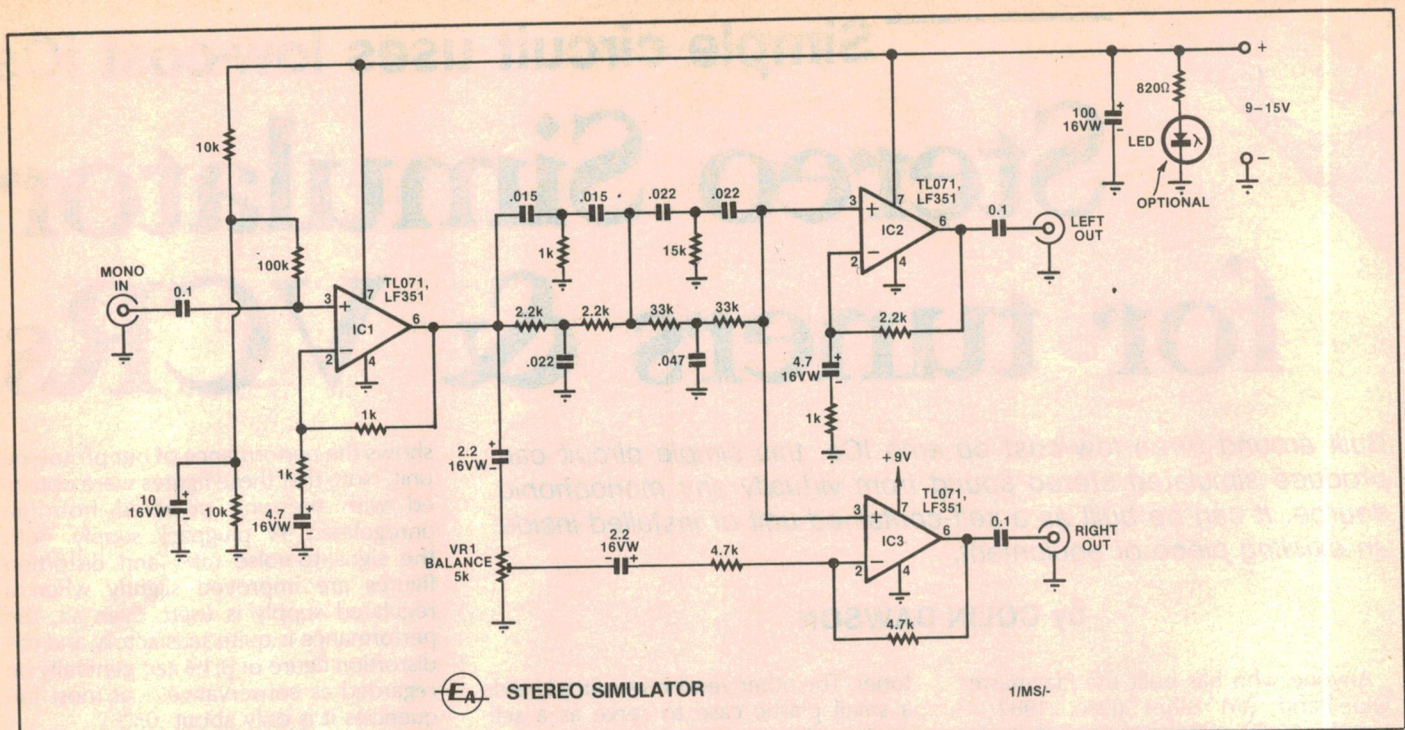This self-contained version of the Stereo Simulator includes the LED power indicator and optional mono/stereo switching. It can be powered from a 9V plugpack or any convenient 9-15V DC supply.



The circuit consists of an op amp buffer (IC1), a twin-T filter network, and output amplifiers IC2 and IC3.

Stereo Simulator

(continued)


What it does do is diffuse the "point source" effect of normal mono, creating a certain amount of artificial separation or spread. The result is a signal which sounds as though it could be stereo — hence the term "stereo simulator."

How it works

The simulator creates "left" and "right" channels from the original mono signal by means of filters. This method has been used in many circuits over the years and in its crudest form is comparable to siting the tweeter of a speaker system on one side of the room and the woofer on the other.

Our circuit employs two twin T filters which cause notches in the frequency response at 200Hz and 5kHz in one channel. This is quite effective, but strictly conventional. The interesting aspect of this circuit is how the signal for the other channel is derived. Usually, this would simply be the unfiltered input signal, but in this circuit is the difference between the input signal and filtered signal. This is a far more realistic approach since the sum of the two outputs gives the original signal, yet the left and right channel signals are quite different.

Fig. 1 shows the response of the two

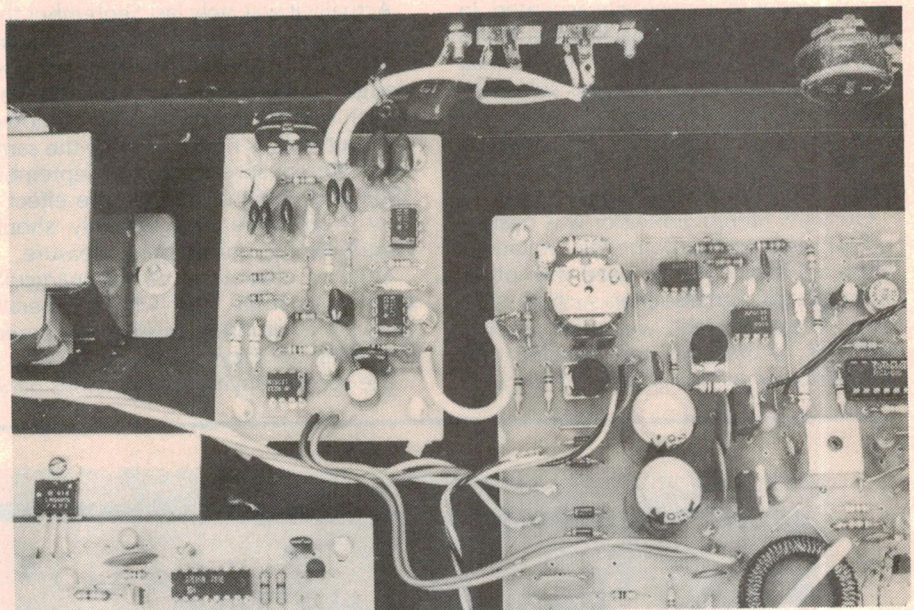

This photograph shows the assembled PCB mounted inside the chassis of the Playmaster AM Tuner. Power for the simulator is derived from the main tuner PCB at right.

SPECIFICATIONS

SIGNAL-TO-NOISE RATIO . . . 60dB (left channel); 56dB (right channel)

DISTORTION (both channels) 0.1%

GAIN (see graph)

CURRENT DRAIN 6.5mA without LED, 17mA with LED

Measurements were taken with respect to 100mV output at 1kHz using an unregulated 9V plugpack supply. Signal-to-noise ratio and distortion figures can be expected to improve slightly with a regulated supply.

channels, with the notches at 200Hz and 5kHz appearing in the left channel. The right channel response features a single 25dB notch centred on 1kHz.

Twin T filters are so named because they consist of two T sections — one section uses an R, 2C network and the other an R/2, C network. When the values are chosen precisely, the filter gives a narrow notch with almost total cancellation at its centre frequency. Actually, the values used in our filter networks are not selected critically and this has resulted in notches of about 20dB. Although this could be improved by choosing "ideal" components, the degree of cancellation is already sufficient and any further improvement would be purely academic.

In fact, if the notches were made very deep and very narrow, the left channel would sound almost identical to the original mono input. On the other hand, we would get very little sound from the right channel since it would consist of just two very narrow bands of signal centred on 200Hz and 5kHz. This is clearly not what we want.

The response of the filters has also been modified to a certain extent by the interaction between stages, since the two filters are directly coupled. We have minimised this interaction, however, by placing the 5kHz filter first — it has a relatively low impedance and is thus not unduly loaded by the higher impedance of the following 200Hz filter. While interaction between the filters could have been completely eliminated by an op-amp buffer stage, the improvement would again be of only academic interest. And, as we've already seen, we don't want the filters to have a really sharp response.

Circuit details

The filter network is driven by a Fet-input op amp buffer (IC1) which isolates it from the line output of the tuner or VCR, etc. A voltage divider consisting of two 10k Ω resistors sets the bias to the non-inverting input to half supply so that the op amp can function from a single supply rail. This bias is applied to IC1 via a 100k Ω resistor, with decoupling provided by a 10 μ F capacitor.

IC1 is configured as a non-inverting amplifier with unity gain and frequency roll-off below 40Hz set by the 4.7 μ F feedback capacitor. The mono input signal is AC-coupled to the non-inverting input (pin 3), while the output (pin 6) feeds directly into the twin T filter network and also, via a 2.2 μ F capacitor, to one side of a 5k Ω trimpot (VR1). The other side of the trimpot is grounded and the signal available on its wiper used to drive the following right channel output stage.

The left and right channel output

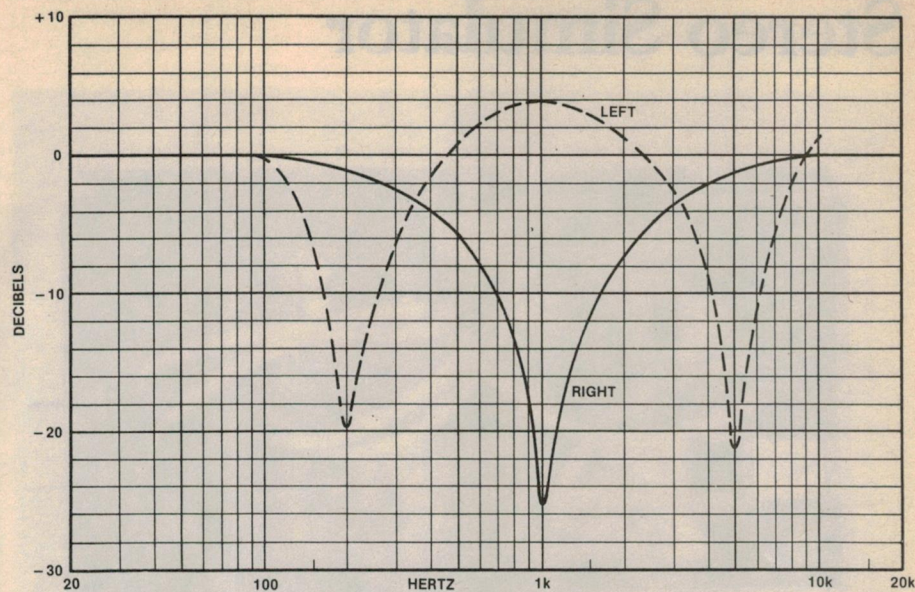


Fig. 1

This graph plots the response of the left and right channels.

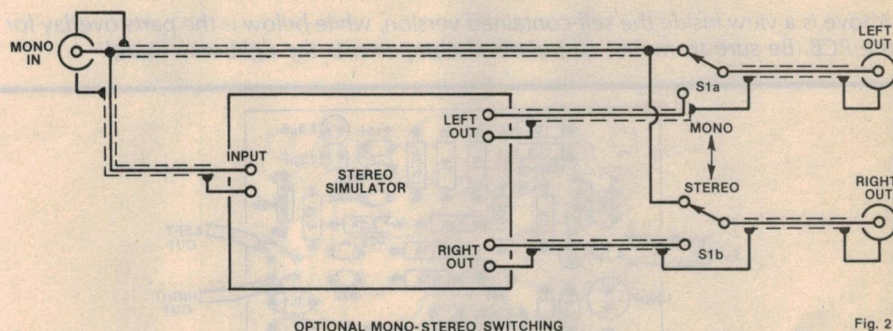


Fig. 2

Wiring details for optional mono/stereo switching. Note use of shielded cable for all input and output connections to the PCB and switch.

stages consist of two more non-inverting amplifiers, again using Fet-input op amps (IC2 and IC3). The filtered signal from the twin T network is applied to the non-inverting input in each case. IC2 applies a gain of around two to this signal which subsequently becomes available as the left channel output. Note that since there is a DC path through the filter network, it is not necessary to provide biasing for IC2 and IC3.

IC3 is wired as a differential amplifier and functions rather differently to IC1 and IC2. In this case, different signals are applied to the non-inverting and inverting inputs — the signal from the twin T filter network appears on the non-inverting input, while the signal on the inverting input is derived from VR1 and is a buffered version of the original mono input. The output of IC3 represents the difference between these two signals.

Thus, when the signals on pins 2 and 3 of IC3 are common (ie, they have the same phase and amplitude), they are cancelled and IC3 has no output. When the signals are no longer common, only

partial (or nil) cancellation occurs depending upon the relative phase and amplitude differences between them.


Note that the gain of IC2 (as set by the ratio of the 2.2k Ω and 1k Ω feedback resistors) compensates for the inherently "lossy" nature of the twin T filter network, at least as far as the left channel is concerned. Trimpot VR1 adjusts the gain of IC3 in the right channel, and functions as both a "depth of stereo" control and a balance control. In fact, the actual setting of VR1 tends to be a compromise between these two functions.

The response curves accompanying this article (Fig. 1) indicate that the output of IC3 has a very deep null at 1kHz. The depth of this null depends on the setting of VR1 and the results indicated are for what is considered an optimum adjustment.

Power for the circuit can be derived from any convenient 9-15V DC supply, eg a 9V plugpack, a 9V battery, or a 9-15V supply rail inside existing equipment. A 100 μ F electrolytic capacitor decouples the supply, while power in-

Construction

ELECTRONICS Australia, January, 1985

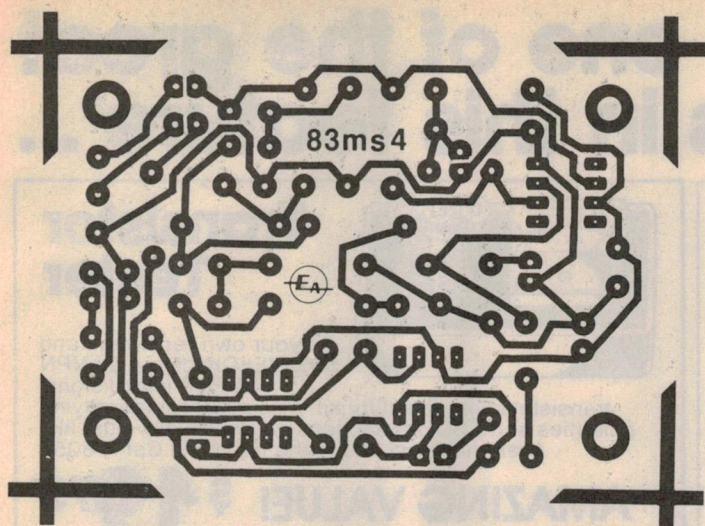

Here are actual size artworks for the PCB and front panel.

measuring 130 x 65 x 40mm. This is fitted with RCA input/output sockets and a power socket, together with the LED indicator and optional mono-stereo switching. A front panel made from self-adhesive Scotchcal material provides an attractive finish to the unit.

The first job is to affix the Scotchcal label to the lid of the box, and drill mounting holes for the switch and indicator LED. This done, mounting holes may be drilled in the box for the RCA sockets, power socket and PCB. As shown in the photograph, the RCA input socket and the power socket are mounted on the left hand side of the box, while the two RCA output sockets are mounted on the right hand side.

The various items of hardware may now be mounted in position and the wiring completed. As before, all input and output connections (including those to the switch) should be run in shielded cable. Connections to the power socket and LED can be run using multistrand hook-up wire. Don't forget to solder the 820Ω resistor in series with the LED.

It is a good idea to check the polarity of the power socket terminals with a multimeter before making the connections to the PCB. You will almost certainly damage the ICs if power is applied with reversed polarity.

To test the unit, first apply power and check that the LED illuminates. If all is well, disconnect the plugpack and connect the simulator into circuit. The mono input accepts the signal from the program source, while the left and right outputs go to the amplifier line inputs. If you have an integrated tuner/amplifier, the tuner signal will be available at the "Tape

Out" outputs. The simulator outputs should then be connected to the "Tape Monitor" inputs on the amplifier.

Apply power and check that everything functions normally with switch S1 in the "mono" position. Finally, switch to "stereo" and adjust VR1 for the most satisfying sound. Your "Stereo Simulator" is now ready for use.

As explained earlier, this device will not endow the music with any directional information. For example, you will not be able to positively identify the lead guitarist as being right of centre. Nevertheless, the simulator has a satisfying "spread" effect and you will certainly know when it is working.



ELECTRONICS AUSTRALIA

STEREO SIMULATOR

OUTPUT L R

STEREO

MONO

INPUT

+

POWER

+

**No. 1
FOR KITS!**

Build one of the great kits in this feature ...


Stereo Simulator Mk II



Get stereo sound from VCR's, mono cassettes, etc - it's easy, and sounds like it's fair dinkum stereo!

Easy to build kit is an ideal add-on: especially at this low price.

\$19⁹⁵ Cat K-3421

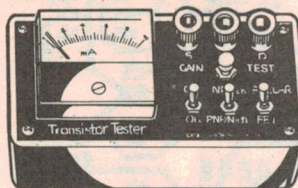


Transistor Tester

Be your own repairman and \$\$\$AVE! Check out all NPN & PNP (small signal) transistors with this nifty kit. Also great for identifying polarities and EBC connections on unknowns - just like every hobbyist has in the junk box! Cat K-3052

AMAZING VALUE! \$19⁷⁵

LED Level Meter

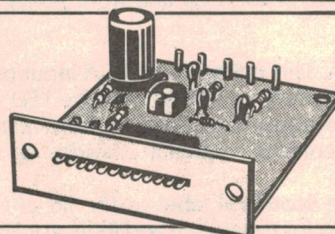Just like those imported snazzy amplifiers costing big \$\$\$! Add a LED Level meter to your system and it will look a million dollars. Stereo is no problem: either sum the signals or build two LED Level Meters! Full connection details included. Cat K-3370



**GREAT
VALUE!**

\$14⁹⁵



Audio Oscillator

Essential piece of gear for every hobbyist, service shop, experimenter, audio buff ... and when you build your own you save! Complete kit includes attractive front panel shown.


- 15Hz to 150kHz range
- Battery Operated
- Sine & Square Wave Output

Cat K-3469

ONLY \$39⁵⁰

Ignition Killer! \$14⁹⁵

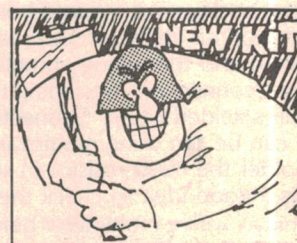You know what's really frustrating to the car thief? When your car won't start! He thinks it's a dud and looks elsewhere! What he doesn't know is that you have an ignition killer fitted! Suits virtually all standard (Kettering) ignition cars, easy to fit - and could save your car being pinched! Cat K-3255



Here's why you should build a

1 EXCLUSIVE! OUR KITS ARE GUARANTEED ...

If you buy one of our kits and, before commencing construction, decide you don't want to build it **for any reason**, return it to the point of purchase in original condition and packaging and we'll refund your purchase price in full!!!

2 EXCLUSIVE! COMPLETE, STEP-BY-STEP INSTRUCTIONS ...

Not just reprints of the magazine articles like the others throw in: we take all the hassles out of building our kits - by giving you an instruction manual that really means something! PLUS we give you a copy of our exclusive booklet: 'Guide to Kit Construction' - all the tips you need - and you won't get them anywhere else.

3 EXCLUSIVE! BRAND NEW, PRIME SPEC COMPONENTS ONLY USED

We guarantee you top quality components in our kits. Not all kit suppliers will give you this guarantee: some have used inferior parts, manufacturer's seconds, etc etc. We ensure that the components we use are equal - and sometimes superior - to those specified in the magazine.



Need a few tools?

Here's Little Dick's Basic Kit Builder's Set...

Soldering Irons



Top quality Antex brand: made in England. Your choice of 240 volt or 12 volt models, each 25 watts. Fast, efficient soldering - and the iron is nicely balanced for fine work.

240V model: comes with soldering stand and hints on good soldering. Cat T-1800 \$24.95

12V model: includes battery clips for use on car battery or power supply. Cat T-1802 \$12.50

Soldering stand to suit 12V iron Cat T-1804 \$4.95

Big roll solder (200g) 18 gauge Cat N-1619 \$6.50



Set Stainless Steel Cutters/Nippers/Pliers

Yes, you can buy cheaper tools: but they won't last nearly as long as these stainless steel types - or do as good a job. If you're buying tools for precision electronic work, it's worth paying just a couple of dollars extra to get the best!

Stainless Steel Transistor Nipper Cat T-3205

Stainless Steel Mini Flat Nose Plier Cat T-3325

Stainless Steel Mini Needle Nose Plier Cat T-3570

Stainless Steel Long Nose Plier Cat T-3565



All one low, low price: **\$8⁵⁰ ea!**

Set Screwdrivers

Quality screwdrivers in all popular sizes - standard flat head and Phillips, too. These are just a few to get you started - you'll find plenty more at your Dick Smith Electronics store!



Baby Size: 100mm long blade Cat T-4075 **75¢**

Popular Size: 150mm long blade Cat T-4090 **\$1.10**


Heavy Duty: 125mm long blade Cat T-4100 **\$1.95**

Phillips Type: 100mm long blade Cat T-4040 **\$1.10**

Parts Drawers

Need somewhere to keep those bits and pieces? Every hobbyist does! Now there's an easy way: our stackable parts drawers come in two styles (one and two drawers per box) and can be stacked vertically and horizontally to give the required number of compartments. You could even find a whole wall with them if you wished! **One drawer per box** Cat H-2584

Two drawers per box Cat H-2585

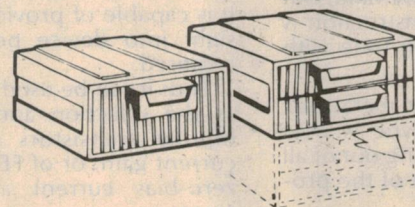

BOTH ONE LOW, LOW

PRICE:

\$3¹⁵

EACH

HUGE RANGE OF OTHER TOOLS AND SERVICE AIDS AT YOUR NEAREST DICK SMITH ELECTRONICS STORE.

Dick Smith Electronics kit...

4 EXCLUSIVE! OUR 'SORRY DICK, IT DOESN'T WORK . . .' SERVICE:

On many of our major kits, we offer an exclusive repair service: just in case you cannot get your kit working. We'll fix any mistakes and replace any parts necessary: all for a fixed, low (nominated) service fee.

Note: This service is available only on specified kits, and we reserve the right to return both kit and service fee if standard of construction makes economic repair impossible.

5 EXCLUSIVE! TECHNICAL BACK-UP FOR EVERY KIT!


Before we place a kit on the market, at least one (and sometimes more) prototypes are built up - just in case there are any problems that might have been overlooked. We liaise with the magazines to ensure that 'bugs' are removed long before the kit reaches you!

6 EXCLUSIVE! OUR OWN KIT RESEARCH AND DEVELOPMENT

In conjunction with the major electronics magazines, our R&D team is continually developing new kits. Such kits as the recently released Teletext Decoder, 2m and 70cm Amateur Transceivers, Power Supplies, Super 80 Computer . . . plus a host of smaller kits.

And more are coming all the time: watch out soon for our new Stereo Television Receiver, UHF CB & Amateur Power Meter. And many more exciting projects on the drawing board for later this year!

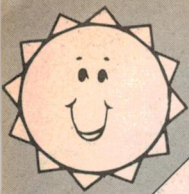THEY
LOOK
SO GOOD
YOUR
FRIENDS
WILL NEVER
BELIEVE YOU
BUILT
THEM!



Check bipolars & FETs with this Simple Transistor Tester

Intended mainly for checking bipolar transistors and FETs, this simple transistor checker can also be used to test most other discrete semiconductor devices. It is easy to build, low in cost, and provides an excellent way of becoming familiar with basic device operation.

by GREG SWAIN & DAVID EDWARDS

The design of this simple transistor/FET checker can hardly be considered new. It was originally described by Jim Rowe in August 1971 and, over the years, has proven an immensely popular project. Literally thousands have been built!

Recently, we decided to take another look at the unit with a view to updating it. The circuit is still perfectly valid, but the original method of construction is now dated and not quite in tune with '85.

In particular, the diecast metal box used to house the prototype is now quite expensive, its cost being out of all proportion to the total cost of the project!

Our approach has been to re-design the unit into one of the low cost plastic "zippy" boxes. At the same time, we have designed a small printed circuit board (the original used tagboard) and provided the unit with a front panel to match our recent RLC Bridge and

Audio Oscillator projects. Total cost of the updated unit should be well below that of comparable commercial testers.

Despite its basic simplicity, the unit is capable of making most of the practical tests normally required when experimenting with transistors or servicing transistorised equipment. It can test both bipolar transistors and FETs, in addition to diodes, SCRs and PUTs. And it is capable of providing a detailed insight into device performance when required.

Thus it can be used for such purposes as the selection and/or matching of bipolar transistors on the basis of current gain, or of FETs on the basis of zero-bias current and transconductance.

Apart from its practical uses as a testing instrument, it also offers a simple and straightforward means whereby a beginner can gain a valuable first-hand insight into practical device operation. There is nothing quite as effective in dispelling some of the

mystery of transistors or FETs as hooking a device up to the checker, and demonstrating to one's own satisfaction that it really does perform as the theory book describes!


The checker can also be used to demonstrate what happens when a bipolar transistor is connected to the supply "the wrong way around", or when the drain and source of a FET are reversed, or the effect on leakage and saturation currents when the temperature rises. All this from only 17 basic parts: a meter, a battery, three toggle switches, one pushbutton, five diodes, and six resistors.

The tests performed by the checker are straightforward. For bipolar transistors, it first measures the leakage-saturation current I_{ceo} , the collector-emitter current which flows when the base is left unconnected. It then applies a known base current to the device, and measures the resulting change in collector current. This gives an indication of the DC current gain, or DC beta.

The test for I_{ceo} is a good preliminary check for bipolar transistors, because there are few faults in this type of device which do not cause a significant increase in I_{ceo} . And those few faults which do not show up in this test will generally make themselves quite apparent in the gain test. Thus although an open circuit in the base, collector or emitter-lead will not show up in the I_{ceo} test, it will certainly become evident in the gain test, as a zero reading!

Actually the checker is designed to test for both I_{ceo} and gain at two alternative current levels. It can test for I_{ceo} on a 0-1 mA scale, and then apply a 2-microamp base current to observe the current gain on what becomes virtually a 0-500 scale. Alternatively it can test for I_{ceo} on a 0-10 mA scale, and then apply a 100 μ A base current to observe current gain on what then becomes a 0-100 scale.

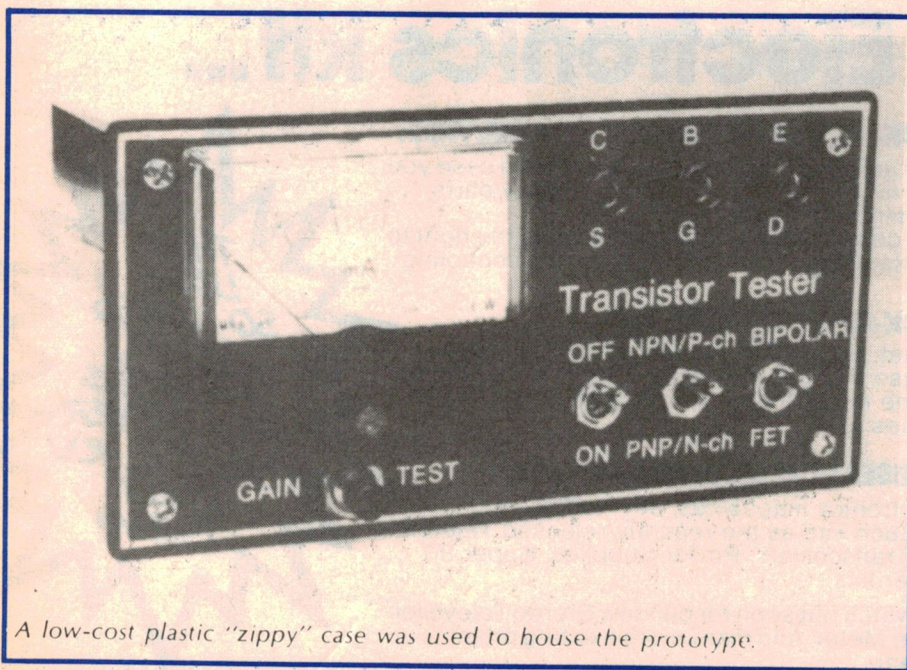The advantage of the two current levels is greater flexibility. The lower current tests are appropriate for modern low power silicon transistors, which tend to have very low I_{ceo} combined with quite high DC beta figures at low current levels. On the other



A low-cost plastic "zippy" case was used to house the prototype.

hand the higher current tests are more appropriate for higher power silicon transistors, and many of the older germanium devices. These tend to have a higher I_{ceo} , and a lower DC beta. The higher power silicon devices also tend to display a more realistic DC beta figure when tested at the higher current level.


For FETs, the checker first measures the zero-bias channel current I_{dss} , the current which flows between drain and source when the gate is either left open-circuited or connected to the source. A reverse gate bias of approximately 1.2 volts is then applied, and its effect in reducing the drain source current may be seen. This gives a measure of the device transconductance (gm). The transconductance is not indicated directly, but may be readily calculated by dividing the observed drop in channel current by 1.2.

The test for I_{dss} is a very useful one for checking FETs, as I_{dss} is one of the main parameters which determine the DC behaviour of a FET in most circuits. It is also a parameter which varies quite significantly among currently available devices, and is therefore an important one to be taken into account when selecting or matching FETs. The transconductance check is also a very useful test, both for straightforward "good-bad" testing, and for selection and matching.

As with the bipolar transistor tests, the FET tests may be performed at either of two current levels. These are in fact the same two current levels used for the bipolar tests, with a meter sensitivity of either 1 mA or 10 mA respectively. With most FETs the 10 mA range will be the more appropriate, as most of the useful devices currently available have an I_{dss} falling within the range 1 mA-10 mA. However the 1 mA range may be useful for checking devices with a very low I_{dss} , and/or a high transconductance.


With the FET tests, the reverse gate bias voltage remains constant at 1.2 V for both ranges. This means that the ranges may be selected purely on the basis of convenience in reading the channel current. It is thus possible to switch from the 10 mA range down to the lower range if the transconductance of a device is sufficient to reduce its current from greater than 1 mA to well below this figure.

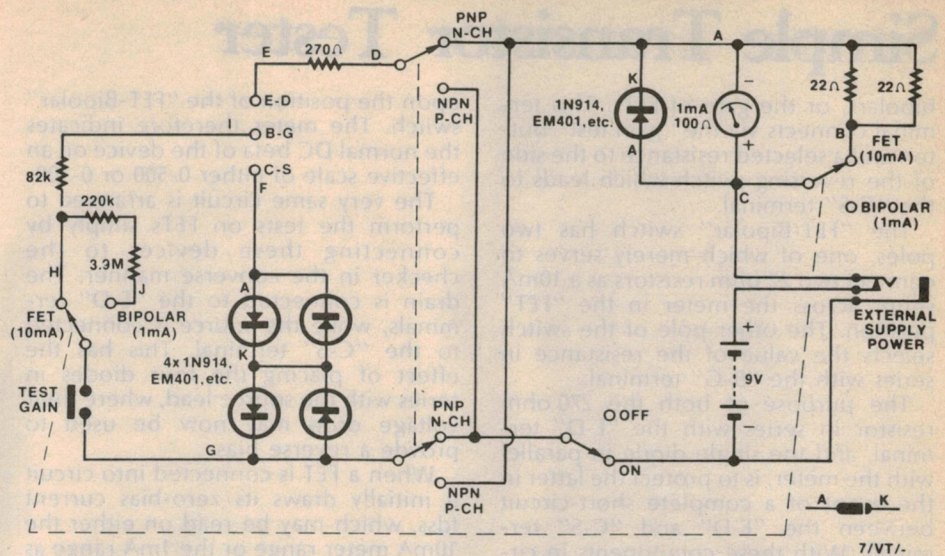Diodes may also be tested on the checker, both for reverse leakage/saturation current I_r , and also for forward conduction. These tests are usually sufficient for "good-bad" testing. As before both a 1 mA and a 10 mA meter range are available for both tests. This makes it possible to test virtually any type of rectifier diode likely to be met, whether of silicon or germanium.



EA SIMPLE TRANSISTOR-FET TESTER

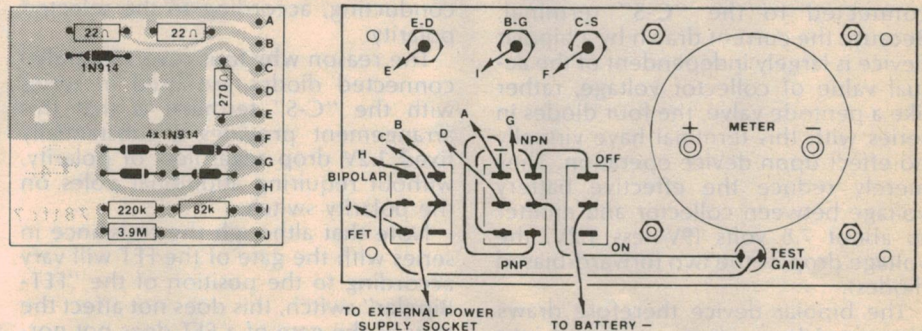Despite its simplicity, the circuit will perform most of the useful tests on the majority of modern discrete semiconductor devices.



The component overlay pattern shows the PC board from the component side. Take care with the orientation of polarised parts.

Other types of diode may also be tested, such as varicap diodes and varactors. It will be possible to test "zener" diodes, but only those having a breakdown voltage above the 9 volts applied by the internal battery of the checker.

Although the checker has basically been designed to test bipolars, FETs and diodes, it can also be used to test various other devices if a little ingenuity is used. Thus it is possible to test sensitive low power SCRs, for example, by connecting them to the checker as for an NPN transistor (anode corresponding to collector, cathode to emitter, etc.), and noting if the device triggers into conduction when current is applied to the gate via the gain test button.

Higher power SCRs may be tested in a similar fashion, but in this case an external resistor may have to be connected between the anode and gate to provide sufficient triggering current to initiate conduction.

Programmable unijunctions or

"PUTs" may be checked in much the same way as low power SCRs, but with the anode and cathode reversed so that they correspond respectively to the emitter and collector of a bipolar. The polarity switch in this case should be set to the "PNP" position.

Refer now to the circuit diagram of the Transistor Checker.

Basically, the unit consists of a 9V battery and a 1mA meter movement in series, connected via a polarity reversing switch to the pair of terminals marked "E-D" and "C-S". The first of these terminals connects to the emitter of bipolar transistors, or alternatively to the drain of FETs; similarly the other terminal connects to the collector of bipolars, or the source of FETs. Note the converse way in which the terminals are used for the two different types of device. The reason for this will be explained shortly, along with the reason for the four diodes in series with the "C-S" terminal.

The third terminal is that marked "B-G", intended to connect to the base of

Simple Transistor Tester

bipolars, or the gate of FETs. This terminal connects via the "gain test" button and a selected resistance to the side of the reversing switch which leads to the "C-S" terminal.

The "FET-Bipolar" switch has two poles, one of which merely serves to connect two 22 ohm resistors as a 10mA shunt across the meter in the "FET" position. The other pole of the switch selects the value of the resistance in series with the "B-G" terminal.

The purpose of both the 270 ohm resistor in series with the "E-D" terminal, and the single diode in parallel with the meter, is to protect the latter in the event of a complete short-circuit between the "E-D" and "C-S" terminals. With these components in circuit the meter is effectively protected from any possibility of electrical damage due to shorts either in the device tested, or due to accidental touching of the test leads.

When a bipolar transistor is connected to the checker, its collector is connected to the "C-S" terminal. Because the current drawn by a bipolar device is largely independent of the actual value of collector voltage, rather like a pentode valve, the four diodes in series with this terminal have virtually no effect upon device operation. They merely reduce the effective battery voltage between collector and emitter to about 7.8 volts (9V less 1.2V, the voltage drop of the two forward-biased diodes).

The bipolar device therefore draws its normal I_{ceo} when connected into the checker with the polarity switch set to the correct position and the battery switch moved to "ON". The current will be read on the meter either on the basic 1mA scale, or on an effective 10mA scale if the "FET-Bipolar" switch has been set to the FET position.

Then when the "gain-test" button is pressed, the base of the device will be connected to the collector supply rail via a resistance producing either 2uA or 100uA of base current, depending

upon the position of the "FET-Bipolar" switch. The meter therefore indicates the normal DC beta of the device on an effective scale of either 0-500 or 0-100.

The very same circuit is arranged to perform the tests on FETs simply by connecting these devices to the checker in the converse manner. The drain is connected to the "E-D" terminals, while the source is connected to the "C-S" terminal. This has the effect of placing the four diodes in series with the source lead, where their voltage drop may now be used to provide a reverse bias.

When a FET is connected into circuit it initially draws its zero-bias current I_{dss} , which may be read on either the 10mA meter range or the 1mA range as appropriate. Pressing the "gain-test" button then has the effect of connecting the gate to a point which is reverse-biased with respect to the source, by the substantially constant 1.2V drop across whichever two of the diodes in series with the source are conducting, according to the selected polarity.

The reason why four reverse-parallel connected diodes are used in series with the "C-S" terminal is that this arrangement provides a substantially fixed 1.2V drop regardless of polarity, without requiring additional poles on the polarity switch.

Note that although the resistance in series with the gate of the FET will vary according to the position of the "FET-Bipolar" switch, this does not affect the tests as the gate of a FET does not normally draw significant current. The function of the "FET-Bipolar" switch is only to adjust meter sensitivity and the series resistance in the base/gate lead, for base current adjustment in the case of bipolar transistors.

The "Bipolar" and "FET" positions marked for this switch are those that will normally be the most appropriate for the majority of devices of each type. However, as explained above, both positions can be used for either device

PARTS LIST

1 case, 130 x 68 x 41mm
1 screen-printed front panel
1 1mA meter, 52 x 49mm rectangular
1 9V battery, Eveready 216 or similar
2 DPDT miniature toggle switches
1 SPST miniature toggle switch
1 momentary contact pushbutton switch
1 PC board, 58 x 51mm, code 78tfc7
5 1N914, EM401 or similar silicon diodes
1 2.1mm DC input jack socket plus suitable metric screws
6 resistors: 2 x 22 ohm, 1 x 270ohm, 1 x 82k, 1 x 220k, 1 x 3.9M (all $\frac{1}{2}W$)
3 banana-type sockets and plugs, for test leads
Hookup wire, PCB pins, battery clip solder, tinned copper wire

NOTE: Components with lower ratings may be used provided their ratings are not exceeded. Components with higher ratings may also be used if physically compatible.

type, depending upon requirements.


Diodes are tested on the checker by connecting them between the "C-S" and "E-D" terminals. The way in which they are connected is not important. In one position of the polarity switch the diode will be forward-biased, and the meter should accordingly give a full-scale reading — unless the diode is defunct. In the other position of the switch the diode will be reverse-biased, and the meter will read the reverse current I_r . With most diodes this should be a very low reading, even on the 1mA range.

As can be seen from the photographs, construction is quite straightforward. All components, with the exception of the switches and input sockets, are mounted on a small printed circuit board measuring 58 x 51mm and coded 78tfc7. The board, in turn, mounts directly across the meter terminals.


Commence construction by fitting all the hardware to the front panel. The front panel of the prototype was made from photosensitive aluminium, but we assume that commercial panels will be available shortly after this article appears. The battery sits directly under the front panel switches, and is packed in pieces of scrap foam to prevent short circuits and to hold it in place.

Refer to the combined overlay and wiring diagram when wiring up the unit. PC stakes are used to facilitate connections from the board to the front panel switches and sockets. The connections are run in rainbow cable, while tinned copper wire is used for inter-switch wiring.

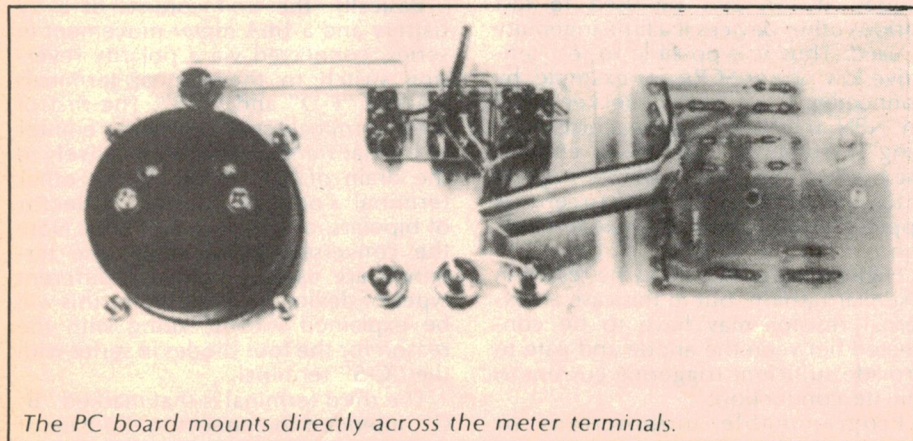The meter used is a Japanese made 52mm rectangular movement of a type which is widely available (model



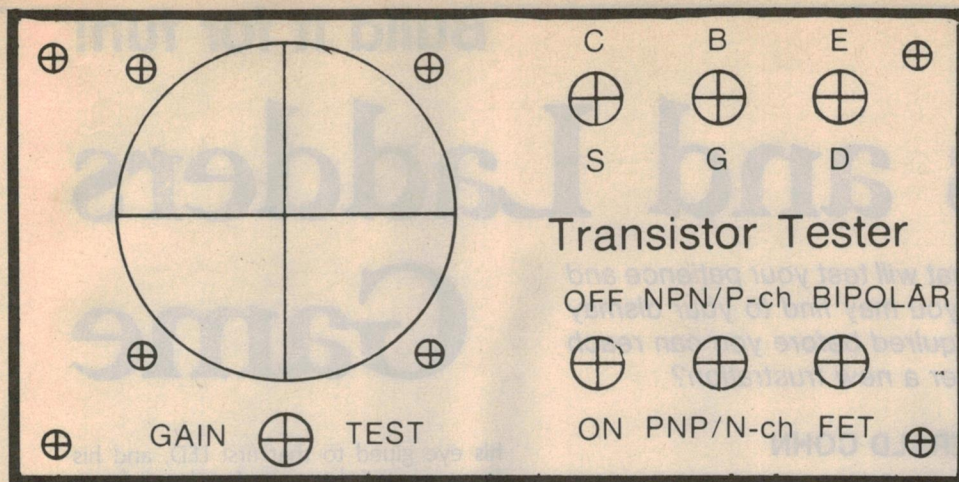The PC board mounts directly across the meter terminals.



Here is an actual size reproduction of the front panel artwork.

MRA45B). It is mounted directly on the front panel, with the "gain-test" pushbutton immediately beneath it.

Since the circuit runs from a 9V supply rail, it can be also powered from one of the now commonly available "plugpack" power supplies. A special input jack socket is used for the external power supply, and this should be mounted in the end of the case furthest from the meter. Constructors may, however, consider this feature as optional.

Operating the checker when it is completed should present few problems, as the control switch markings clearly show the various functions. However, one type of testing situation where the user may need guidance is where the polarity of the device to be tested is not known.

The circuitry of the checker is such that checking a device with the polarity switch in the incorrect position will generally not cause damage to either the device or the checker. However, there is still the problem of interpreting the readings obtained, in order to decide the correct polarity.

In most cases the readings given by the checker are themselves the best

guide to the correct polarity. With bipolar transistors, incorrect polarity is usually indicated by an abnormally high I_{ceo} reading, together with a DC beta reading which is either very low or effectively zero. Hence, if this combination of readings is obtained, the idea is to change to the other polarity and see if the results improve. If they do, then the original polarity was clearly wrong; but if the results are the same as before, then either the device is a dud or you have its connections jumbled.

With FETs an incorrect polarity setting generally does not show up in the I_{dss} test, because the channel of most FET devices is symmetrical and conducts equally in either direction. However, incorrect polarity will immediately show up when the "gain-test" button is pressed: the meter reading will increase rather than decrease, revealing that the gate is being forward-biased instead of reverse-biased. This effect should always be taken as a sign that the polarity switch has been set to the incorrect position.

There may be some occasions, when testing bipolar transistors, where it is difficult to decide whether the

leakage/saturation current I_{ceo} is acceptably low, or "too high". This matter is one for which there is no simple answer, because a "good" germanium device may have an I_{ceo} many times higher than a "faulty" silicon device — particularly if it is a high-gain power type.

Temperature also plays a part. With germanium devices I_{ceo} roughly doubles for every 8-10 degrees C rise in temperature, while with silicon devices it doubles for every five degrees C rise. Also the I_{ceo} of a device is roughly proportional to its gain, so that the gain should also be taken into account.

In general any silicon bipolar transistor which produces a significant I_{ceo} reading on this checker, at any normal temperature, should be regarded as suspect. All except the very high-gain, high-power types should give virtually zero reading, even on the 1mA range.


Unfortunately no similar rule-of-thumb can be given for germanium devices, some of which may exhibit quite a high I_{ceo} . The best plan with these is to compare them with a known good device, if one is available. Failing this, all you can do is make the decision on the basis of the gain check. If the current increases quite substantially when you press the gain button, then the device is probably a good one.

Whether the device is a silicon or germanium type, make sure that it is cool before testing it. A device just unsoldered from a circuit and still quite warm can give an abnormally high leakage reading, even though it may be quite normal.


Finally, a brief note about comparing the device parameters as measured by this checker with those given in manufacturers' data. If you want to do this, and there is no reason why you should not, the main thing to watch is the symbols used.

For bipolar transistors, if you cannot find I_{ceo} listed for the device you are concerned with, try looking for I_{co} — the two are identical. If this is not listed either, the data may alternatively give I_{cbo} or I_{co} , the collector-base saturation current. But as this is equivalent to I_{ceo} divided by the gain of the device, it is not hard to convert between the two. Most manufacturers use the symbol h_{FE} to represent DC beta, so that it is the figure or figures listed under this symbol which should be used for comparison.

Where FETs are concerned, the symbol I_{dss} is almost universally used for zero-bias drain current, so that there should be no problem with that parameter. But be careful where transconductance is concerned, as two different symbols are used: Y_f and g_{mo} . Fortunately, the definitions of both are sufficiently close to the test performed by our checker to make the figures comparable in practice.

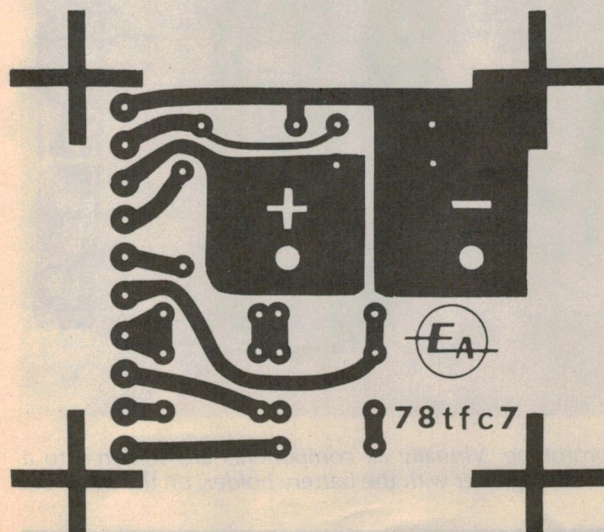

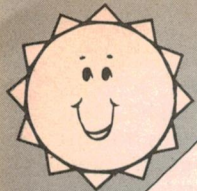At left is an actual size reproduction of the PCB pattern.



Build it for fun!

LEDs and Ladders Game

Here is a low cost electronic game that will test your patience and sense of timing. Seemingly simple, you may find to your dismay that literally hours of patience are required before you can reach the top. Why not build it and discover a new frustration?

circuit design by GERALD COHN

The idea for this fiendish device was originally hatched in the fertile imagination of one David Edwards, and a suitable circuit published in our March 1976 issue. Now, nine years later, the time has come to present an updated version that is both lower in cost and easier to build.

As you can see from the photographs, the game consists of a small box, fitted with a switch, 16 small light emitting diodes (LEDs), and an illustrated front panel. The illustration is a schematic drawing of a well, with a ladder reaching from the bottom to the top. The LEDs are arranged on the rungs of the ladder, representing successive foot positions as the ladder is climbed, with the topmost LED on the ground at the top of the well.

When the CLIMB switch is pressed, the

bottom LED commences flashing at a 0.75Hz (approx) rate. The object of the game is simply to light successive LEDs on the ladder by appropriate manipulation of the CLIMB button. Success is signified when the topmost LED is illuminated.

The trick in the game is that the CLIMB switch can only be operated when a LED is on. When this condition is satisfied the LEDs illuminate in turn, to simulate the effect of a light climbing the ladder.

If, however, the CLIMB switch is pressed when no LED is illuminated, the player is surprised and infuriated to find that when a LED comes on again he has slipped back towards the bottom of the well. Just how far down the well the player slips depends on how long the button is pressed while the LED is off, and how far he has progressed up the ladder!


So, having limbered up his wits, as well as his switch operating finger, our player attacks the infernal machine again. With

his eye glued to that first LED, and his finger poised, he waits for that light to come on. Flash! the LED emits, his finger stabs the button, and the light commences to climb!


One! two! three! four LEDs emit in turn, the button is released, and a fraction of a second later, the LED goes out. With bated breath, our player scans the LEDs, and is rewarded by seeing the fourth LED come on again. Once more he stabs at the button, once again the light commences to climb.

Some time later, the 15th LED casts a ruddy glow over the perspiring face of our player, who decides to stop for a short time to wipe his brow. Those last few steps had seemed to be harder to climb than the earlier ones; in fact, he'd only just managed to go from the 14th to the 15th rung in one go.

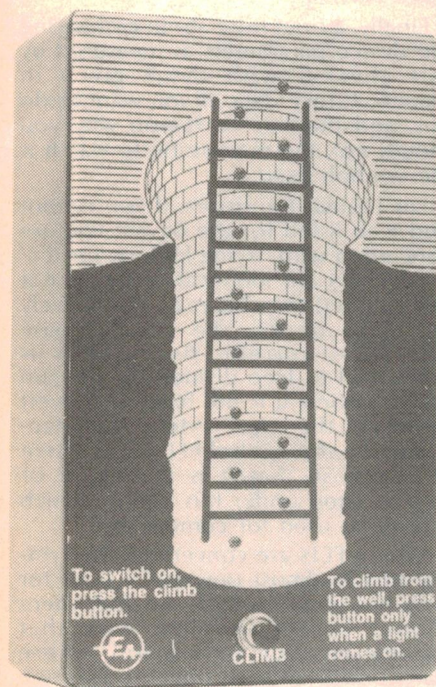
Directing his attention back to the game, our hero is horrified to find that he's slipping back down the ladder. Now only the 14th LED is alight. Desperately, he punches mindlessly at the button, the LED climbs up higher, just reaches the top, and then goes out. And he's still



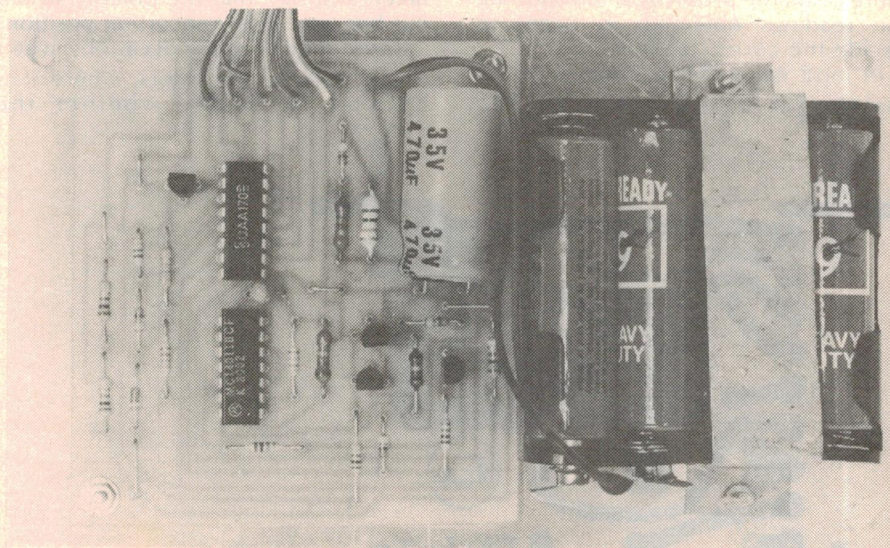What could be easier? Just press the CLIMB button to light successive LEDs on the rungs of the ladder.



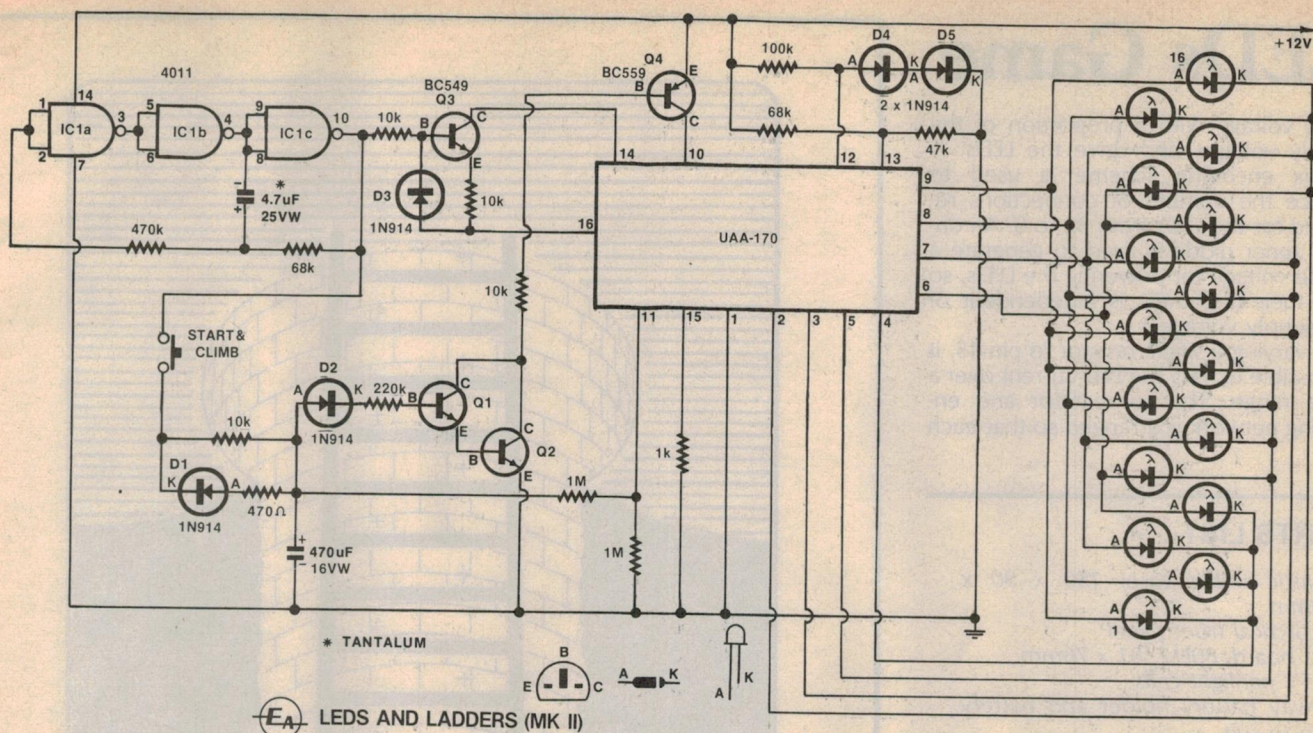View inside the completed prototype. Virtually all components are soldered to a small PC board which is mounted, together with the battery holder, on the lid of the case.



The circuit basically consists of a CMOS clock oscillator (IC1a, IC1b and IC1c) and a UAA170 LED driver IC.

pressing the switch!

With a heart-rending groan, he releases it, and then watches dejectedly as a LED near the bottom of the ladder flashes merrily. Some minutes later, he musters his courage, and once more commences to climb.

Just in case you're wondering whether or not it is possible to reach the top, we can assure you it is. In fact, the 1976 version had a little man at the top waving to show that he had managed it. We haven't been quite so corny this time!

HOW IT WORKS


Let's now take a look at the circuit diagram and see exactly how the game operates. It's really very simple and consists essentially of a CMOS clock oscillator and a UAA170 LED driver IC.

The clock circuit uses a 4011 quad NAND gate IC with gates IC1a, IC1b and IC1c arranged as a standard three-inverter CMOS oscillator. The frequency of oscillation is set by the 68k resistor and the 1uF tantalum capacitor and is about 0.75Hz. Output from the oscillator is derived from pin 10 and takes the form of a square wave with an amplitude only slightly less than the supply voltage.

This signal is fed to a large (470uF) electrolytic capacitor via the CLIMB switch and a diode/resistor network.

The charge on the capacitor is used to represent the distance up that ladder that the player has climbed. It works like this: If the CLIMB button is pressed when the oscillator output is high, the diode is reverse-biased and the 470uF capacitor is charged via the 10k resistor. When the button is released, the capacitor slowly

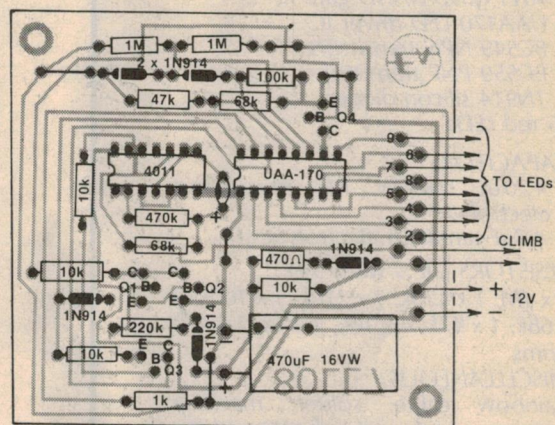This wiring diagram shows the PC board as viewed from the component side. Make sure that all polarised components (ICs, transistors, diodes & electrolytic capacitor) are correctly oriented.



discharges through the two 1M resistors and the base-emitter junctions of the Darlington transistor pair (the time constant is very long so that, for the moment, we will assume that the capacitor retains its charge indefinitely when the button is released).

If, on the other hand, the CLIMB button is pressed when the oscillator output is low, the diode is forward biased, and the capacitor discharges rapidly through the 470 ohm resistor.

Since the capacitor is charged from a constant voltage, the voltage across the capacitor follows an exponential law with respect to time. This means that the initial rate of change of voltage is much higher than the rate towards the end of the charging period.

Thus a given closure time of the CLIMB switch will propel the "player" quite a few rungs up the ladder if he is near the

bottom, but only one rung or less if he is near the top. This is why our hypothetical player found the going harder towards the top of the ladder.

A second feature arising from this exponential curve is that the rate of discharge is greatest at the top of the ladder, so that an error in timing there produces a greater fall down the ladder than a corresponding mistake at the bottom. Now you can begin to see why the game is so infuriating.

The second section of the circuit monitors the capacitor voltage and uses this information to drive a LED display. Heart of this is the UAA170 IC, a 16-pin DIL plastic encapsulated device distributed in Australia by Siemens Industries. It should be readily available from your usual components supplier.

Internally, the UAA170 consists of a set of 15 comparators. These compare the

LEDs Game

input voltage with a proportion of the supply voltage, and drive the LEDs. A matrix encoding scheme is used to reduce the number of connections required for the LEDs from 32 to 8. An on-chip zener diode is used to generate a stable voltage for powering the LEDs, so that their brightness is independent of the supply voltage.

By varying a single resistor to pin 15, it is possible to vary the LED current over a wide range. The comparator and encoding network is arranged so that each

PARTS LIST

- 1 plastic utility case, 150 x 90 x 50mm
- 1 Scotchcal front panel
- 1 PC board, 80LL7, 81 x 76mm
- 8 1.5V penlight cells
- 1 8-way battery holder and battery clip to suit
- 1 N/O pushbutton switch

SEMICONDUCTORS

- 1 4011 quad NAND gate IC
- 1 UAA170 LED driver IC
- 3 BC549 NPN transistors
- 1 BC559 PNP transistor
- 5 1N914 silicon diodes
- 16 red LEDs

CAPACITORS

- 1 470uF 16VW PC mounting electrolytic
- 1 4.7uF tantalum electrolytic

RESISTORS (all 1/4 watt, 5%)

- 2 x 1M, 1 x 470k, 1 x 220k, 1 x 100k, 2 x 68k, 1 x 47k, 4 x 10k, 1 x 1k, 1 x 470 ohms.

MISCELLANEOUS


- Rainbow cable, solder, machine screws, nuts, washers, scrap aluminium etc.

NOTE: Ratings are those used on the prototype. Components with higher ratings may generally be used providing they are physically compatible.

LED is illuminated in turn, so that when they are arranged in a line, the effect is of a point of light moving along the line.

Pins 12 and 13 are the reference inputs to the comparators. The voltage applied to pin 12 becomes the lower threshold, while the voltage applied to pin 13 becomes the upper threshold. We have referenced pin 12 to 1.2V by means of diodes D4 and D5 to compensate for the turn-on voltage of Darlington transistor pair Q1 and Q2. This means that the first LED will turn off only when the voltage on the control input (pin 11) exceeds 1.2V.

The 16th LED will be illuminated when

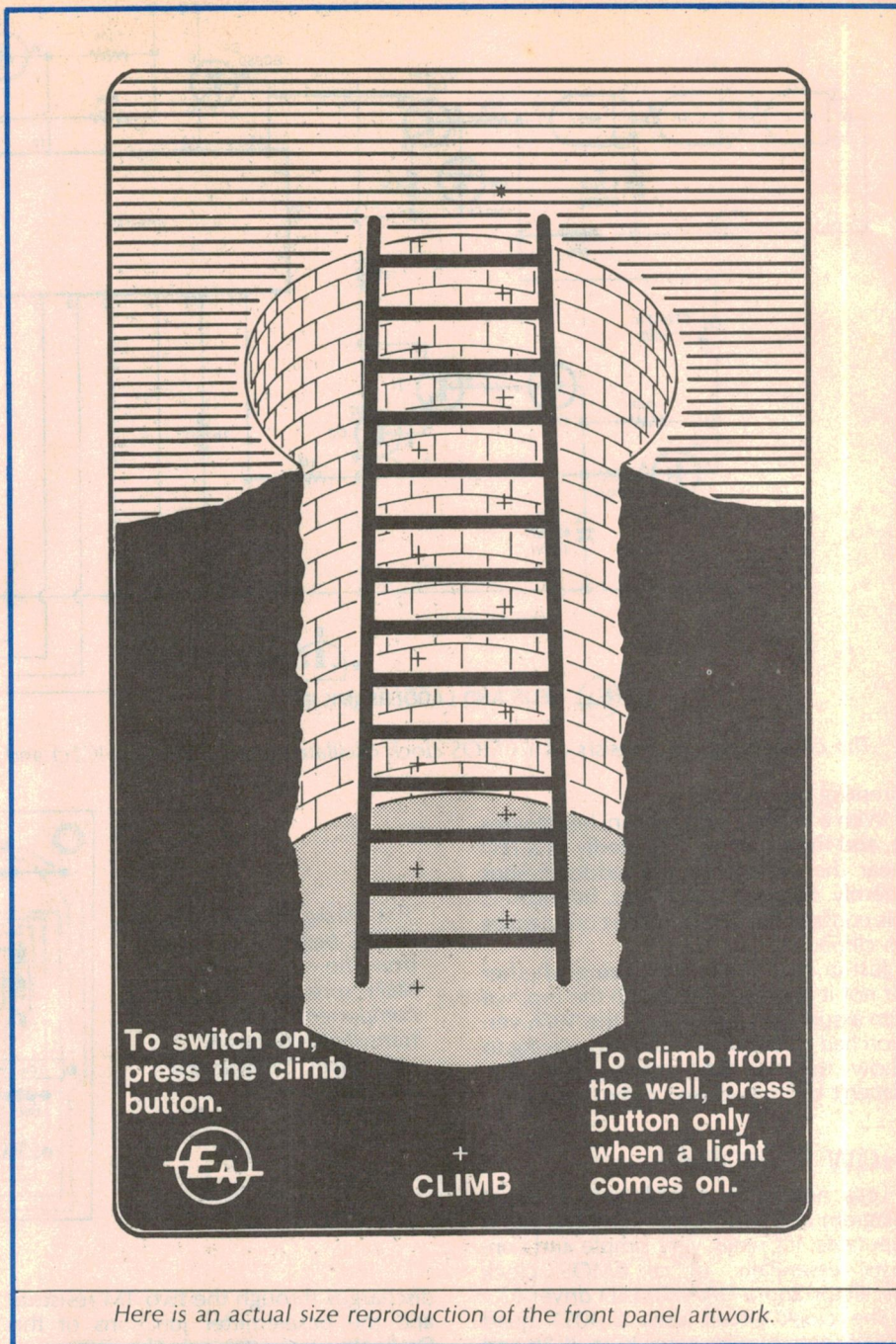

Here is an actual size reproduction of the front panel artwork.

the voltage on the control input exceeds the voltage on pin 13, while for voltages in between these two extremes, corresponding LEDs will be illuminated. Note that when the threshold between two LEDs is being crossed, both LEDs will be partially illuminated.

The control voltage is applied to pin 11 from the voltage divider formed by the two 1M resistors. These values have been chosen in conjunction with the values for the divider connected to pin 13 to ensure that it is possible to turn on the 16th LED.


Although we stated earlier that the loading on the 470uF electrolytic capacitor was negligible, this is not strictly so. The two 1M resistors, in conjunc-

tion with the impedance presented by pin 11, plus the input resistance of the Darlington pair as well as the leakage resistance of the electrolytic itself, combine to slowly discharge the capacitor. This discharge is most noticeable when the capacitor is highly charged, and accounts for the "slipping back" observed by our hypothetical player. This adds to the difficulty of the game.

The stabilised LED driving voltage is made available at pin 14, and is normally connected to pin 16 via a suitable resistor. In this case, transistor Q3 is included in series with a 10k resistor, and the output of the CMOS oscillator used to switch the transistor on and off. This, in turn, pulses the LEDs, eliminating the

WHAT? ANOTHER BOOK ON PERSONAL COMPUTERS?

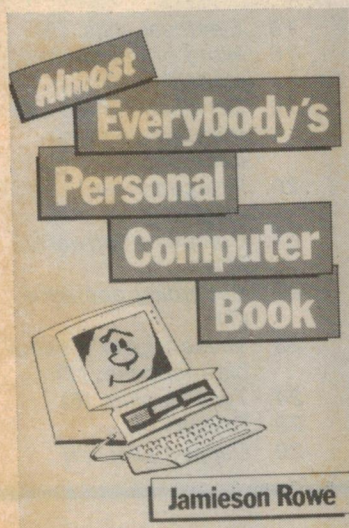- * Behind the myths and jargon
- * Data processing made simple
- * Software and hardware explained



* How to care for and keep your personal computer

JUST \$8.95
POSTAGE INCLUDED

You won't need a degree in mathematics or any previous knowledge of electronics or computers to understand **ALMOST EVERYBODY'S PERSONAL COMPUTER BOOK**. It will not make you an instant expert on every aspect of personal computers, but it will give you a good basic understanding of what they're all about.

Jim Rowe is presently the managing editor of **ELECTRONICS AUSTRALIA**, **ELECTRONICS TODAY**, **SONICS** and **YOUR COMPUTER** magazines.

☐ Please send me copies of "ALMOST EVERYBODY'S PERSONAL COMPUTER BOOK" for just \$8.95

Name Address
..... Postcode Phone

☐ Cheque*/Money Order* enclosed for \$8.95, or bill my ☐

Bankcard ☐ American Express Card ☐ Mastercard

Card No.

□ □ □ □ □ □ □ □ □ □ □ □ □ □ □ □

Card expiry date Signature

Detach this coupon and mail it in an envelope to: FREEPOST No. 4, THE FEDERAL PUBLISHING CO. P/L, P.O. Box 227, WATERLOO 2017.
(No postage stamp required if posted in Australia.) *Make cheques/money orders payable to THE FEDERAL PUBLISHING CO. P/L.

ADVERTISING INDEX

ADVERTISER	PAGE
Acetronics	110
Active Electronics	58
Altronics	47, 48, 49 50, 51, 52
Amtex Electronics	17
CQ Electronics	110
David Reid Electronics	57
Delsound	11
Department of Defence	40, 41
Dick Smith Electronics	IFC, 22 23, 72, 73, A2, A8, A9 A18, A19, A24, A25 A31, A32
Electronics Australia	21, 32, 43, 71, 80, 93, 110, 112
Elmeasco Instruments	79
Emtronics	59
Federal Publishing Co.	81, 112
Gammatron Pty Ltd.	89
Geoff Wood Electronics	76
Hi-Com Unitronics	43
Ice Acoustics	106
Jaycar Electronics	12, 13 66, 67, 102, 103
Jimmy Romanous	110
JWD Electronics	110
Philips	107
Pioneer	2
Radio Despatch Service	20
RCS Radio Pty Ltd.	110
Rod Irving Electronics	9, 29 70, 86
Stotts Correspondence College ..	99
Timegate	110
TEAC	OBC
Vanfi (Aust)	IBC
Zap Electronics	4, 5

FUNDAMENTALS OF SOLID STATE


Fundamentals of Solid State has been reprinted, revised and updated showing how popular it has been. It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised texts very heavy going. It begins with atomic theory, diode types, unijunction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A glossary of terms and an index complete the book. Fundamentals of Solid State has also been widely adopted in colleges as recommended reading — but it's not just for the student, it's for anyone who wants to know just a little bit more about the operation of semiconductor devices.

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017.
PRICE \$4.50 OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017. **PRICE \$5.40.**

JANUARY CROSSWORD

ACROSS

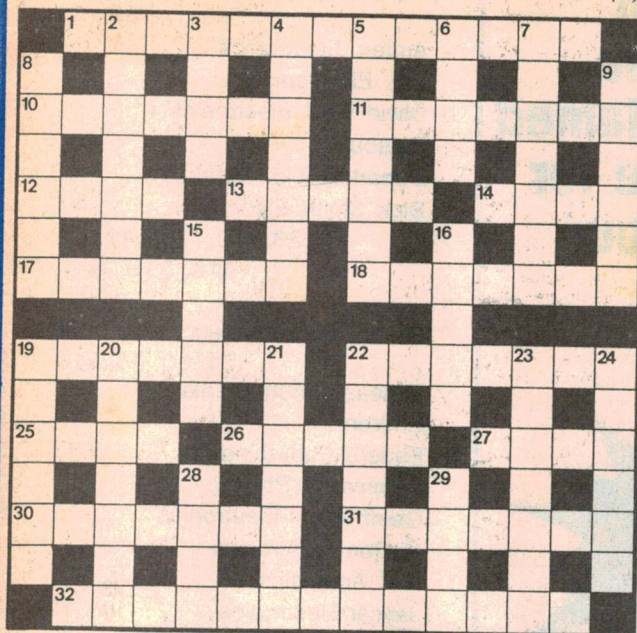1. An increase in signal strength. (13)
10. Lightning arrestors may have these. (3,4)
11. Kind of inductor. (7)
12. Tonal range. (4)
13. Frequencies of about 1 gigahertz. (1-4)
14. Not impecunious. (4)




17. Inverter. (3,4)
18. Who produced the FET in 1958? (7)
19. Cut a female thread. (4-3)
22. Type of amplifier. (5, 1, 1)
25. Toroid core. (4)
26. Electrical pioneer. (5)
27. Elementary particle. (4)
30. Record-making unit. (7)
31. CRT fault. (3,4)
32. Said of many iron alloys. (13)


DOWN

2. Navigational satellite. (7)
3. Solder constituent. (4)
4. Type of link. (7)
5. Enclosure for your stereo, TV, etc. (7)
6. Type of switch. (4)
7. Enthusiastic reception. (7)
8. Common electrode. (6)
9. Pattern-maker. (6)

SOLUTION FOR NOVEMBER

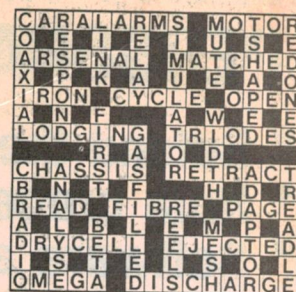

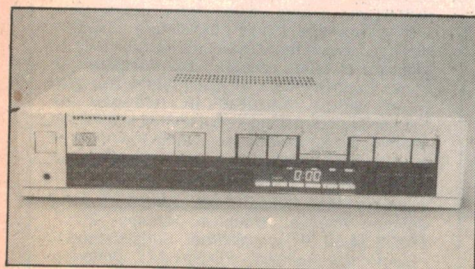15. Electrical units. (5)
16. Word of the phonetic alphabet. (5)
19. Sensitive meters can measure its symptoms. (6)
20. Interconnected magnetic flux. (7)
21. Computer software. (7)
22. Recording operation. (7)
23. These trigger a sensible response. (7)
24. Type of plug. (6)
28. Crystal. (4)
29. Capped joint. (4)



Next month in Electronics Australia*

Philips Stereo TV Receiver

TV receiver design has come a long way in the last few years. Next month we will detail all the new circuit techniques and features of the Philips stereo TV receiver.

Marantz CD player reviewed

The Marantz CD-84 is an up-market CD player with full programming facilities and infrared remote control. February Electronics Australia carries a detailed review. (Note: review held over from January due to space restrictions).

Low-cost Door Minder

Just starting out in electronics? Here's a project designed especially for beginners. When someone interrupts a light beam, it sounds a warning buzzer.

Busker's Amplifier

This handy amplifier is completely portable and is capable of operating from either the mains or a 12V battery. It features guitar and high-level inputs, 17W RMS output power, an in-built loudspeaker, and bass and treble controls. It's just the thing for busking or for guitar practice at home.

* Although these articles have been prepared for publication, circumstances may change the final content.

EA marketplace EA marketplace

FOR SALE

SCANNER LISTINGS: 27-510Mhz. Over 1600 Vic stations listed in freq and alpha sorted order. \$7.95. Kasp Electronics PO Box 408, Noble Park 3174.

EX-ABC AUDIO TAPES: 1/4" wide on 10 1/2" metal spool, \$6.85; plastic spool, \$5.85; 7" spool, \$2.25; 5" spool, \$1.25. Post extra. Also in stock: 1/2", 1" and 2" tapes. Waltham Dan, 96 Oxford St, Darlinghurst, Sydney. Phone (02) 331 3360.

TRANSISTORS: BC546, 547, 548, 549, 556, 15c ea, BD139 30c ea, 2N3055 90c ea. 5mm LEDs: red 10c ea, grn 14c ea, yell 15c ea. IN4148 4c ea. Zeners: 1W 3.3V, 8.2V, 15c ea. Post and pack only \$1.00 to LMF Products, PO Box 384, Cootamundra, 2590.

NEW RADIO VALVES: For entertainment or industrial use. Waltham Dan, 96 Oxford St, Darlinghurst, Sydney. Phone (02) 331 3360.

AMIDON FERROMAGNETIC CORES: Large range for all receiver and transmitter applications. For data and price list send 105x220 SASE to: R.J. & U.S. Imports, PO Box 157, Mortdale, NSW 2223.

BLACKTOWN NEXT TO TELECOM OFFICE
Electronic Components
PC Boards, Computer Repairs
OPEN 7 DAYS
(02) 621 5809
30 Campbell St BLACKTOWN NSW
CQ ELECTRONICS

HAVE ANY OF YOUR FRIENDS TOLD YOU LATELY...? ABOUT ACETRONICS MINI BULK BUY DISCOUNT SYSTEM. IF YOU HAVE RUN 'MONEY' DRY OVER THE HOLIDAYS THEN YOU HAVEN'T BEEN DEALING WITH ACETRONICS PCBs LAST YEAR. DO YOURSELF A FAVOUR SEND LARGE SAE FOR MONEY SAVING CATALOGUE.

ACETRONICS PCBs, PO BOX 76, YAGOONA 2199. TELEPHONE (02) 645 1241.

JWD ELECTRONICS

- MANUFACTURES YOUR PCB'S IN LESS THAN 48 HOURS ON EPOXY.
- WE HAVE NO MINIMUM ORDER!! (MIN. CHARGE 100 CM2).
- WE ALSO DESIGN ARTWORKS AND ASSEMBLE PCB'S.
- RING FOR A QUOTE OR REFER TO DEC. ISSUE E.A.

IT'S AS SIMPLE AS SENDING YOUR ARTWORK TO:

JWD ELECTRONICS
P.O. BOX 341
RIVERSTONE NSW 2765
PHONE: (045) 73 6097

CAT PC SOFTWARE

Mission S1

is an Adventure/Simulation for the DSE CAT Personal Computer. You control an Experimental Space Vehicle, The TSV1 on its first mission. Disc-\$20.00

Mail order only

TIMEGATE 27 Hunter St.
Malvern 3144

TEK 549 STORAGE CRO: With C20 polaroid camera. VG cond, plus spares \$1100. Precision GR oscillator 1218-B 900-2000MHZ with P/S, \$325. Transponders 9GHZ with magnetron; unused, sealed, \$125. National BW VTRS NV3020E, \$125 each, working. All above carriage extra. S. Dekker, Box 437, Gawler, 5118.

SLIM LINE DISK DRIVES: For Apple II only \$225!! Insurance, 90 day warranty, postage, tax included. Disk interface card \$45, hobby card \$9.50, ribbon for CP80/EX80/BX80/DP80 etc. \$9.00, 1000 1/4W resistors \$10.00. No postage required. Write for catalogue. Sultan Micro, PO Box 232, West Ryde 2114.

VINTAGE RADIO CHASSIS: Part sets, Philips Eliminators, Horn Loudspeaker, volumes Harmsworth Wireless Encycl; \$350 the lot. S. Dekker, Box 437 Gawler 5118.

RCS. RADIO PTY. LTD.

Established 1933

IS THE ONLY COMPANY
WHICH MANUFACTURES AND
SELLS EVERY PCB & FRONT PANEL
published in EA and ETI

651 Forest Road Bexley 2207
AUSTRALIA

RING (02) 587 3491 FOR INSTANT PRICES
24-HOUR TURNAROUND SERVICE

DISPLAY ADVERTS IN MARKETPLACE are available in sizes from a minimum of 2cm X 1 col rated at \$15 for a col cm. Ad sizes may be increased up to a maximum of 10 col cms.

CLASSIFIED RATES \$3.60 for 40 letters or part thereof per insertion payable in advance. Minimum 80 letters.

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

CHEAP ELECTRONIC COMPONENTS: Low as 4c each polycaps, electros, diodes, 2c resistors — 70c a 100 same. Croc clip jump leads \$1.90 per 10. 500 mix resistors \$2.95. Postage 50c. Send for free list. Diggerman Electronics Box 33, Coramba 2450.

SUPER 80: software and hardware still available. For info, write to: Matrix Software, PO Box 291, Kensington 2033.

SPEECH SYNTHESISER

BASED ON THE ADVANCED SPO256 CHIP & PRICED \$44.00 IT IS BY FAR THE BEST VALUED SPEECH SYNTHESISER EVER. CONNECTS TO ANY PARALLEL O/P. A MANUAL CONTAINING SAMPLE PROGRAMS IS INC. ON BOARD LED TO MONITOR HANDSHAKING, TONE & VOLUME CONTROL, AUX CONNECTION SOCK. SEND YOUR MONEY ORDER OR A SELF ADD ENV. FOR MORE DETAILS TO:
JIMMY ROMANOUS 2/6 DAINTREY CRES
RANDWICK 2031. NSW.

projects & circuits

Number 3

THE CONTENTS:

Audio, Video Projects

Video Amplifier for Computers and VCRs; Video Enhancer; Vocal Cancellor; Stereo Simulator for Tuners and VCRs; Guitar Booster for Stereo Amplifiers.

Automotive Projects

Transistor-Assisted Ignition System; Breath Tester Checks Blood Alcohol Level; Low Fuel Warning Indicator; Speed Sentry for Cars; Audible Turn Signal Indicator.

Mains Power Control Projects

Musicolour; Photographic Timer; Driveway Sentry; Touch-Lamp Dimmer.

Power Supplies & Test Equipment

Battery Saver for Personal Portables; Dual Tracking $\pm 22V$ Power Supply; 3 1/2-Digit LCD Capacitance Meter; In-Circuit Transistor Tester.

Miscellaneous

Nail Finder; Portable 3 1/2-Digit Heart Rate Monitor. 10 Year EA Project Index.

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017, **PRICE \$4.50** OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017, **PRICE \$5.40.**



1983 issue of this magazine. It would seem from the portion of the circuit diagram that you sent that your set is an ideal candidate for this conversion.

Infrared TV remote control

I recently completed construction of your Infrared TV Sound Control but have encountered difficulties. After a number of tests on the transmitter board, I have come to the conclusion that all three oscillators are running at several times the quoted frequencies. Using the specified 10k Ω resistor and .0082 μ F capacitor, the 10kHz oscillator (IC1d) has a frequency of 50kHz.

Changing the timing capacitor to .047 μ F or the resistor to 56k Ω gives the required 10kHz frequency.

Similarly, the 5ms and 1ms oscillators give negative-going pulses of about 1ms and 0.1ms respectively every 42ms. I have not experimented with changing component values here as I would like to ask if you can shed any light on these results and confirm that 10kHz is the correct transmitter frequency.

I also note that the signal pulse on the base of the Darlington transistor is about twice what it is on the collector, which again appears to be incorrect unless the current drawn by the infrared LEDs causes this low reading. (K.F., Albion Park, NSW).

● Your problem lies with the 4093 NAND Schmitt trigger IC. It seems that the hysteresis of a 4093 varies according to the manufacturer, something that we were unaware of at the time of publication.

If you were supplied with either the Philips HEF4093B, SSS SCL4093B or Motorola MC14093B device, then the following circuit changes should be made: (1) increase the 2.2k Ω resistor on pin 2 of IC1a to 6.8k Ω ; (2) increase the 18k Ω resistor on pin 12 of IC1b to 47k Ω ; and (3) increase the 10k Ω resistor on pin 6 of IC1d to 33k Ω .

The circuit is correct for the National CD4093BC, RCA 4093B and SGS HCC/HCF4093B types.

The voltage reading recorded at the collector of the BD681 is correct and is simply the saturation voltage of the transistor.

Flickering digits on capacitance meter

Some time ago I built your Digital Capacitance Meter (EA March 1980) and have found it to be a very useful piece of equipment indeed. However there is one annoying little problem. The right hand digit flickers rapidly between

Electronics Australia Reader Service

"Electronics Australia" provides the following services:

PHOTOSTAT COPIES: \$3 per project, or \$6 where a project spreads over multiple issues (price includes postage). Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries. We reserve the right to supply complete back issues instead of photostats, where these are available.

CHASSIS DIAGRAMS: For the few projects which require a custom metal chassis (as distinct from standard cases) dyeline plans showing dimensions are normally available. \$3 including postage.

PC BOARD PATTERNS: High contrast, actual size transparencies: \$3, including postage. Please specify positive or negative.

PROJECT QUERIES: Members of our technical staff are not normally available to discuss individual projects, either in person at our office, or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the last three years.

Charge \$3. We cannot provide lengthy answers, undertake special research, or discuss design changes. Nor can we provide any information on commercial equipment.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" or submitted without fee may be answered in the "Information Centre" pages, at the discretion of the Editor.

COMPONENTS: We do not sell electronic components. Prices and specifications should be sought from advertisers or agents.

BACK ISSUES: Available only until our stocks are exhausted: \$3 (includes post and packing and storage fee).

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 227, Waterloo 2017.

zero and one. When a capacitor is attached the flickering ceases and all is well, but remove the capacitor and away she goes. This fault only shows up on the Microfarad range; on the other two ranges the display is rock steady.

I have noted the errata and made the changes you recommend. I see that I am not the only one who has this problem and I refer to a letter from R.E. of Panawonica, WA in the Information Centre on page 141 of November 1981 EA. I followed your suggestions to that writer and would swear that everything relating to switch S1b is OK. Can you help me with this please. (W.Y., Belmont, NZ).

● The flickering of the least significant digit which you describe is quite normal for this project. This only happens when there is no capacitor connected to the Cx terminals, and only when in the μ F range. This occurs because the auto nulling circuit is switched out when this range is selected.

While we agree that this may be mildly annoying, be assured that it is not due to a fault of any kind. We feel that the minor nature of the problem does not warrant any modifications being made. If the flickering becomes annoying, why not turn the meter off, or on to another range?

Autodim affected by control tones

I have been reading over the last few issues of people having problems with the Autodim project (Jan, 1981). I have built 14 of these dimmers and not had any problems yet, but one!

All 14 of these dimmers have worked successfully first time, though when

dimming from full brightness to "off" at some stages the light would fluctuate, not flicker. This occurred at different times during the dimming cycle. This light fluctuation lasted approximately 5-10 seconds: "not much to worry about" you say, but I am using the dimmers to create a false sunrise and sunset in bird aviaries and need a stable effect.


I borrowed an oscilloscope from work and checked all waveforms listed in the article; they were found to be correct. Next step was to watch the mains waveform for any deviation: shock horror. At precisely the time when the lights acted up, the mains waveform took on a ripple effect, though still maintaining a 50Hz sine wave.

Since the sync signal is taken directly from the mains could this be upsetting the circuit? I noted that the output of IC1a changed its high & low periods during this time. Is this the carrier signal used by the council to switch hot water services? Would the problem be within the dimmer or could it be the mains? Is there anything else I could check for? (E.B., Busby, NSW).

● The effect that you describe is indeed due to the control tones used by the supply authorities to switch off-peak hot water systems. The control tones have a frequency of about 1kHz and an amplitude of around 20 volts peak-to-peak.

While we have not had any complaints about tones affecting this circuit before, it should be reasonably easy to de-sensitise the circuit. One suggestion (which we have not tried) is to connect a 10k Ω resistor in series with the signal line from D3 and a shunt .033 μ F capacitor from pin 9 of IC1a to the neutral line.

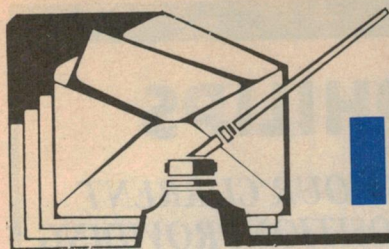The extra parts can be easily added to the back of the PC board.



Information centre

Problems with 40W inverter

Recently I bought a 12/240V 40W inverter (EA, May 1982) kit and find some problems which I hope you may help overcome. Firstly, I was supplied with a PL18/40VA transformer which had two 9V windings. I wired the transformer in and, on turn-on, had severe voltage drop problems.

With an 11W 240V fan the voltage was 190V and with a 30W TV 185V. With the frequency switch set to variable the voltage increased by 20V. In the fixed mode one 2N3055 runs warmer than the other. After checking the circuit I changed the transformer to a PL12/40VA and noticed, with the 11W fan, that the voltage rose to around 230V. With the TV, the voltage was the same.

In the fixed mode the voltages drop to 220V and 210V respectively. I used a Tandy colour burst crystal and changed both ICs, as well as checking all the other components. I would like some advice on the problem of voltage drop, and would welcome suggestions. (D.F., Marsden, Qld).

• First of all, we recommend that you return to using the original transformer for this project. If the rest of the circuit is working properly, and the input voltage is correct, this transformer will provide the correct output voltage.

Make sure that the battery or power supply that you are using is capable of

providing 12V at 3 or 4 amps. If this is OK, run the inverter in the fixed mode and measure the voltage across the transformer primary. This should be about 24V AC. Under these conditions the unloaded transformer secondary voltage should be about 275V AC.

Similar results should be obtained using the variable frequency oscillator. If there is still a significant difference, it is most likely due to a fault in this oscillator, since there is nothing to go wrong in the fixed one — either it will work properly or it will not work at all.

It is normal for one transistor to run warmer than the other in the fixed mode due to the slightly uneven duty cycle at the output of IC2 (5369).

EA Car Burglar Alarm

In the May 1984 edition of *Electronics Australia* you published a Deluxe Car Burglar Alarm project, which I have built and find excellent. This alarm is set to sound for two minutes and then reset. Could you please tell me if there is any way to modify the circuit or change component values so that the alarm would sound for more than two minutes and then reset.

The two minute alarm may be adequate for some but for someone like myself, who is a fair distance from his car most of the day, a longer alarm period gives the owner more chance to hear it. Keep up the good work as we do appreciate it. (J.G., Thornbury, Vic).

• It is quite easy to increase the alarm time for the Car Burglar Alarm. All you have to do is increase the value of either R3 or C2 on the Q output of IC3a. For example, increasing R3 to 1.5M should increase the alarm time by 50%.

There is a limit to how far you can go though. If the capacitor leakage current is greater than the charging current, the alarm will never shut off.

VHF-UHF conversion for B&W TV set

I have a Princess colour TV set which I was told will not work in conjunction with a computer as it does not have UHF channel selection. I would like to modify the antenna board and/or the VHF tuner to accommodate a computer input without the expense of removing the existing VHF tuner and substituting a UHF tuner. Could you advise me if this is possible and provide me with a schematic diagram for this alteration. (H.P., North Ryde, NSW).

• It is not practical to convert your VHF only television into a combined VHF/UHF receiver. By far the simplest solution is to purchase a ready made UHF-VHF down converter. This could then be connected between the television set and your computer.

A more satisfactory result could be obtained by feeding composite video directly into the TV. This was explained in some detail in the article on the video amplifier which appeared in the August

Notes & Errata

BEACHCOMBER METAL LOCATOR (December 1984, 3/MS/111): the power supply section of the circuit diagram (top right) incorrectly shows -9V at the top and +9V at the bottom. The polarities should be transposed.

STRESS MONITOR (May 1984, File 3/EG/28): the meter specified for this project was 0-250μA. This should have been 0-1mA, although any meter of up to 2.5mA would be acceptable.

DECODER FOR AM STEREO (October 1984, 2/TU/54): the two 0.47μF capacitors must be tag

tantalums, not PC electrolytics as listed in the parts list.

16K RAM CARD FOR APPLE II (November 1984, 2/CC/91): pin 5 of IC1b and pins 1 and 13 of IC6a should all be tied to Vcc instead of as shown on the schematic on page 37. Also, pin 1 of IC3b should be shown connected to pin 13, not pin 12.

Other corrections to the article are as follows:

Equation 3 on page 39 should read

$$A^*12 = A13 \oplus \text{BANK} + A12$$

Equation in Table 4 should read

$$R(tn + 1) = (A0 \oplus A1)(tn)$$

Lines 7 and 8 in column 3, page 39, should read

If A3 is logic 0 then BANK = 0

If A3 is logic 1 then BANK = 1

Equation 4 should read

$$\text{REN}(tn + 1) = (A0 + A1)(tn)$$

Under the heading *Boolean algebra* on page 41, all equations are missing either the complementary symbols or the exclusive circle around the OR symbol to make it XOR. These equations should read as follows:

$$a \cdot \bar{a} = 0 \dots \dots \dots (1)$$

$$a + \bar{a} = 1 \dots \dots \dots (2)$$

$$(a \cdot b) + (\bar{a} \cdot \bar{b}) = a \oplus b \dots \dots \dots (3)$$

$$\bar{a} + \bar{b} = \overline{a \cdot b} \dots \dots \dots (4)$$

$$a \cdot b = \overline{a + \bar{b}} \dots \dots \dots (5)$$

Finally, readers are advised that the author has changed his address to PO Box 167, Ascot Vale, Victoria 3032.

broadcaster Robert Parker has managed to win from his collection of historic 78s. While not without his critics, he certainly has my support.

This Duke Ellington recording opens with "East St. Louis Toodle-oo", "Black and Tan Fantasy" and "Creole Love Call", all from 1927 originals; then follows "Saturday Night Function" and "Cotton Club Stomp" (1929), "Mood Indigo" (1930), and an ear-catching "Daybreak Express" (1933). Four more tracks follow from the '40s, the album ending up with an 18-minute suite under the collective title: "Black, Brown and Beige" (1944).

As with the Glen Miller album (Sept '83) and New Orleans Jazz Classics (Dec '83), the sound on this one is virtually free from 78rpm surface noise, but with enough treble, bass, dynamics and reverb to give the old tracks a totally new lease of life.

Which of the records you buy can be governed purely by your partiality to artists and titles. (W.N.W.)

made its debut in London, followed by appearances in Canada, France, Scandinavia and the Far East.

Recorded in the Oldcatholic Church, in Utrecht, Holland, during October 1983, the sound is very clean, with glass-hard transients, and a touch of building ambience to add warmth to sound. The playing itself is first-rate.

As a first choice, I imagine that most would prefer an orchestral version of the work as, for example, the commendable Delos recording featuring Gerard Schwarz, Elmar Oliveira and the Los Angeles Chamber Orchestra. (The digital LP and CD versions were reviewed in Feb. '81 and Aug. '84).

But, popular as the "Seasons" may be, one might hesitate to invest in more than one orchestral version, whereas the guitar group can offer a quite different sound. The themes are the same, but it is left to the trio to interpret, on their most percussive of instruments, the birdsongs, the summer breezes, the north wind, the thunder and the lightning.

A word of advice: set the volume to a level that your amplifier will handle comfortably, but move your chair a little closer than normal to the stereo speakers. The whole performance will take on a more intimate, more vivid quality. Alternatively, try listening to it on a good pair of headphones.

In short, well worth a hearing if you're at all partial to the sound of the classical guitar. (W.N.W.).



DEVOTIONAL ALBUM

WORSHIP II. Church in the City. Stereo LP. Star Song SSR-0046. [From Word Records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135.]

As might be imagined, Worship II is a sequel recording to an earlier and successful release from Star Song entitled simply "Worship". The music itself is provided by a group of gifted musicians and singers attached to Church in the City, Houston, Texas — affiliated with the Assemblies of God.

The title of the album may not be very imaginative but it is certainly appropriate. In keeping with the generally fundamentalist approach of the affiliated group, the lyrics are either scripture paraphrases or direct expressions of devotion and worship. They are set out in full on the inner sleeve and can be followed easily, throughout.

However, while the lyrics are conservative, the musical treatment is contemporary, without being extreme. Backing includes guitars, pianos, trumpet, flute, recorder, percussion and bass, with strings over-dubbed later.

Many of the songs appear to have been composed by members of the group and, while their titles may be unfamiliar, their themes will be self-evident:

Lord, I've Got a Song — Jesus Is the Name I Love — Fixing Our Eyes on Jesus — Your People Thank You — Hear, Oh Israel — June 24 and 25 — Glory to God in the Highest — Life-Giving Blood — Isaiah 43 — The Wind of the Spirit — Worthy is the Lamb — If It Had Not Been the Lord.

The sound quality is well up to normal standards and, all told, it adds up to a pleasant album of contemporary group/congregational singing which should find ready family acceptance. (W.N.W.)

PHILIPS

IS YOUR CURRENT POSITION PROVIDING THE REWARDS AND SATISFACTION THAT YOU REQUIRE?

Philips are world wide leaders in the design and manufacture of electronic products and have operations in all capital cities and major regional centres throughout Australia employing more than 4000 employees.

As a result of our continual advancements in high technology equipment and increasing sales we are continually searching for experienced and qualified technical staff for our service centres throughout the country.

Our product range is extremely diverse, ranging from consumer products such as Natural Colour Stereo T.V. receivers, Laser Video and Audio players and the latest in Video Recorders and cameras to our Professional Range of products such as Micro Processor Controlled 2-way Radio Equipment, Data Communications Information Equipment, Micro Processor based PABX/Traffic Controllers and Defence Systems.

To service the exceptional range of products it is important that we have the right technical staff, therefore we are seeking to employ a number of technicians in different fields in SYDNEY, MELBOURNE, BRISBANE and ADELAIDE.

Essentially, applicants will have some form of formal training, for example an E. & C. Certificate, Radio Trades Certificate or similar. However, the most important quality we seek in a Technician is **experience**.

As can be appreciated experience is closely attuned to the type of product serviced, but as a guide the persons we are seeking should have sound experience in any of the following areas:

- CTV, VCR and Audio Servicing, both field and workshop;
- Fault finding on hard unit systems using digital micro processor techniques;
- The servicing of 2-way radio equipment both UHF and VHF in digital and analogue circuitry;
- In servicing Electronic Office Equipment and Financial Systems including Electronic Funds Transfer using digital logic.

As would be expected, wages and conditions are excellent and staff benefits include superannuation after a qualifying period.

If you have had experience in any of the above areas and you are interested in positions in any of the locations mentioned, forward a detailed resume, outlining in full your qualifications and experience, also highlighting your particular area of interest to:

Mr C. N. Westacott
Personnel Officer



PHILIPS INDUSTRIES HOLDINGS LIMITED
443 Concord Road
Rhodes, N.S.W. 2138.

PHILIPS — We want you to have the best

IMPROVE YOUR HI-FI WITH SPIKES!!!

If you've built your own speakers or turntable you'll know that overseas research recommends the use of spikes for speaker stands or turntable tables.

Super-hardened!

Height adjustable!

Gold flashed!

**NOW THEY ARE
AVAILABLE
IN
AUSTRALIA!**

Sets of 8

**ICICLES
SPIKES**

\$14.95

per set
+ \$1 p&p

STANDS

SUPER QUALITY
HIGH RIGIDITY
LOUDSPEAKER
STANDS TO FIT
BOOKSHELF SIZE
SPEAKERS
DRILLED FOR
SPIKES (EXTRA IF
REQUIRED.)
MEDIATE
CONSTRUCTION
SEMI-GLOSS
FINISH

\$75

per pair
+ \$5 p&p

Available black or brown
H 435mm W 250mm D 350mm

Other sizes available on request

Allow 28 days for delivery
Anywhere in Australia

Payment by Cheque or Money Order


ICE ACOUSTICS

**29 Ravenhill Road,
Turramurra, NSW, 2074**

Please send me sets icicles
..... black stands
..... brown stands

NAME
ADDRESS
STATE POSTCODE

RECORDS AND TAPES

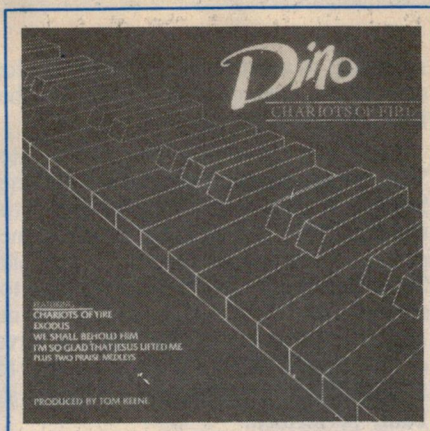

GOSPEL PIANO

Dino: Chariots of Fire. Stereo LP, Liht LS-5819. [From Word Records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135. Phone (03) 729 3777.]

In the September issue, I expressed some reservation about Dino's "Majesty" album on the grounds that the Title Track (not "little" track, as printed) did not "hang together too well" as pure audio, even though possibly very successful as a stage presentation.

This album has much the format, with featured tracks at the beginning and end of each side, separated by long medleys of Gospel themes, old and new, on solo piano. The essential difference is that this is a studio performance, unbroken by applause or comment. Indeed, the medley on each side blends naturally into the final track, lending considerably more cohesion to the presentation.

Side one opens with an ambitious arrangement of "Chariots of Fire", mainly with synthesiser backing. It closes with the popular and tuneful "Exodus" theme, with orchestra and chorus. In between is a medley of nine well known hymn tunes, improvised and ornamented in the Dino manner.

Side two begins with "We Shall Behold Him", with orchestral backing, followed by another presentation on solo piano, described as a "Praise Medley". The closing track is "I'm So Glad That Jesus Lifted Me", done with instrumental backing and with progressive key changes, finally accelerating to full take-off speed!

The surface is quiet and the sound well balanced but, on peaks, it lacks the subtle "unstressed" quality that distinguishes the latest generation of audiophile LPs. That apart, Dino's "Chariots of Fire" has what it takes to make it a favourite for family listening. (W.N.W.)

JAZZ LIVES AGAIN

Duke Ellington: A Memorial. The Great Bands in Digital Stereo — Vol. II. RCA Victor LP VPL1-0436.

In a moment of inattention, I put this disk on the turntable under the impression that it was an American re-release. My immediate reaction, a few bars into the first track, was that they hadn't taken long to copy the techniques being used by Robert Parker to re-record and revitalise old 78s, as per our story on page 20 of the September '83 issue.

A few moments later, I looked again at the jacket and the reason for the sonic similarity was obvious: it was a Robert Parker transcription on a local RCA release and is, in fact, the second in the series specifically mentioned in our September article.

I recount the incident, not to draw attention to my own lapse of memory, but to emphasise the distinctive quality that recording engineer and ABC



GUITAR TRIO

Vivaldi: The Four Seasons. Played by the Amsterdam Guitar Trio. Stereo LP, RCA Red Seal VRL1-7474.

In his jacket notes, John W. Duarte points out that these popular, pictorial works were originally the first four in a set of twelve violin concertos, published in Amsterdam in 1725. As such, he suggests, Vivaldi would be unlikely to have objected to their adaption for three guitars, especially when played by a trio as capable as the one featured here.

Comprising Johan Dorrestein, Oiga Franssen and Helenus De Rijke, the Group was formed in 1978, after the members had completed their studies at the Sweelink Conservatorium. The Trio

TAPES

INTEREST

then, despite an obvious discontinuity, a quite surprising strength and consistency of tissue") but to my ear these pieces reflect a mighty respect for Schumann rather than hint at the later composer of those three great operas, *Salome*, *Elektra* and the *Rosenkavalier*.

To me their only interest is historical. The Sonata is as early as Op. 5, the Five Piano Pieces still earlier. Gould offers them in minutely controlled playing. Great variety of inflection is delivered with unquestionable authority. Certainly all pieces show unusual understanding of the piano's capabilities. And the digital recording makes the piano tone very faithful indeed.

A funeral march owes much to Beethoven and, as well as the very noticeable Schumann influence, there are also hints of Brahms. Of the best of Richard Strauss there is no sign, though there is a nice tune in the fourth of the Five Pieces. (J.R.)

MAKROPOULOS

Opera founded on the play by Karel Kapek. Elisabeth Soderstrom, Peter Dvorsky, Vladimir Krejcik, Anna Czakova, Vaclav Zitek, Beno Blachut and others with the Chorus of the Vienna State Opera and the Vienna Philharmonic Orchestra. Conducted by Sir Charles Mackerras. Two Decca analog discs in box with annotations by John Tyrrell. D44D2.

I must start by saying the translation of the Czech title into *The Makropoulos Case* leaves one with the wrong impression of the libretto of Janacek's opera which, by the way, he wrote himself. The notable Janacek scholar, John Tyrrell, who writes a splendid account of the work taking up five odd pages in the brochure accompanying the two-record set, suggests that William Mann's version of the *Makropoulos Document* gets much closer to the composer's meaning.

I must warn readers that a first run through will confront the listener with some puzzles, and perhaps a second one too. Before either I recommend reading Tyrrell's notes with great care. It will pay great dividends.

The *Makropoulos Case* makes the fifth and last Mackerras Janacek

recording of what can be regarded as the composer's five current operas in the international repertoire.

I first met the work in Paris in the late '60s when Mackerras conducted the Sadler's Wells Opera Company in it with the great late Marie Collier in the name part at the Chatelet theatre — the old Sarah Bernhardt. When I went behind to see him after the show he was engaged in a loud altercation with the representative of the French Radio, forbidding him to broadcast the performance as it was so badly performed.

The stage manager, who was translating Mackerras' expostulations into fluent French, answered my statement that I hadn't noticed anything go wrong with I thought rather cryptically: "You would have done if you knew it as well as you know *Madam Butterfly*." I had never met him before. That my wife and Mackerras' wife had to scour Paris the next morning to rescue his tail suit from a locked theatre and get it to Orly airport in time for Mackerras to use it in Prague that night is another story.

There is a habit among Czech singers to distort lines. In spoken Czech the accent always falls on the first syllable of the word with an unaccented lengthening of the second syllable and all this made more difficult in the Moravian accent of the language. I am explaining all this at such length in the hope that it might help you through the first few tries to unravel the problems in this elusive work and that you will find it as


rewarding as I did.

Among Tyrrell's extensive notes is a description of Czech pronunciation. This will be valuable to any libretto follower since the unfamiliar clusters of consonants has the accent almost always on the second syllable. Mackerras explained to me at supper after the show that the real difficulty in getting a perfect performance was in the rhythmic complexity of Janacek's vocal lines. Mackerras, by the way, had spent many years in Czechoslovakia and had learned to speak fluent Czech — even Janacek's provincial Moravian dialect.

The story is based on a novel by the writer Karel Kapek who became world famous with two plays, *RUR Rossum's Universal Robots* and *The Insect Play*. Both are politically slanted.

The *Makropoulos Case*, in brief, deals with the subject of longevity. The heroine is 300 years old, has acquired great riches, had a long list of lovers ("one cannot love for ever") and is now thoroughly fed up with life. The account of what happens to her I will leave to Janacek's eloquent music which indulges itself in many interesting side tracks, all in the composer's inimitable short ejaculated phrases and skilful assembling of them into a smooth and logical whole. I cannot praise this music too highly.

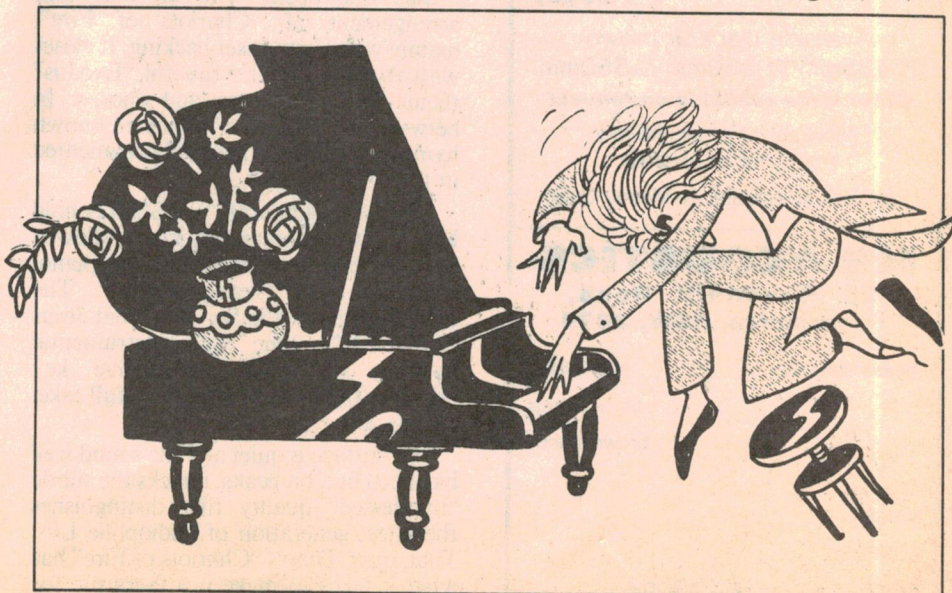The music is splendid to my, nowadays, more tutored ear and the recording brilliant. The main themes are illustrated in Tyrrell's splendid notes and there should be nothing left, after two or three tries, to give you anything but very much pleasure — even delight. (J.R.)



RAVEL

Scheherazade, Three poems of Mallarme, Madagascon Songs, Five Popular Greek Melodies, Song of the Lentisque Gatherers, and Don Quixote to Dulcinea. With the BBC Symphony Orchestra and Members of the intertemporary Ensemble Conducted by Pierre Boulez. CBS Masterwork Analog Disc M39023.

Heather Harper strikes 12 at once with a rivetting performance of Ravel's Asia, as fine a song as any written this century. It is so dominating that it makes the other two in the trio sound modest, fine as they are, by contrast. She is in great voice.

That she takes it at such a steady tempo adds to its majesty. The emotion changes as the singer goes through a long list of what she would love to see and experience in Asia. In her opinion Asia is a "wonderful old land of nursery-foes where fantasy sleeps like an empress in her enchanted forest" to the penultimate sinister stanza where she would like to see "a smiling headsman cut an innocent neck with his great curved oriental sword".

Slow sensuous phrases alternate with gorgeous bursts of music, and a studious veiled tone gives way to full throated thrusts, leading to the shattering climax.

I am not exaggerating when I write that the effect is overwhelming. So much so that the older two beautifully delivered songs in the bracket sound like vocal etudes.

Not the least surprising is the amount of passion Pierre Boulez evokes in the BBC Symphony Orchestra. I have always regarded him as a very cool gentleman, rather more like a bureaucrat than an ardent voluptuary. The orchestra provides exactly the right background for all the many varied Ravel songs, perhaps the most pendulous ever to be recorded on one disc.

Of the other items in the Scheherazade Suite, of which Asia is the first, there is the tranquil atmosphere of the Enchanted Flute, its beautifully played flute solo, and the subtly androgynous The Indifferent One in which sex of the "invited one" is quite plainly male while that of the host who importunes the him to enter and stay is never made clear.

Heather Harper shares the other Ravel songs with soprano Jill Gomez, Jessie Norman — who I think is the most glorious soprano to be born on this planet since Kirsten Flagstad — and baritone Jose Vin Dam. All sing attractively, thoughtfully paying devoted attention to French style with its difficult long legatos and light, almost flippant, interludes. This is a disc that I can recommend with great enthusiasm, especially to those who love French music as much as I do.

A list of the songs included is contained in the titles above the review. (J.R.)

LISZT

Piano Concerto in E Flat. Piano Concerto in A Major. Svyatoslav Richter (piano) with the London Symphony Orchestra conducted by Kiril Kondrashin. Philips Sequenza Analog Disc 412 006-1.

The photograph of Richter on the sleeve shows a balding man with white sideboards, very different from the sturdy, tough-looking fellow of some 20 years ago when he was welcome with worldwide acclamation. He was recording in London when I was there in the early 1960s and, as the PR man at Philips, Leslie Gould, was a friend of mine, I learned a lot about him.

He was never allowed out of sight by a sort of keeper, a fellow-Russian. He never left the recording studio for meals; all were sent in and carefully examined by his "companion". No alcohol was allowed and it was rumoured that drink was one of his problems. He remained a firm favourite for years. Other great pianists came but Richter remained peerless in the piano music of Schumann.

There is much reverberation in the opening bars of the E Flat Concerto and Richter's interpretation is very romantic indeed, with many rubatos and hesitations against a background of dazzling technique. It could be described as "gamey" — what the French mean by the word "faisande," with an acute accent on the last letter — in short, hung till high.

But even with the rubatos thrown in his statements remain masterful, though the style would be more appropriate to Chopin.

Liszt created a new form in this concerto, a fact skillfully explained in the sleeve notes and which lack of space prevents me from quoting here. Richter retains his beautiful touch, though some of his rubatos become irritatingly beyond credibility, torturing the line quite out of shape.

One novelty in interpretation occurs in the very first bars of the introduction which is taken majestically instead of vigorously — quite largo, in fact. The famous triangle notes in the finale, from which the concerto takes its name, go unheard on my very good equipment. Where they should be heard as a solo there is just silence.

Whenever Richter increases his speed he scintillates. The orchestra, except when it disappears under a long piano trill, is always in good balance. Inexplicably, this trill dominates to such an extent that the band, which has a dainty theme, seems to suddenly get modest, at least for a while at any rate.

As to the A Major Concerto, after several years away from it the first lovely theme still worked its magic on me. But it is taken so very slowly — I know it is marked "sustained adagio" — that it sacrifices some of its beauty. The horrid march sequence towards the end has lost none of its vulgarity but by contrast Richter takes the quicker portions at a dazzling speed. Despite this fleetness each note receives its correct value.

In the middle of the work, the cello solo of the main theme is most beautifully played. On the whole the orchestra plays very well and there are always Richter's sparkling runs. Incredibly, it gets still faster to a glorious finish. (J.R.)

STRAUSS (RICHARD)

Sonata in B Minor, Op 5. Five Piano Pieces Op 3. Glenn Gould (piano). CBS Masterworks Digital Disc D38659.

This is the late Glenn Gould's last recording and it is a pity that this eccentric but highly gifted artist is wasted on such trivial material. But such was the nature of Gould who, controversially, warmly supported the student Strauss' trivialities.

True and notable English critic, the late Ernest Newman, mentioned them with some respect ("There is now and

SOUNDERS

SIREN - the ever popular mechanical siren. 12V operation with a sound level pressure of 116dB. Comes with mounting bracket. Cat. LA-5265

ONLY \$29.95

WEATHERPROOF SIREN HORN

12V DC operation with deafening wail. Current drain 500mA approximately. Attractive off-white PVC finish. Cat. LA-5700

VALUE AT \$22.50

THIS MONTH ONLY \$19.50

5 WATT 8 OHM HORN - Fully weatherproof and with unique voice coil construction for dependability on full drive. Cat. AS-3180

ONLY \$9.95 Has plastic flare

116dB of "TWEETIE PIE"

This incredible little piezo screamer (measuring 57L x 33H) emits a 116dB wail. It sounds like a very loud canary. The sound at close range is almost unbearable. If you mount it inside your car and your alarm fires, a would be thief would probably be scared half out of his wits! Ideal for any component high noise alarm application. Simply connects to 12V DC.

Cat. LA-5255

ONLY \$24.95

30V 1 AMP POWER SUPPLY KIT

Brand new design with two ranges of current limit in special plastic case.

Cat. KA-1574 Ref: EA January 1985

\$64.50

Ref: EA Jan 1985

NEW



Jaycar
ELECTRONICS

NOW OPEN BURANDA QUEENSLAND

LOW COST STEREO HEADPHONES

Ideal replacement for walkie stereo units. Hi Fi sound. Cat. AA-2015

ONLY \$6.95

NEW

LOW COST QUALITY MICROPHONE

Looks like the \$70 plus units but at a staggering price. Unbelievable sound quality. Low impedance.

★ Supplied with 2.9 metre of cord and 1/4" phone plug
★ Attractive silver colour
Cat. AM-4090

GRAB THIS! \$19.95


VCR STEREO ADAPTOR

★ Converts mono sound of standard VCR's or TV's, AM radio etc to pseudo-stereo signal

★ 1 x RCAS socket input, 2 x RCA socket output
★ NOT A KIT, built, tested and guaranteed
★ Complete with plug-pack
★ Dimensions: 110 x 130 x 32mm
Cat. AV-6506

ONLY \$37.50

NOW OPEN BURANDA QUEENSLAND

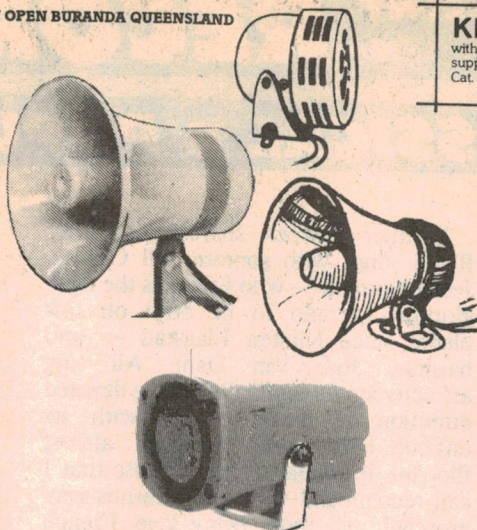

QUALITY PROBE CASES


We have secured a small quantity of probe cases. They can be used for digital (i.e. logic probes, pulsers etc) or for analog purposes (signal injectors etc).

PROBE CASE 1: Measures 155(L)x25(D)mm. It has a chrome metal body tube. A stout insulated probe is fitted at one end with a grommet/cap on the other. Weight 88 grams.

PROBE CASE 2: Identical to the above except that the body is a clear acrylic tube. Overall length 135(L)x25(D)mm. Weight 25 grams.


Probe 1 Cat. HB-6310 \$8.95

Probe 2 Cat. HB-6311 ONLY \$6.95

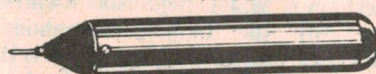

KEYSWITCH - This is the standard solid barrel type with 19.5mm mounting hole required. SPST action. Two keys supplied. Cat. SM-0130

ONLY \$6.95

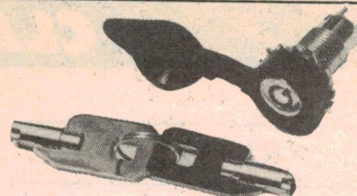

AUTOMOTIVE KEYSWITCH

This special automotive unit features a rugged neoprene rubber boot that clips over the weather-exposed part of the switch - even the keys are special tube types. Size of hole required only 12mm. Cat. SM-1032

ONLY \$4.95

'THE RED FLASHER'


Is your car safe? Well why not make sure by installing the Red Flasher. Thieves stay away from cars with flashing lights and this unit looks so good they're bound to think you have an alarm fitted, whether you have or not!

We supply a quality Swiss pushbutton illuminated square switch and electronics to make it flash plus 2 deterrent stickers.


Cat. KJ-7000

ONLY \$20.95

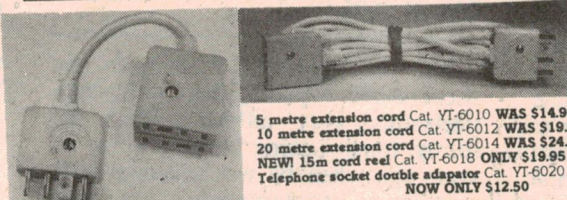AT LAST! LOW COST TELEPHONE EXTENSION CORDS!



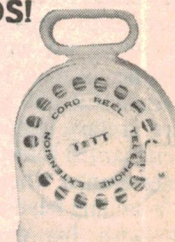5 metre extension cord Cat. YT-6010 WAS \$14.95 NOW \$12.95
10 metre extension cord Cat. YT-6012 WAS \$19.95 NOW \$15.95
20 metre extension cord Cat. YT-6014 WAS \$24.95 NOW \$22.95
NEW! 15m cord reel Cat. YT-6018 ONLY \$19.95
Telephone socket double adaptor Cat. YT-6020 WAS \$19.95
NOW ONLY \$12.50



THE ULTIMATE AMPLIFIER?

The staff of "Electronics Australia" have been working for over 12 months now on an ambitious project. The project? An integrated amp with input facilities for wide dynamic range sources such as compact discs and the new stereo Hi Fi VCR's.

Apart from this the amp has incredible features. Among them:

- ★ Torodial power transformer for very low hum radiation
- ★ Virtually ZERO screened wiring (almost no other wiring as well).
- ★ Massive heatsinks
- ★ Electronic input switching
- ★ Almost all parts mounted on one giant PCB so assembly is enormously simplified
- ★ Over 100 watts per channel genuine

Here is what EA (a conservative bunch usually) say about their new amp -

"The best integrated amplifier design ever published".

"A no compromise design. . ."

"Here is a stereo amplifier that will equal or better any commercial amplifier design regardless of price".

(Quotes from EA December 1984 Page 95)

Right now Jaycar is tooling up for this project. We will have a full kit available in MARCH. As you have come to expect from Jaycar our kit will reflect the "no compromise" philosophy. You will not be disappointed.

Jaycar
ELECTRONICS

Incorporating ELECTRONIC AGENCIES

NUMBER 1 FOR KITS

MAIL ORDER VIA
YOUR PHONE

VISA



NSW: SYDNEY 117 York St. Tel. (02) 267 1614

CARLINGFORD Cnr. Carlingford & Pennant Hills Rd. Tel. (02) 872 4444

CONCORD 115/117 Parramatta Rd. Tel. (02) 745 3077

HURSTVILLE 121 Forest Rd. Tel. (02) 570 7000

QLD: BURANDA 144 Logan Rd. Tel. (07) 393 0777

MAIL ORDERS: P.O. Box 480, AUBURN NSW 2144. Tel. (02) 643 2000

For all other information (i.e. P&P, shop hours etc) see other ads.

START YOUR OWN BUSINESS!

Many people will come back from their X'mas holidays to find their house has been burgled. They do not know that they can have electronic burglar alarm protection at a modest cost. Modern burglar alarm components from Jaycar enable you to easily make domestic premises more secure. So why not use your technical skills to install alarms in your neighbourhood in your spare time. You will make money and provide a community service as well.

★ ★ ★ PRODUCT OF THE MONTH ★ ★ ★

ACP-2 LOW COST STEEL ALARM CONTROL PANEL

This is the first low-cost but professionally made steel encased unit that we have seen. It has most of the main features of professional control boxes including:-

- ★ Lockable baked enamel steel box. Tamper switch can be fitted.
- ★ Space in box for back-up rechargeable batteries.
- ★ Facility to connect remote key switch. (Alarm will latch if remote key wiring is cut, whether alarm is "on" or "off").
- ★ Built in siren driver.
- ★ Relay output control provides 12V DC for sirens, bells etc.
- ★ N.O. instant and N.C. delay alarm loops for perimeter protection.
- ★ Will operate as fire alarm as well. (Has fire/smoke sensor inputs)
- ★ Different siren tone for fire/burglary
- ★ Diagnostic audible and visual alarm circuit status indicators
- ★ Simple one-key operation. Ideal for non-technical people to operate once installed.
- ★ Built in PANIC button
- ★ Separate timing and latching relay outputs with high current contact ratings
- ★ (The above could be used to operate automatic telephone dialler etc.)
- ★ Dimensions 230(H) x 170(W) x 70(D)mm
- ★ Weight 1.5kg without standby batteries.

This unit would normally cost at least \$200 elsewhere (even WITHOUT steel box). Jaycar has secured this product for you at a fantastic breakthrough price.

Cat. LA-5165



Believe it or not the ACP-2 is only

Power supply with facilities
to recharge Gel battery.
Cat. MP-3018
\$34.90

\$119!

Get battery to suit
Cat. SB-2480
\$24.50

**DON'T PAY
\$199
NEW**

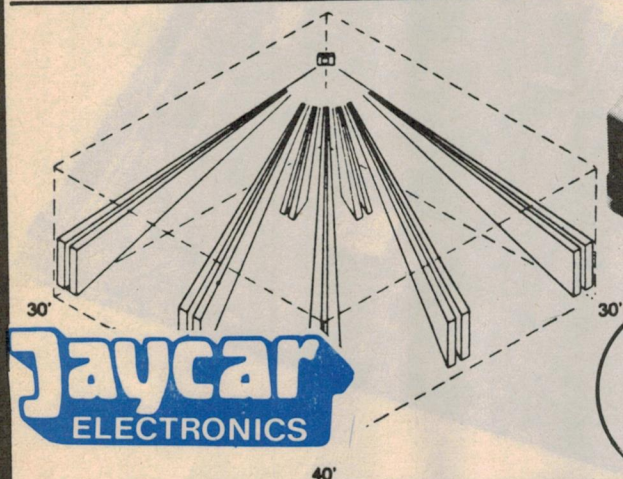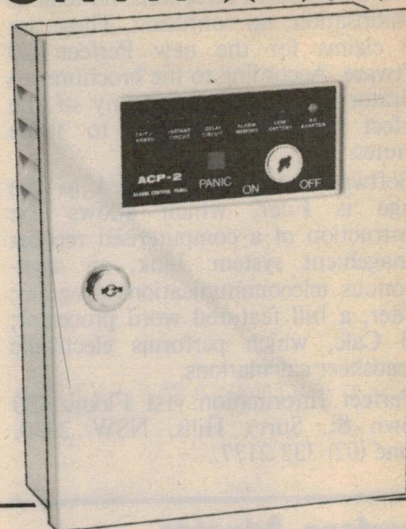

PASSIVE INFRA-RED DETECTOR

Jaycar breaks the \$100 price barrier. Bulk buying by Jaycar has enabled us to pass on large savings on popular Passive Infra-Red detectors. PIR's (as they are known in the trade) are the most popular method of detecting movement in open areas. They are very reliable and being passive (i.e. they are not transmitters like microwave or ultrasonic sensors) they false trigger a lot less. For a technical description see page 21 of our 1984 Catalogue. The only drawback in the past was their fairly high cost. Now you have no excuse to install one (or two) as part of your alarm system. (Please note that the illustration is indicative of PIR. We reserve the right to ship units of similar performance but possibly different physical appearance).
Cat. LA-5015


**ONLY
\$99**

SECURITY CABLE - 4 core, flexible stranded
conductors (7 x 0.18) in tough outer sheath.
Cat. WB-1590
60¢/metre - 100m roll \$38.00

EXTERNAL SIREN COVER

Louvered painted steel. Size for 5" horns or sirens. Special tamper switch on bracket.
(Included).

Cat. LA-5110

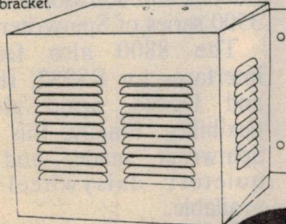

\$23.50



ALARM STICKER - A durable self adhesive sticker that clearly tells a would be thief that an alarm is fitted. Does not refer to a particular type of alarm - creates more doubt in the thieves mind.
Cat. LA-5100

95¢ each or 85¢ for 10 or more


PRESSURE MATS - A very underrated & reliable sensor. Once installed (we admit that lifting carpet can be a hassle) they can usually be forgotten about forever. Ideal for placing at vulnerable window locations. 800 x 520mm.
Cat. LA-5002

ONLY \$16.95 - N.O. contacts

WINDOW TAPE & BLOCKS

Simply stick tape in place and terminate with circuit blocks. 32 metre roll 6.4mm wide.
Cat. LA-5050

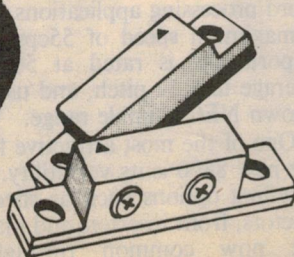
**ONLY \$7.50 per roll
Circuit Blocks Cat. LA-5060 ONLY 45¢ ea**



HEAVY DUTY REED/MAGNET

Used for roller-shutter doors, tilting garage doors or any wide-gap application. Supplied with strong magnet, flexible conduit connector etc.
Cat. LA-5073

**Magnet Protected
Housing**

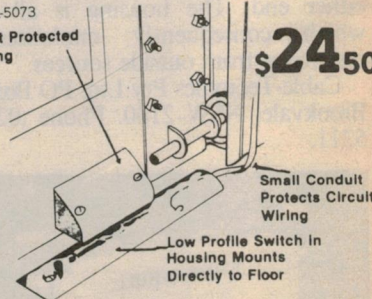

\$24.50

REED SWITCH & MAGNET

Complete assembly of a reed switch and powerful magnet. Can be screw mount or self-adhesive.

NORMALLY CLOSED (when in proximity of magnet)

Cat. LA-5070

NORMALLY OPEN (when in proximity of magnet)

Cat. LA-5071

**BOTH TYPES SAME PRICE
\$2.95 ea or \$2.50 ea for 10 or more**

Perfect Software — it's easy!

No complicated directions, no tedious memorisation, no confusion. These are the claims for the new Perfect 2.0 Software. According to the brochure, an operator can learn to use any of the Perfect programs in two to three minutes.

Software currently included in the range is Filer, which allows the construction of a computerised records management system; Link, an asynchronous telecommunications program; Writer, a full featured word processor; and Calc, which performs electronic spreadsheet calculations.

Perfect Information: 1st Floor, 480 Crown St, Surry Hills, NSW 2010. Phone (02) 332 2177.

Interface Adapter

Cable-Tectonics are now manufacturing a range of RS-232 Adapter Units designed to interface with various type of computer and peripheral equipment. They eliminate the need for operators to make changes to the cable connecting the equipment where standard and null conditions are required.

The unit which is small and designed to be fitted in-line with the cable is available with or without a null selector switch. The switched model can be used either "as-is" (wiring pins one to one) or by using the switch to change pins 2 and 3 so that they are in a null condition.

Three models are available with either male pins at both ends, female pins at both ends or male and female pins at either end. The housing is all metal which consequently minimises interference from outside sources.

Cable-Tectonics Pty Ltd: PO Box 126, Brookvale, NSW 2100. Phone (02) 938 5211.



Single card CMOS system

JED Microprocessors report that, in the first two months of production, over 50 of their single board computers have been sold. The computer is designed and built in Australia and is aimed at data logging and control applications.


It is a completely CMOS design, compatible with the STD bus and uses the National NSC800 CPU. This allows it to take advantage of the Z80 instruction set. It can also be programmed in XTBASIC, a version

of BASIC generated by JED and tailored for control applications.

The board is particularly suitable for applications where low power consumption and small size are important — the CMOS logic means that the board has a power consumption of only 0.5W.

Only a single JED STD/800 card is needed for up to 56K of memory, RS232 serial I/O, 30 bits of parallel I/O, two 16 bit counter/timers, eight analog inputs (8 or 10 bit) and a real-time clock.

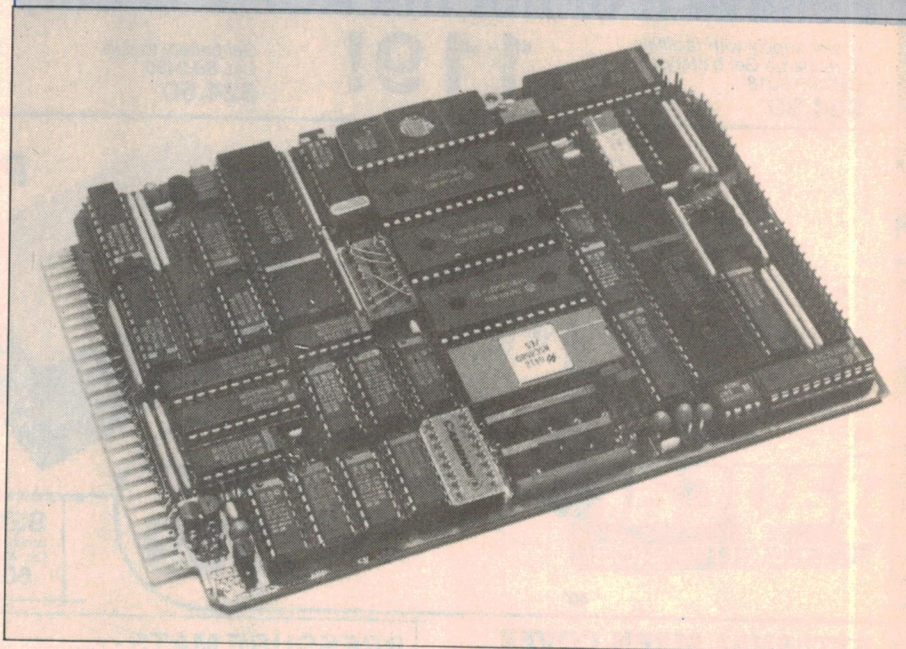JED Microprocessors Pty Ltd: PO Box 30, Boronia, Vic 3155. Phone (03) 762 3588.



New high speed printer from NEC

Datascape, the largest Australian distributor of NEC printers, have just announced the release of the new high speed Spinwriter — the model 8800.

The 8800 replaces the popular 7700 series which for many years has been a workhorse for heavy duty and high speed word processing applications. It features a maximum speed of 55cps and, more importantly, is rated at 50 cps using average text 12 pitch, and uses the well known NEC thimble range.

One of the most attractive features of the new 8800 is its versatility. All paper handling options such as sheet feeders, tractors, front inserters and many others are now common throughout the Spinwriter range. It uses the same

ribbons and accessories as the 2000 and 3500 series of Spinwriters.


The 8800 also features plug-in interfaces for RS232, IBM, Centronics and Diablo, again giving the user flexibility. Finally, this is the quietest Spinwriter made, and possibly the quietest daisywheel-type printer available.

Datascape Pty Ltd: 44 Avenue Rd, Mosman 2088. Phone (02) 969 2699.



COMPUTER PRODUCTS

Adam computer now stands alone

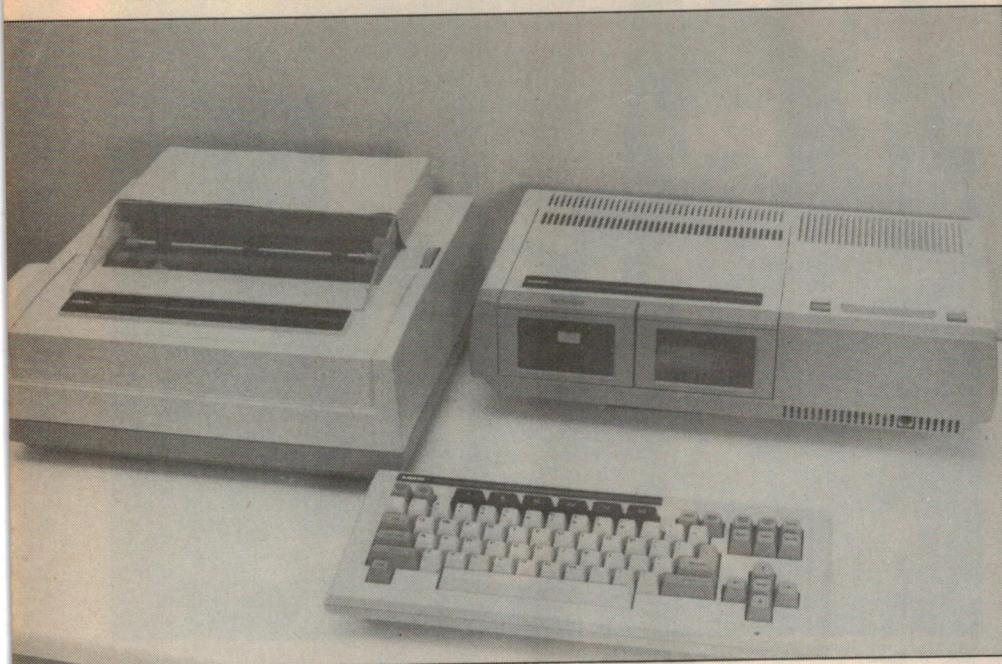

Following the sales success of the Module 3 Adam home computer, Computer Distributors Australia have announced the release of a stand-alone Adam. It will be targeted at the small business and office market, but will be available through department stores and electrical retail outlets.

The standard Adam has 80K of memory and 36 columns configuration, although 114K and 80 columns are available as an option. This option, together with the daisywheel printer and high speed digital cassette drive as standard inclusions position the package ideally for the small business computer market. A CP/M dedicated disk drive is to be released during 1985, together with 20 CP/M software titles.

Besides the printer and cassette drive, the stand-alone Adam package includes processor, keyboard and interfaces necessary to have the system fully operational — there are no additional expenses.

Computer Distributors: 26 Cross St, Brookvale, NSW 2100.

2 Gigabytes on laser disc

New technology from France offers a solution to the problem of accumulating libraries of data disks and tapes for Australian computer users.

Distributed in Australia by Pulsar Electronics, the new Gigadisc uses solid-state laser technology and will store 1000 Megabytes (one Gigabyte) of data on each single or double-sided disk cassette.

Gigadisc can be connected to almost any computer via the Small Computer System Interface (SCSI), and allows the direct accessing of any record.

Developed by the French company

Thomson-CSF, the computer peripheral can record and store data, text, digital images and speech for a period of at least 10 years.

A computer interface controller can be integrated into the Gigadisc unit, which can handle up to eight Gigadisc units. Associated with this controller is an automatic error detection and correction module.

With the use of the innovative laser technology, writing on the Gigadisc is achieved by the thermal alteration of a metallic film on the disc while reading is done by a laser diffraction technique.

Pulsar Electronics: Catalina Drive, Tullamarine, Vic 3043. Phone (03) 330 2555.



Apple launches computer service plan

Apple Computer Australia Pty Ltd announced a local "AppleCare" service plan for its range of personal computers. It is intended to provide an alternative, low-cost, extended warranty and service plan for Australian Apple buyers. It will be available immediately from more than 100 Apple dealers around Australia, and is designed to cover all Apple systems locally available.

The plan provides cover against unexpected repair costs, no matter how many times these might arise during the term of the agreement. Modular repair systems and careful qualification by Apple of repair centres are expected to result in fast repair service.

The annual cost of an AppleCare carry-in service plan contract will vary from about \$72 per year on an Apple IIe to about \$156 on a 512K Macintosh. Older Apple products, such as the Apple II+, will also be eligible for cover.

Further information can be obtained from Apple Computer Australia Pty Ltd, 37 Waterloo Rd, North Ryde, NSW, 2113. Phone (02) 888 5888.

IRH to handle Seiko components


IRH Components has been appointed Australian agents for Seiko Instruments and Components. Seiko products now available from IRH include liquid crystal displays, fibre optics and thermal printers.

Seiko Instruments and Components are specialists in the production of liquid crystal displays including modules providing up to 80 characters per line and multicolour displays using electro-deposited colour filters.

Seiko also produce a wide range of quartz crystals and crystal oscillators using a photolithographic process which reduces the effect of ageing.

Further information on the Seiko range of products is available from IRH Components, 53 Garema Circuit, Kingsgrove 2208. Tel (02) 750 6444 or (03) 484 5021.

12 and 24V fluoros

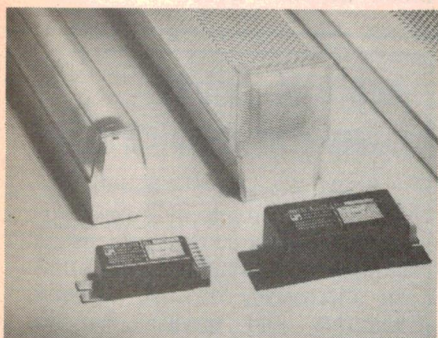

Selectronics, manufacturers of a wide range of transformers and wound components, have just released a series of low voltage fluorescent lamps designed to operate from 12V and 24V DC supplies.

Powered by the Selectronics designed Invert-A-Lite, these new lamps are available in 13W, 18W and 36W ratings. All units are complete and fully wired ready for installation and have been exhaustively tested in a wide range of lighting environments.

Diffusers are available as optional extras for the 18W and 36W models and the 13W model is supplied complete with a diffuser. Tubes are supplied with all models.

As well as industrial, commercial, general and emergency lighting, the lamps are ideal for domestic, caravan, camping, boating and solar applications.

Selectronic Components Pty Ltd: 25 Holloway Dr, Bayswater, Vic 3153. Phone (03) 762 4822.

INTERESTED IN ELECTRONICS? THEN WHY NOT TURN YOUR HOBBY INTO A CAREER?



Alan Mulraney, Stott's Graduate, in his workshop.


In this fast-changing electronic world people with interest and **training** are going to be in demand. Turn your interest into a lucrative career in any one of the following fields:

**Computers • Industrial Controls • Medicine
Radio Communications • Domestic Radio & Television**


Electronics plays an important role in these and many other fields. With a Stott's Home Study Course, training is easy, and will prepare you for a career in the manufacture, installation, commissioning, sales or servicing of electronic equipment.

You'll have experienced, professional instructors who will guide you through an integrated theory/practical program. They'll give you individual attention and advice, and prompt replies to all test assignments and queries. And best of all, you'll study at your own pace, in your own home.

Send the coupon today. It may be the smartest move of your life.



Stott's
CORRESPONDENCE COLLEGE



The name to trust in correspondence education.

Please send me free, and without obligation, full details of the following courses:

_____ (PLEASE PRINT)

MR. MRS. MISS _____ AGE _____

ADDRESS _____

_____ POSTCODE _____

Stott's undertake that no sales counsellor will visit you.

The Stott's range of courses in Electronics is:

- Intro to Electronics
- Digital Electronics for Technicians/Servicemen
- Microprocessors
- AM Radio Receivers
- Radio/TV Servicing
- Colour Television

Melbourne, 140 Flinders Street, 3000. Tel: 63 6212

Sydney, 383 George Street, 2000. Tel: 29 2445

Brisbane, Suite 3, 65 Mary Street, 4000. Tel: 221 3972

Adelaide, 226 Pulteney Street, 5000. Tel: 223 3700

W. Perth, 25 Richardson Street, 6005. Tel: 322 5481

Hobart, 150 Collins Street, 7000. Tel: 34 2399

New Zealand, Box No. 30 990, Lower Hutt. Tel: 676 592

ALA/ST5303/EA185

High efficiency switchmode power supplies

A new family of triple- and quadruple- output 50 and 65W switchmode power supplies is now available from Semiconductor Circuits, Inc. Fixed voltage output combinations include triples of $+5V/\pm 12V$, $+5V/\pm 15V$, and quads of $+5V/\pm 12V/-5V$ and $+5V/\pm 15V/-5V$ with model-defined output current levels.

The CF Series is designed to furnish cost-effective, reliable power for microprocessor, associated memory and interface chips, disk drives, and video display terminals. Ten models achieve verified minimum Mean Time Between Failures (MTBF) of 100,000 hours. Operating efficiency of 75% (type) over the entire input range enhances reliability by maintaining cooler operation despite input voltage variations.

All models can be configured to operate from either 90 to 130VAC or 180 to 230VAC inputs at 47 to 63Hz. Input protection includes surge limiting of inrush current and on-card fusing of the AC input. All outputs are free of chip-damaging overshoots for specified operating conditions. The outputs are overvoltage clamped and short-circuit protected to output common. Total output power is limited to 150% of full rated output, and output hold up time is 16 minutes.


Further information from The George Brown Electronics Group, 174 Parramatta Road, Camperdown, NSW, 2050. Phone (02) 519 585.

Minicomputer power supply

Scientific Electronics advise the availability of a new switchmode power supply specifically designed for a wide range of minicomputers and peripherals. Designated the SM350AE4, it is the latest in a broad range of switchmode models for the computer industry.

The SM350AE4 has five output rails: $+5.2V$ at 25A; $+12V$ at 6A; $+2V$ at 6A; $-5V$ at 2A; and $-12V$ at 2A. Input is 180-280V AC 45-65Hz and 90-140V AC 45-65Hz. It incorporates overvoltage protection on the 5V and 12V rails. Other features are reset and power fault signals, remote on-off facility, remote input voltage selection, and overvoltage protection on the 5V and 12V rails.

Designed and manufactured in

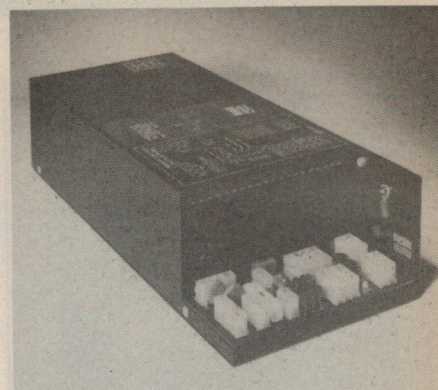

Australia by Scientific Electronics, the SM350AE4 is fully supported by a five-year guarantee and complete local technical back up.

Further information from Scientific Electronics, PO Box 127, Bayswater, Victoria, 3153. Phone (03) 762 5777.

Function generator from Elmeasco

Elmeasco Instruments advise that Exact Electronics has just announced the Model 627 13MHz Function Generator. The unit offers sine, square and triangle waveforms, inverted waveforms, variable symmetry waveforms and DC offset. Frequencies from 100 microhertz to 13MHz may be selected using nine overlapping ranges. Within each range the frequency may be varied over a ratio of 1300:1 either remotely, from the front panel or using an external VCF voltage.

Operating modes include: Run (continuous waveform), Gate (continuous only while gated), Trigger (single cycle waveform with each trigger) and Inhibit (no waveform at output except during GPIB trigger commands; ie, external and manual triggers are inhibited).

All numerical parameter values are selected and displayed on a $3\frac{1}{2}$ -digit LED display. These parameters are: frequency, amplitude, offset, symmetry and calibration sequence number. A decimal point and range LEDs determine the multiplier. Amplitude range is 10mV p-p to 10V p-p into 50 Ω , offset range is to $\pm 5V$ peak into 50 Ω , and symmetry range is 5%:95% to 95%:5% with 1% resolution. Additional front panel LEDs annunciate the non-numerical parameters which are selected.

Operational parameters current when the unit is powered down are stored in non-volatile memory and recalled when the generator is powered up.

Further information from Elmeasco Instruments Pty Ltd, PO Box 30, Concord, NSW 2137. Phone (02) 736 2888.


Solid aluminium capacitors

Philips Electronic Components has released a new range of long-life solid aluminium capacitors.

These single-ended capacitors are potted in a square epoxy resin case with tightly controlled dimensions. This means that the capacitors sit flush on a PCB surface, enabling them to withstand severe shock and vibration. They are intended to replace tantalum capacitors in applications where high reliability is required.

The 124-series is for filtering, smoothing, coupling and decoupling in general and industrial applications — especially in automotive and mobile equipment. Capacitance range is 0.1 to 68 μF , with a tolerance on nominal capacitance of $\pm 20\%$ (or $\pm 10\%$ on request). Rated voltage range is 6.3 to 40V. The capacitors have a basic specification to IEC384-4 (long-life grade), with a category temperature range of -55 to $+85^{\circ}C$, and climatic category of 55/085/56 (to IEC68).

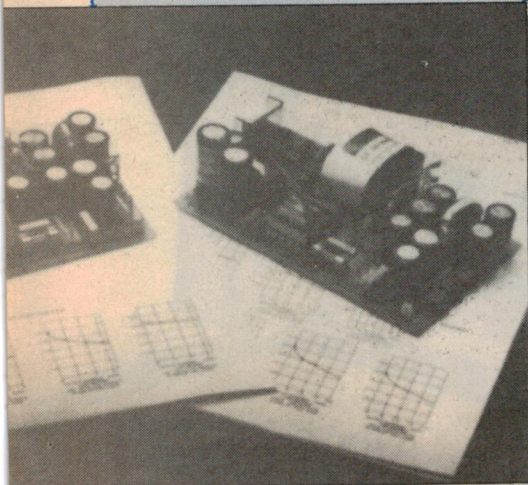Further information from Philips Electronic Components and Materials, PO Box 50, Lane Cove, NSW, 2066. Phone: (02) 427 0888.





Wheelchair batteries

The most commonly heard complaint about electric wheelchairs concerns the restriction of mobility caused by either poor battery performance and/or the problems associated with the handling, maintenance and charging of that battery. Recent developments in lead acid battery technology have largely overcome these difficulties.

One of the companies at the forefront of these developments over the last decade is Gates Energy Products, an American manufacturer whose products are distributed in Australia by Warburton Franki.

Central to the new technology is the recombining electrolyte principle — developed entirely by Gates — which is a process where the majority of the active gassing is kept within the battery. User advantages that result from this process are: no maintenance, no corrosive gassing, no terminal corrosion and air transportation with no restriction.

The two additional areas in which Gates have significantly improved lead acid battery design are in the use of pure lead grids and cylindrical plate construction.

With the greater need to provide disabled persons expanded mobility, especially in electric wheelchair applications, Gates batteries provide far greater range and power. Combined with this advantage is the airline industry acceptance of these batteries for unrestricted carriage with commercial airlines.


Warburton Franki: 7 Birnie Ave, Lidcombe, NSW 2141.

New releases from Technico

Technico have just released three new mains filters from Belling Lee. Available in 1, 2, or 4 amp versions, the L2144 is a switched filter incorporating a fuse. It is suitable for use with business machines or microcomputers. The Y2127 is a high-performance filter intended for use in data processing and has a current rating of 1mA. Where low earth leakage is important, the Y23243 filter with a current rating of 6A would be suitable.

Also new to Technico are Bussmann fuses and fuse holders and EG & G Wakefield heatsinks.

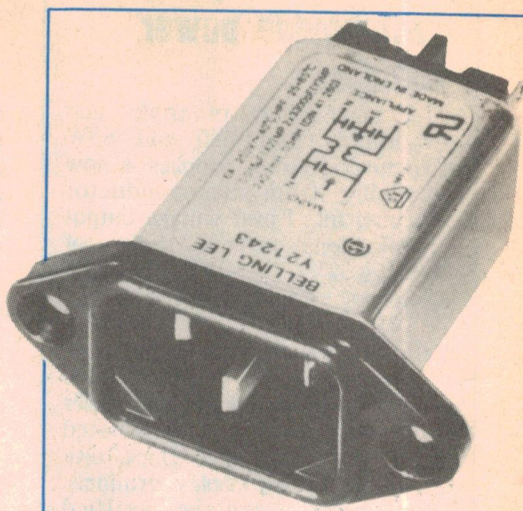Technico: 67 Mars Rd, Lane Cove, NSW 2066. Phone (02) 427 3444



Desoldering unit from Cooper Tools

A particularly versatile desoldering unit manufactured by Cooper Tools at Albury, Australia, has been released by Weller. The DS600 is a temperature controlled desoldering device which is completely self-contained, requiring only a 240V AC power source for operation.

Designed for the service industry, the DS600 has a number of features, including a built-in air supply, a unique pushbutton vacuum control built into the desoldering tool handle, and a

temperature controlled desoldering head to 370°C.

The DS600 is housed in a lightweight all metal case, fitted with a carry handle. A convenient power cord storage area is included with a quick connect/disconnect locking plug on the iron lead.

Further information from The Cooper Tool Group Limited, PO Box 366, Albury, NSW 2640. Telephone (060) 21 5511 or telex AA56995.





Versatile Eprom programmer

A powerful and versatile intelligent EPROM Programmer has been launched and is available from Elmeasco Instruments.

Called the XP640, the unit has been designed to provide advanced programming and editing facilities for all EPROMs and most EEPROMs in common use, but without the addition of personality cards or modules which are so often required with other programmers currently on the market.

The XP640 boasts a whole host of facilities.

Its multi-page video output and 16-character display enables editing and programming data to be presented as comprehensive visual displays. Memory is a massive 64K x 8 RAM and both 8 and 16-bit programming can be accommodated. The RS232C interface supports 16 formats with transmission rates of 19.2K band.

Amongst other facilities the comprehensive RAM editor features ASCII display, RAM editor, page select, define/shift/copy/fill block, split, shuffle, insert, delete, search and replace.

Elmeasco: 15 McDonald St, Mortlake, NSW 2137. Phone (02) 736 2888.

New arc welder from Arlec

Arlec Pty Ltd has introduced a new, improved version of the Weldmate 140 arc welder: The Weldmate model 240. The Weldmate model 240 portable arc welder is designed to operate from any standard domestic 240V power supply through a 15A outlet.

The Weldmate is designed to enable an inexperienced operator to achieve professional results after relatively little practice. It will weld steel up to 8mm thick.

Among the many features is a graduated scale to indicate the most suitable current for a particular size of welding electrode. The current is simply



adjusted by means of a handwheel on the front of the unit.

Supplied complete with everything needed to immediately tackle construction and maintenance jobs in the home and workshop, the Weldmate kit contains a face mask, electrode holder, earth clamp, cables, wire brush, chipping hammer, a selection of electrodes, operating instructions and a 32-page illustrated "Guide to Welding" manual.

It may also be used on thin sheet metal for brazing and spot welding in conjunction with the carbon arc torch, specifically designed for use with the Weldmate.

The BK130 carbon arc torch produces an "electric flame" which is ideal for brazing thin, worn or rusty steel and non-ferrous metals and functions as a practical alternative to an oxy-acetylene torch for those applications where arc welding is unsuitable.

It is available from Arlec as a complete carbon arc brazing kit and includes a carbon arc torch, carbon rods, wrap-round headshield, flux impregnated abrading rods and an attachment enabling the torch to be converted for spot welding.

Further information form Arlec Pty Ltd, PO Box 170, Box Hill, Victoria, 3128. Phone (03) 895 0222.

RS-232C fibre optic link

Data Cable Pty Ltd has introduced a new fibre optic RS-232C data link which has many advantages over traditional coaxial cable including the elimination of electromagnetic and radio frequency interference.


Called FO-232, it is a full duplex optical modem designed for the transmission of asynchronous data via fibre optic cable.


The FO-232 can transmit data up to two kilometres at a full bit rate of 19.2Kb per second or greater, and has absolute electrical isolation.

Data Cable's new FO-232 is used for linking peripherals, remote terminals and process multiplexers to computers, and for inter-building, interconnections and local area networks.

The FO-232 from Data Cable is completely plug to plug compatible with existing RS-232C 25 pin connectors meeting EIA RS-232C and CCITT V.24.

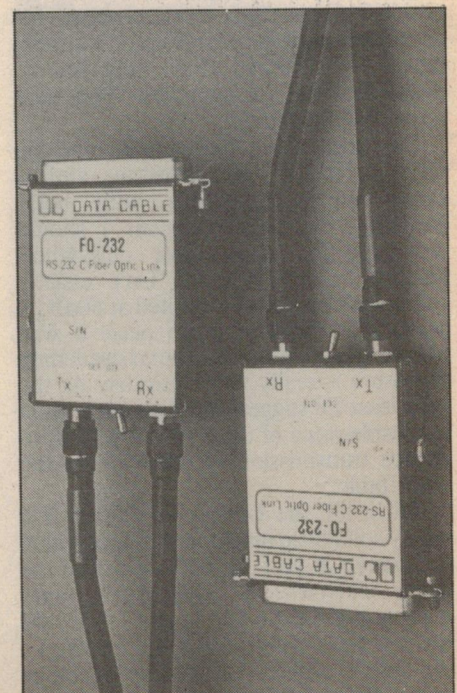Data Cable: Cnr Croydon & Lincoln Rds, Croydon, Vic 3136. Phone (03) 725 0933.



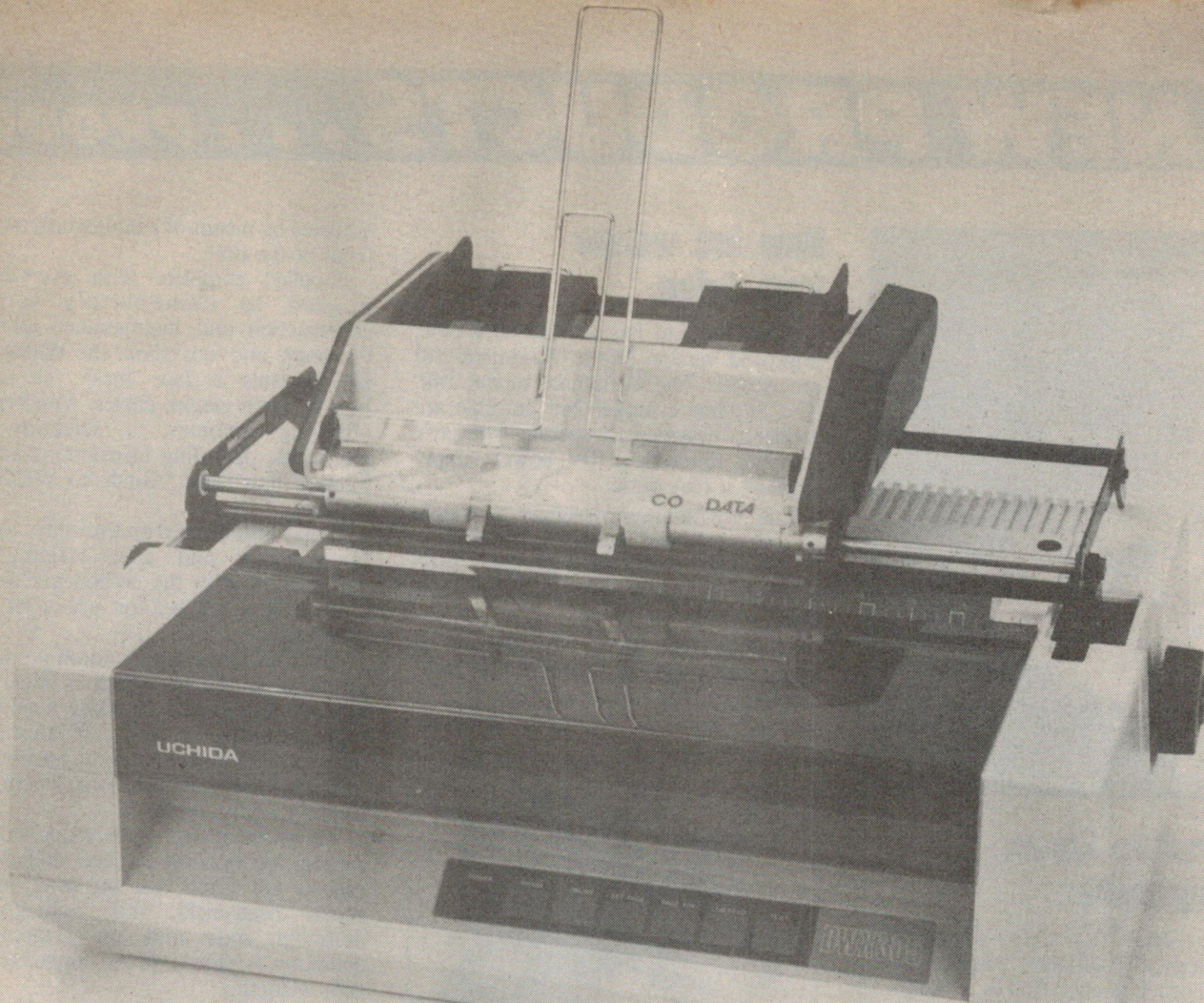

This view shows the Uchida DWX305 with the optional cut-sheet feeder attachment.

By the way, the basic DWX-305 is friction feed and really handles only single sheets of paper. There is an optional forms tractor attachment, for continuous stationery, and also a cut-sheet feeder — although these may not be available from all suppliers. You may have to shop around.

I've been using the sample machine with an IBM PC and Wordstar, and it seems quite compatible with both. Probably the only comment I should make is that like most daisywheel printers, the DWX-305 isn't exactly quiet; the noise level is quoted at 60dB (A scale). So unless you can place it well away from you, a sound-deadening enclosure is really very desirable. At the very least I'd suggest that you place it on a suitable piece of thick industrial felt, to reduce transmission of vibration to the work table.

All in all, the Uchida DWX-305 is a pretty solid little machine and good value for money. If you can't afford one of the faster daisywheels, and don't mind waiting that little bit longer, it would make a good choice for home or office. As noted earlier, the review machine came from Electrical Equipment Ltd,

Measurement and Control Division, at 192 Princes Highway, Arncliffe NSW 2205. Telephone (02) 597 1155. The quoted price is \$450 plus 20% sales tax.

A cut-sheet feeder attachment is available for an additional \$299 plus tax, and as shown in the picture a feeder was actually supplied with the printer sent for review. It clips quite easily into the top of the printer, having a gearwheel which meshes with an existing gear on the typing platen shaft.

The feeder is a fairly simple affair, and has fixed mechanical gearing. This means that it automatically loads in a new sheet when the printer platen has turned to advance the paper by 12 inches (305mm) — regardless of the actual length of the paper. Note that this doesn't mean that you can only use paper sheets cut to 305mm long, just that this is the maximum length of paper you can use with the feeder. So standard A4 letterhead paper is fine, or smaller sheets, but F4 "foolscap" is too long.

Unlike the DWX305, the feeder is actually made in Germany, and has an operator's manual written in rather clipped "German English". Most of it is fairly easy to follow, although I found

the part on setting the "Top of Form" rather glib and superficial. This is unfortunate since this setting is actually rather tricky — you have to synchronise the feeder's mechanical top of form setting (ie, the point when it has just stopped feeding in a new sheet) with the top of form setting in the printer's electronics.

It's not too difficult to do this once you get the hang of it, but the manual isn't too helpful. You also have to make sure that the printer's rear DIP switch is set for 12 inches of paper feed in response to a form-feed control character, and then ensure that your computer software does in fact send form-feed characters. I found this out the hard way — my version of Wordstar was set to send repeated line feeds instead of a form feed, and I couldn't get it to work properly with the feeder until I changed it to send form feeds!

Despite these minor hassles, the feeder does seem to perform quite well. It should be quite valuable when the printer is to be used in an office environment, although the limitation on maximum paper length seems unfortunate in view of its price. (J. R.)

Uchida DWX305 daisywheel printer

Uchida's DWX305 is one of the "new breed" of daisywheel printers, priced at below half the cost of earlier models. Jim Rowe has been putting it through its paces, and in this review he explains the features and performance you can expect — together with those you can't.

Japanese manufacturers have tended to dominate the "small computer" printer market for the last four or five years, with a string of models offering more features and better prices than those from other countries. However this dominance has been more in the dot-matrix area than with letter-quality printers. Although their daisywheel printers have generally been cheaper than the competition, their price tags have still tended to put them out of reach of most personal computer buyers.

Until recently, that is. In the last year or so a "new breed" of low-cost daisywheel printers has emerged from Japan, with retail prices well below the thousand dollar mark. The Uchida DWX-305 is one of the new breed, being currently sold by a number of local firms at prices varying quite considerably but averaging around \$550. The machine for review actually came from the importers and distributors, Electrical Equipment Ltd.

The obvious question to ask about this kind of low-cost printer is what you miss out on, compared with the more expensive models. It is print quality, speed, features, reliability — or what?

Having used the sample DWX-305 for a while now, it seems to me that the main thing it sacrifices is speed. While advertised by some firms as capable of 20 characters per second, its actual printing speed in practice seems to be closer to 15 cps on normal text. This rises to about 18 cps when repeating characters. The 'carriage return' and form feed functions are also relatively slow, although in the case of carriage returns this is partly compensated by the fact that it can print bi-directionally.

Of course the average printing speed is still about 40% faster than all but the quickest human typists, so it's not exactly crawling along. In fact it's probably quite OK for most normal correspondence printing — particularly if your computer or word processor has a print spooler of some kind. But if you're used to one of the faster (and more expensive) daisywheels, you'll certainly notice the drop in speed.

When it comes to print quality, reliability and features, the Uchida seems to compare quite closely with its more expensive brothers. Print quality with a standard multi-strike carbon ribbon is very crisp and even, although just noticeably lighter than the output from a golf-ball typewriter. It seems to be quite sturdily made, and the sample has done a lot of printing so far without missing a beat.

The features it offers include a choice of either bi-directional logic seek printing or proportional printing (standard 1/120 inch increments), choice of three pitches (1/10, 1/12 or 1/15 inch), fractional line feed (1/48 inch increments) for superior and inferior figures, and a choice of four levels of print impression. The maximum paper width is 330mm (13 inches).

The DWX-305 responds to standard 7-bit ASCII code, and accepts the

standard control codes. This includes the "escape sequence" extended control codes now used on most ASCII printers for setting printing mode and fractional control of both print head and paper feed.

There are six membrane-type pushbuttons and four LED indicators on the printer's front panel. The pushbuttons are for online/offline switching, error reset, setting top of the page, form feed, line feed and test print. The last four only operate when the printer is set to offline status. The four LEDs indicate power, online, error status and test mode.

There are two 8-way DIP switches on the rear of the printer, which are scanned by the inbuilt microprocessor when power is first applied and when a specific escape code sequence is received (ESC-SUB-I). Only one bank of switches is functional on the Centronics-interface model, the switches being used to set it for various functional options: serial or line-print mode, auto linefeed with carriage return or not, line feed pitch (6 lpi or 3 lpi), page length select (11 or 12 inches), printing pitch (10/12/15 cpi) and hammer impact (three settings).

The DWX-305 measures 550 x 365 x 162mm (lxdxh) and has a mass of 9.5kg. Its power consumption is 20 W when idling and 80-100 W when printing. It is rated to operate at temperatures up to 40°C, and up to 85% relative humidity (non condensing).

The Uchida's 96-character print wheels are compatible with those for the QUME 'Sprint 3' printer, as are the ribbon cartridges (which are of the 'Multistrike IV' type), so both should be fairly easy to obtain.

SPECIFICATIONS — UCHIDA DWX305 PRINTER


Print head	Daisywheel
Print speed	15cps
Print direction	Bidirectional
Interface	Centronics parallel
Max paper width	330mm (13 inches)
Line feed pitch	6 lpi or 3 lpi
Printing pitch	10, 12 or 15 cpi
Price	\$450 plus sales tax

VIC-20

this case the +5V line of the expansion port must be isolated from the expander board supply.

A method of constructing the buffer

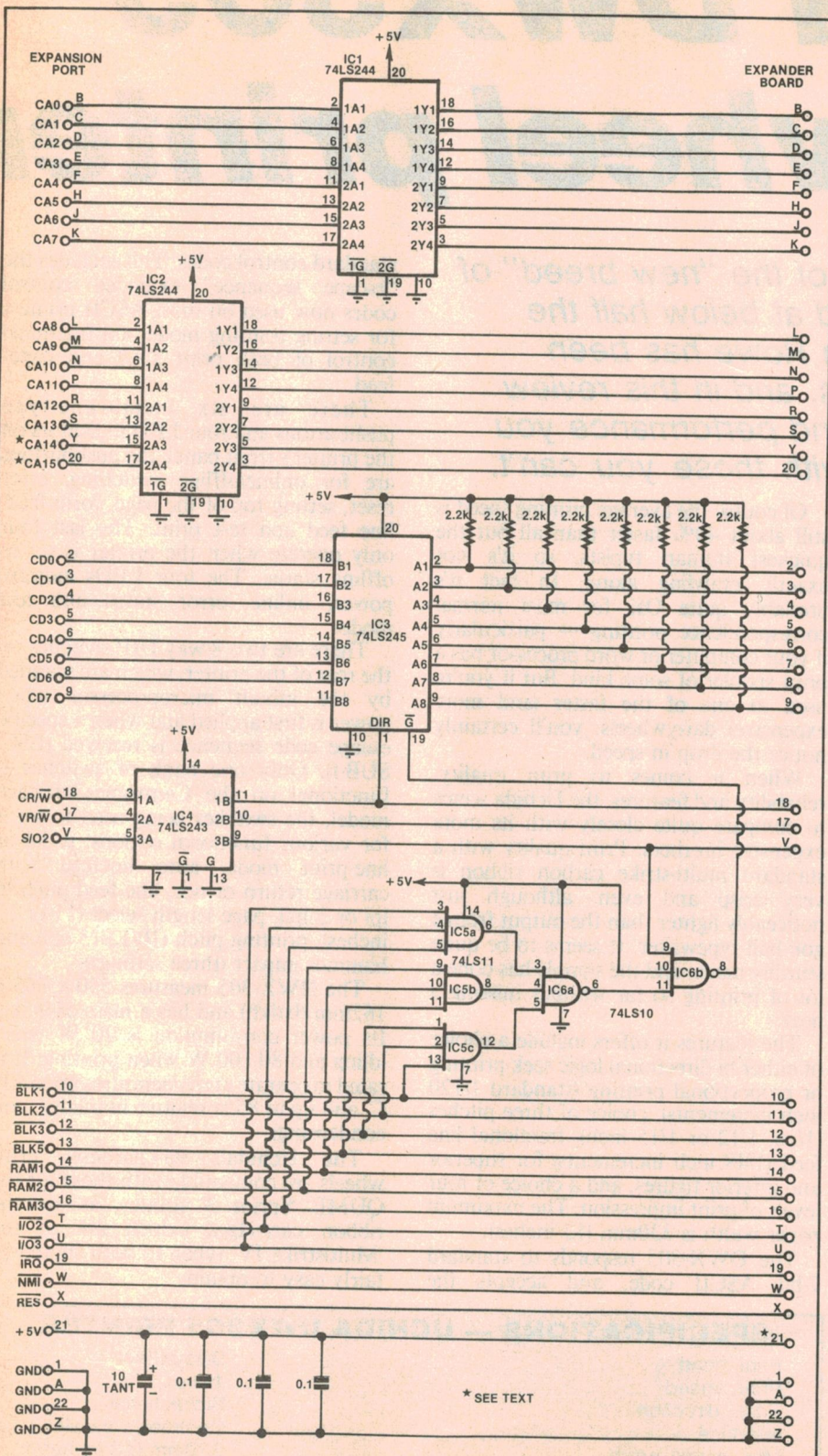
circuit is to use a double sided printed circuit board which is housed in a spare cartridge case. The unit can then be plugged into the VIC-20 expansion socket and connected to the expander board by ribbon cable and edge connector.



This diagram shows the Expansion Port Buffer add-on. It can be built into a spare expansion cartridge case.

BASIC ELECTRONICS

Price \$4.50

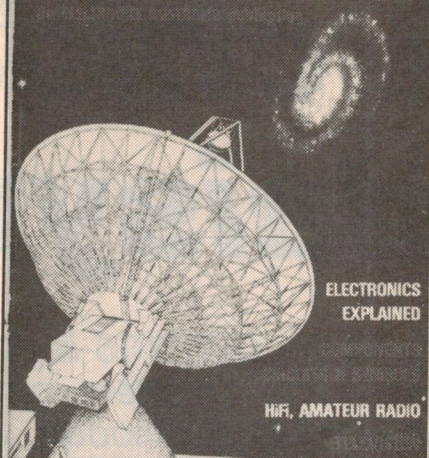


Basic Electronics, is almost certainly the most widely used manual on electronic fundamentals in Australia. It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. Begins with the electron, introduces and explains components and circuit concepts, and progresses through radio, audio techniques, servicing, test instruments, etc.

If you've always wanted to become involved in electronics, but have been scared off by the mysteries involved, let Basic Electronics explain them to you.

CHAPTER HEADINGS:

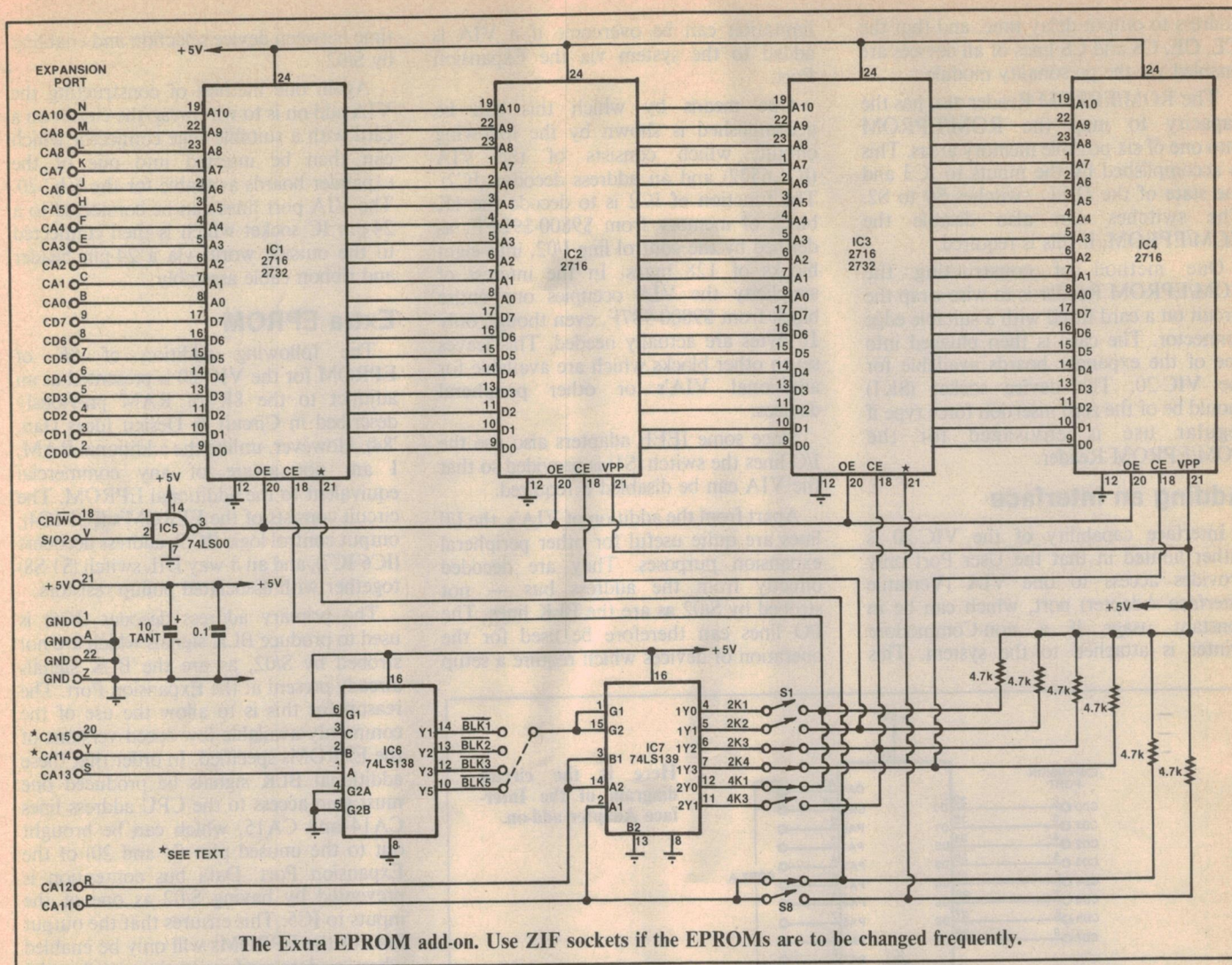1. Background To Electronics
2. Basic Electrical Concepts
3. Batteries and Cells
4. Magnetism, Inductance and AC
5. Capacitance and Capacitors
6. Basic Circuits
7. Semiconductor Devices
8. Reading Circuits
9. Radio Transmission
10. Radio Reception
11. Simple Radio Receivers
12. Building Simple Receivers
13. More Complex Receivers
14. Power Supplies
15. More Basic Concepts
16. Receiver Alignment
17. Simple Projects To Build
18. Test & Measuring Instruments
19. The Electronics Serviceman
20. Amateur Radio Stations
21. Audio Equipment & Techniques
22. Stereo Sound Reproduction
23. Television — Basic Concepts
24. The Television Receiver
- Appendix: Colour Television Basics

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017, PRICE \$4.50 OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017, PRICE \$5.40.



VIC-20

with a circuit diagram of the VIC-20. A circuit diagram can be found in either "VIC Revealed" or the "VIC-20 Programmer's Reference Guide".

The address bus is buffered by IC1 and IC2 while the commonly used control lines CR/W, VR/W and S/O2 are buffered by IC4. The control lines BLK1 to I/O3 are not buffered since they would not be heavily loaded by devices on the expander board. The control lines IRQ, NMI and RES are also not buffered in order that their "wire-OR" capability is maintained.

In contrast to the previously mentioned unidirectional buffers the data bus uses a bidirectional buffer (IC3). This is necessary since the CPU (6502A) is capable of both reading from and writing to devices located on the expander board. The direction of data transfer being controlled by the CR/W line. The CR/W is used instead of VR/W so that the data direction is established independently of the enabling of IC3.

The enabling of IC3 is controlled by IC5 and IC6 to ensure that only valid data is placed on the CPU data bus. The enabling of IC3 must only occur when the address bus is stable and when a device on the

expander board is being addressed. Address bus stability is ensured by strobing with S/O2 while expander board selection is defined by the state of the memory select lines BLK1 to I/O3.

The control lines BLK1 to RAM3 are strobed by S/O2 within the VIC-20. The I/O lines are not, hence the presence of S/O2 as one of the inputs to IC6b. One could replace IC5 and IC6a by a 74LS133 but this device is expensive and difficult to obtain. The pullup resistors ensure that the state of the expander board data bus is always defined.

The address lines CA14 and CA15 have been added so that the entire address bus is available at the expansion port. To add these address lines the VIC-20 must be dismantled and the circuit board removed. Direct connections can then be made underneath the circuit board from the CPU address lines A14 and A15 (pins 24 and 25), to the unused pins (Y and 20) of the expansion port.

The buffer circuit can be powered from the VIC-20 but for improved reliability of the VIC20 power supply, a separate supply should be used for the expander board. In



address to output delay time, and that the CE, OE, CS and CS lines of all devices are enabled via the personality module.

The ROM/EPROM Reader also has the capacity to map the ROM/EPROM into one of six possible memory areas. This is accomplished by the inputs to IC3 and the state of the D.I.L. switches S0 to S2. The switches can also disable the ROM/EPROM, if this is required.

One method of constructing the ROM/EPROM Reader is to wire-wrap the circuit on a card fitted with a suitable edge connector. The card is then plugged into one of the expander boards available for the VIC-20. The device socket (SK1) should be of the zero insertion force type if regular use is envisaged for the ROM/EPROM Reader.

Adding an interface

Interface capability of the VIC-20 is rather limited in that the User Port only provides access to one VIA (Versatile Interface Adapter) port, which can be in constant usage if a non-Commodore printer is attached to the system. This

limitation can be overcome if a VIA is added to the system via the Expansion Port.

One means by which this can be accomplished is shown by the following circuit, which consists of the VIA (IC1, 6522) and an address decoder (IC2). The function of IC2 is to decode the 1K block of memory from \$9800-\$9BFF, as defined by the control line I/O2, into eight blocks of 128 bytes. In the interest of simplicity the VIA occupies one entire block from \$9800-\$987F, even though only 16 bytes are actually needed. This leaves seven other blocks which are available for additional VIA's or other peripheral devices.

Since some IEEE adapters also use the I/O lines the switch (S1) is provided so that the VIA can be disabled if required.

Apart from the addition of VIA's, the I/O lines are quite useful for other peripheral expansion purposes. They are decoded directly from the address bus — not strobed by S/O2 as are the BLK lines. The I/O lines can therefore be used for the operation of devices which require a setup

time between device selection and enabling by S/O2.

Again one method of constructing the VIA add-on is to wire wrap the circuit on a card with a suitable edge connector which can then be inserted into one of the expander boards available for the VIC-20. The VIA port lines can be connected to a 24-pin IC socket which is then connected to the outside world via a 24-pin header and ribbon cable assembly.

Extra EPROM

The following addition of 8K of EPROM for the VIC-20 is presented as an adjunct to the 8K of RAM previously described in Circuit & Design Ideas (Jan. '84). However, unlike the additional RAM, I am not aware of any commercial equivalent to the additional EPROM. The circuit consists of the EPROM's (IC1-IC4), output control logic (IC5), address decoders (IC6-IC7), and an 8-way DIL switch (S1-S8) together with associated pullup resistors.

The primary address decoder (IC6) is used to produce BLK signals which are not strobed by S/O2, as are the BLK signals already present at the Expansion Port. The reason for this is to allow the use of the commonly available low speed versions of the EPROMs specified. In order that these additional BLK signals be produced one must gain access to the CPU address lines CA14 and CA15, which can be brought out to the unused pins (Y and 20) of the Expansion Port. Data bus contention is prevented by having S/O2 as one of the inputs to IC5. This ensures that the output lines of the EPROMs will only be enabled when a data-read operation, under the control of S/O2, is in progress.


The secondary address decoder (IC7) is enabled by the relevant BLK signal (link selectable), and uses the address lines CA11 and CA12 to produce two 4K memory block selects as well as four 2K memory block selects. The 4K and 2K block selects allow for a mixture of 4K (2732) and 2K (2716) EPROMs. It should be noted however that IC2 and IC4 can only be 2716s, whereas IC1 and IC3 can be of either type.

The device type which is to be used for IC1 and IC3 is established by the state of the DIL switch (S1-S8). As shown IC1 is a 2732 while IC4 is a 2716. The switch states must be such that memory overlap does not occur, which is why IC2 is not selected in the given example.

Expansion port buffer

There are numerous expander boards available for the VIC-20. However, some of these boards are not buffered. Should one desire to add buffering then the following approach presents one method whereby this can be accomplished. Operation of the circuit is the best understood when studied in conjunction

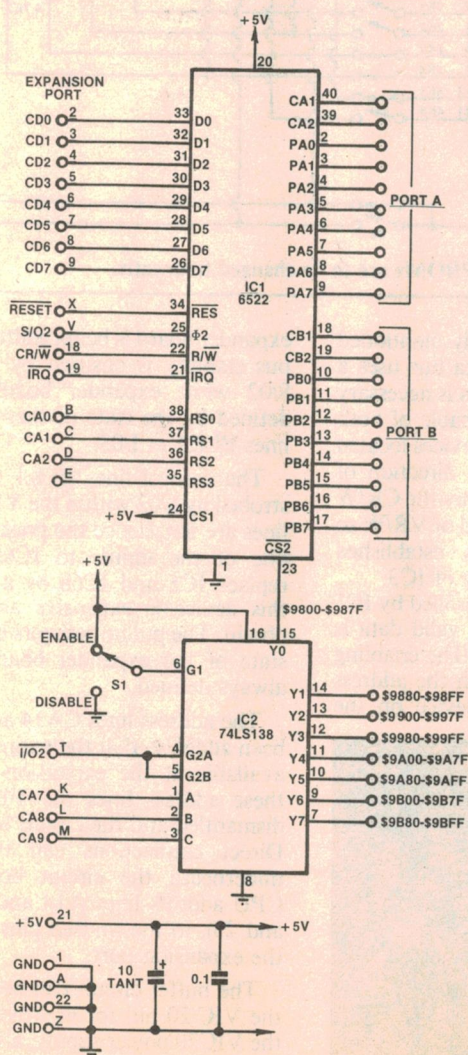Here is the circuit diagram of the Interface Adapter add-on.



ADD-ONS for the VIC-20

by L. Murakami

Attention VIC-20 owners! Want to build a ROM/EPROM reader? How about an extra PIA? These circuit ideas and two others are described in this VIC-20 'special'.

First let's take a look at the ROM/EPROM reader. This was designed to meet the following objectives: 1. Read devices having different pinouts; 2. Read devices having different functional behaviour; 3. Read the commonly available low speed versions of many devices; 4. Map the devices anywhere in the available memory space (necessary with devices having the auto-start facility).


In order that the ROM/EPROM Reader can accommodate devices having different pinout configurations, "personality" modules are employed. The personality module consists of a 16-pin header which has been hard-wired for the ROM/EPROM that is to be read. This module is inserted into the personality module socket (SK2), thereby configuring the ROM/EPROM socket (SK1) for that particular device. The module shown has been strapped for an Intel type 2716 EPROM for which the CE and OE lines are permanently enabled. The reason for this course of action is twofold.

Successful reading

Firstly the CE line is enabled so as to ensure the successful reading of the slower versions of ROM/EPROM devices which incorporate a power down feature. This approach overcomes the maximum CE to output delay time, which would be a problem if the BLK lines were used to enable these devices directly. The BLK lines are unsuitable since they are active only when S/O2 is active: its duration is too short for the above timing parameter. With the device permanently enabled, the power down feature cannot be utilised, however this is not of major consequence as only one device is affected.

Secondly the OE line is enabled since IC1 is used for output data control. IC1 is needed for those devices which have a common chip enable/output control line eg, 2532. IC1 serves to isolate the VIC-20 data bus from the output lines of the ROM/EPROM which are now continually active due to the permanent device enabling, as mentioned above. The enabling of IC1 is controlled by IC2 which ensures that IC1 will be enabled only when the ROM/EPROM is being addressed and a data-read operation is in progress.

The conclusions to be derived from the above discussion are that ROM/EPROM read timing is now substantially that of

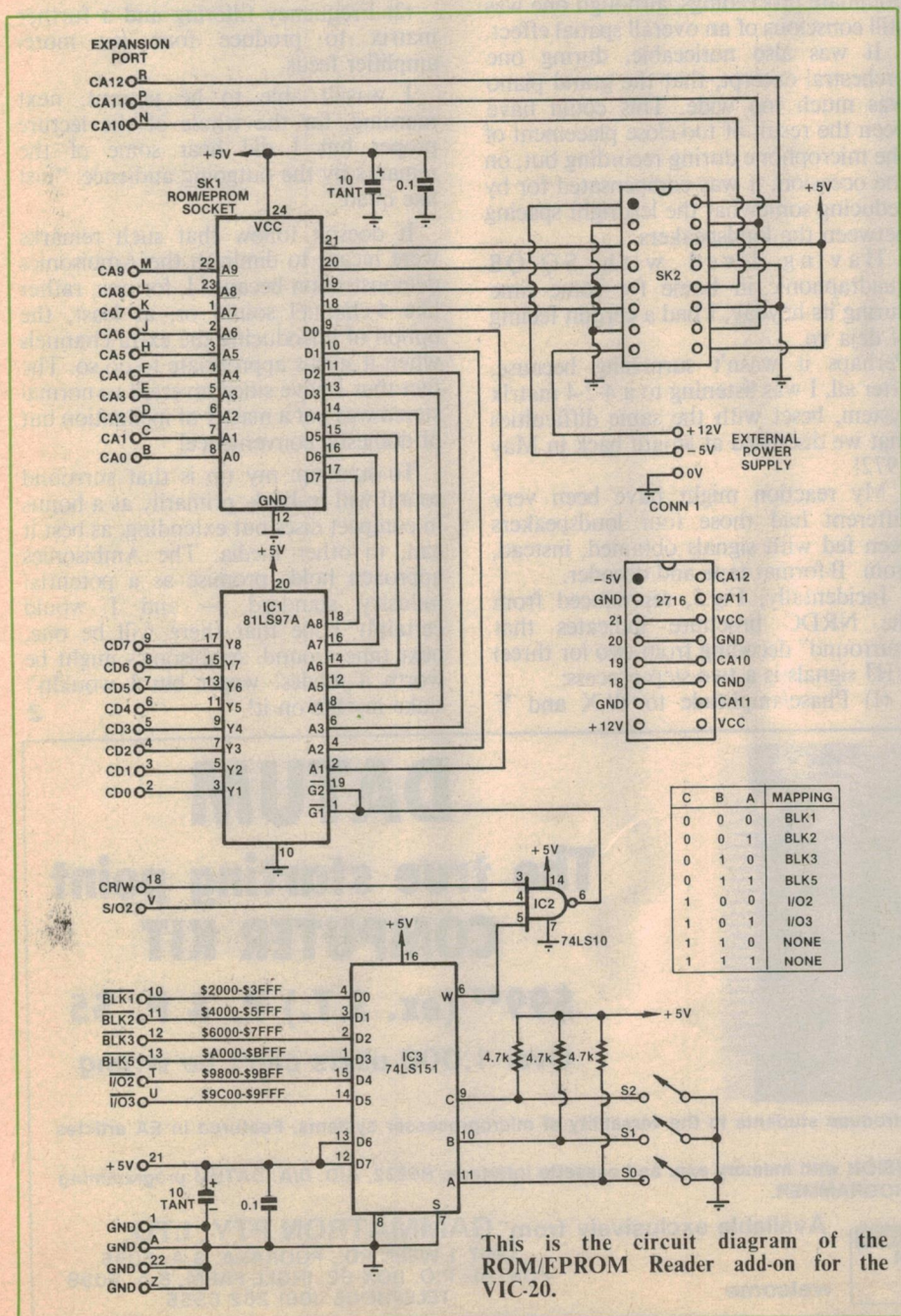

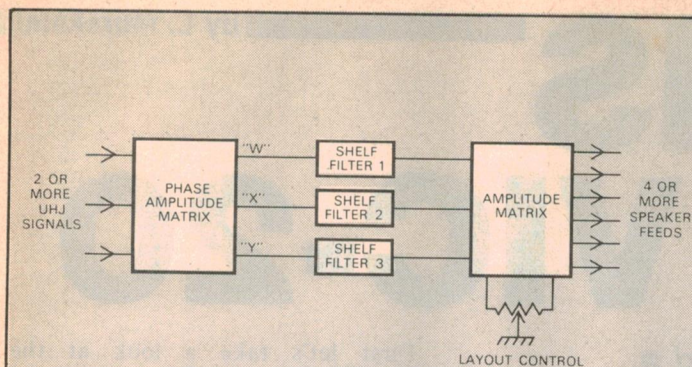


Fig 5: In its least pretentious form, Ambisonics offers four outputs from two input channels. They claim superior results, presumably because their decoding involves phase, amplitude and frequency.

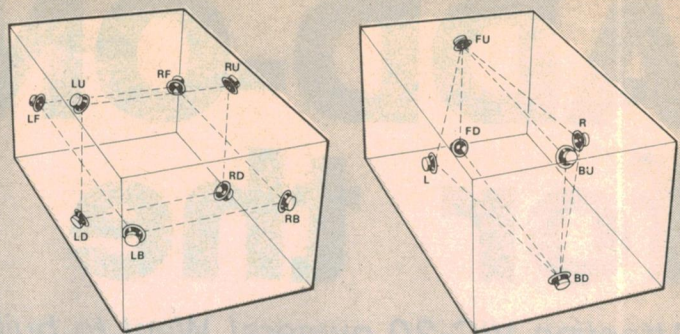


Fig 6: If the Ambisonics group have their way, you may end up with four signal channels from, say, compact disc, decoded to feed six or eight loudspeakers in a "periphonic" array!

and acoustics".

For the demonstration, the lecturer used recordings which had been made with a Calrec Mark IV microphone, encoded into 2-channel UHJ and recorded on Beta cassette in a Sony F1 portable digital recorder. The recordings include a carol service in the Guilford Cathedral plus orchestral excerpts from Elgar's "Gerontius" and the Moussorgsky/Ravel "pictures at an Exhibition".

The demonstration equipment, set up in the ballroom of the Melbourne Hilton, included a 2-channel to 4-channel decoder, four power amplifiers and four Quad ESL-63 loudspeaker systems — spaced out from the corners of the seating area, as in Fig.4.

By chance, I happened to be around during the previous evening, when the equipment was being set up by Robin Maconie and his assistant, Erdo Groot, a graduate of the Tonmeister course.

Moving around the room, it was immediately apparent that one needed to be somewhere near the centre of the listening area to experience good all-round balance. Moving towards any one

of the loudspeakers caused its output to dominate proceedings, although one was still conscious of an overall spatial effect.

It was also noticeable, during one orchestral excerpt, that the grand piano was much too wide. This could have been the result of too-close placement of the microphone during recording but, on the occasion, it was compensated for by reducing somewhat the left/right spacing between the loudspeakers.

Having lived with SQ/QS quadrasonic in home for some time during its heyday, I had a certain feeling of déjà vu.

Perhaps it wasn't surprising because, after all, I was listening to a 4-2-4 matrix system, beset with the same difficulties that we discussed at length back in May 1972!

My reaction might have been very different had those four loudspeakers been fed with signals obtained, instead, from B-format tape and decoder.

Incidentally, Fig.5, reproduced from the NRDC brochure indicates that "surround" decoding from two (or three) UHJ signals is a two-step process:

(1) Phase/amplitude to W,X and Y


resultants, followed by

(2) Frequency filtering and a further matrix to produce four (or more) amplifier feeds.

I wasn't able to be present, next morning, for the whole of the lecture proper but I did hear some of the remarks by the outgoing audience: "just like quad!"

It doesn't follow that such remarks were meant to diminish the Ambisonics demonstration because I, for one, rather like 4-channel sound or, at least, the option of introducing the extra channels when it seems appropriate to do so. The fact that I have since reverted to normal stereo was not a matter of inclination but of domestic convenience!

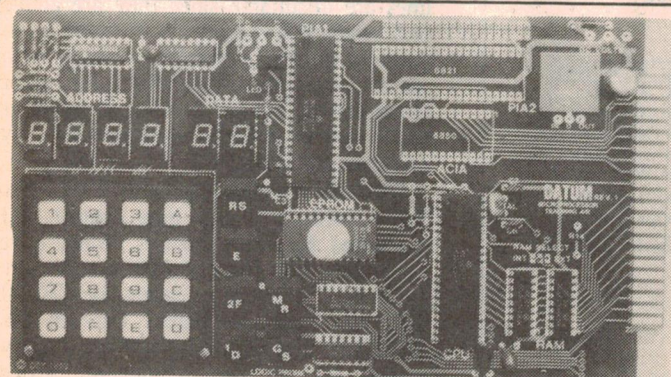To sum up: my tip is that surround sound will be back, primarily as a bonus in compact discs but extending, as best it can, to other media. The Ambisonics approach holds promise as a potential industry standard — and I would certainly hope that there will be one, next time around. Ambisonics might be worth a modest wager but I wouldn't stake my life on it!



Developed by S.A. Institute of Technology to introduce students to the versatility of microprocessor systems. Featured in EA articles November, December, '82 and January '83.

The DATUM range now includes: DATUM EXTENSION with memory exp. and cassette interface, RS232, A/D, D/A. DATUM programming manual, DATUM applications manual. EPROM PROGRAMMER.

Send SAE for further information.



Available exclusively from **GAMMATRON PTY. LTD.**

UNIT 1 WEEN RD., POORAKA, S.A. 5095
POSTAL: P.O. BOX 62, INGLE FARM, S.A. 5098
TELEPHONE: (08) 262 6555

welcome

Fig 3: The Ambisonics system as envisaged by NRDC. Signals from a soundfield mic., pan-pot system, &c, are mastered as W,X,Y and Z components, then decoded into software to meet requirements. Note that the UD-4/CD-4 "discrete" type disc is included in their options.


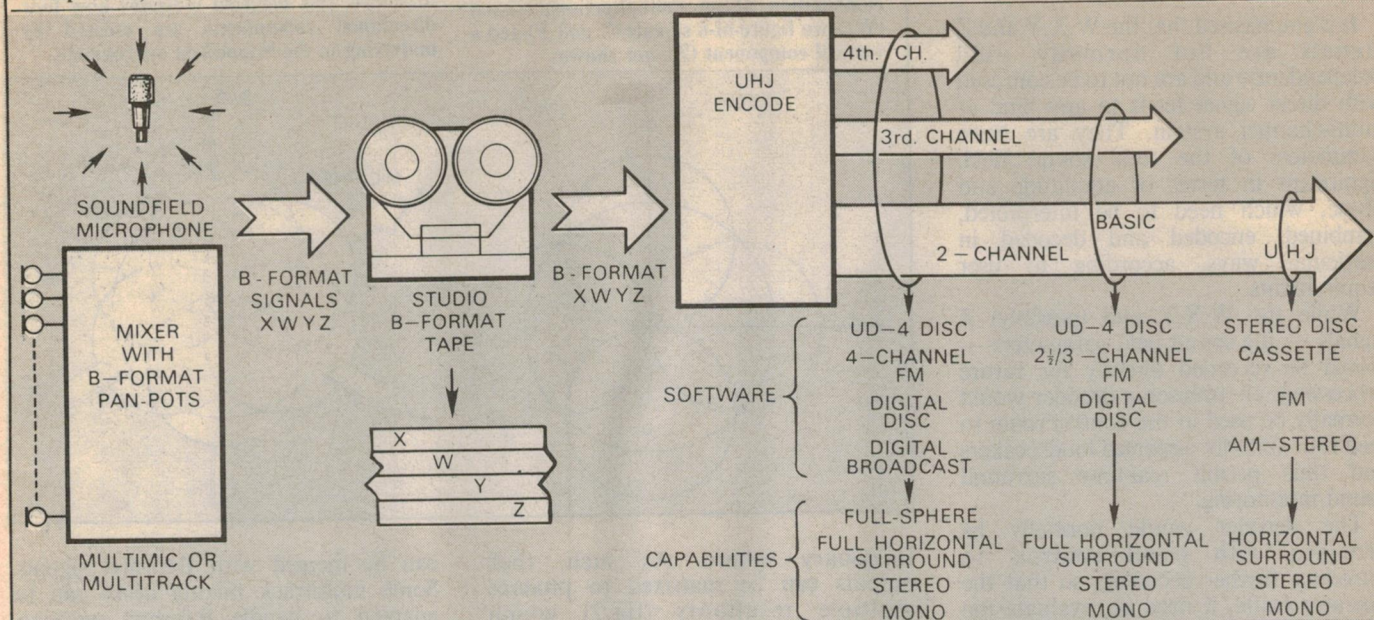


Fig 4: In Melbourne, the system was set up as per this NRDC diagram, using two UHJ inputs from a Sony digital cassette source, with decoding to feed four amplifier channels and four loudspeakers (drawn solid).

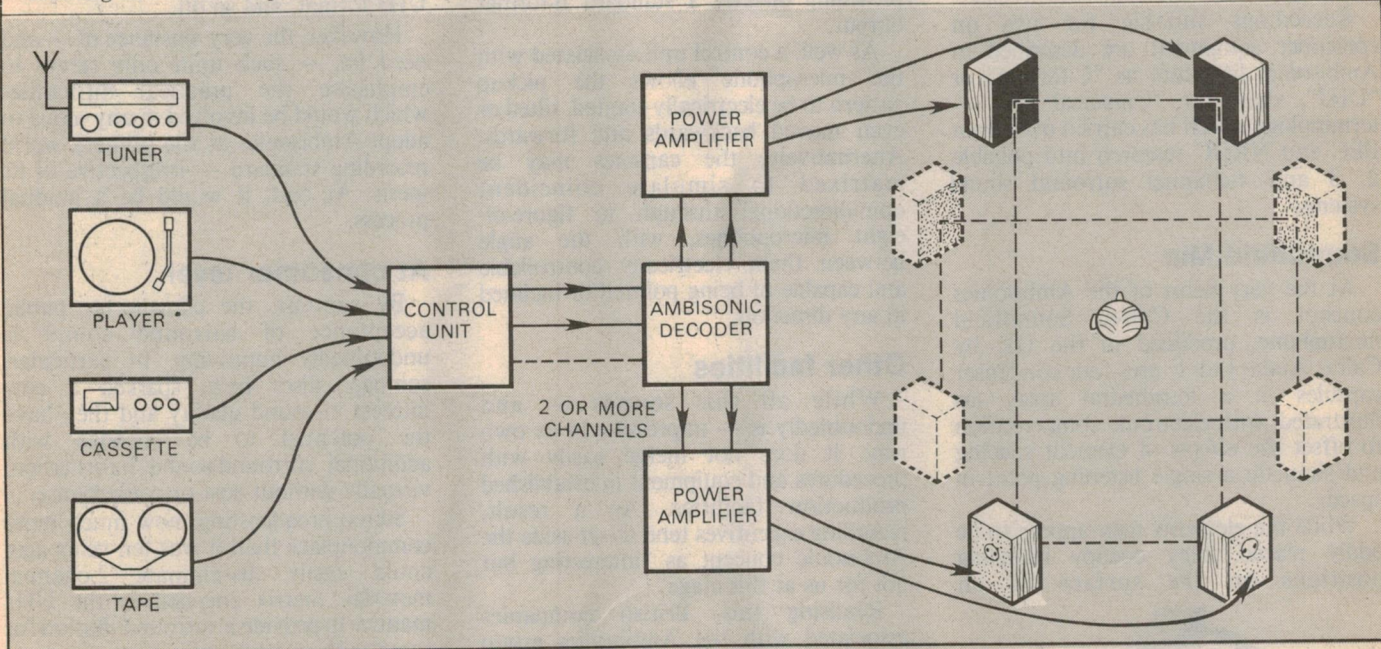

Ambisonics

small labels, have the market to themselves.

That the Ambisonic group has all this in mind is evident from the accompanying diagram (Fig.3) from NRDC, which currently holds the international patent rights for Ambisonics technology.

And therein lies the logic of the Ambisonics system. It offers a master recording standard which can reputedly capture on digital tape the "total sound" parameters of any given performance. In

real time, or at any time, that basic B-format information can be converted by standardised procedures into any form required by the consumer market: from 6-channel periphonic through to humble mono.

Is it the best way of accomplishing that end result, without getting bogged down in patent rights and liabilities? The answer to that, I imagine, will depend very largely on the tractability or otherwise of the NRDC!

Back to Melbourne

At the AES Convention, the Ambisonics demonstration was

presented by Robin Maconie, MA (Hons), composer and lecturer in music and technology at the University of Surrey, UK.

While emphasising the logic and the merit of digitally based Ambisonics technology, both for mastering and consumer UHJ derivatives, he pointed out that his principal involvement was in connection with the "Tonmeister" course at the University of Surrey. Based on a German concept, it is described as "a first degree music course combining traditional studies in music theory and history with a full training in practical sound recording with associated physics

Ambisonics

It is emphasised that the W,X,Y and Z signals are not normally used independently and are not to be confused with direct signal feeds to any kind of multi-channel system. They are basic parameters of the total sound field, significant in terms of amplitude and phase, which need to be interpreted, combined, encoded and decoded in particular ways, according to user requirements.

While the W,X,Y and (possibly) Z signals — the sound field parameters — would be recorded directly for future processing, an ambisonic decoder would normally be used in the control room to feed four suitably dispersed loudspeakers and thus permit real-time surround sound monitoring.

The decoder would normally be provided with panel controls to introduce further decoding, so that the operator could, if need be, evaluate the sound as it would be in consumer 3-channel, 2-channel or even mono formats.

Recordings suitable for use on consumer equipment are described in Ambisonics literature as "C-format" or "UHJ", short for "Universal HJ" — terminology which has carried over from BBC and NRDC research into possible 2, 3 and 4-channel surround sound systems.

Soundfield Mic

At the very heart of the Ambisonics concept is the Calrec Soundfield microphone, produced in the UK by Calrec Audio Ltd. It uses four condenser capsules in a tetrahedral array (as illustrated) with electronic compensation to offset the effects of element spacing and simulate a single listening point in space.

While the elements may appear to be oddly placed, they occupy sampling positions on the surface of an



Fig 1: In the Ambisonics system, the original soundfield is recorded as a combination of an omnidirectional signal (W), two figure-of-8 signals (X and Y) and a vertical component (Z), not shown.


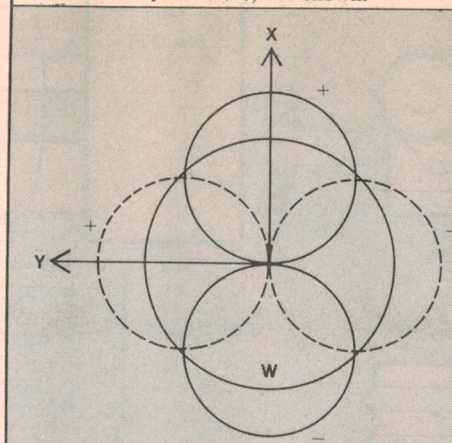


Fig 2: Reproduced from the Calrec brochure, this diagram indicates how four directional components are created by matrixing in the Soundfield microphone.

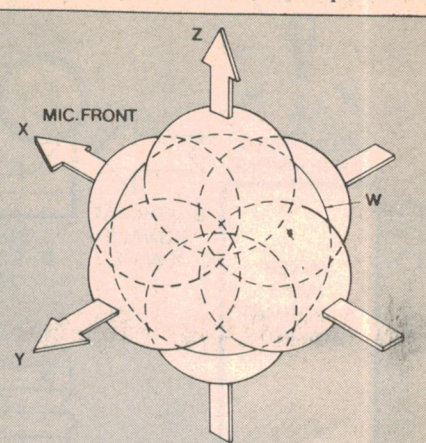

imaginary sphere. As such, their outputs can be matrixed to produce multiple resultants (fig.2) which correspond to the polar responses and signals of Fig.1: W,X,Y and Z, thus providing directly a standard B-format output.

As well, a control unit associated with the microphone allows the pickup pattern to be electrically rotated, tilted or even moved backwards and forwards. Alternatively, the capsules may be matrixed to simulate coincident omnidirectional through to figure-of-eight microphones, with the angle between them electrically controllable and capable of being pointed or inclined in any direction.

Other facilities

While all this sounds — and undoubtedly is — impressive in its own way, it does not merge easily with procedures and equipment in established production facilities. As a result, recording executives tend to set aside the Ambisonic concept as "interesting but not for us at this stage".

Realising this, British companies associated with the Ambisonics group have recently developed and announced equipment which may help bridge the gap. Apart from Ambisonic monitor/decoders, mentioned earlier, they list a pan rotate unit, B-format converters, UHJ encoder/transcoders, &c.

With such units, monitoring facilities in a control room can be expanded to cope with B-format surround sound and its UHJ derivatives. Signals from conventional mono microphones, &c.

The Calrec Mark IV Soundfield microphone, with outer cover removed. Outputs from the four capsules are normally multi-matrixed to produce signals in accordance with Ambisonics B-format requirements.

can be merged with B-format signals. Some multitrack mixing desks can be adapted to handle B-format working. Conventional stereo and quadraphonic signals can be transcoded into simulated UHJ format, and so on.

However, the very existence of — and need for — such units only serves to emphasise the practical difficulties which would be involved in any move to adopt Ambisonics as the primary world recording standard — irrespective of its merit. At best, it would be a gradual process.

At consumer level

By contrast, the climate for public acceptance of surround sound is undoubtedly improving. In particular, compact discs have sparked a new interest in sound quality and they have the potential to be encoded with additional surround-sound information, virtually without cost or compromise.

Stereo broadcasting, now much more commonplace than it was ten years ago, could easily disseminate 2-channel material, matrix encoded in the UHJ manner to provide a surround illusion for those with suitable equipment.

FM broadcasters would have the further advantage of being able to transmit a supplementary signal which, while offering only a modest response, could substantially improve the surround effect, using so-called 2-1/2 channel UHJ encoding.

Interestingly, hifi VCRs, with their FM-stereo plus analog tracks, would also appear to be candidates for 2-1/2 channel surround encoding.

And who knows? Given a substantial move in these areas, black discs and stereo cassettes could easily reappear in quantity with surround sound encoding — this time in UHJ. At the moment, Nimbus in the UK, and one or two other

rie

Rod Irving Electronics

425 HIGH STREET,
NORTHCOTE VICTORIA.
Ph:(03)489 8866 489 8131
48-50 A'BECKETT STREET,
MELBOURNE VICTORIA.
PH:(03)347 9251
Mail Order and
correspondence:
P.O. Box 235
NORTHCOTE 3070

**YOU WON'T GET
BORED OVER
THE HOLIDAYS
WITH THESE
GREAT
SPECIALS!!
GREAT 'IN
STORE' BAR-
GAINS TOO!**

Call in at either 2
of our convenien-
tly located stores:
48-50 A'Beckett
St., Melbourne
425 High St.,
Northcote.
Or take advan-
tage of our Mail
Order Depart-
ment.
Write to:

MAIL ORDER CENTRE
ROD IRVING ELECTRONICS
P.O. BOX 235
NORTHCOTE 3070

or phone ...
**MAIL ORDER
HOT LINE**



481 1436



POSTAGE RATES

\$1-\$9.99	\$1.50
\$10-\$24.99	\$2.00
\$25-\$49.99	\$3.00
\$50-\$99.99	\$3.50
\$100-\$199	\$5.00
\$200-\$499	\$7.50
\$500 plus	\$10.00

"We wish you a
Merry Christmas
and a Happy New
Year!"
from all at Rod
Irving Electronics.


PRINTERS GALORE



Juki printer

Professional daisy wheel
printer 18 CPS full incremental
model Diablo 630 emulation
Large range of daisy wheels
8K internal buffer available.


Was \$950 Now \$790

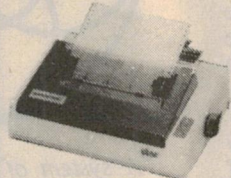

Star Gemini 10

120 CPS logic seeking
Italics, graphics and down-
loadable characters sets
Friction and tractor
9 x 9 matrix, Hi res. graphics.
Low cost typewriter ribbon.


Was \$499 Now \$430

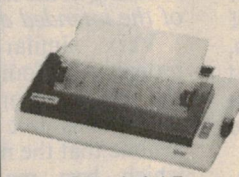

Star Gemini 15

120 CPS logic seeking
Italics, graphics and down-
loadable characters sets.
Friction and tractor
9 x 9 matrix, Hi res. graphics.
Low cost typewriter ribbon.


Was \$899 Now \$729

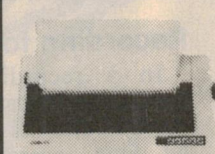

Star Radix 15

Excellent fast printer
200 CPS eats up the pages
With an amazing 16K internal
buffer you won't waste any
time.
Has near letter quality mode,
graphics, and font variation.


\$1,395

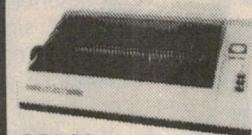

CPA80

The next generation of "80"
type printers. 100 CPS, internal
buffer expandable to 4K, Greek
as well as italics. Dip switches
accessible at the top. The print
quality is the same as its
forerunner. Square pins and
film ribbon make it unbeatable.

Was \$475 Now \$395

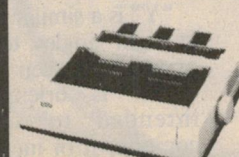

ENP1091

The latest addition to our range.
Has a near letter quality mode.
120 CPS. Down loadable
character set. Graphics, Italics,
emphasized etc.


Was \$500 Now \$420

NATIONAL RECHARGEABLE DRILL/SCREW DRIVER EZ505

- ★ Quick 1 Hr Charging
- ★ 4 Stage Torque Control
- ★ 2 Speed Switch
- ★ Handle Storage Compart-
ment
- ★ Forward/Reverse Operation
- ★ National Quality
- ★ Spare Battery Pack Available

Cat. T12320

\$149.00

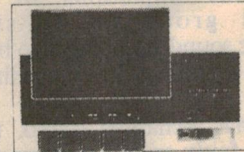

RITRON (ZETA) DATASETTE

For data loading and saving,
this Micron Datasette suits
most home computers and
features tape counter, monitor
function for audio verification
and slide volume control for
output level.

Cat. C14900

\$29.95




WELLER WTCNP SOLDERING STATION

- The WTCNP Features:
- ★ Power Unit 240 V AC
 - ★ Temperature controlled iron,
24 V AC
 - ★ Flexible silicone lead for ease
of use
 - ★ Can be left on without fear
of damaged tips!

The best is always worth having.

Cat. T12500

\$89.50

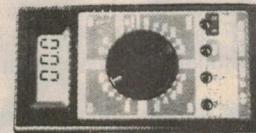

WE HAVE DONE IT AGAIN!!

New multimeter at unbeatable
value for under \$40! The new
YU FONG YFE-1030C

- features:
- ★ Large 3 1/2 digit display, (1 1/2
inch high)
 - ★ Autopolarity, "-" display for
Negative input
 - ★ High over-load protection for
all ranges
 - ★ Over-load display, highest
figure "1" or "1" alone glows.
 - ★ Power consumption 20mW
approx.

Cat.

\$39.95



CAR ALARM

- ★ Fully Automatic System.
- ★ High Reliability, ease of
installation.
- ★ Multifunctional, prevents all
doors, hood, trunk lid from
being stolen.
- ★ Power Supply by DC 12 V
(1 V-15 V) car battery.
- ★ Ear-bursting siren output
10 W/112 dB

Normally \$49.95, this month ...

Cat. C14220

\$44.95

MONITOR MADNESS

COLOUR IS HERE IN
A BIG WAY!!



PHOENIX V

- Pal Suits Apple, Commodore
even your V.C.R!
★ Pal and RGB
★ Normal Res.
★ 13" CRT Dot Pitch 0.65mm
★ Horiz. Resol. 320 TV Lines
★ Vert. Resol. 560 TV Lines
★ Display Characters
1000 Ch. (40 x 25)
★ 16 Colours (Pal)
★ Green Text Display

Cat. X14522 ~~\$449~~ \$399

PHOENIX IV

- Suits IBM RGB input
★ RGB, TTL
★ High Resolution
★ 13" CRT Dot Pitch 0.31mm
★ Horiz. Resolution 720 dots
★ Vert. Resol. 240 TV Lines
★ Display Characters 2000 Ch.
(80 x 25)
★ Display Colours
8 Colours and Intensity
★ Green Text Display

Cat. X14520

\$690


RITRON 1



Our most popular model in a
steel cabinet to minimise R.F.I.
interference. Prices include tax.
Make sure you get in early.

1-4	5-9	10+
Cat. X14500 (Green)		
\$139	\$135	\$129
Cat. X14500 (Amber)		
\$139	\$135	\$129


RITRON II

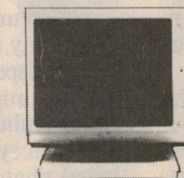

Swivel base monitor in stylish
case.

1-9	10
Cat. X14506 Green	
\$169	\$159
Cat. X14508 Amber	
\$169	\$159

RITRON III

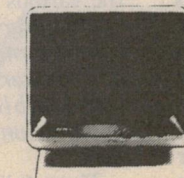

Great resolution, swivel base.
Amber only. Prices include tax.
Buy now for Xmas

1-4	5+
Cat. X14510	\$169 \$159

Errors and Omissions Excepted



TDK VIDEO TAPES AT BARGAIN PRICES!

VHS:	E60	\$12.50
	E120	\$12.50
	E180	\$11.80
	E240	\$22.40
BETA:	L250	\$13.50
	L500	\$14.40
	L750	\$17.50



FAIRCHILD TTL DATA BOOKS

Just arrived! This book is the
same as used in the Victorian
Education System. Includes
data on new Fast series.
Limited stock 500 only.

Cat. B10050


\$14.95



BRAND NEW FANS

Not noisy pullouts! Stacks of
uses in power amps, computers,
hotspot cooling etc. Anywhere
you need plenty of air.

Cat. T12461	240V	4 1/2"	\$16.95
Cat. T12463	115V	4 1/2"	\$16.95
Cat. T12465	240V	3 1/2"	\$16.95
Cat. T12467	115V	3 1/2"	\$16.95
10 Fans (mixed) less 10%			

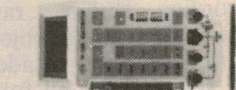

DIGITAL MULTIMETER

- YFE YF1100 FEATURES
- ★ Large, easy to read 3 1/2 digit
display
 - ★ Facilities for transistor and
diode testing.
 - ★ Clearly laid out front panel.
 - ★ 10A DC AC range
 - ★ Priced to undersell the
others!

Cat. A16025 \$59.50




TRANSISTOR NIPPERS

Normally \$7.95! This Month
Cat. T12070 \$6.95



Normally \$9.95 This Month
Cat. T12050 \$6.95

Errors and Omissions Excepted

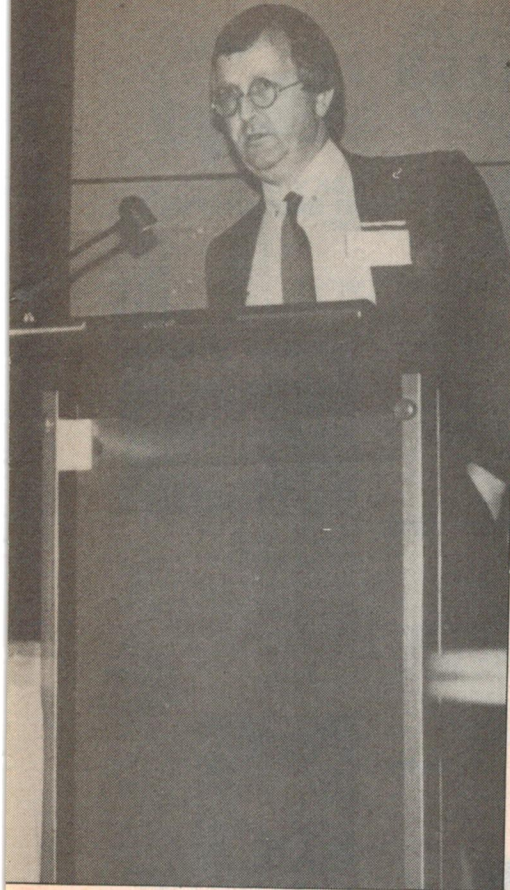

But things didn't work out that way. With all the doggedness and detachment of an academic group, proponents of Ambisonics kept plugging away, with practical assistance from the BBC and ITA and sympathetic input from overseas sources.

From material picked up at the Melbourne AES Convention, it is apparent that the attention of the Ambisonics group is currently focused on recording studios, rather than consumers. Their prime objective, right now, is to see the format adopted as an industry standard for all future master recordings.

From Ambisonics masters, engineers would then hopefully produce compatible Ambisonics style derivatives in whatever format market requirements might dictate: mono, 2-channel stereo, 2-1/2 or 3-channel surround, 4-channel surround, or full sphere "periphonic" involving six channels or more!

The job ahead of Ambisonic proponents is therefore to convince recording interests, recording engineers, producers and anyone else who matters in that area, that they should begin to draw on Ambisonic techniques and a growing inventory of Ambisonic hardware to produce future recordings.

That, by so doing, they would not only enhance the quality of normal stereo or mono software, but they would also be building an inventory of master recordings against the day when true surround or even periphonic sound is

introduced once again to the domestic scene.

In short, that Ambisonic technology is unrivalled in what it has to offer, in terms of planning for the future.

Old-style 4-channel

A brochure from the British National Research Development Council (NRDC) re-affirms the objections of the Ambisonic group to old-style quadraphonic sound, claiming it to be an unacceptable extension of ordinary stereo.

Conventional 2-channel stereo, they say, relies on fairly critical placement of the loudspeakers for an acceptable aural illusion. They must not be too close together but, equally, the illusion suffers if the angle subtended at the listening position is too great.

Again, stereo works well only when the listener is facing the loudspeakers. If the listener turns his or her back to them, the aural illusion of direction and spread normally suffers. Side-on to the loudspeakers, the illusion is usually quite poor.

According to the Ambisonic group, these observations are crucial to the evaluation of an old-style quadraphonic system as, for example JVC/RCA's CD-4 "discrete", which is credited with better inter-channel separation than any of its contemporaries.

To localise a sound in the frontal sector, signals of appropriate relative amplitude are fed to the LF (left front) and RF (right front) loudspeakers. For a sound on the listener's right, signals are fed to the RF and RB (right back) loudspeakers. Similarly for the remaining sectors.


Unfortunately for any such system of "four way stereo" or "surround stereo", the loudspeaker pairs must subtend an average angle of $360/4$ or 90-degrees at the listening position — too large for a satisfactory inter-speaker, amplitude-based phantom image. Says the NRDC brochure:

"This is true even in the front sector; it is worse for a pair of speakers behind, and is worse still for a pair at either side".

The brochure goes on to claim that the system is really limited, at best, to signals which can be manually pan-potted into the various stereo pairs.

"No practical directional microphone can perform this switching between pairs of speakers accurately. Thus it is impossible to realise 'discrete quadraphony' from any natural sound field".

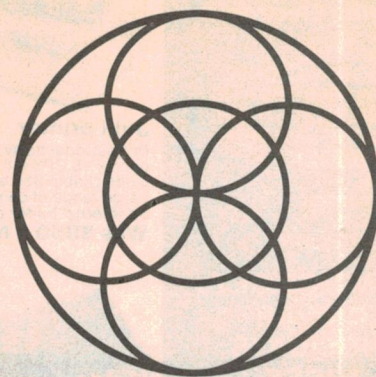Then follows a huge jump in logic, which has tended to characterise Ambisonics literature through the years — to the detriment of its credibility:



"A system of direct sound which is able to reproduce the directionality of indirect reverberant sounds, as well as direct sources, is termed 'Ambisonic'."

"Ambisonics is based upon encoding a directional pattern of sound, and decoding in the listening room an illusion of the intended directional effect. . ."

Very similar observations could probably be found in the literature on the various other — and now discarded — systems but the reader is left to assume that the newest system is the one which best meets the objective — presumably by making more effective use of frequency, amplitude and phase relationships. Charitably, with the benefit of years of additional research, the assumption could well be valid.

Recording format

In a recording situation, what Ambisonic literature describes as the "total directional sound field" is defined by four separately recorded signals conforming to their so-called "B-format", as illustrated in Fig.1. (It obviously provides the basis for the Ambisonics logo).

The four signals involved in the B-format are designated by the letters W, X, Y and Z.

"W" is described as an omnidirectional or "pressure" signal, which represents the summation of all incident sounds at the microphone position, irrespective of direction.

"X" is a version of the program as would be intercepted by a figure-of-eight microphone, coincident with source "W". Its two lobes, forward looking (+) and rearward looking (−), each have a gain of 3dB relative to the omnidirectional pattern.

"Y" is a similar figure-of-eight pattern, at right angles to "X" and nominally oriented between left (+) and right (−).

"Z" is orientated vertically and intended to sense the "height" component of incident signals. Whether or not the Z signal is required or appropriate depends on the nature of the sound being recorded.

AMBISONICS AT THE AES MELBOURNE CONVENTION

Right: Robin Maconie presenting his lecture at the AES Melbourne Convention: "Digital Ambisonic Recording at Surrey University".

To many audio enthusiasts, the term "Ambisonics" will suggest little more than an obscure system of surround sound that the British have talked about for years but done little with, outside the laboratory. There's more to it than that, however.

Back in the early '70s, the audio industry decided that the time had come to introduce listeners to a new and exciting concept: 4-channel, quadraphonic "surround" sound.

All agreed that any such system should be compatible, to the extent that 4-channel recordings must be directly playable in stereo or mono mode on existing equipment. But, instead of settling on a common encoding system for the additional two channels of signal information, individual companies opted for their own variant, which they then set about promoting at the expense of all the others!

To add to the confusion, a small but influential group, headed up by JVC and RCA, rejected the simpler matrix encoding method altogether, promoting instead the CD-4 "Discrete" system, with the rear channel information modulated, in part, on to a supersonic carrier, which they recorded in the groove, along with the regular stereo audio signals.

In a two-part article in the May and June '72 issues, we listed no less than thirteen major Japanese companies and the thirteen names by which their respective 4-channel systems were currently identified. These were subsequently rationalised down to three or four but, by then, the damage had been done and, in the minds of the public, a large question mark hung over the whole idea of surround sound.

Whether the marketing chaos was responsible for buyer rejection of surround sound has long been a matter for debate, but the very idea of four loudspeakers in the living room was sufficient to prompt plenty of opposition at a domestic level. Confusion about



Below: Erdo Groot, a graduate of the University of Surrey Tonmeister Course, was responsible for the technical arrangements at the presentation.

systems could easily have been an excuse, rather than a reason for not buying!

Ambisonic system

It was into this unreceptive situation that Ambisonics was born, with reports from the UK suggesting (as I remember it) that a research team from Reading University had come up with a radically new approach to surround sound. It avoided many of the shortcomings of existing systems and offered improved spatial perception, with the further option of using extra loudspeakers on

either side of the listening position — and overhead!

To an industry which had recently been exposed to exaggerated claims from countless sources, reports from an academic group in Britain about yet another system were scarcely exciting. Even less so was the prospect of stringing still more loudspeakers around the walls and ceiling of the listening room.

So, when "quadraphonic" sound was effectively laid to rest by the consumer hifi industry, one might have expected that Ambisonics would have been interred along with SQ, QS, and CD-4.

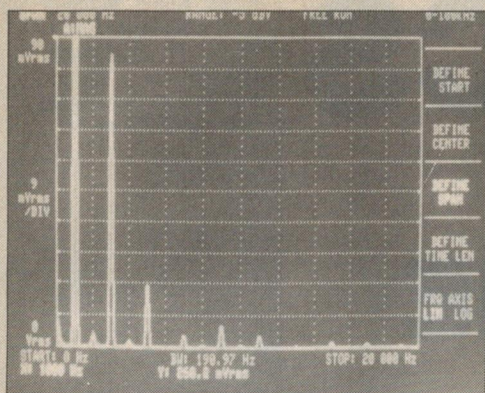


Fig. 9: output from the harmonic wave analyser is in the "frequency domain". The amplitude of the fundamental and each harmonic can be read directly. Scales are linear; 9.0mV (RMS) per division vertical. The horizontal scale (2kHz per division) gives the actual frequency of each harmonic.

Fig. 10 right: same load current i_{RL} as Fig. 5 but now supplied by a class AB output stage wherein each output transistor Q7 and Q8 conducts for approximately 318° ; ie $(138^\circ + 180^\circ)$ per cycle. The sum ($i_{Q7} + i_{Q8}$) equals the output current i_{RL} .

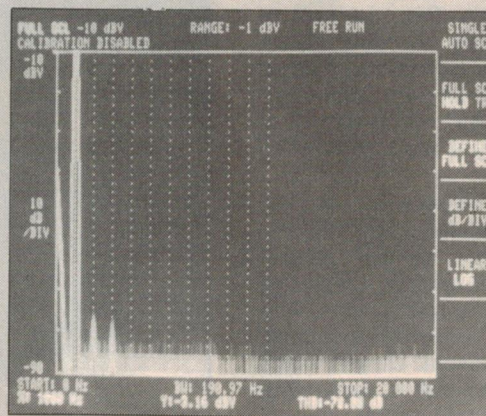
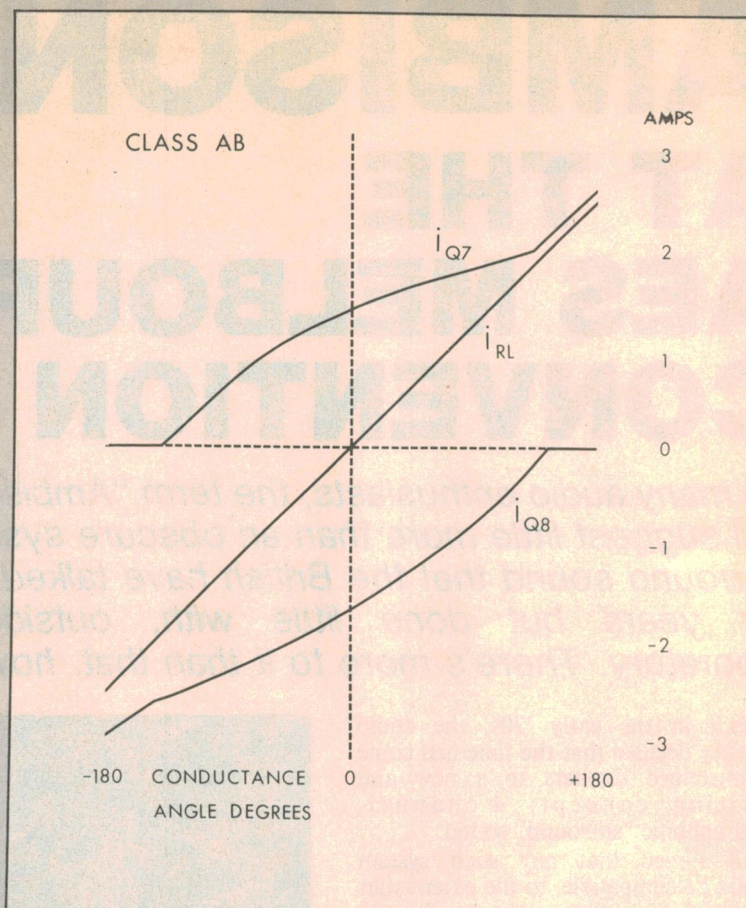


Fig. 11: frequency domain output from the harmonic wave analyser of class AB output stage. Log scale vertical shows each harmonic amplitude at 10dB per division. Linear horizontal frequency scale is 1kHz per division. Second and third harmonics are clearly seen at -75dB, others lost in noise.

Class AB amplification is an intermediate state of operation in between class A and class B wherein each transistor conducts for less than a full cycle, but for more than half of every cycle. It conducts over some angle between 360 degrees and 180 degrees. This is illustrated in Fig. 10 where an output ramp current (RL) and resulting transistor currents are shown. This class is known for efficiency which is better than

class A, but less than that of class B. Class AB is a whole range of operating conditions satisfying: $180^\circ < \text{conducting angle} < 360^\circ$.

For the 318° per cycle class AB output stage, as Fig. 10, the distortion levels are quite low as shown by the output of the harmonic waveform analyser Fig. 11. In this last figure log scales in dB are used as the harmonic amplitudes are small. The THD is -73dB or, if you like,

.03%. The horizontal axis is still linear in frequency, this time with dotted vertical lines each at 1kHz. The fundamental is off scale at the top, the 2nd and 3rd harmonics about equal in amplitude, and other harmonics present but blurred by noise. No feedback was used here.

Next month we shall discuss the various bias systems used for amplifier output stages and the ways in which negative feedback is applied.

OP AMPS Explained

Just what conducting angle and class is achieved by a given circuit is determined by the bias for the output transistors. The bias voltage is added in with the signal to drive points P and Q in Figs. 2, 3 and 4. The class has far reaching influence upon the available power output, the type and percentage of distortion, the amplifier efficiency and heating. Personal opinions run strong in some quarters, each class having its own devotees among the faithful. Before we detail the bias circuits let's define the classes.

Class-A amplification means that the transistor is conducting continuously even when there is no output. Figs. 1 and 2(a) are Class A, and this class is well known as historically the oldest. Of all transistor circuits, those in class A give the least distortion (before feedback is applied).

Unfortunately this is at the price of lowest efficiency as much power is wasted in simply heating the transistor because it is conducting even when not producing any useful output.

Class-B amplification is a circuit bias condition such that each transistor conducts for exactly half the time, and we say each has a conducting angle of 180° every cycle. Fig. 5(a) shows a ramp output current (RL) changing from negative to positive as the transistors conduct in turn. That small area in the centre is enlarged in Fig. 5(b) to show that because transistors cannot turn on abruptly, there is a small part of the input voltage cycle time when neither output transistor is conducting. The result is that the output current is not an image of the input voltage; ie, we have distorted output at the cross-over points. This class is more efficient as the conducting transistor produces output.

The art of power amplifier design centres around:

- Methods devised to provide the exact bias.
- How to minimise crossover distortion.
- Minimisation of another cause of distortion — the nonlinearity of transistors.

Fig. 6 shows a fundamental class-B stage before any corrective measures against crossover distortion are applied, while Fig. 7 shows its output voltage in response to a sine wave input voltage. The resulting distortion is severe. In this case, the input is swinging between 1.0

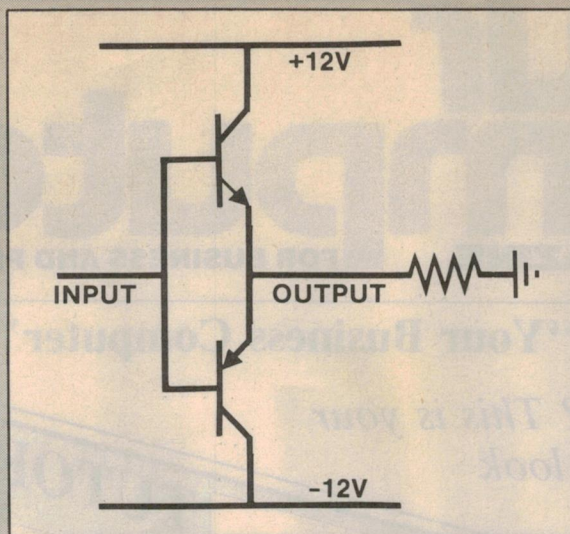


Fig. 6: fundamental class B output stage before any distortion-prevention steps are added.

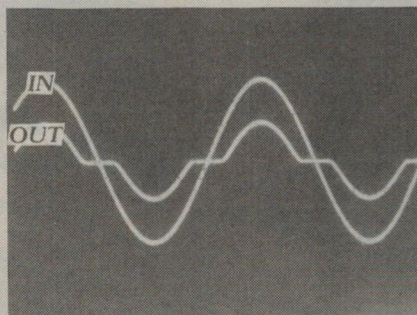


Fig. 7a: sinewave input to a fundamental class B output stage before any precautions against crossover distortion are applied. The output is very distorted at each zero crossing. $V_{in} = \pm 1.0$ volt; $V_{out} = \pm 0.45$ volt; frequency = 1.0kHz; and THD = 33%.


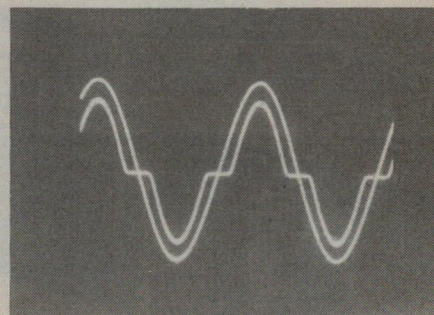


Fig. 7b above, right: same output stage as in Fig. 7a, but somewhat larger input signal resulting in a little less distortion.

Fig. 8: the test bench, with test amplifier constructed on breadboard in centre, Tektronix and BWD sinewave oscillators at left, dual power supplies centre. At right is a frequency counter (top), oscilloscope (centre), and a HP Harmonic Wave Analyser.

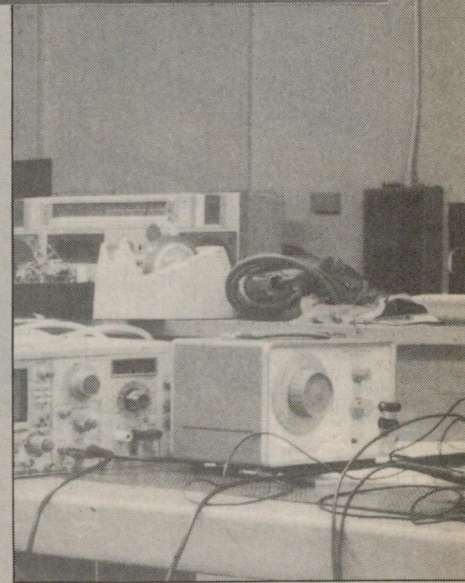

volt and -1.0 volt.

For conduction, the NPN transistor base is always 0.55 volts more positive than its emitter (in this case). Therefore, while the input is $+1.0$ volt, output is $+0.45$ volt, and output follows input faithfully all the way down the sine wave until input is 0.55 volts, at which point the output has slid down to zero. While the input continues on down to zero, the output cannot do anything but stay at

zero because the transistor is cut off.

Similar remarks may be made about the bottom PNP transistor. The overall result, as Fig. 7 displays, is an output which is part of a sine wave some of the time, and zero and remainder.

For this reason crossover distortion sounds worse at low volume output, and not so bad at high power output. Fig. 7(b) shows a little less distortion resulting from a somewhat larger signal input.

your computer

MAGAZINE FOR BUSINESS AND PLEASURE

\$2.95


Incorporating "Your Business Computer"

Into computing? This is your magazine! Just look what's in it for you!

NEWS



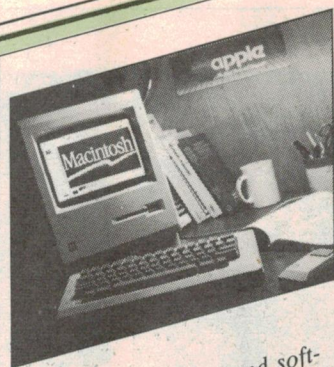'Your Computer' brings you all that's interesting, innovative and inventive in the microcomputing world — news of products, plans and politics to keep you up-to-date with what's going on in this fast-moving industry.



The latest machines and software from all the computer manufacturers are reviewed each month in 'Your Computer'. Keep up-to-date with what's available, and use our reviews to help you assess which products are most useful for you.


REVIEWS

TUTORIALS




Les Bell

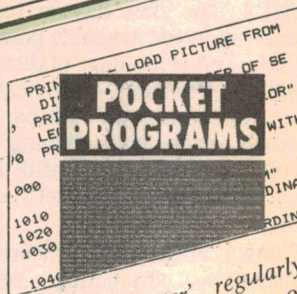'Your Computer's' tutorials include regular series on such popular subjects as the BASIC programming language and dBase II, probably the biggest-selling database program of them all. Written by such well-known industry experts as Les Bell, they're an invaluable aid to learning how to make computers work for you.



'Your Computer' regularly publishes all kinds of programs written both by professional programmers and readers, and ranging from games to business uses, utilities to additions and alterations to well-known programs. All kinds of computer users and enthusiasts will find programs to suit them in our pages!

PROGRAMS

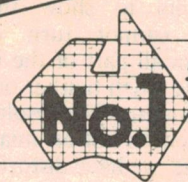


AUSTRALIA'S TOP-SELLING COMPUTER MAGAZINE

AUDITED SALES

Your Computer

is a magazine for all computer users and enthusiasts — there's something for everyone in our pages. We cover games and utility programs for hobbyists, and every second month we publish 'Your Business Computer' as a separate section for business computer users. 'Your Computer' offers topical features on all aspects of the computing world, written in understandable everyday language, along with reviews of new products to help you find your way round the fast-growing market, and regular columns giving specific advice on all the most popular brands of microcomputer. If computers play any part in your life at all, don't miss your monthly issue of 'Your Computer' — without it, you just won't know what's going on!

Available at your newsagent now!

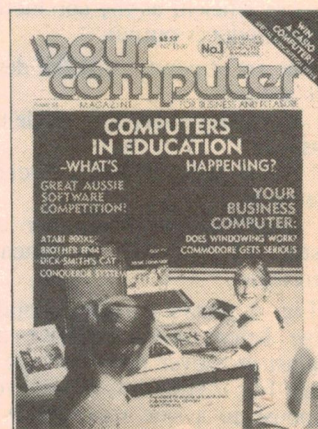

ELECTRONICS AUSTRALIA HANDBOOKS

Are you an
enthusiast?
A student?
A hobbyist? Or
a complete
beginner?



Whatever your
interest in
electronics,
we've a book
to suit
your needs!

FUNDAMENTALS OF SOLID STATE

Now in its second reprinting — which shows how popular it has been! It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised texts heavy going. It begins with atomic theory, diode types, unijunction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A glossary of terms and an index complete the book. Fundamentals of Solid State has also been widely adopted in colleges as recommended reading — but it's not just for the student, it's for anyone who wants to know just a little bit more about the operation of semiconductor devices.

BASIC ELECTRONICS

As a basic text for the electronics enthusiast, Basic Electronics is almost certainly the most widely used manual on electronics fundamentals in Australia. It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. It begins with the electron, introduces and explains components and circuit concepts and progresses through radio, audio techniques, servicing test instruments, television, etc. If you've always wanted to become involved in electronics, but have been scared off by the mysteries involved, let Basic Electronics explain them to you. Easy-to-understand diagrams and text make this the perfect book for you. We've even included five simple electronic projects for you to try your hand at building!

DIGITAL ELECTRONICS

Electronic equipment now plays an important role in almost every field of human endeavour and every day, more and more electronic equipment is "going digital". Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and Introduction to Digital Electronics can give you that grounding. Tens of thousands of people — engineers, technicians, students and hobbyists — have used the previous editions of this book to find out what the digital revolution is all about. The new fourth edition has been updated and expanded, to make it of even greater value. No previous knowledge of digital electronics is necessary — the book covers all basic concepts from scratch.

PROJECTS & CIRCUITS

If you like building electronic projects in your spare time, you can't afford to miss out on this exciting book of popular projects. Just look what's inside! **Audio & Video projects:** Video Amplifier for Computers and VCRs; Video Enhancer; Vocal Cancellor; Stereo Simulator for Tuners and VCRs; Guitar Booster for Stereo Amplifiers. **Automotive Projects:** Transistor-assisted Ignition System; Breath Tester; Low Fuel Indicator; Speed Sentry; Audible Turn Indicator. **Mains Power Control Projects:** Musicolour; Photographic Timer; Driveway Sentry; Touch-lamp Dimmer. **Power Supplies and Test Equipment:** Battery Saver for Personal Portables; Dual Tacking $\pm 22V$ Power Supply; $3\frac{1}{2}$ -Digit LCD Capacitance Meter; In-Circuit Transistor Tester. Plus EA's 10-year project index!

Available from: Electronics Australia Book Sales, 140 Joynton Avenue, Waterloo, NSW 2017.
Phone (02) 663 9999.

FROM HOBBYIST TO PROFESSIONAL – FLUKE MUST BE YOUR FIRST MULTIMETER CHOICE FOR FEATURES, QUALITY AND VALUE

FREE VINYL POUCH
worth \$19.60
with every handheld multimeter
purchased during December and January



FLUKE MULTIMETERS CARRY A ONE YEAR MINIMUM WARRANTY AND ARE BACKED BY COMPREHENSIVE SPARE PARTS, CALIBRATION AND SERVICE

1 8050A

- 4½ digit bench portable • 0.03% basic accuracy • 10uV, 10nA, 10mohm sensitivity • True RMS to 50kHz • dB with 16 reference impedances • Relative reference for comparing values • Mains/Battery option

8010A 8012A (similar to 8050A)

- 8010A has 10A range and true RMS • 8012A has low ohms (0.001ohm resolution) • Both have conductance • Mains/Battery option

2 8020B

- 3½ digit • 0.1% basic accuracy • Eight functions including conductance • Continuity beeper

3 8021B 8022B

- 3½ digit • 0.25% basic accuracy • Diode test • Continuity beeper (8021B only)

4 8024B

- 3½ digit • 0.1% basic accuracy • 11 functions including temperature with K type thermocouples • Peak hold on voltage and current • Logic detection and continuity testing • Audible and visible indicators

5 8026B

- 3½ digit • 0.1% basic accuracy • True RMS to 10kHz • Conductance to 10,000Mohm • Diode test and continuity beeper

6 8062A

- 4½ digit • 0.05% basic accuracy • Similar to 8060A without counter and dB • Relative reference • True RMS to 30kHz

7 8060A

- 4½ digit • 0.05% basic accuracy • True RMS to 100kHz • Frequency counter to 200kHz • dB and relative dB • Microprocessor self diagnostics • Relative reference for comparing values • Direct resistance to 300Mohm

LOW COST 70 SERIES WITH ANALOG & DIGITAL DISPLAY

**3 YEAR
WARRANTY**

8 73

- 3200 count display • 32 segment bar graph • 18 ranges • Automatic power down • 10A current range • Autorange • 0.7% basic accuracy • 2000 hour battery life

75

- All the features of the 73 plus:
• Audible continuity tester • Autorange/Range hold • 0.5% basic accuracy • Low mA range

77

- All the features of the 75 plus:
• Touch Hold function • 0.3% basic accuracy • Multipurpose protective holster

ACCESSORIES INCREASE THE VERSATILITY OF YOUR FLUKE MULTIMETER

An extremely wide range of accessories is available for your Fluke multimeter.

SOLD & SERVICED IN AUSTRALIA BY

ELMEASCO

Instruments Pty. Ltd.

Elmeasco Instruments Pty Ltd – incorporated in N.S.W.

NEW SOUTH WALES
15 Macdonald Street,
MORTLAKE
P.O. Box 30, CONCORD
NSW 2137
Tel: (02) 736 2888
Telex: AA25887

VICTORIA
12 Maroonah Highway,
RINGWOOD
P.O. Box 623, RINGWOOD
VIC 3134
Tel: (03) 879 2322
Telex: AA36206 ELMVIC

QUEENSLAND
243 Milton Road,
MILTON
P.O. Box 2360, BRISBANE
QLD 4001
Tel: (07) 369 8688
Telex: AA44062

SOUTH AUSTRALIA
99 King William Street,
UNLEY
P.O. Box 1240, ADELAIDE
SA 5001
Tel: (08) 271 1839
Telex: AA88160

WESTERN AUSTRALIA
20 Barcomb Way,
GOSNELLS
P.O. Box 95, GOSNELLS
WA 6110
Tel: (09) 398 3362

OP AMPS Explained

However the most important point against such a choice would be thumps in the loudspeaker on switch-on. These are caused by the coupling capacitor charging currents.

The design of Fig. 3(b) using collector output (common emitter configuration) gives:

- (a) Voltage gain in the output stage.
- (b) Easy design of overcurrent protection (by insertion of a current sense resistor in the emitter lead).
- (c) If live mounting of transistor is desired, both can be mounted on one common heatsink.
- (d) Less DC drift [as consequence of (c)] because the transistors will be at same temperature.
- (e) Easier integration onto one silicon wafer [as consequence of (c) and (d)] and high voltage gain make this scheme a natural for power integrated circuit operational amplifiers (eg, National's LH0021).

About the only limitation on the above advantages incurred are:

- (a) Somewhat higher output impedance, (so heavier feedback needed to compensate).
- (b) If live mounting of transistors is used, the body of the heatsinks adds to the collector output capacitance (an embarrassment in power op amps where heavy feedback is used).

Quasi-Complementary designs are an attempt to obtain the advantages of the fully complementary arrangements without using a large PNP transistor. Fig. 4 illustrates a double emitter follower or Darlington (a), using two NPN transistors, and an "augmented emitter follower", (b), sometimes known as a "compound pair".

The Darlington of Fig. 4(a) acts as one NPN emitter follower with voltage gain about 0.85, high input impedance, very low output impedance and low distortion.

The compound emitter follower of Fig. 4(b) appears to the user somewhat like a Darlington made of two PNP transistors yet is not. It is useful only when large enough PNP transistors are not available, yet NPN types are. Such a situation applied years ago to domestic size transistors, but not now. However the same situation applies still to the commercial or industrial world when very large output currents of the order of a kiloamp are needed.

Fig. 4(c) is a quasi-complementary output stage. For hifi amplifiers, its characteristics were never the best for a

number of reasons:

- (a) Impedance looking into P is lower than that looking into Q.
- (b) Output impedance from the bottom section is not quite as low as from the top section, and the top and bottom voltage gains are different.
- (c) Because of the foregoing statements, it is difficult to reduce distortion to very low levels no matter what drive circuits or feedback systems are employed.

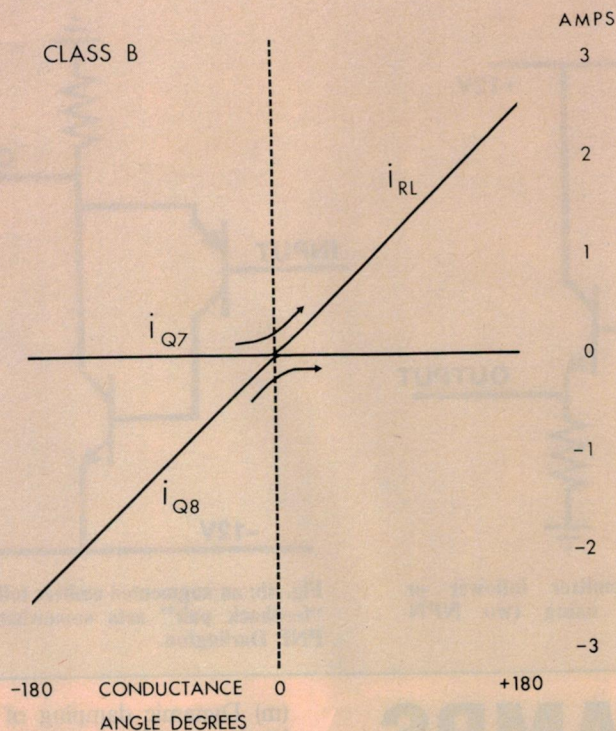


Fig. 5a: when a class B amplifier with output transistors Q7 and Q8 supplies a linear ramp waveform current to a load resistance R_L the current i_{RL} is composed of two components i_{Q7} and i_{Q8} as the transistors take turns in supplying the current. Imperfect crossover at the centre, shown enlarged in Fig. 5b, is the cause of crossover distortion.

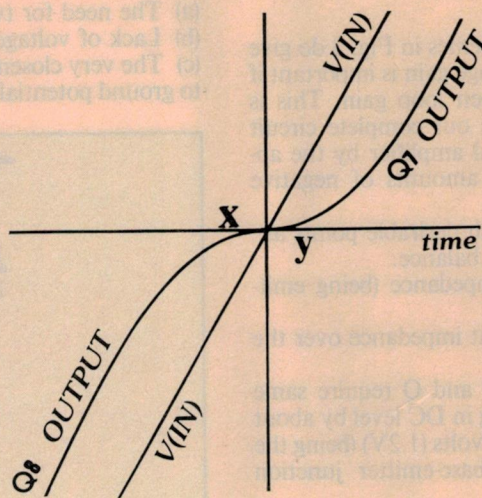


Fig. 5b: enlarged centre section of Fig. 5a shows crossover distortion caused by the inability of transistors Q7 and Q8 to turn on or off abruptly.

Class of amplification is defined by considering one full cycle of the input signal. If an output transistor is biased to conduct continuously, we say it is conducting over 360° of every cycle. If a different transistor is arranged to conduct only for part of each cycle, we say its conducting angle is less than 360° each cycle. Class names are given to denote such different conditions.

Continued on page 82

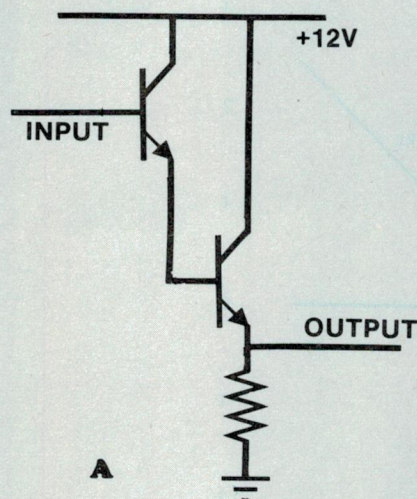


Fig. 4a: double emitter follower or Darlington stage using two NPN transistors.

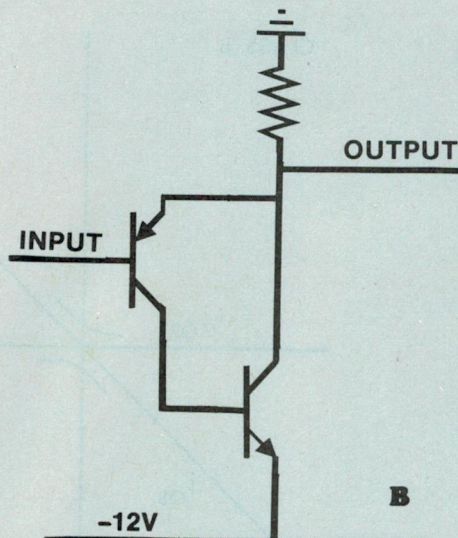


Fig. 4b: an augmented emitter follower or "feedback pair" acts somewhat like a PNP Darlington.

OP AMPS Explained

But all three schemes in Fig. 3 do give current gain. Voltage gain is important if we desire high open loop gain. This is necessary to make our complete circuit one big operational amplifier by the application of large amounts of negative feedback.

Fig. 3(a) has such desirable points as:

- (a) Symmetry and balance.
- (b) Low output impedance (being emitter followers).
- (c) Constant output impedance over the whole cycle.
- (d) Drive points P and Q require same signal, but differing in DC level by about plus and minus 0.6 volts (1.2V) (being the sum of the two base-emitter junction voltages).
- (e) Drive requirements balanced about ground potential.
- (f) Moderate input impedance to bases (because they are emitter followers).
- (g) DC coupled, ie, pass band extends down to zero frequency.
- (h) Although two power supplies are required, they each need only moderate voltage.
- (i) Useful current gain.
- (j) Can drive motors, coils, lamps, heaters and any other DC loads.
- (k) Very heavy feedback can be used (if desired) as the DC coupling causes no phase shift at low frequencies.
- (l) The low output impedance is not degraded at very low frequencies.

(m) Dynamic damping of loudspeakers by the amplifier is not degraded at very low frequencies.

(n) Little or no trouble in switch-on conditions (due to dual power supplies).

Criticisms levelled at the circuit Fig. 3(a) are:

- (a) The need for two power supplies.
- (b) Lack of voltage gain.
- (c) The very closeness of the drive points to ground potential (claimed as an advantage above) may be embarrassing to the designer of the over-current protection section.

And as a consequence of the DC coupling:

(d) Any drift in the DC level causes erroneous output; for example, causing a shift in loudspeaker cone resting position.

(e) Failure of an output transistor or its drive circuits can apply full rail DC voltage to the output, possibly burning out a very expensive loudspeaker.

(f) If you wish to use live heatsinks (ie no insulation between transistor and heat-sink) for optimum cooling, Figs. 3(a) and (c) require two separate insulated live heatsinks.

A circuit designer who chooses Fig. 3(c) rather than 3(a) probably makes this choice because:

(a) Most of the advantages of an emitter follower output stage will apply.

(b) It will need only one power supply rail.

(c) DC drift problems can be largely disregarded.

(d) An amplifier malfunction won't damage the loudspeakers.

(e) As the left side of the capacitor rests at about half the positive rail voltage, a polarised electrolytic capacitor, large enough for adequate bass response, can be used.

(f) The capacitor can be placed inside the main feedback loop (not usually done), thus removing any effects of capacitor impedance at low frequencies.


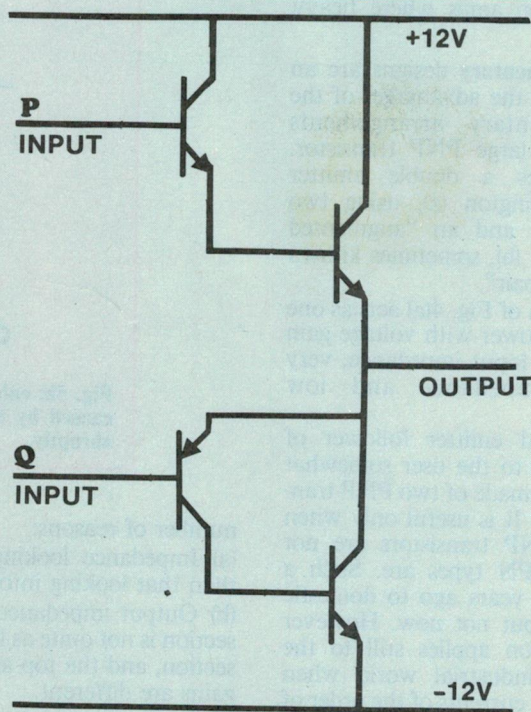


Fig. 4c: quasi-complementary output stage. Note that the impedance looking into point P is lower than looking into point Q, while the top and bottom voltage gains are different.

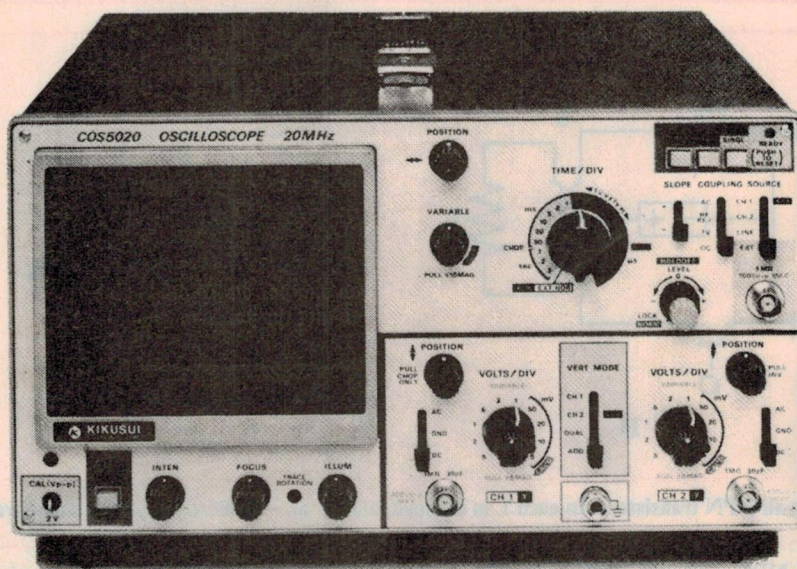

KIKUSUI 20MHz DUAL TRACE SCOPE

\$539⁰⁰ EX TAX **INC**
\$625⁰⁰ INC TAX **PROBES**

**Compact and easy to operate for
hobbyists and professionals**

- 5mV/div sensitivity
- Hold-Off function
- CH1, CH2, Dual, Add, X-Y modes
- Intensity modulation
- 5mS to 2uS sweep delay
- 0.2uS to 0.5S/div sweep range

FUJITSU PLUGS AND SOCKETS

We are now stocking an extensive range of quality Fujitsu plugs and sockets. Gold-palladium-over-nickel contacts. Double action IDC mechanism for reliable connections. PCB terminations are solder-over-nickel for easy soldering.

STRAIGHT PCB HEADERS FCN704 SERIES

10 pin Straight Header	\$3.00
14 pin Straight Header	\$3.20
16 pin Straight Header	\$3.46
26 pin Straight Header	\$4.54
34 pin Straight Header	\$5.00
50 pin Straight Header	\$5.95



RIGHT ANGLE PCB HEADERS FCN705 SERIES


10 pin Right Angle Header	\$3.00
14 pin Right Angle Header	\$3.20
16 pin Right Angle Header	\$3.46
26 pin Right Angle Header	\$4.54
34 pin Right Angle Header	\$5.00
50 pin Right Angle Header	\$5.95



SOCKET CONNECTORS


FCN707B Series

10 way socket connector	\$3.37
10 way socket connector	\$3.37
14 way socket connector	\$4.26
16 way socket connector	\$4.50
26 way socket connector	\$5.46
34 way socket connector	\$6.13
50 way socket connector	\$7.25

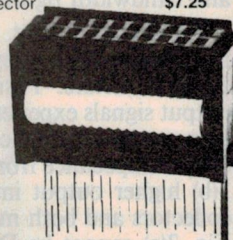

D TYPE
FCN777 Series


25 pin female D type	\$10.90
25 pin male D type	\$8.99

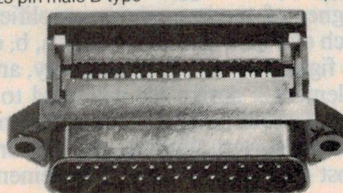

IDC CONNECTORS

FCN707 Series

34 way plug	\$6.84
50 way plug	\$7.65

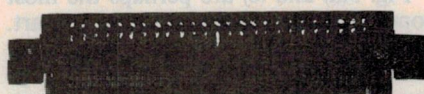


**NOW STOCKING
A COMPLETE
RANGE OF HC CMOS**

MM74HC00N	1.05	MM74HC251N	1.77
MM74HC02N	1.05	MM74HC253N	1.99
MM74HC04N	1.05	MM74HC257N	1.77
MM74HC08N	1.05	MM74HC27N	1.05
MM74HC107N	1.49	MM74HC280N	8.21
MM74HC10N	1.05	MM74HC299N	10.00
MM74HC112N	1.49	MM74HC30N	1.22
MM74HC113N	1.49	MM74HC32N	1.47
MM74HC11N	1.21	MM74HC354N	9.58
MM74HC123N	4.05	MM74HC356N	9.58
MM74HC125N	3.13	MM74HC365N	4.73
MM74HC132N	2.40	MM74HC366N	4.72
MM74HC133N	1.22	MM74HC367N	4.72
MM74HC138N	2.11	MM74HC368N	4.72
MM74HC139N	1.88	MM74HC373N	4.90
MM74HC147N	2.38	MM74HC374N	4.90
MM74HC14N	1.69	MM74HC390N	2.90
MM74HC151N	1.75	MM74HC393N	2.90
MM74HC153N	1.97	MM74HC4002N	1.04
MM74HC154N	4.63	MM74HC4020N	2.71
MM74HC157N	1.47	MM74HC4040N	2.71
MM74HC158N	1.77	MM74HC4049N	1.81
MM74HC160N	2.52	MM74HC4050N	1.81
MM74HC161N	2.52	MM74HC4075N	1.04
MM74HC162N	2.52	MM74HC4078N	1.04
MM74HC163N	2.40	MM74HC423N	4.05
MM74HC164N	2.43	MM74HC42N	1.92
MM74HC174N	1.92	MM74HC4538N	4.51
MM74HC175N	1.92	MM74HC533N	4.90
MM74HC192N	2.76	MM74HC534N	4.90
MM74HC193N	2.76	MM74HC640N	4.06
MM74HC194N	2.10	MM74HC643N	4.06
MM74HC195N	2.10	MM74HC688N	6.52
MM74HC20N	1.05	MM74HC73N	1.49
MM74HC240N	4.17	MM74HC74N	1.49
MM74HC241N	4.17	MM74HC75N	1.70
MM74HC242N	3.79	MM74HC76N	1.49
MM74HC243N	3.79	MM74HC85N	3.00
MM74HC244N	4.17	MM74HC86N	1.31
MM74HC245N	4.71	MM74HCU04N	1.09

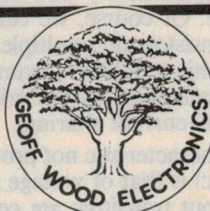8.30 to 5 Monday to Friday, 8.30 to 12 Sat.
Mail Orders add \$3.00 to cover postal charges.
Next day delivery in Sydney add \$5.00.

All prices INCLUDE sales tax.

Tax exemption certificates accepted if line value exceeds \$10.00.




GEOFF WOOD ELECTRONICS PTY LTD

Incorporated in N.S.W.

656A Darling St, Rozelle 2039


(One door from National Street)

Tel: **810 6845**

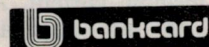


\$10.00 minimum

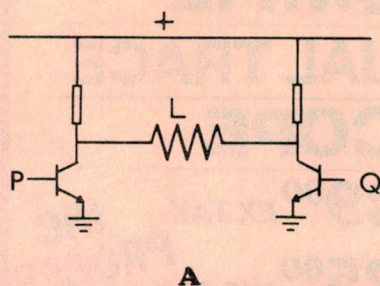
specialising in electronic components for the professional and hobbyist.



A

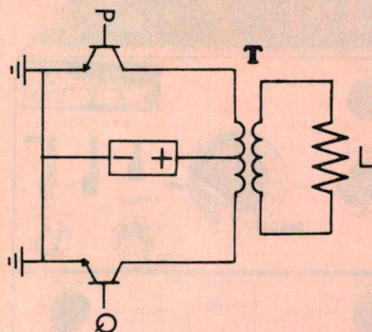

B

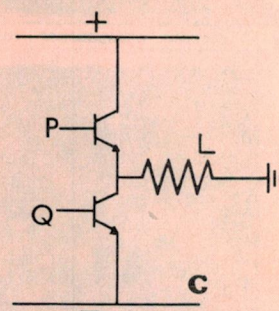

C

Fig. 2a, b, c: Three examples of output stages using all NPN transistors. In each L is the load, and + or - indicates a power supply rail.

MT6010 rated at 450 volts/500 amps (peak values).

Such a two kilowatt transistor is an example of a range of NPN transistors with current ratings all the way up to 1.2 kiloamps. Yes, gentle reader, the days when electronics was falsely labelled "light current work" have now passed into history — today we have users asking for power operational amplifiers of kiloamp (1000 amps) output capability.

Each design in Fig. 2 does, unfortunately, carry a few penalties if our love is hifi music, DC coupling or simplicity with low voltage output. The transformer T in Fig. 2(b) is a problem by dint of its weight, cost and introduced distortion. In addition, it prevents DC coupling. The configuration of Fig. 2(c) certainly can be DC-coupled but is non-ideal on three counts:

(a) Inputs P and Q must be out of phase.
(b) Inputs P and Q are at very different levels, and worse — the level of P follows the output voltage but the level of Q does not.

(c) Output impedance is different on each half cycle, being lower when the upper transistor is conducting (emitter follower configuration), and higher when the lower transistor is supplying output (common emitter configuration). This non-symmetry can be a designer's headache when either DC drift or a large feedback factor are critical considerations. Certainly feedback can be (and is) used to smooth out this difficulty, but many designers prefer to have one less problem to solve.

A design philosophy attributed to J. S. Coombs is: "Let's not use feedback to make a poor design acceptable; rather we should apply feedback to a good design to make it excellent". For all medium voltage, medium current, AC- or DC-coupled or hifi applications then consider:

Complementary Symmetry types, ie

one NPN and one PNP as in Fig. 3, so-called because the NPN and PNP transistor pair complement each other in all their characteristics. At least we hope they do. Many manufacturers produce such transistors expressly for this purpose. Examples include 2N5686 (NPN) and 2N5684 (PNP), both with 50 amp ratings and having similar power gain and bandwidth figures.

All circuits in Fig. 3 are at least symmetrical because they use complementary transistors. Positive and negative output signals experience the same open-loop output impedance. Fig. 3(a) has low output impedance from the emitters, Fig. 3(b) higher output impedance from the collectors and both may be DC-coupled. Fig. 3(c) cannot be DC-coupled because it uses a single power supply.


Possibly the biggest question facing a designer of modern power amplifiers is which of Fig. 3 should be used: a, b, or c? The figures are fundamental only, and to implement a design we will need to add many embellishments, such as balancing resistors, current limiters, and any one of a host of different drive arrangements.

In each version, the top transistor provides the positive half-cycle of load current and the bottom transistor provides the negative half. First let us compare the three basic ideas.


Fig. 3(a) and (c) are perhaps the most popular at the present state of the art. This is because between them they satisfy all requirements save one if large enough complementary pair transistors are available. Of course, we can always connect transistors in multiple parallel groups to achieve higher current rating, paying due attention to the added problem of equal current sharing.

The one characteristic not provided by Fig. 3(a) or (c) is that of voltage gain. As all their output transistors are connected as emitter followers (otherwise known as

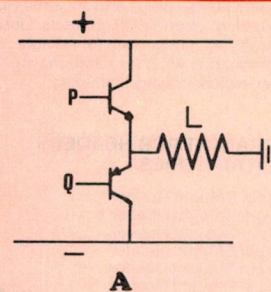
the common collector configuration), the output transistor voltage gain is slightly less than one. Contrast this with Fig. 3(b) where the "common emitter configuration" or "collector output" gives worthwhile voltage gain.



A

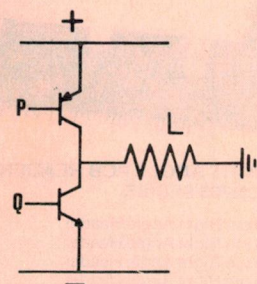

B

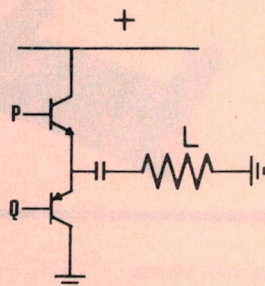

C

Fig. 3a, b, c: Three schemes commonly used in power amplifiers employing complementary output transistors.

OP AMPS Explained

Part 10

Whether it is obvious or not, most power amplifiers are in fact operational amplifiers. They have large open-loop gain and a high degree of negative feedback applied to keep distortion to a low value.

The loads driven by early power amplifiers were almost entirely loudspeakers, but in our modern electronic age many other devices require driving with considerable power. As well as the desire to fill our homes with many watts of pure clean hifi sound from multi-way loudspeaker systems, we now also need to drive many other devices.

Early power amplifiers used a small amount of negative feedback to reduce errors and distortion. Modern amplifiers may use DC-coupling throughout and, because of their open-loop bandwidth, lots of negative feedback can be a feature. Many are in fact power op amps, consisting of early stages with large signal gain followed by output stages capable of high current.

Considering power amplifiers in general, we meet a collection of special terms which may be new to some readers. Let us amuse ourselves by defining these. Considering output stages and their properties (before any feedback is applied) we have:

Single sided output: illustrated in Fig. 1, uses one output power transistor which must be conducting continuously. Current through the load flows from the +12V supply or "rail", via transistor collector and emitter, thence through whatever emitter circuit Z is chosen, to ground or zero. Considering only linear systems, we are interested in cases where the current varies in amplitude but does not stop flowing. Because there is only one supply and the load L is connected to it, current through the load can only be in one direction, ie, downwards in this figure.

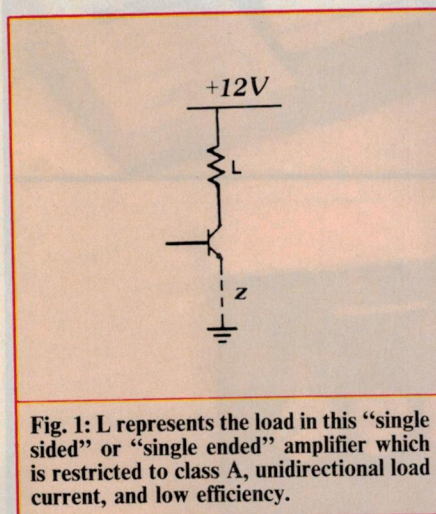


Fig. 1: L represents the load in this "single sided" or "single ended" amplifier which is restricted to class A, unidirectional load current, and low efficiency.

This simple configuration could operate a controlled heating element where the inability to pass current in the reverse direction is of no consequence. However it is inadequate for loads such as loudspeakers or DC motors.

Push-pull output: uses two (or more) power transistors. This allows current to be driven either way through the load L as in Fig. 2. By definition, push-pull designs are driven by two equal but out-of-phase signals at the base circuits, P and Q. Predating transistor circuits by about 30 years when first applied to valve circuits, the name "push-pull" was originally borrowed from Welsh narrow gauge railway terminology.

Historically, valves could only be made to pass current in one direction using electron flow. No one ever got around to inventing a valve for reverse

current direction using positron flow. Because of this, the configurations in Fig. 2 were easily carried across to transistors of one type, shown here using all NPNs. By reversing supply polarity, PNP transistors could be accommodated.

Fig. 2(b) is adapted from the most popular valve design but the need for a transformer was always a problem, being costly, heavy and a prime source of non-linearity distortion.



However the transformer has desirable properties like step-up voltage ratio and primary-secondary isolation, so Fig. 2(b) is still used for many high voltage output requirements. Outstanding among modern uses are the DC-to-DC and DC-to-AC inverter circuits.

Same polarity types, ie both NPN or both PNP, may also form a design known as "single ended push-pull" [Fig. 2(c)]. Only a single end of the load is connected to the amplifier, yet current can flow both ways through the load and push-pull (ie, out-of-phase) drive is required for each transistor base P and Q. When drive P is negative and Q is positive, load current flows form ground through the load via the bottom transistor to the negative rail.

There is a one possible danger; if any circuit delays ever cause both transistor bases to be simultaneously driven positive (even for a few microseconds) a destructively large current would flow from the positive rail straight down through the low impedance path of both transistors to the negative rail. Design precautions to prevent this are mandatory.

Both Figs. 2(b) and (c) are suitable for very large power amplifiers and DC to AC inverters because they require only NPN transistors. In the present state of transistor manufacturing technology, the highest-rated transistors are manufactured only in NPN types. For example, consider the Toshiba 2SD698 rated at 200 volts/600 amps or the Power Tech

for your bucks!

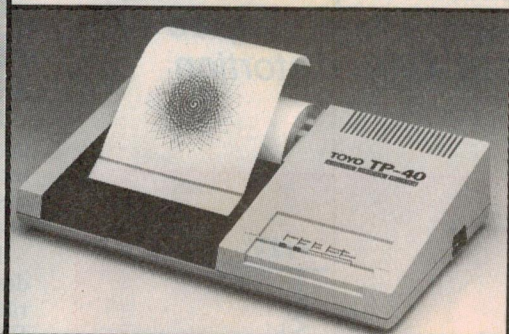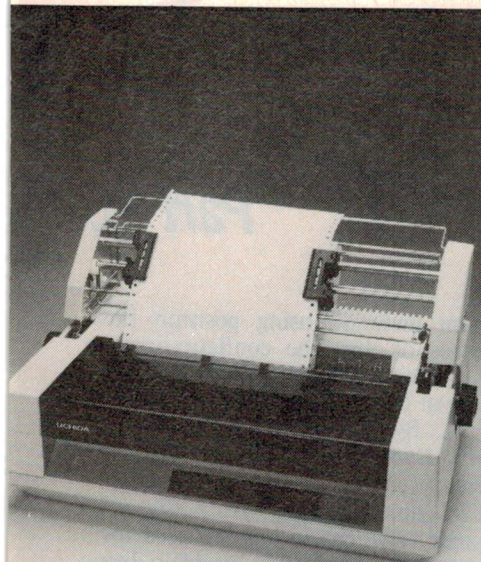

Uchida Daisywheel Printer

Top quality printing at a budget price. Prints at 18 cps and offers a choice of 3 pitches plus proportional. Standard Centronics type interface. Cat X-3270

Save \$120
Now only **\$575**

Tractor feed shown is optional (Cat-3273 @ \$99.50).

Quality Japanese Hi-Res Monitors

Green: X-1222 **\$249** each
Amber: X-1227

TP-40 Four Colour Printer Plotter

Incredible performance at a bargain price. Centronics type interface. Cat X-3245

LAST YEARS PRICE \$229
Now only **\$99**

Apple II software compatible CAT!

Australia's best value 64K Computer. That's the CAT. It's the best of both worlds: the very latest and most powerful hardware, plus the ability to run a very broad range of tried-and-proven software. If you want a machine which is software compatible with thousands of popular programs and which is supported by a reputable dealer, our CAT with emulator is good value. Check the CAT out at your nearest Dick Smith Electronics Computerstop. It purrs.

Save \$232 on CAT system!

	Cat. No.	Normally
Basic CAT Computer	X-7500	\$ 699.00
Disk Drive	X-7505/6	\$ 349.00
Disk Controller	X-7510	\$ 149.00
RF Modulator	X-7550	\$ 34.90
		\$1231.90

SPECIAL OFFER!
VALUE AT ONLY **\$999**



*Or \$81 deposit and \$8.31 per week over 48 months to approved applicants.

Dick Smith Electronics Pty Ltd

COMPUTERSTOP



nearest Dick Smith Electronics Centre.

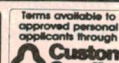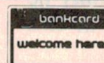

A882

More bytes

First shipment sold out in days . . .
So popular we've had to air-
freight new stocks in . . .
The greatest value you'll ever
see . . .

That's the new Bondwell 14 Portable computer: EXCLUSIVE to Dick Smith Electronics

Simply brilliant! That's the all-new Bondwell 14 portable personal computer. Small wonder it has become one of America's top-selling computers in just a few short months – and now the same thing is happening here in Australia.

It's everything you've ever wanted in a computer and much, much more besides: small enough to go anywhere with you, yet large enough to do virtually any computing job.

This incredibly powerful personal portable operates from the world-standard CP/M system: which means there will always be an incredibly large range of software available for it. For virtually any purpose.

That's if you ever need any other software: the Bondwell 14 comes with over \$1200 worth of top quality business software (including Wordstar word processing!).

Look at what else you get:

- Twin double density, double sided disk drives inbuilt (360K capacity each)
- 9in amber screen inbuilt – for minimum glare and fatigue
- Standard parallel and twin RS-232C interfaces inbuilt
- 16 user definable keys for incredibly easy use
- CP/M version 3.0 including a host of utility software – even a SPEECH synthesiser (it can read to you in English!)
- Ergonomically designed keyboard & durable cabinet for complete portability
- PLUS over all this famous Micropro bundled software: Wordstar, Calcstar, Mailmerge, Datastar, Reportstar – worth over \$1200.00! Cat X-9000

OVER \$1200 WORTH OF SOFTWARE FREE!

All this
for **\$2295**
only

*Or from \$233 deposit and \$18.23 per week over 48 months to approved applicants. Commercial Leasing also available!



Dick Smith Electronics Pty Ltd

COMPUTERSTOP



Your one stop computer shop at your

rie

Rod Irving Electronics

425 HIGH STREET,
NORTHCOTE VICTORIA.
PH:(03)489 8866 489 8131
48-50 A'BECKETT STREET,
MELBOURNE VICTORIA.
PH:(03)347 9251
Mail Order and
correspondence:
P.O. Box 235
NORTHCOTE 3070

Call in at either 2
of our convenient-
ly located stores:
48-50 A'Beckett
St., Melbourne
425 High St.,
Northcote.
Or take advan-
tage of our Mail
Order Depart-
ment.
Write to:

MAIL ORDER CENTRE
ROD IRVING ELECTRONICS
P.O. BOX 235
NORTHCOTE 3070

or phone ...


MAIL ORDER
HOT LINE

481 1436



POSTAGE RATES


\$1-\$9.99	\$1.50
\$10-\$24.99	\$2.00
\$25-\$49.99	\$3.00
\$50-\$99.99	\$3.50
\$100-\$199	\$5.00
\$200-\$499	\$7.50
\$500 plus	\$10.00

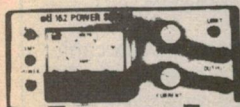

30 V/1 A FULLY PROTECTED POWER SUPPLY

The last power supply we did
was the phenomenally popular
ETI-131. This low cost supply
features full protection, output
variation from 0V to 30V and
selectable current limit. Both
voltage and current metering is
provided. (ETI Dec. '83).


ETI-162 \$49.50

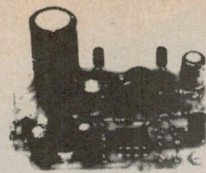

PARABOLIC MICROPHONE

Build a low cost parabola, along
with a high gain headphone
amplifier to help when listening
to those natural activities such
as babbling brooks, singing
birds of perhaps even more
sinister noises. The current cost
of components for this project
is around \$15 including sales
tax, but not the cost of batteries
or headphones. (EA Nov. '83)


83MA11 \$15.00

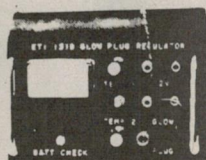

MODEL ENGINE IGNITION SYSTEM

Get sure starts every time and
no more glow plug burnouts on
your model engines. (ETI June
'83)


ETI-1516 \$41.50

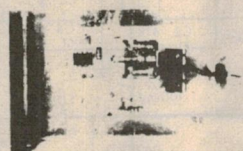

CAR IGNITION KILLER

Most car burglar alarms are
easily circumvented, but not
this cunning "Ignition Killer".
This sneaky anti-theft device
uses a 555 timer to place an
intermittent short circuit across
the points. Until disabled by its
hidden switch the circuit effective-
ly makes the car undrive-
able — a sure deterrent to
thieves! (EA Feb. '84).

84AU1 \$16.95
(Our kit includes the box)

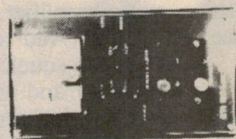


LOW OHMS METER

How many times have you
cursed your Multimeter when
you had to measure a low-value
resistance? Well with the "Low
Ohms Meter" you can solve
those old problems and in fact
measure resistance from 100
Ohms down to 0.005 Ohms.
(ETI Nov. '81).

ETI-158 \$34.50

VIDEO AMPLIFIER

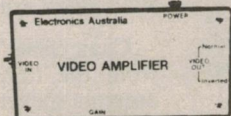

Bothered by smeary colours,
signal beats and RF inter-
ference on your computer dis-
play? Throw away that cheap
and masty RF modulator and
use a direct video connection
instead, it's much better! The
Video Amplifier features adjust-
able gain and provides both
normal and inverted outputs.
Power is derived from a 12V DC
plugback supply. (EA Aug. '83).


83VA8 \$15.00



MOSFET POWER AMPLIFIER

Employing Hitachi Mosfets, this
power amplifier features a 'no
compromise' design, and is
rated to deliver 150 W RMS
maximum and features
extremely low harmonic, tran-
sient and intermodulation dis-
tortion. (ETI Jan. '81).


Cat. ETI 477 \$63.00

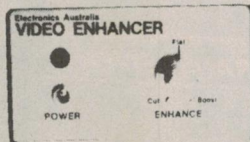

VIDEO ENHANCER 100's SOLD

Like tone controls in a hi-fi
amplifier, touch up the signal
with this Video Enhancer.
(EA Oct. '83).


83VE10 \$35.00

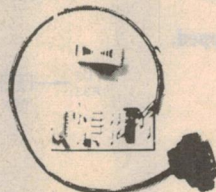

RADIOTELETYPE CONVERTER FOR THE MICROBEE

Have your computer print the
latest news from the inter-
national shortwave news ser-
vice. Just hook up this project
between your shortwave
receiver's audio output and the
MicroBee parallel port. A simple
bit of software does the decod-
ing. Can be hooked up to other
computers too.

(ETI Apr. '83) \$20.00

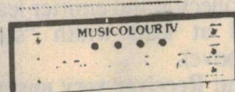

MUSICOLOR IV

Add excitement to parties, card
nights and discos with EAs
Musicolor IV light show. This is
the latest in the famous line of
musicolors and it offers
features such as four channel
"color organ" plus four channel
light chaser, front panel LED
display, internal microphone,
single sensitivity control plus
opto-coupled switching for
increased safety. (EA Aug. '81).

81MC8 \$84.00



FUNCTION GENERATOR

This Function Generator with
digital readout produces Sine,
Triangle and Square waves
over a frequency range from
below 20Hz to above 160Hz
with low distortion and good
envelope stability. It has an
inbuilt four-digit frequency
counter for ease and accuracy
of frequency setting. (EA April
'82)

82AO3A/B \$79.50

THE BRILLIANT SERIES 5000

STILL GOING STRONG
INDIVIDUAL COMPONENTS TO MAKE UP A
SUPERB HIFI SYSTEM.

By directly importing and a more technically orientated organisa-
tion, ROD IRVING ELECTRONICS can bring you these products at
lower prices than their competitors. Enjoy the many other advan-
tages of RIE Series 5000 kits such as "Super Finish" front panels at
no extra cost, top quality components supplied throughout. Over
1,000 Sold.

For those who haven't that time and want a quality hi-fi, we also sell
the Series 5000 kits Assembled and Tested.



POWER AMPLIFIER


WHY YOU SHOULD BUY A "ROD IRVING ELECTRONICS"
SERIES 5000 POWER AMPLIFIER.

- ★ 1% Metal Film resistors are used where possible.
 - ★ Aluminium case as per the original article.
 - ★ All components are top quality.
 - ★ Over 1000 of these kits now sold.
 - ★ Super Finish front panel supplied at no extra cost.
- Please note that the "Superb Quality" Heatsink for the Power
Amplifier was designed and developed by ROD IRVING
ELECTRONICS and is being supplied to other kit suppliers.

SPECIFICATIONS: 150 W RMS into 4 ohms
POWER OUTPUT: 100 W RMS into 8 ohms (±55 V SUPPLY)
FREQUENCY RESPONSE: 8 Hz to 20 KHz +0.04 dB 2.8 KHz to 65
KHz +0.3 dB NOTE: These figures are determined solely by passive filters
INPUT SENSITIVITY: 1 V RMS for 100 W output
HUM: 100 dB below full output (flat)
NOISE: 116 dB below full output (flat) 20 KHz bandwidth
2nd HARMONIC DISTORTION: <0.001% at 1 KHz 10 0007% on Prototypes at 100 W output using a
±56 V SUPPLY rated at 4A continues <0.003% at 10 KHz and 100 W
3rd HARMONIC DISTORTION: <0.0003% for all frequencies less than 10 KHz and all powers below
clipping
TOTAL HARMONIC DISTORTION: Determined by 2nd Harmonic Distortion (see above)
INTERMODULATION DISTORTION: 0.003% at 100 W (50 Hz and 7 KHz mixed 4:1)
STABILITY: Unconditional

Cat. K44771

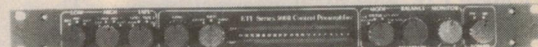Normally \$319, \$299
packing and post \$10



PREAMPLIFIER

THE ADVANTAGES OF BUYING A "ROD IRVING ELECTRONICS"
SERIES 5000 PREAMPLIFIER KIT ARE:

- ★ 1% Metal Film Resistors are supplied.
 - ★ 14 Metres of Low Capacitance Shielded Cable are supplied (a
bit extra in case of mistakes).
 - ★ English "Lorlin" switches are supplied (no substitutes here).
 - ★ Specially imported black anodised aluminium knobs.
- Available Assembled and Tested. (We believe that dollar for dollar
there is not a commercial unit available that sounds as good.)

SPECIFICATIONS:
FREQUENCY RESPONSE: High level input: 15 Hz 130 KHz +0. -1 dB Low Level input: conforms to
RIAA equalisation ±0.2 dB
DISTORTION: 1 KHz <0.003% on all inputs (limit of resolution on measuring equipment due to noise
limitation)
S/N NOISE: High Level input: master full with respect to 300 mV input signal at full output (1.2V) >92 dB
flat > 100 dB A weighted MM input: master full with respect to full output (1.2V) at 5 mV input 50 ohms
source resistance connected >86 dB flat >86 dB A weighted MC input: master full with respect to full out-
put (1.2V) and 200 uV input signal >71 dB flat >75 dB A-weighted

Cat. K44791

Normally \$289, \$259
PACKING AND POSTAGE \$10



THIRD OCTAVE GRAPHIC EQUALIZER

SPECIFICATIONS:
BANDS: 28 Bands from 31.5 Hz to 16 KHz.
NOISE: <0.008 mV, sliders at 0, gain at 0 (-102 dB0).
20 KHz BANDWIDTH DISTORTION: 0.007% at 300 mV signal,
sliders at 0, gain at 0; maximum 0.01%, sliders at minimum.
FREQUENCY RESPONSE: 12 Hz-105 KHz, +0. -1 dB, all controls
flat.
BOOST AND CUT: 14 dB.
Cat. K44590

1 Unit...\$199


2 Units...\$379

PACKING AND POSTAGE \$10

SERIES 4000 SPEAKERS

- 8 Speakers On \$295
- 8 Speakers with Crossovers \$499
- Speaker Boxes (assembled with
grill and speaker cutout) \$299
- Crossover Kits \$199
- Complete kit of parts (speakers,
crossovers, screws, innerband
boxes) \$799
- Assembled, tested and ready
to hook up to your system \$849

Errors and Omissions Excepted

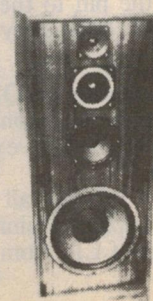



UHF Transceiver

Symptom: PLL will not lock.

Cause: Switching diodes D20, D21, D23, do not saturate as their internal impedance is too high at this frequency (40-50MHz).

Cure: Replace with BA244 diodes. Later kits supplied with BA244 diodes.

Symptom: PLL will not lock.

Cause: L16 (base Q23) incorrectly supplied as 10mH.

Cure: Change L16 to 10 μ H.

Symptom: PLL will not lock.

Cause: Capacitors C78, C79 (5.6pF), C80 (4.7pF) and C81 (3.3pF) supplied for VCO physically too large.

Cure: Replace with physically smaller capacitors.

Symptom: PLL will not lock. VCO will not run.

Cause: Statically damaged Q18, Q19.

Cure: Replace Q18, Q19.

Symptom: Low RF power output.

Cause: Transmitter high pass filter operating at incorrect frequency.

Cure: Rewind L19, L20, L21 with 5mm diameter, not 10mm.

Symptom: Low RF power output.

Cause: Poor or no earthing of predriver and driver transistor cases (Q25, MRF629; Q26, MRF629.)


Cure: Use PCB pins to earth predriver and driver transistor cases. PC board provides for this. A good low impedance earth is essential for correct operation. Solder the pin to the metal case of the transistor. Use plenty of heat.

Symptom: Low RF output from transmitter tripler (Q24, 2N3948).


Cause: (a) Component leads too long; (b) L18 does not have enough inductance to resonate.

Cure: Shorten all component leads around tripler to minimum. Increase the diameter of L18 from 1/8in to 9/64in.

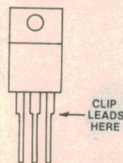Below: this diagram shows how the leads of the RF output transistor should be clipped.



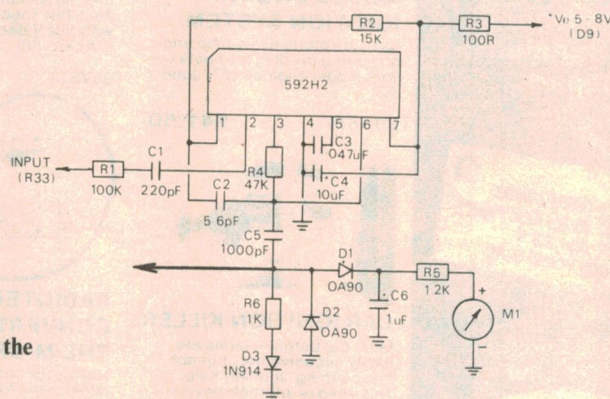Right: adding an RF power meter. Position the extra wire near the antenna socket.



Symptom: Low RF power output (2W).

Cause: Excessive collector and emitter lead lengths on RF output transistor Q27, MRF660.

Cure: Collector and emitter leads must be clipped at lead width "step" (see diagram above).

Symptom: Receiver very unstable.

Cause: BRF90 (Q7) has excessive gain.

Cure: Change R20 bias resistor from 10k Ω to 15k Ω .

Symptom: When the receiver is muted, but operating with a high volume level setting, a faint hiss can be heard from the speaker.

Cause: Audio leakage through the audio amplifier.

Cure: Add a 1N914 diode in series with the squelch output (pin 14) of the MC3357 and rewire as shown in the accompanying circuit. Note, however, that this causes the squelch to open and close with a "thump". (See diagram next page.)

General comments

Voltage regulators: zener diodes D22 and D19 should be 400mW types. Early kits were supplied with 1W types, but these do not regulate correctly due to low idle current. One symptom of this poor regulation is that, if a mains power supply is used, hum may appear on transmit unless the supply is particularly pure.

RF power meter: It is possible to add an RF power output indicator with very little effort. Connect a piece of single conductor cable (bell wire) from the vicinity of the antenna socket to the junction of C5 (1000pF)

and R6 (1k Ω) on the S meter circuit board. Position the antenna socket end of the wire to give full scale reading on transmit (when correctly loaded) and secure to the circuit board using spare wax from the VCO or some other suitable adhesive.

Coax cable: The piece of coax cable from the transmitter output to the antenna socket can be replaced with a piece of tinned copper wire. This is easier, and may increase the transmitter power output marginally. It may also increase the spurious radiation slightly, but this may be regarded as inconsequential at this frequency.

FEEDBACK ON THE **UHF/VHF** **Transceivers**

Two of the most popular projects described in this magazine in recent years have been the two amateur transceivers available in kit form from Dick Smith Electronics: the "Explorer 1" UHF (70cm) transceiver in September, October, and November 1983 and the "Commander" VHF (2m) transceiver in June and July 1984. Over 700 UHF and 400 VHF sets have been built at the time of writing.

Naturally, with projects of this complexity, there will always be a small proportion of builders who encounter problems. Fortunately, Dick Smith Electronics provided a backup service whereby these problems could be sorted out and, at the same time, categorised for the benefit of other constructors. The following is a summary of the problems prepared by Garry Crapp, VK2YBX/T, General Manager of DSE Research and Development Division.

By far the most predominant reason for non-operation is dry solder joints. It should be stressed that most semiconductors can withstand 300°C at 1.5mm from the junction for 10 seconds. They are rarely destroyed by excessive heat. Constructors should not be scared to use adequate heat when soldering.

At the risk of repeating what has been said many times before, a proper soldered joint can only be made when the pieces of metal to be joined are heated to a

temperature which will melt the solder. It is not sufficient to melt the solder with the iron; the joint must be hot enough to do this also.

Some constructors have changed components in an attempt to achieve better transmitted audio, easier VCO lock, extra transmitter power etc. In this regard it should be appreciated that the transceiver was designed to satisfy the Department of Communications Radio Bulletin RB250. There are no specifications covering amateur equipment, but RB250 covers UHF CB equipment, and it was felt that this was a suitable standard to adopt.

In all the cases investigated so far, such modifications have caused the set to transgress the RB250 specifications. For this reason, modifications are not recommended unless the builder is fully aware of the RB250 specifications and has the facilities to make the appropriate measurements.

Apart from poor soldered joints and other assembly faults, the following less obvious problems were encountered.



8 SECTOR BURGLAR ALARM KIT...

REF: EA Jan 1985

★ 2 delay sectors ★ 6 instant sectors ★ Steel box ★ Price includes battery ★ Siren driver ★ Variable exit/entry delay ★ Can use N.C. & N.O. on the one circuit!!
Cat. KA-1580



NEW KIT

ONLY \$139

NOW OPEN BURANDA QUEENSLAND

ELECTRIC FENCE

Ref: EA September 1982



\$15.00

Mains or battery powered, this electric fence controller is both inexpensive and versatile. It should prove an adequate deterrent to all manner of livestock. Additionally, its operation conforms to the relevant clauses of Australian standard 3129. (Kit does not include automotive ignition coil which is required).

Cat. KA-1109

CQAM STEREO DECODER KIT - Ref: EA October 1984
Set of parts for this project including PCB, 10uH choke, MOC13020 IC. (Whistle filter coil extra - Cat. EE-3814 ONLY \$19.95)
Cat. KA-1555 **ONLY \$19.95**

DRILL SPEED CONTROLLER **NEW**

This brand-new design gives you better speed regulation over previous drill controller designs. It's also easier to make as all parts are mounted on the PCB. All parts supplied including special high voltage MR754 diode.

Cat. KA-1555 **ONLY \$24.95**

Ref: EA Dec 1984

ETI 446 AUDIO LIMITER - This simple project is used as a volume compensator for P.A. etc.
Cat. KE-4092

GREAT VALUE AT \$12.00


RAILMASTER KIT

REF: EA SEPTEMBER 1984

This is the most up to date train controller kit we've seen in a long time. It offers all those wanted features including inertia, full overload protection and walk around throttle. Kit includes front panel, correct console box and all parts.

Cat. KA-1560


\$79.95

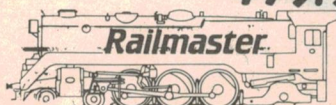

Fast talker with all the right answers **MultiModem**

Down the street or across the world, MultiModem speaks the language. ★ 300 Baud full duplex, 1200 Baud half duplex or 600 Baud half duplex, answer or originate ★ CCITT and Bell standards ★ Auto answer and connect ability ★ Plugs straight in (hardwire phone) ★ Superior VLSI chip performance: works reliably with -43dBm signal with S/N ratio of 6dB ★ Telecom approval C84/37/1135

Cat. XC-4820

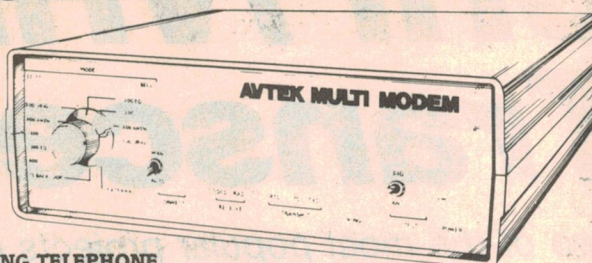


only \$349 INCLUDING TELEPHONE

DELUXE METAL DETECTOR **NEW KIT**

REF: EA December 1984

This very sensitive unit works as well as units costing hundreds more! Features special English-made quality case and pre-wound and sealed head assembly. Looks just like the \$700 plus units! (All parts supplied).
Cat. KA-1554

\$239

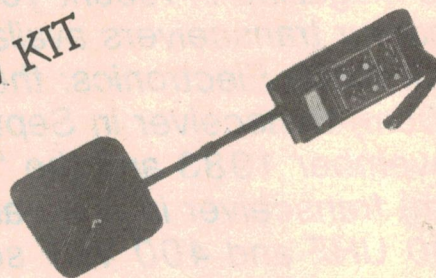

Jaycar ELECTRONICS

IN-CIRCUIT TRANSISTOR

TESTER - Ref: EA September 1983.
When built this simple kit will enable you to 'TEST IN-CIRCUIT' transistors, SCR's and diodes without the need to desolder!
Cat. KA-1119

ONLY \$15.00 GREAT VALUE

LCD THERMOMETER - Ref: EA Feb '82.
15mm high 3 1/2 digit readout unit that can measure from around 100 degrees C to below freezing. Very accurate - supplied with 2 sensors.
Cat. KA-1404

**NORMALLY \$74.50
A FEW LEFT AT ONLY \$64.50**

LCD HEARTRATE MONITOR

If you are concerned about the condition of your heart then this is the unit for you. Large liquid crystal readout and all readings are taken by optical sensors - great value to those who exercise!
Cat. KA-1466

TREMENDOUS VALUE AT \$69

ETI 1515 MOTOR SPEED

CONTROLLER - This kit enables you to control the speed of electric motors such as found in drills, saws, grinders, blenders etc. Reasonably constant speed over varying loads.
Cat. KE-4031

NORMALLY \$19.95 NOW \$14.95

NEW

NOW OPEN BURANDA QUEENSLAND

STEAM SOUND SIMULATOR

Ref: EA December 1984
Features infra-red optical switch to synchronise "chuffs" with wheel rotation.
Cat. KA-1562

\$15.95


DIESEL SOUND SIMULATOR WITH LIGHTING CIRCUIT FOR RAILMASTER

REF: EA NOVEMBER 1984

You will be amazed how authentic this kit sounds. Kit includes PCB and all parts for sound effects as well as all the components for the lighting circuit.

Cat. KA-1561

\$19.95

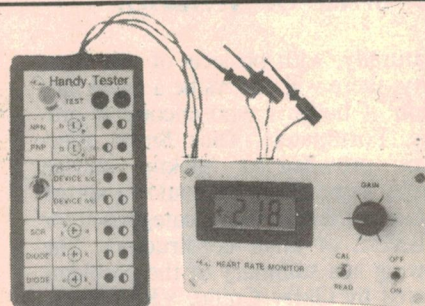

OUT THEY GO!! SUBWOOFER AMP SPEAKER CABINET

Ref: EA July 1982
We have a few left of these quality speaker box cabinet kits. The kit is finished in an attractive black vinyl with a modern speaker cloth cover, factory mounted on a frame. The specially made port tube is provided along with speaker connector etc.

**NORMALLY \$79 SAVE \$30
THIS MONTH \$49**

(Please allow \$8 for post & packing as they are fairly heavy).
Cat. KA-1454 (Subwoofer speaker extra)
Subwoofer speaker to suit Cat. CW-2119 **\$89.50**



SEE OUR OTHER ADS ON PAGE 13 FOR ADDRESS PANEL AND OTHER INFORMATION

UNBELIEVABLE KIT CLEARANCE SALE

JAYCAR IS CLEARING THE DECKS FOR NEW KITS IN '85

SENSATIONAL PRICES ON 5000 AMP-SYSTEM KITS

Check the SPECIAL PRICES for the famous ETI 5000 series deal of a lifetime.

**FAMOUS JAYCAR "BLACK MONOLITH"
SERIES AMP - NORMALLY \$319.00
THIS MONTH**

\$295 SAVE \$24.00

For further savings check the package deal below

**FAMOUS JAYCAR "BLUEPRINT" 5000
SERIES PREAMP - NORMALLY \$299
THIS MONTH**

\$265 SAVE \$34.00

Check below for package price FURTHER savings!

**FAMOUS JAYCAR 1/3 OCTAVE GRAPHIC
EQUALISERS! (5000 SERIES)
NORMALLY \$199 EACH
THIS MONTH**

2 FOR \$300!!

For FURTHER savings check

THIS SPECTACULAR PACKAGE DEAL

PACKAGE DEAL No.1

Buy the 5000 Black Monolith Power Amp and 5000 Blueprint Preamp TOGETHER for only \$498!

That's right, save over \$120 on normal prices or over \$60 if bought separately from this months SPECIAL prices!

PACKAGE DEAL No.2

Buy the following:

Power Amp 5000 "Black Monolith"	NORMALLY \$319.00
Preamp 5000 "Blueprint"	\$299.00
Graphic 5000 Equalisers (2 off)	\$398.00
	NORMALLY \$1016.00

THIS MONTH YOU GET THE LOT FOR

ONLY \$699!!!

THAT'S A MASSIVE SAVING OF \$317 (i.e. YOU VIRTUALLY GET THE "BLACK MONOLITH FREE) EVEN AT THE SPECIAL INDIVIDUAL PRICES IN THIS AD IT IS STILL A MASSIVE SAVING! - Special freight deal: anywhere in Australia \$12!! REMEMBER! WE TAKE NEARLY ALL THE CREDIT CARDS & FINANCE CAN BE ARRANGED ON THE SPOT.

NOTE: If demand temporarily exceeds our ability to supply kits we may part ship. This will get you started on what is after all a fairly ambitious project. We will only honour the prices, however, if you order NOW. . .

ARE WE FAWLTY?

WE'RE DOING IT ON PIANO KITS TOO!

**FAMOUS JAYCAR "LYREBIRD" 73 & 88
NOTE PIANOS AT THE LOWEST COST EVER**

Even lower than our low, low prices in September last year. We are phasing these kits out now for new lines in '85. They are still technically superior to many more expensive ready-built AND have better tone, touch sensitivity etc for **FAR LESS MONEY.**

**73 NOTE: NORMALLY \$475
ON SPECIAL LAST SEPT. \$375**

Jaycar ELECTRONICS THIS MONTH \$325

SAVE AN ASTOUNDING \$150!!

**88 NOTE: NORMALLY \$589
ON SPECIAL LAST SEPT. \$425**

THIS MONTH \$399

SAVE AN UNBELIEVABLE \$190!!

Remember each kit is the same quality as our normal kits. The kits contain a stand (similar BUT NOT THE SAME) as the one shown in the illustration. A beautifully imported Italian keyboard is part of each kit as well as a realistic looking soft (sustain) pedal (imported from England) is also supplied. All pre-cut woodwork is supplied.



**GAD!
they've never
been
cheaper!!**
**JAYCAR
ELECTRONICS**


ARE WE BALMY? IS THE SUMMER SUN GETTING AT US?

This month you can grab the KJ-6655 Hall Effect kit for - wait for it - **ONLY \$19.95!** That's right! \$10 off normal low price!

**NOW SAVE \$10
ONLY \$19.95**


HALL EFFECT SWITCH VANE INTERRUPTED

**NORMALLY \$19.95
THIS MONTH \$16.95**

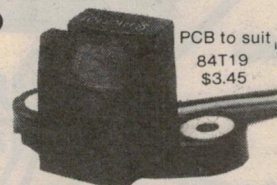

PCB to suit
84T19
\$3.45

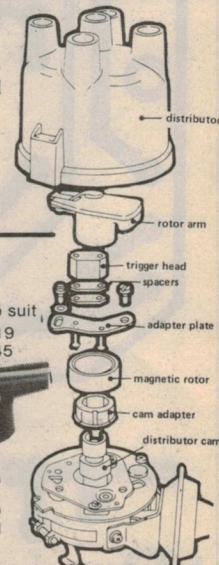If you have a car that won't take the Jaycar KJ-6655 Hall Effect Kit (i.e. an Australian six or V8) this could be for you! It is the SIEMENS (German) made Hall Switch. It will operate from -30 to +130°C. A simple soft iron vane cut with appropriate slots will commutate the unit.
Cat. HK-2101



the load switch. If all is well, the power LED will light and you will be able to vary the output voltage from 3V to 30V using the range switch and the voltage control pot.


Check that the voltage reading on the supply meter and on your multimeter are the same. Note the vacant component position adjacent to the 330k Ω and 33k Ω resistors. This will allow you to trim the voltage readings by adding a high value resistor if necessary.

Assuming that all is well, open the load switch, select the 0-15V range and wind the voltage control fully anticlockwise. Now set the current limiting control to about half way on the 1A range, select the 1A range on your multimeter and close the load switch.



The multimeter should indicate a current of about half an amp, although the supply's meter will probably show something quite different at this stage (don't forget to switch the meter to "amps"). Adjust the current limiting control so that the multimeter reads 1A, then adjust trimpot VR3 so that the supply's meter reads the same.

Finally, vary the current limiting control and check that the meter reading corresponds closely to that on the multimeter. Your 30V/1A Power Supply is now ready for use.

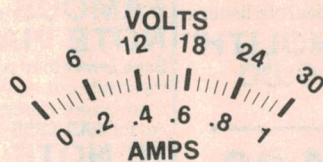Below, right: actual size reproduction of the front panel artwork. Finished boards and panels will be available from parts retailers.



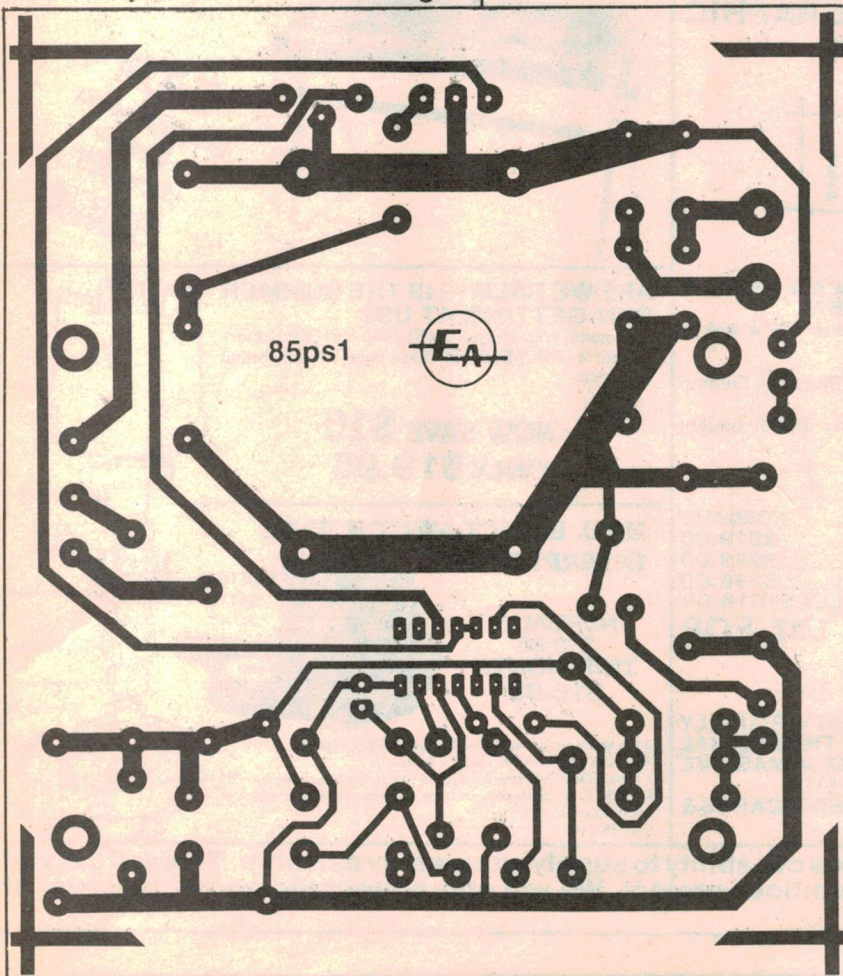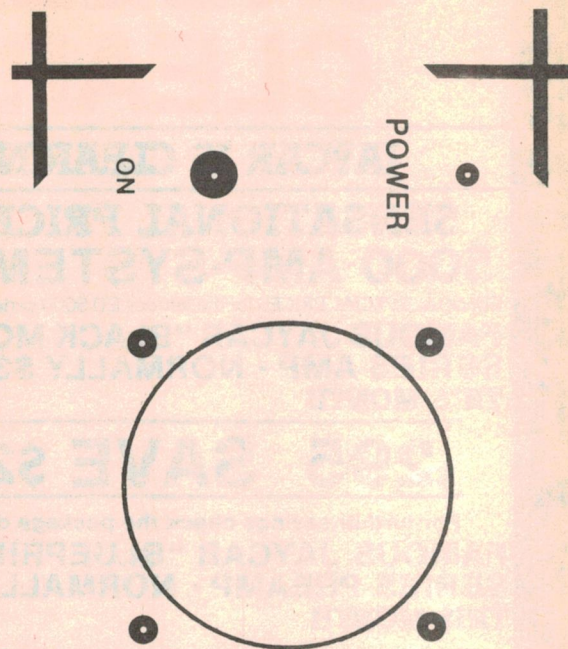Use this actual-size artwork to re-calibrate the meter.



At left is an actual size reproduction of the PC artwork.

Benchtop power supply

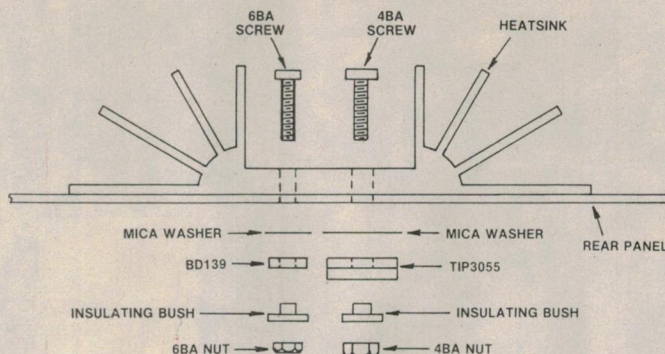


Fig. 2: mounting details for the power transistors and heatsink.

to the rear panel using a cord clamp grommet and the active and neutral wires terminated at the fuseholder and power transformer respectively. The mains earth wire should be connected to one of the solder lugs and a separate earth lead run to the rear panel.

We recommend that heat shrinkable tubing be fitted to the fuseholder, transformer and mains switch terminations. This will prevent accidental contact with the mains while the unit is being worked on. Make sure


that you use mains-rated hookup wire for the connections to the mains switch.

Note that the mains switch must be of all-plastic construction and should not be a miniature type.

Finally, go over your work and make sure that all the wiring is correct. Everything OK? You are now ready for the smoke test!

Setting up

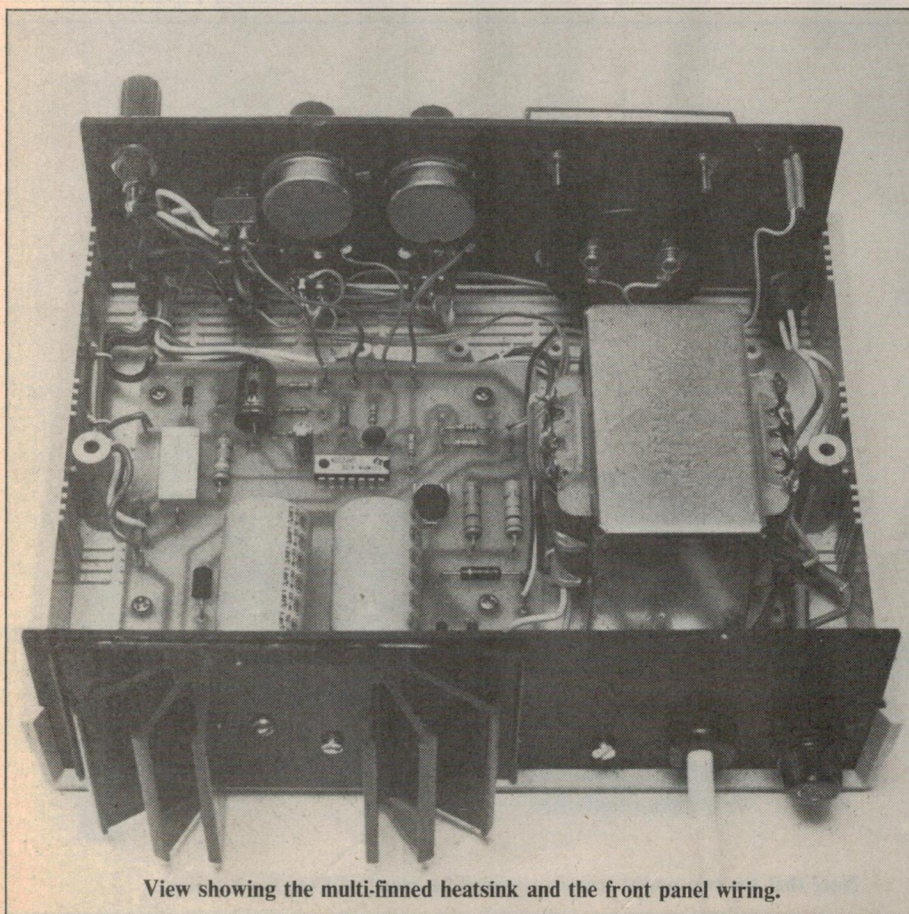Connect your multimeter across the output, switch the supply on and close



View showing the multi-fin heatsink and the front panel wiring.

PARTS LIST

- 1 PC board, code 85ps1, 105 x 111mm
- 1 plastic case, 200 x 160 x 70mm (W x D x H), with metal rear panel, Altronics H0480
- 1 Scotchcal front panel artwork, 195 x 65mm
- 1 mains transformer, 30VAC and 24VAC at 1A, Arlec 6672 or equivalent
- 1 SPST 240V 2A toggle switch, all plastic construction (not miniature type)
- 3 DPDT miniature toggle switches
- 1 SPDT miniature toggle switch
- 1 MU45 0-1mA panel meter
- 3 binding post terminals: 1 red, 1 black, 1 green
- 1 mains cord and plug
- 1 cord clamp grommet
- 1 fuseholder, panel mount type
- 1 150mA fuse
- 1 heatsink, high efficiency fan type, 105 x 58mm
- 4 solder lugs
- 15 PC stakes
- 2 plastic knobs (black)
- 1 metre mains rated cable
- 2 metres hookup wire (10 x 0.2mm)
- 4 stick-on rubber feet

Semiconductors

- 1 TIP3055 NPN transistor plus mounting hardware (mica washer and insulating bush)
- 1 BD139 NPN transistor plus mounting hardware
- 5 1N4002 diodes
- 1 33V 1W zener diode
- 1 red LED plus mounting bezel
- 1 LM723, μ A723 voltage regulator IC

Capacitors

- 2 2500 μ F 50V axial electrolytics
- 1 100 μ F 50V axial electrolytic
- 1 4.7 μ F 16V PC electrolytic
- 1 0.1 μ F metallised polyester (greencap)
- 1 820pF ceramic

Resistors (1/4W, 5% unless stated)

- 1 x 330k Ω , 1 x 33k Ω , 1 x 4.7k Ω , 1 x 2.2k Ω 1W, 1 x 1.8k Ω , 1 x 1.2k Ω , 1 x 1k Ω , 1 x 470 Ω 1/2W, 1 x 270 Ω , 1 x 100 Ω , 1 x 3.9 Ω 1W, 1 x 1.5 Ω 5W, 2 x 1 Ω 1W.

Potentiometers

- 1 5k Ω linear potentiometer
- 1 1k Ω miniature horizontal trimpot
- 1 500 Ω linear potentiometer

Miscellaneous

Machine screws and nuts, heat shrinkable tubing, cable ties, etc.

We estimate that the parts for this project will cost

\$60-65

This includes sales tax.

when they are being installed. Transistors Q1 and Q2 should be mounted at full lead length.

We recommend that PC stakes be used to terminate all external lead connections. You will require 15 PC stakes in all.

Once the PC board has been completely assembled, attention can be turned to the case. Spray the Scotchcal artwork with a hard-setting clear lacquer (eg, Estapol) to prevent scratches, then carefully affix it to the front panel. The artwork can then be used as a template for drilling holes for the front panel hardware.

You will also have to drill holes in the rear panel for the fuse holder and for mains cord entry. The wiring diagram and the photographs show the positions for these holes.

The major items of hardware can now be positioned in the case. The PC board is secured to four internal mounting posts using self-tapping screws while the power transformer is bolted to the case using machine screws and nuts. Note the solder lug under the nut nearest to the rear panel.



We used medium duty hookup wire (10 x 0.2mm) for all the wiring which carries the full supply current, and light duty hookup wire for the pot, meter and LED wiring.

Heatsinking for the power transistors is provided by the rear panel and by an external multi-finned heatsink. The heatsink used in the prototype is a standard high-efficiency fan type measuring 105 x 75mm. This must be trimmed to a length of 58mm before installation.


The procedure is to install the rear panel and to then mark and drill the mounting holes for the power transistors. This done, the rear panel can serve as a template for the heatsink mounting holes.

Both transistors must be insulated from the rear panel using mica washers and insulating bushes (see Fig. 2). Smear heatsink compound on all mating surfaces (including the rear of the heatsink), then bolt the assembly together using machine screws and nuts. Finally, use your multimeter to check that the metal tag of each device is indeed isolated from the rear panel and the heatsink.

The three-core power flex is anchored

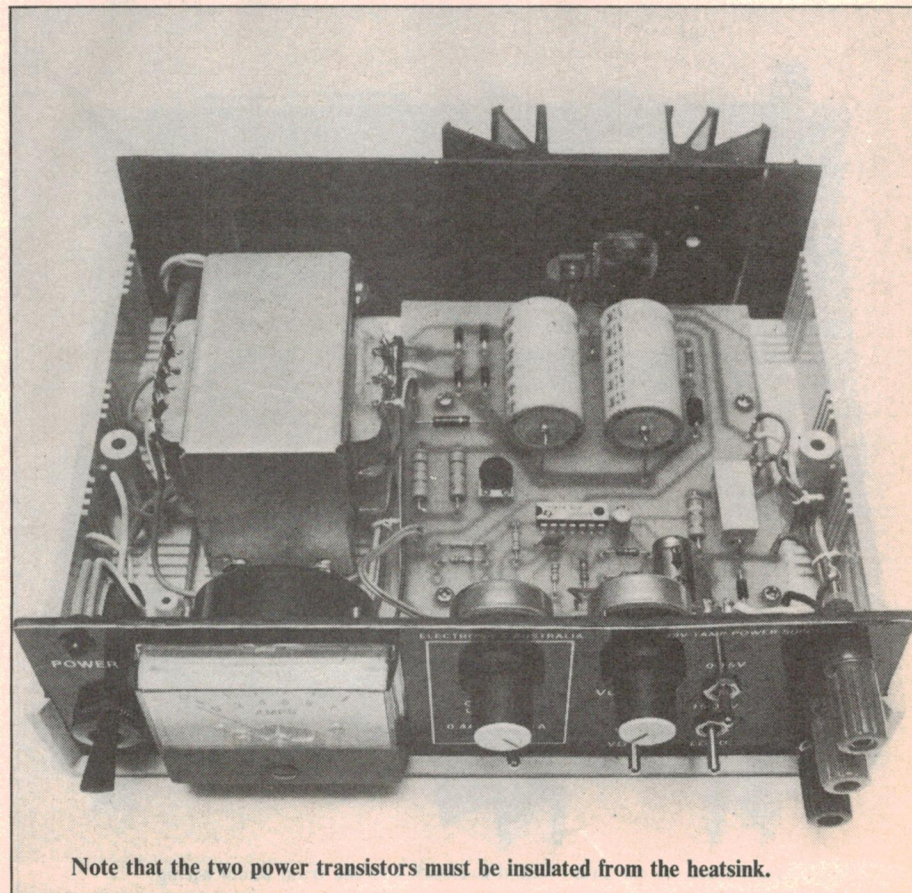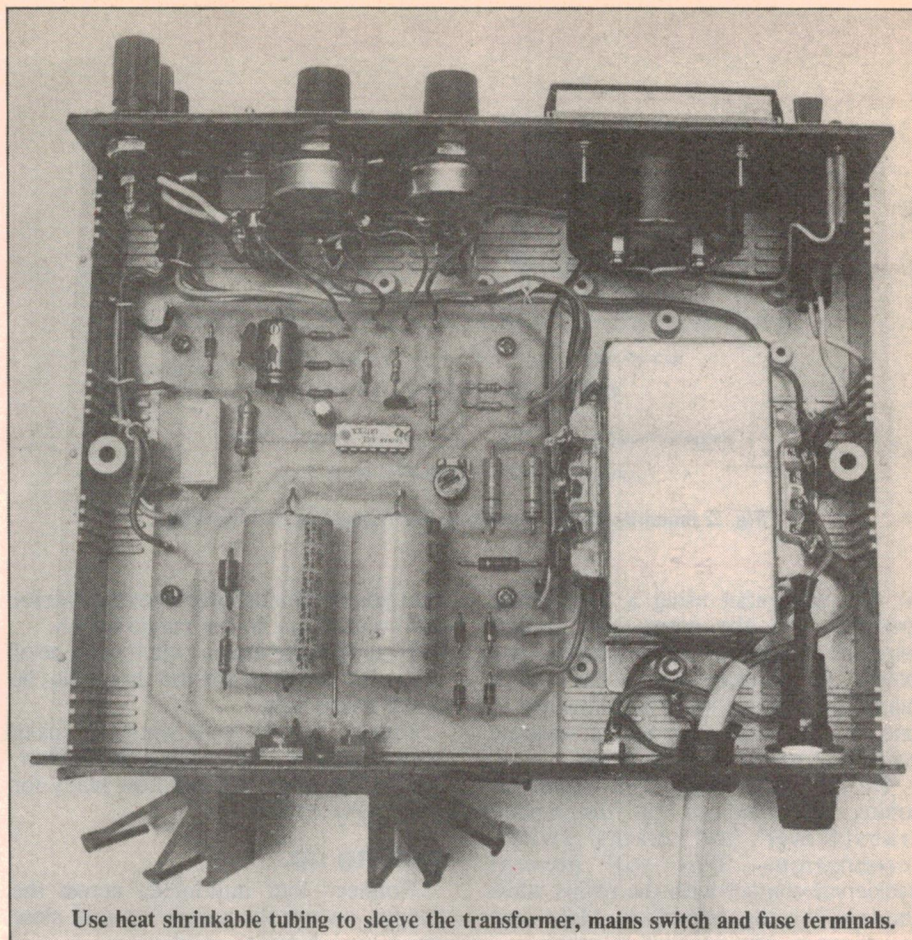

Benchtop power supply

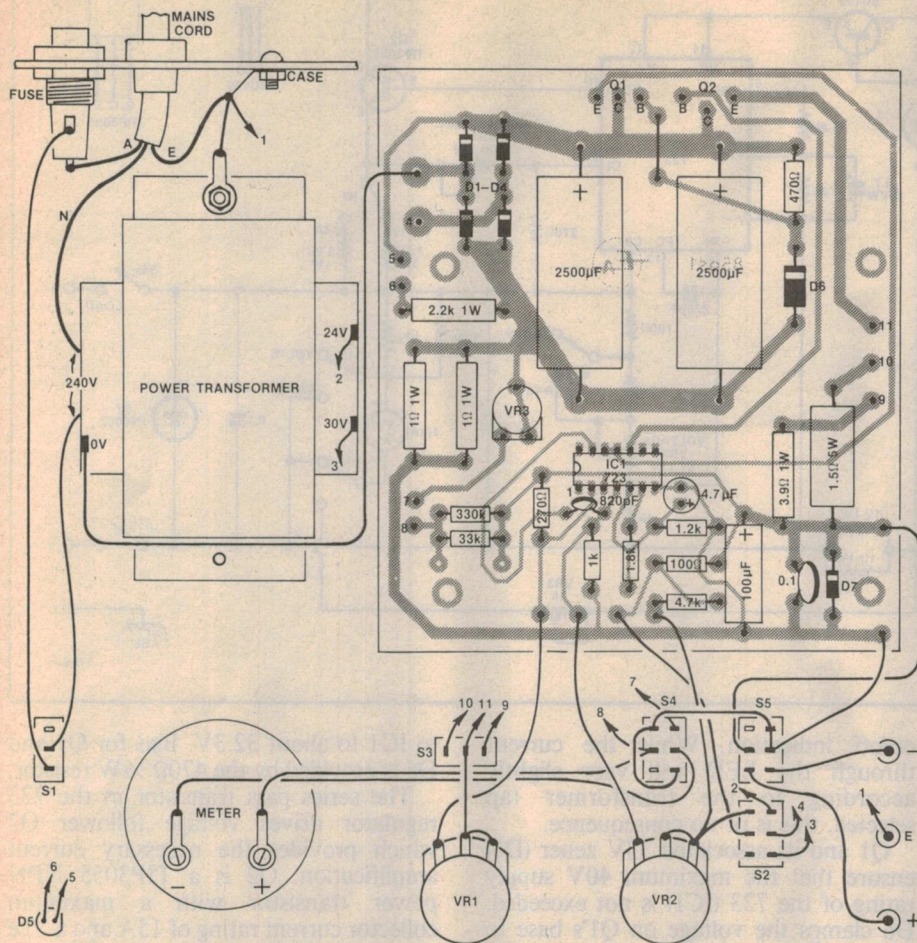

Use medium duty hookup wire (10 x 0.2mm) for all wiring which carries the full supply current (see text). Take care with the orientation of the semiconductors and electrolytic capacitors.

adequate for the job at hand.

Unfortunately, having set the input voltage on Q2's collector to obtain a maximum 30V output, there is a potential dissipation problem when drawing high current at low voltage. This problem was overcome by switching the secondary winding of the transformer.

Thus, for output voltages above 15V, S2a selects the 30V tap on the transformer. For outputs less than 15V, the 24V tap is selected to reduce the dissipation in Q2.

Voltage regulation

Let's now take a look at how the voltage regulator works.

The error amplifier in the 723 is connected as a non-inverting amplifier with variable gain. The input to this amplifier is fixed at about 2.8V by the potential divider formed by the 1.8k Ω and 1.2k Ω resistors. The input to this divider is the reference voltage source built into the 723 chip. A 4.7 μ F capacitor is included to improve the output noise characteristic.

On the 0-15V range, switch 2b is closed, so the feedback resistance (the resistance between the output of the supply and the inverting input of the error amplifier) can be varied between 100 Ω and 5k Ω . This corresponds to an amplifier gain of between 1.1 and 6.1, or an output voltage of between 3.1V and 17.4V.

With switch 2b open, the gain of the amplifier is adjustable between 5.8 and 10.8, corresponding to output voltages of between 16.5V and 30.8V.

Depending upon the position of S3, the load current from the emitter of Q2 flows through either a 1.5Ω or 3.9Ω resistor to derive a voltage for the current limit function. The resulting voltage is applied to a potential divider network (VR1 and 270Ω in series) and thence to the base of the internal current-limit transistor in the 723.

As we've already seen, the current-limit transistor controls the series pass transistor in the 723 regulator. This, in turn, controls voltage-follower Q2. When the current reaches a preset level, the drive to Q2 is reduced and

current limiting takes place.

S5 is the load switch and is used to switch the lines leading to the output terminals. This facility is particularly handy. It allows us to remove the load voltage without having to switch the supply off or adjust the voltage setting.

The $0.1\mu\text{F}$ capacitor prevents switching transients from being delivered to the output while D7 provides protection in the event that a reverse voltage (eg, from a charged capacitor) is applied to the output terminals. The $100\mu\text{F}$ capacitor ensures stability of the supply under all conditions.


The metering circuitry is quite straightforward. In the voltage mode, a 30k Ω resistor formed by the parallel combination of a 330k Ω and a 33k Ω resistor is switched in series with a 1mA meter across the supply. This means that the meter will read 30V full scale. In the current mode, the meter is connected across a 0.5 Ω resistor (made up from two 1 Ω resistors connected in parallel) in series with the negative supply line. A 1k Ω trimpot is used to adjust the meter so that it reads 1A full scale.

Construction

The 30V/1A Power Supply is housed in an attractive plastic instrument case measuring 200 x 160 x 70mm. This should come supplied with a PVC front panel and a 2.5mm black anodised rear panel for heatsinking. A Scotchcal front panel was fitted to the prototype but some kit retailers may prefer to supply screen-printed panels.

All the circuitry, with the exception of the major hardware items (switches, pots, transformer, etc) is accommodated on a printed circuit board measuring 105 x 111mm and coded 85psl.

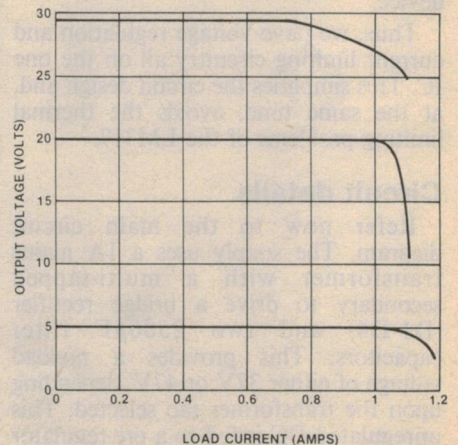No special procedure need be followed when assembling the PC board although the job will be much easier if the smaller components are installed first. Note carefully the orientation of the diodes, transistors, IC and electrolytic capacitors



These load curves plot the performance of the prototype. The maximum load current is maintained at 1A for voltages up to 27V.

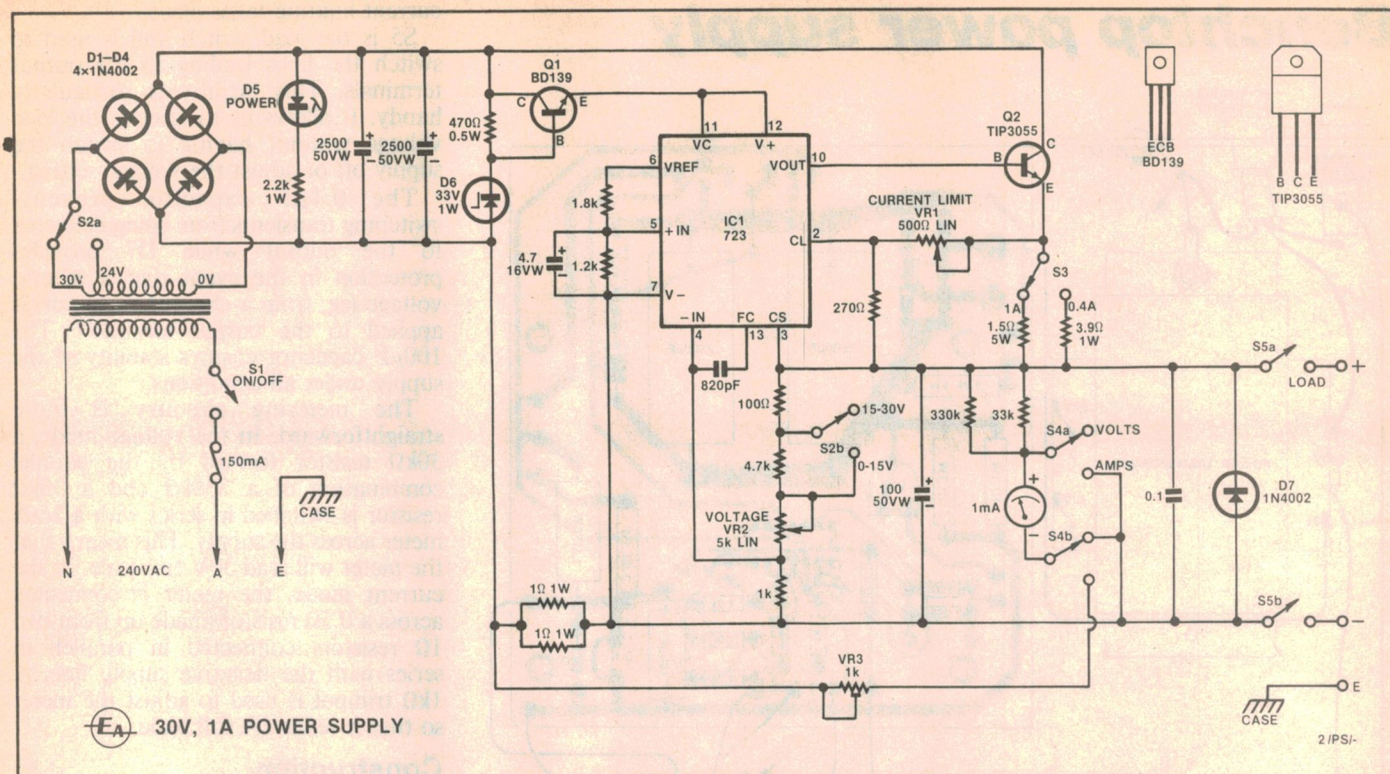


Fig. 1 shows the internal workings of the 723 regulator. It consists of a series pass transistor, an error amplifier and a voltage reference source. The error amplifier compares a proportion of the output voltage with the internal reference voltage source and continually adjusts the base current to the series pass transistor to provide a regulated output.

The maximum current rating of the series pass transistor is 150mA, so some form of external current amplification is required to provide a reliable 1A supply.

One particularly attractive feature of the 723 is the in-built current limiting circuitry. When the output current reaches a preset value, the internal current-limit transistor turns on and reduces the base drive to the series pass device.

Thus, we have voltage regulation and current limiting circuitry all on the one IC. This simplifies the circuit design and, at the same time, avoids the thermal limiting problems of the LM317.

Circuit details

Refer now to the main circuit diagram. The supply uses a 1A mains transformer with a multi-tapped secondary to drive a bridge rectifier (D1-D4) and two 2500µF filter capacitors. This provides a no-load voltage of either 37V or 47V, depending upon the transformer tap selected. This unregulated DC is fed to a pre-regulator stage (Q1) and to the output stage (Q2).

LED D5 and its associated 2.2kΩ current limiting resistor provide power

on/off indication. While the current through the LED will vary slightly according to the transformer tap selected, this is of no consequence.

Q1 and its associated 33V zener (D6) ensure that the maximum 40V supply rating of the 723 (IC1) is not exceeded. D6 clamps the voltage on Q1's base to 33V, thereby limiting the supply voltage

to IC1 to about 32.3V. Bias for Q1 and D6 is provided by the 470Ω ½W resistor.

The series pass transistor in the 723 regulator drives voltage follower Q2 which provides the necessary current amplification. Q2 is a TIP3055 NPN power transistor with a maximum collector current rating of 15A and a Vce rating of 70V, which is more than

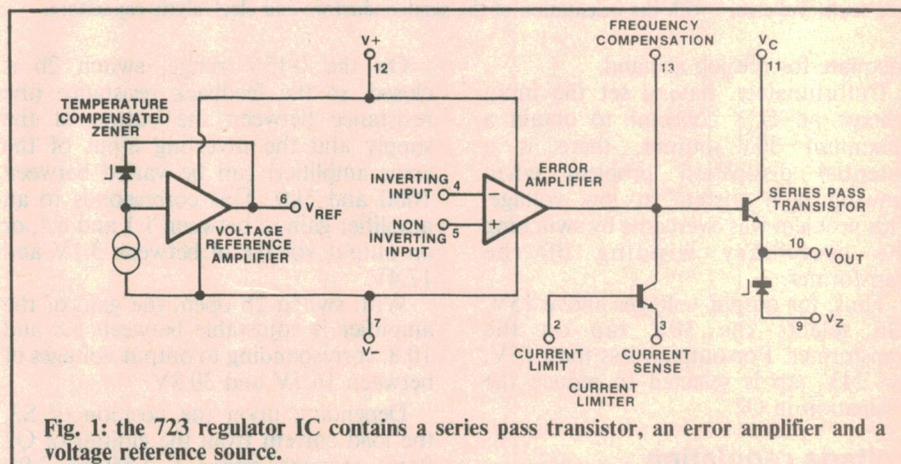


Fig. 1: the 723 regulator IC contains a series pass transistor, an error amplifier and a voltage reference source.

SPECIFICATIONS — EA 30V/1A SUPPLY

Output voltage	3-30V variable over two ranges, 0-15V and 15-30V
Output current	0-1A up to 27V (see load curves) with variable current limiting
Load regulation	Better than 0.2% from zero to full load
Output ripple	Less than 2mV RMS at full load

New design features current limiting

30V/1A benchtop power supply

This 30V/1A power supply features variable output voltage from 3 to 30V, variable current limiting over two ranges, overload protection and switchable voltage/current metering.

by GREG SWAIN & FRANCO UBAUDI

According to kit retailers, the most popular power supplies with hobbyists are the 30V/1A models. That's not surprising when one considers that most solid state circuitry only requires a single-sided supply of between 5V and 30V at currents up to half an amp or so.

The truth is, most hobbyists don't need an all-singing, all-dancing supply with digital readouts and other fancy whatnots. They do, however, demand a few refinements such as metering, load switching, short-circuit protection and adjustable current limiting. All of these features have been included in this new design.

If you're in the market for a 30V/1A power supply, this is definitely the one to go for. Most of the circuitry is built onto a single PC board, the parts are all readily obtainable and it's easy to build.

With this power supply, you get superior specifications for very little extra money. This unit is capable of

providing a full 1A output over virtually the entire voltage range. Other kit designs currently on the market provide a 1A output over only part of their voltage range due to inherent thermal limitations.

Other features of this new design include load switching, power on/off indication, and the provision of a separate ground terminal. There are two ranges for current limit plus two voltage ranges, all selected by means of toggle switches. The current limit ranges are 0.15-0.4A and 0.4-1A, while the voltage ranges are (nominally) 0-15V and 15-30V.

In practice, the current limit and voltage ranges overlap slightly to ensure continuity.

Current limiting

The adjustable current limiting facility is particularly useful. It offers two main advantages: first, it protects the supply in

the event that the output is short-circuited; second, it protects any circuitry run from the supply from damage by excessive current due to a fault condition. There's nothing worse than having circuitry go up in smoke while you're trying to troubleshoot a tricky problem.

In the interests of economy, we elected to use a single meter and switch between voltage and current measurements. Admittedly, it would be nice to have dual meters but, unfortunately, the cost is prohibitive. Meters are expensive and, in addition, we would require a much larger (and more expensive) case to provide the necessary front panel area.


The accompanying graph and the specification panel document the performance of the prototype. As can be seen, the load regulation is better than 0.2% from zero to full load while the output ripple is less than 2mV RMS. The maximum load current is maintained at 1A right up to 27V output, after which the load curve falls away due to transformer losses.

Design considerations

Initially, we considered using an LM317 three-terminal regulator as the basis for the design but soon ran into difficulties. Despite various approaches, we were unable to come up with a cost-effective circuit that would deliver 1A over the full range due to thermal limiting in the LM317. Another drawback was that an additional op amp was required to provide current sensing, thereby adding to the circuit complexity and cost.

Eventually, we rejected the LM317 in favour of the 723 regulator IC. Originally introduced by Fairchild as the uA723, this device is also available from National Semiconductor as the LM723 and from other manufacturers with similar "723" designations.

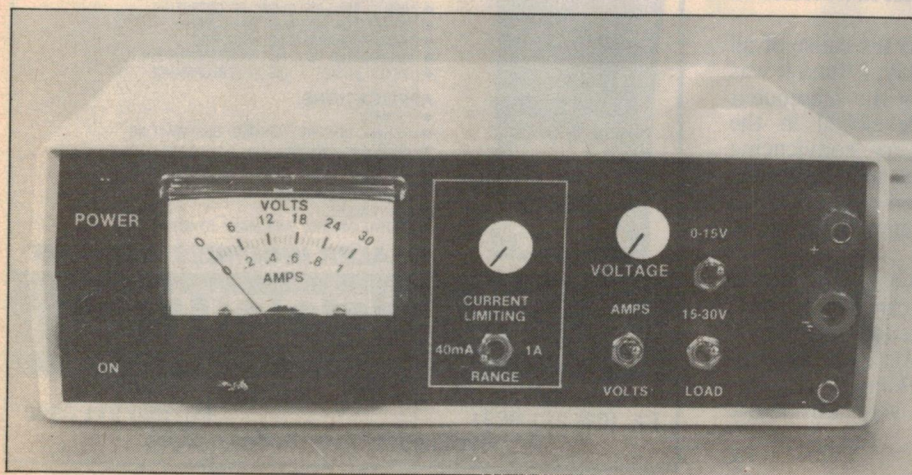Left: this new 30V supply provides a 1A output over virtually the entire voltage range. The meter is re-scaled by removing the plastic cover and attaching new artwork.



Serviceman

should have been 25V, and a width control which didn't work.

I decided to stoke up the CRO and check some waveforms. Of particular interest were waveforms 81 and 90, 81 being at the junction of L779 and C778, and 90 being at the emitter of TR690. Waveform 81 is shown as a negative going spike, at the horizontal rate and about 150V, and it showed up as the right shape but closer to 200V. Waveform 90 was supposed to be a rather peaky sine wave of about 8V p-p, at the vertical rate, but was actually a miniature replica of waveform 81, at about 20V p-p.

Unfortunately, apart from confirming that something was wrong, this didn't help much. I went back to the 25V rail, confirmed that it was still at 28V, and began to make some other measurements. I was particularly interested in the voltage at the junction of D776/777 which is not given anywhere on the circuit or in the manual. As measured, it read a little over 2V (DC) which, intuitively, I felt was suspect.

It was at this stage that somebody up there smiled on me. I had to leave the set to answer a house call involving loss of sound in, would you believe it, a Kriesler 59-1 chassis. The fault was easily fixed but I could hardly wait to get my meter on that diode junction. It read 12.5V.

Back at the shop I took another long hard look at the circuit. I had tested virtually every component which might be pertinent, and there was still something wrong. Which could only mean that I had not tested a vital component, or that one of my tests was inadequate.

Eureka!

My gaze fell on the two diodes. I had pulled them out and tested them with a meter, which had given conventional readings. But could one of them have a "funny" in it? I pulled them both out again and fitted two new ones. And that was it. Everything came back to normal. The 25V rail was spot on and the width, initially inadequate because I had left the control in its minimum position, responded immediately when I adjusted it.

And that was the last fault. It remained only for me to tidy up the mess on the deflection board, give all the adjustments the once over, and I had a set which was virtually as good as new. The owner was delighted, in spite of the fact that the cost, as I had warned him, was pretty substantial. (I didn't charge for changing the line output transformer, and it wasn't worth changing it back again).

As for the theory behind the various component failures, and which came first and started the whole sequence of events, I'm afraid I pass. I did establish fairly conclusively that it was diode D777 which had failed, and that it was apparently breaking down at voltages above those which I used to test it. (A lesson to be learned there).

But whether it was the primary failure, and the cause of all the other failures must remain in doubt. Frankly, I think it was the main offender, but as to the mechanism of the subsequent failures, or how the rogue voltage was developed in the convergence section, I cannot offer any very convincing theory. One point to note, however, is that the set's behaviour on the bench indicated that it could have been working in an acceptable (to the customer) form for a long time with the faulty diode.

I am also convinced that the flashover from the EHT lead to the 4.7kΩ resistor was a furphy as far as the other faults were concerned. There is little doubt that it happened and that, if allowed to continue, it would have created its own chain of failures, but it wasn't the cause of the other faults.

So, as I said at the beginning, it was not a very satisfactory "apples bit".

But if anybody out there has any ideas...

SCAN AUSTRALIA

WITH WORLD'S BEST SCANNING RECEIVERS



AR2001

FOR THE BEST PRICE IN TOWN. FOR THE BEST SCANNER IN AUSTRALIA

**WORLD'S FIRST CONTINUOUS COVERAGE
THREE MODE COMMUNICATIONS RECEIVER
& SCANNER**

Features

- 25-550 MHz Continuous
- NBFM — For Communications
- WBFM — For BC8TV monitoring
- AM For Air Band
- 20 CH Memory
- Clock Priority CH

\$499

POCKET SIZE SCANNER

SC-4000

**NO COMPROMISE PROGRAMMABLE
HAND-HELD SCANNER THAT
EVERYBODY CAN AFFORD!**

FEATURES:


- 160 MEMORY CHANNELS
- 9 BAND — POLICE, GOVERNMENT, MILITARY, LAND MOBILE, CB, AMATEUR, RADIO TELEPHONE ETC.
- OVER 45,000 CHANNELS
- UNIQUE SPLIT PROGRAMMING SYSTEM
- AUTOMATIC FREQ. STORAGE
- PRIORITY CHANNEL
- LCD DISPLAY
- PROG SCAN/SEARCH RATE
- 24 HOUR CLOCK AND MANY OTHER FEATURES

SPECIFICATIONS:

- FREQ. RANGE: 26-28MHz, 68-88MHz, 138-176MHz; 380-512 MHz
- SENSITIVITY: 0.5μV-1μV depending on Band
- SCAN RATE: 16 CH/SEC
- AUDIO OUTPUT: 0.5W

COMES COMPLETE WITH NICAD BATTERY, CHARGER AND ANTENNA

ONLY \$399

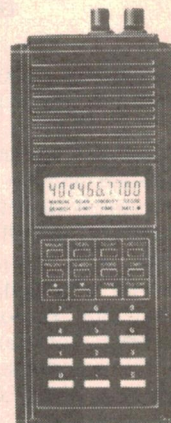

NEW

Personal 2-way
radio here at last!

"EMTRON ACE"

A QUALITY 40-CH HIGH POWER UHF CB HAND-HELD TRANSCEIVER • DESIGNED FOR AUSTRALIA
DOC APPROVED

FEATURES:

- 40 CHANNEL OPERATION
- HIGH (2.5W)-LOW (0.5W) RF OUTPUT
- OFFSET FOR REPEATER OPERATION
- NICAD RECHARGEABLE BATTERIES
- ILLUMINATED DIAL FOR NIGHT OPERATION
- SMALL IN SIZE — BIG IN PERFORMANCE

APPLICATIONS:

- FARMING
- FISHING, BOATING, HUNTING, BUSHWALKING
- BUSH FIRE CONTROL
- AG SHOWS
- SECURITY
- CONSTRUCTION SITES
- CAR RALLIES
- CROWD CONTROL AND MANY OTHERS

DEALER INQUIRIES WELCOME



EMTRONICS

Retail Division of EMONA ELECTRONICS P/L

All Mail to: PO Box K21, Haymarket, NSW 2000
Ph: (02) 211 0531 Ph: (02) 211 0988
94 Wentworth Ave, Sydney, 2000.



ACTIVE ELECTRONICS

289 LATROBE STREET, MELBOURNE 3000 PH. 602 3499

9am-5.30pm MON-THURS 9am-8.30pm FRIDAYS 9am-12noon SATURDAY

NEW YEAR SPECIALS!

ALL YOU HAVE EVER WANTED IN AN ELECTRONIC STORE - AND MORE!

MAIL ORDER HOTLINE. (03) 67 1312

DRIVE SPECIALS


TANDON 8" SLIMLINE

Normally \$695

slashed to


\$499

to clear.

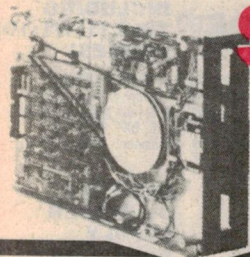

Disk Drives at *Super Savings*

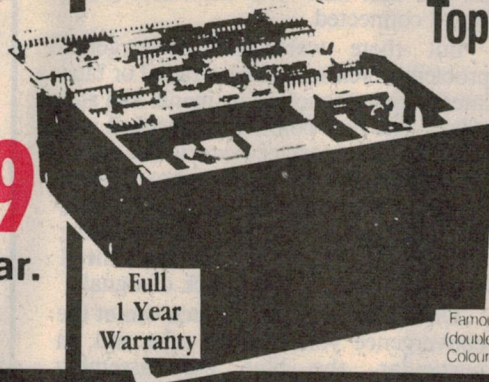Top Quality 5 1/4" Floppy Disk
Drives Model 51



Full
1 Year
Warranty

\$180.00

Including Tax

Famous M.P.I. brand full height, single side, 40 track, 250K capacity (double density). Standard interface, suit Dick Smith System 80, Tandy TRS 80, Colour Computer, Microbee, Acorn, etc. Tested and in original boxes.

12 MONTHS
WARRANTY



GREEN
NV1290 x

\$165

**TOP BRAND
MITSUBISHI
MONITORS**

AMBER
NV1290 x

\$175

*** WE STOCK OVER 2000 DIFFERENT SEMI-CONDUCTORS, TEST GEAR, INSTRUMENT CASES, TRANSFORMERS, RESISTORS, CAPACITORS, ETC. WE STOCK THE BIGGEST RANGE FOR THE HOBBYIST IN MELBOURNE.**



**SPECIAL THIS
MONTH WITH
HITACHI V212**

**FREE
SET OF CRO
PROBES**

**HITACHI & FREE DELIVERY
ONLY \$695 COMPLETE**


V-212 DC~20MHz, Dual Trace

● CRT = 6" square with internal graticule ● Vertical Deflection = Sensitivity: 5mV/div to 5V/div $\pm 3\%$, Max. Sensitivity: 1mV/div to 1V/div $\pm 5\%$ at x 5 Magnifier extends, Bandwidth: DC to 20MHz (-3dB), DC to 7MHz (-3dB) at x 5 Magnifier extends, Modes: CH1-CH2-ALT-CHOP-ADD ● Horizontal Deflection = Sweep Time: 0.2 μ s/div to 0.2s/div $\pm 3\%$, Max. Sweep Rate: 100ns/div at x 10 Magnifier extends ● X-Y Operation (CH1: X, CH2: Y) = Phase Error: 3° from DC to 50kHz ● Dimensions = 310(W) x 130(H) x 370(D)mm/12.3 x 5.2 x 14.6 in. ● Weight = 6.0 kg/13.3 lb.

10 PACK SPECIALS

10 x 74LS245	\$9.50	10 x 4013B	\$3.80
10 x 74LS32	\$2.50	10 x 4093B	\$3.90
10 x 74LS74	\$2.90	10 x BUX80	\$37.00
10 x 7400	\$3.90	10 x BU126	\$13.00
10 x 7402	\$3.90	10 x 2716	\$49.50
10 x 7416	\$5.40	10 x 2764	\$99.50

* * * POST & PACKING FOR GOODS SENT BY STANDARD MAIL IN AUSTRALIA ONLY. * * *	
Order Value	P & H
\$5	\$9.99
\$10	\$24.99
\$25	\$49.99
\$50	\$99.99
\$100 or more	\$7.50
* * *	

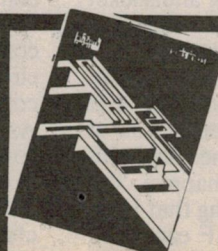

**DATA BOOK
\$5.00**

incl. post & packed to anywhere in Australia.

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

MAIL ORDER

Serviceman

I also decided to take a punt on reconnecting the frame circuit, in the hope that I could get it working. After what I had been through so far, finding the frame fault was a breeze. It was transistor TR651, a BD235 and the "top" one in the frame output pair. Since its collector was connected almost directly to the spurious 70 volts, it was not surprising to find that it had broken down.

A replacement was quickly fitted and I switched on again. And this time things started to work; I had frame deflection and I had a picture. It was a good picture too, considering everything, and provided final confirmation that the picture tube was in excellent condition. It was a great morale booster, and I felt, for the first time, that it was worthwhile pushing on with it.

But there was still a lot to be done. Quite apart from the rogue voltage, the horizontal scan had dropped back when the frame circuit came good, and I began to wonder about the line output transformer. As I mentioned at the beginning, this had been replaced by the previous serviceman, but it was a different brand from the original.

This was not necessarily wrong. The particular make, of German origin, is used in a number of continental sets and is sold as a replacement for the Philips and similar type transformers. On the other hand, my own experience with them has not been the happiest. Some have failed after quite short periods, and they have proved to be incompatible with some circuits using the Philips type.

Since I had the correct transformer type in the junked K9 I decided to fit and restore this part of the set to original condition. After all, there just could be something funny about the replacement unit. Alas for my hopes. The set performed exactly as it had before. Oh well, it was worth a try.

So it was back to the east-west modulator. Looking at the circuit again I realised that there was a section I had tended to ignore; a winding on the line transformer labelled "Y" and "Z", the "Y" connecting to the modulator circuit and the "Z" connecting to the convergence board via pin 4 of plug and socket 705, and pin 3 of plug and socket 802. Could the rogue voltage be coming back from the convergence board?

It was easy enough to check. I simply pulled the plug PL802, reasoning that temporary lack of convergence was of little importance at this time. And this was when things started to happen. The behaviour looked so promising that I was encouraged to refit the $3.3\mu\text{F}$ capacitor, C759, and try again. This brought the set

almost back to normal. Horizontal deflection was now about nine-tenths of the screen width (R779 was still open) and, most important, the 25V rail had now dropped to about 28V; nearly right but not quite.

So what was wrong on the convergence board? Access to this is from the front of the set, below the tuner, and one glance was enough to confirm that all was not well. The blue radial convergence coil, T820, was well and truly cooked and this prompted me to check its associated components. A 22Ω resistor, R820, was also visibly cooked and a 33Ω variable resistor, R817, went "crunch, crunch" when I tried to adjust it.

Once again the old K9 came to the rescue with a good T820 and I soon had the board back to normal. I re-fitted plug 802 and switched on, with the happy result that the set worked as before, but for the first time with the convergence board connected.

But there were still convergence problems. Neither the blue radial or blue lateral convergence adjustments had any effect. The first point to be checked was whether the correct waveforms were being fed to the convergence board and a quick check on the red/green adjustment, T815, indicated that they were working as they should. So, for the moment, I assumed that it was not lack of signal.

On this basis the next check was at the convergence yoke on the tube and, in particular, the blue coil assembly connected to plug and socket 953. These are clipped into the scan coil assembly and are quite easily removed. And one glance was enough; it, too, had been cooked. Only one of the windings, the blue lateral, or static, winding (shunted by two resistors) had been affected, but severely enough to distort the end of the former.


So I dived into the K9 again, fished out another coil, and clipped it into place. And that fixed that; the blue convergence snapped back into place almost spot on. It needed only a touch to complete the correction.

But that was not all. When I replaced the 1Ω resistor, R779, the horizontal scan expanded until it neatly filled the screen. In fact, the set looked as though it was behaving normally and I might have been pardoned for believing that it could go back to the customer.

The only snag was that the width control, a $22k\Omega$ pot, R679, in the base circuit of TR688, wouldn't work. Nor could I work out why it wouldn't work. As far as I was concerned all the components in that part of the circuit, including the two transistors, TR688/690, had been thoroughly checked and pronounced OK. So the two symptoms I had were a 28V rail which

Looking to purchase instruments

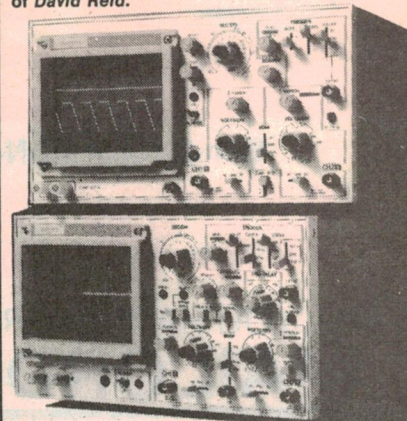We are stockists of Hitachi, Fluke, Trio, Goodwill, Meguro, Aaron and Kikusui: so if you're in the market for an oscilloscope, think of David Reid.



**35MHZ
MEGURO
MO-1252**

**\$749⁰⁰
INCLUDING TWO
(1:1/1:10) PROBES**

35 MHz 2-channel with Trigger Delay
• Sensitivity: 5mV/div — 10V/div; 1mV/div at x5 MAG •
Bandwidth: DC or 10Hz — 35 MHz • Sweep Mode: NORMAL,
AUTO, SINGLE, DELAY • Trigger Delay: INTEN'D, DELAY'D; 1us
— 100m S • Trigger Source: INT, LINE, EXT, EXT/10 • X-Y
Operation; & X-Axis modulation

**20MHZ
MEGURO
MO-1251**

**\$525⁰⁰
INCLUDING
TWO (1:1/1:10)
PROBES!**

20 MHz 2-channel with component tester
• Sensitivity: 5mV/div — 20V/div; 1mV/div at x5 MAG •
Bandwidth: DC or 10Hz — 20 MHz • Sweep Mode: NORMAL,
AUTO • Trigger Source: INT, CH2, LINE, EXT • X-Y
Operation; & Z-Axis modulation • Component Tester: for R, L,
C & diodes

**GPS-3030
DC POWER
SUPPLY**

\$193⁰⁰

Provides 30V at 3A

**GPS-3060
DC POWER
SUPPLY**

\$334⁰⁰

Provides 30V at 6A

- Short circuit protected
- Auto constant voltage, constant current indication
- High line and load regulation
- Similar to GPS3030




**GAG-808A
AUDIO
GENERATOR**

\$199⁰⁰

Covers 10Hz
to 1MHz

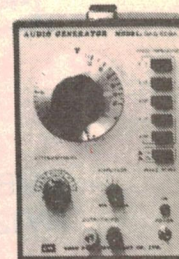- 20Vp-p open circuit output • Sine and Square wave outputs • External sync • 600 ohm output impedance



ALL PRICES SHOWN DO NOT INCLUDE SALES TAX. ADD 20%

These are just a few of the many 100's of up-to-date Electronic items on display at:



DAVID REID ELECTRONICS LIMITED

127 York Street, Sydney, 2000
or Telephone (02) 267 1385

Dick Smith Electronics: Always No 1 for Kits!

You've seen the claims. Everyone reckons they're number one for kits. There is only **one** Number One: Dick Smith Electronics. Here's why:

- Over 100,000 kits produced each year
- Over one million kits sold (that's a lot of kits!)
- Over one hundred different kits stocked
- Over thirty people employed full time in producing kits
- Over five hundred thousand dollars worth of parts held in stock purely for kit production - backed up with over five million dollars worth of warehouse components at call!

PLUS!

- Fully computerised kit production system based on an IBM System 38 computer. It's the only way!
- In-house technical services back up such as R&D, technical manual preparation, quality control, service, etc etc.
- Over 60 stores to serve you throughout Australia and New Zealand PLUS the most reliable mail order service in existence ...

Dick Smith Electronics: No 1 in Kits.

STORE LOCATIONS

NSW

Cnr. Swift & Young Sts.
Panmatta Rd & Melton St
T55 Terrace Level
Shop 1, 65-75 Main St
613 Princess Hwy
Oxford & Adelaide Sts
531 Pittwater Rd
Campbelltown Mall, Queen St
Shop 3, 235 Archer St Entrance
147 Hume Hwy
162 Pacific Hwy
315 Main St
4 Florence St
Elizabeth Dr & Bathurst St
450 High St
173 Maitland Rd, Tighes Hill
Lane Cove & Waterloo Rds
George & Smith Sts
The Gateway, High & Henry Sts
818 George St

Albury 21 8399
Auburn 648 0558
Bankstown Sq. 707 4888
Blacktown 671 7722
Blakehurst 546 7744
Bondi Junction 387 1444
Brookvale 93 0441
Campbelltown 27 2199
Chatswood Chase 411 1955
Chullora 642 8922
Gore Hill 439 5311
Gosford 25 0235
Hornsby 477 6633
Liverpool 600 9888
Maitland 33 7866
Newcastle 61 1896
North Ryde 88 3855
Parramatta 689 2188
Penrith 32 3400
Railway Sq 211 3777

6 Bridge St
125 York St
Tamworth Acde & Kable Ave
263 Keira St
ACT
96 Gladstone St
VIC
Creswick Rd & Webster St
145 McCrae St
Shop 46, Box Hill Central, Main St
Cnr Hawthorn Rd & Nepean Hwy
260 Sydney Rd
Nepean Hwy & Ross Smith Ave
205 Melbourne Rd
291-293 Elizabeth St
Bridge Rd & The Boulevard
Springvale & Dandenong Rds
QLD
293 Adelaide St
166 Logan Rd
Gympie & Hamilton Rds

Sydney 27 5051
Sydney 267 9111
Tamworth 66 1961
Wollongong 28 3800
Fyshwick 80 4944
Ballarat 31 5433
Bendigo 43 0388
Box Hill 890 0699
East Brighton 592 2366
Coburg 383 4455
Frankston 783 9144
Geelong 78 6766
Melbourne 67 9834
Richmond 428 1614
Springvale 547 0522
Brisbane 229 9377
Buranda 391 6233
Chermside 359 6255

Shop 205, Indooroopilly
Shopping Town
Cnr Queen Elizabeth Dr & Bernard St
Cnr Gold Coast Hwy & Welch St
Bowen & Ruthven Sts
Ingham Rd & Cowley St. West End
SA
Wright & Market Sts
Main South & Flagstaff Rds
Main North Rd & Darlington St
24 Park Terrace
WA
Wharf St & Albany Hwy
166 Adelaide St
William St & Robinson Ave
Centenary Acde, Hay St
TAS
25 Barrack St
NT
17 Stuart Hwy

T.B.A.
Indooroopilly 27 9644
Rockhampton 32 9863
Southport 38 4300
Toowoomba 72 5722
Townsville 212 1962
Adelaide 298 8977
Darlington 260 6088
Enfield 281 1593
Salisbury 451 8666
Cannington T.B.A.
Fremantle 328 6944
Perth 321 4357
Hobart 31 0800
Stuart Park 81 1977

Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days, or unforeseen circumstances might hold up shipments so that advertised lines are not in the stores by the time the advert appears. And very occasionally, an error might slip through our checks and appear in the advert (after all, we're human too!). Please don't blame the store manager or staff, they cannot solve a dock strike on the other side of the world, nor fix an error that's appeared in print. If you're about to drive across town to pick up an advertised line, why not play it safe and give them a call first - just in case! Thanks.

Dick Smith Electronics

HEAD OFFICE & DS XPRESS ORDER SERVICE

P.O. Box 321, North Ryde, N.S.W. 2113. Tel: 888 3200

SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone your order and Bankcard - it's so simple! (02) 888 2105
orders only on this number. Enquiries: (02) 888 3200

POST & PACKING CHARGES

Order Value	Charge	Order Value	Charge
\$ 5.00-\$ 9.99	\$2.00	\$50.00-\$99.99	\$6.00
\$10.00-\$24.99	\$3.50	\$100 or more	\$8.00
\$25.00-\$49.99	\$4.50		

Terms available to approved personal applicants



DICK SMITH ELECTRONICS

PTY LTD

(SA Credit facilities available through
Custom Credit Corp. 422 King William St. Adelaide)

you can have all the features
of expensive commercial amps
at a fraction of their price

...when you build the

Playmaster Mosfet Amp

Why not build your own amplifier — and save a fortune?

Thousands of these Playmaster Mosfet Stereo amplifiers have now been built — many by virtual beginners! It's so easy: every detail of construction is carefully and thoroughly detailed in our exclusive step-by-step instruction manual!

You'll have a superb quality amplifier, better than many you'd pay hundreds of dollars more for. It will look so good that your friends will never believe you built it!

- State-of-the-art POWER MOSFETS
- Low noise FET input pre-amps
- Over 50 watts per channel
- Speaker switching plus loudness and muting controls
- Low distortion, high performance circuitry
- Complete with our famous step-by-step instruction manual



Cat. K-3515

ONLY
\$199⁰⁰

EXCLUSIVE! Professionally designed 'scratch grain' front panel matched with fully imported deluxe knobs. Beware of other kits which don't look a tenth as good!

**DICK SMITH
ELECTRONICS**

PTY LTD

No 1 FOR KITS!

COMING SOON:

EA's brilliant new high power Mosfet Amplifier — over 100w per channel, absolutely latest technology. See our ads next month for full details!

Car Ignition Killer

entry of the connecting leads. This hole should be fitted with a small rubber grommet to prevent damage to the lead insulation.

Installation of the unit is probably the most important part of the construction. To enable the unit to function effectively, it must remain undetected by the potential thief. This not only means hiding the unit itself and disguising any exposed wiring, but locating the unit so


that the sound of the relay operating cannot be heard.

The best place for the unit is probably in the engine bay against the firewall. Power for the unit should be taken from the ignition wire, preferably at a point remote from both the ignition switch and the coil. This reduces the chances of a thief spotting the extra lead when "hotwiring" the car. A single-pole on-off switch, accessible from the driver's position, should be placed in the power lead running to the unit so that the unit can be disabled and the car driven normally.

It goes without saying that this switch should also be well hidden.

The earth wire should be connected to the nearest earth point, which may actually be inside the case if this is electrically connected to the vehicle chassis (say via self-tapping screws). The most exposed connection is the wire leading to the negative or points side of the coil. This connection should be disguised by using wiring similar in appearance to the existing coil leads, and by bundling the leads together.

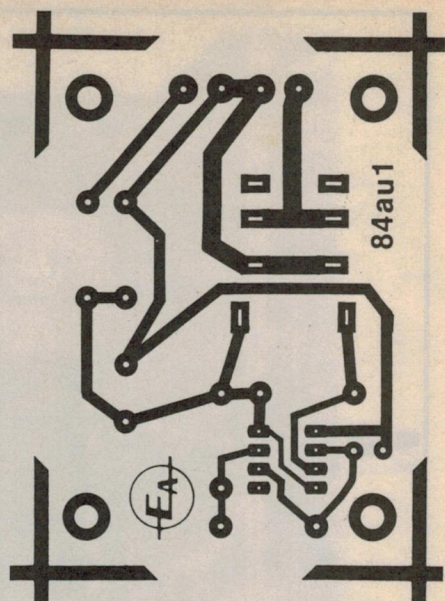Once the unit is installed, it can be checked for correct operation. First, switch the unit off and check that the car can be started and that the engine runs normally. Now switch the unit on — the engine should run normally for a few seconds, then cut out. It should now be possible to restart the engine after a short delay, whereupon the engine should again run normally for a few



Above is the actual size PCB artwork.

PARTS LIST

- 1 PCB, code 84au1, 69 × 48mm
- 1 aluminium case, 102 × 70 × 51mm
- 1 4-way PC-mounting terminal block
- 1 DPDT 12V relay with 10A 120VAC contacts
- 1 SPST toggle switch
- 4 6mm or 8mm spacers
- 1 small rubber grommet

SEMICONDUCTORS

- 1 555 timer IC
- 1 15V 1W zener diode
- 1 1N4001 diode

CAPACITORS

- 1 1000μF 25VW PC electrolytic
 - 1 2.2μF 16VW PC electrolytic
- RESISTORS (¼W, 5% unless stated)
- 1 × 2.2MΩ, 1 × 220kΩ, 1 × 22Ω ½W

MISCELLANEOUS

Machine screws and nuts, self tapping screws, automotive hook-up wire, solder etc.

seconds before cutting out.

If your car's engine is very easy (or very hard) to start you may wish to alter the engine run and stop times we have chosen. This can be done quite easily by changing either of the two timing resistors or the timing capacitor. The formulae for the time periods in seconds are:

- Engine run time = $0.685(R_A + R_B)C$;
- Engine stop time = $0.685(R_B)C$.

In our circuit, $R_A = 220k\Omega$, $R_B = 2.2M\Omega$, and $C = 2.2\mu F$. By substituting these figures into the above equations, we get an engine run time of 3.6 seconds and an engine "kill" time of 3.3 seconds.


LED Level Meter


CONTINUED FROM PAGE 27

mally, for a stereo deck, two of these amplifiers would be required, each driving a separate LED array. The 10k trimpot is used to adjust the gain of the amplifier. The 100k trimpot in the LED Level Meter should be adjusted for maximum sensitivity, allowing the gain of the amplifier to be set as low as possible.

The amplifier operates from a nominal 12V DC supply, the same as that produced by the 9VRMS transformer and rectifier combination in the LED Level Meter. As the current drain is only of the order of 10mA, the amplifier can be simply connected in parallel with the meter.

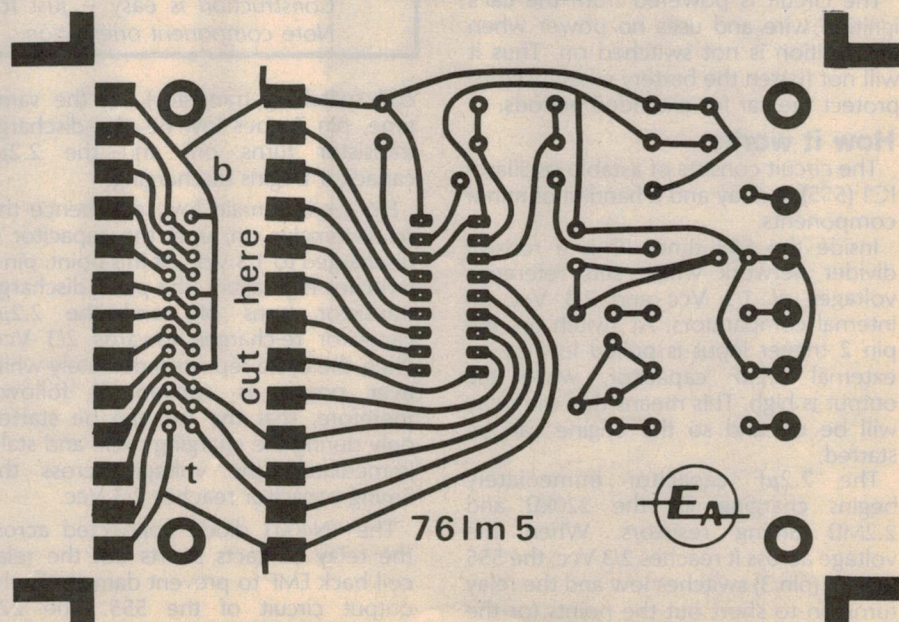The amplifier gain should be adjusted so that 0VU corresponds to the red LED just emitting. If you are replacing a mechanical movement, simply adjust the gain so that both the meters read the same on a sine wave signal with a frequency of about 1kHz.



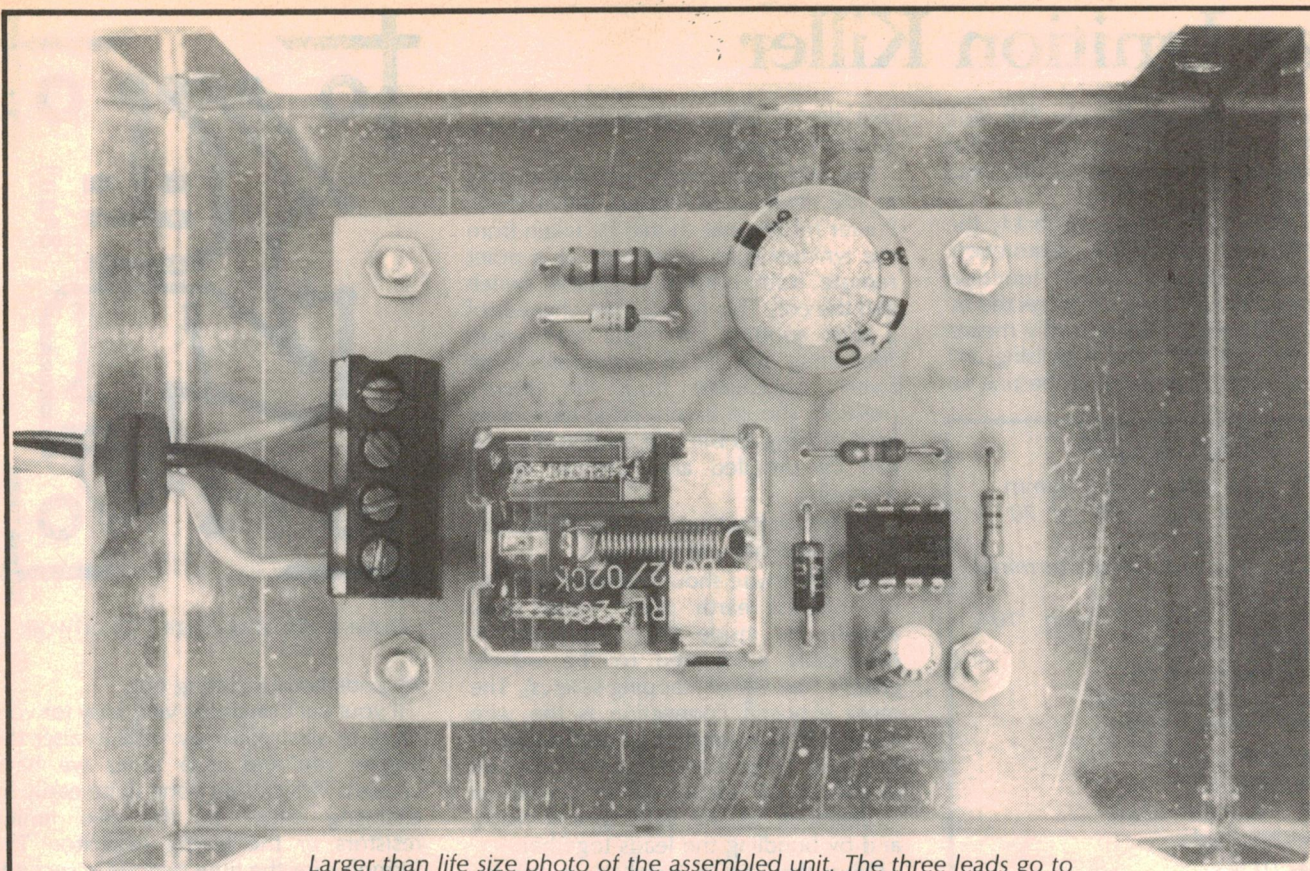

Larger than life size photo of the assembled unit. The three leads go to the disable switch, chassis and coil negative.

the oscillator output goes low, causing the relay to operate and short out the car's points. With no points signal the ignition system cannot produce a spark and so the engine dies. A few seconds later the oscillator output returns to the high state, the relay turns off and the contacts open. The engine can now be started and will run for a few seconds until the next low cycle of the oscillator.


The circuit is powered from the car's ignition wire and uses no power when the ignition is not switched on. Thus it will not flatten the battery when used to protect the car for extended periods.

How it works

The circuit consists of astable oscillator IC1 (555), a relay and a handful of minor components.

Inside the 555 timer IC is a resistor divider network which sets reference voltages of $1/3 V_{cc}$ and $2/3 V_{cc}$ on internal comparators. At switch on, the pin 2 trigger input is pulled low by an external $2.2\mu F$ capacitor, while the output is high. This means that the relay will be off and so the engine can be started.

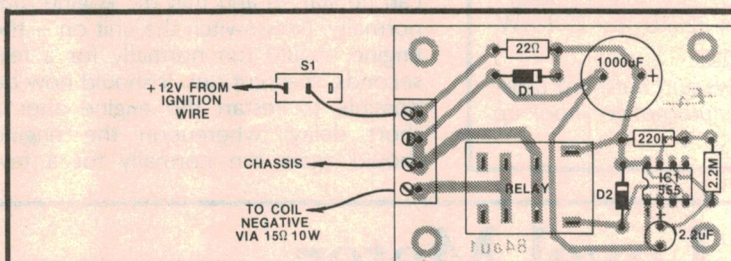The $2.2\mu F$ capacitor immediately begins charging via the $220k\Omega$ and $2.2M\Omega$ timing resistors. When the voltage across it reaches $2/3 V_{cc}$, the 555 output (pin 3) switches low and the relay turns on to short out the points (or the



Construction is easy – just follow this parts overlay diagram. Note component orientation.

coil switching transistor). At the same time, pin 7 goes low (ie, the discharge transistor turns on) and the $2.2\mu F$ capacitor begins discharging.

Pin 3 will remain low, and hence the relay remains on, until the capacitor is discharged to $1/3 V_{cc}$. At this point, pin 3 switches high again, the pin 7 discharge transistor turns off, and the $2.2\mu F$ capacitor re-charges towards $2/3 V_{cc}$. Thus, the cycle repeats indefinitely while ever power is applied. It follows, therefore, that the car can be started only during the charging cycle and stalls immediately the voltage across the timing capacitor reaches $2/3 V_{cc}$.


The 1N4001 diode connected across the relay contacts shorts out the relay coil back EMF to prevent damage to the output circuit of the 555. The 220Ω

resistor, 15V zener and $1000\mu F$ capacitor provide supply line filtering and decoupling. The 15V zener clamps supply line transients to 15V, thus protecting the 555 from excessive voltages.

Construction

Construction is straightforward with all parts except the switch mounted on a small printed circuit board (PCB) coded 84au1 and measuring $69 \times 48mm$. This is housed in a metal case measuring $102 \times 70 \times 51mm$, although any similarly-sized plastic case would also be suitable.

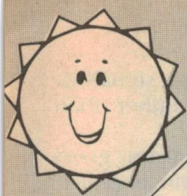We mounted the PCB assembly on the lid of the case using four 6mm brass spacers and machine screws and nuts. A small hole was drilled in the end of the lid closest to the terminal block to allow



Sneaky anti-theft device to build

Car Ignition Killer

Car burglar alarms are fine except that most are easily circumvented. This cunning anti-theft device is cheap, easy to fit, and effective.

We may be in the midst of an economic recession, but no such recession has been reported in the car theft "industry". Last year, more than 70,000 cars were stolen in Australia, this despite the existence of car steering locks and the increasing use of car burglar alarms.

A problem concerning the car alarm concept is how to make it most effective. One philosophy — usually expounded by the commercial alarm manufacturers — is that the alarm is most effective if its presence is clearly advertised and made obvious. The thief will then, according to theory, bypass that vehicle and attack one whose owner has not been astute enough to fit the "Little Beaut Red and Green Flashing Car Alarm". (What would happen if everybody fitted the "Little Beaut... etc" is not clear).

But that question aside, the opposite alarm philosophy contends that a warning sticker only makes the thief aware that there is an alarm to be circumvented. And professional thieves are not above familiarising themselves with the various commercial alarms and how best to disable them.

In fact many car alarms can be effectively disabled by the simple measure of disconnecting or cutting the horn wires without lifting the bonnet. It

is not generally realised that most horns can be reached without much effort from underneath the vehicle. An experienced thief can pull this trick in a few seconds.

Even if the alarm does sound, the thief usually has sufficient time to disable it. Surveys have shown that people tend initially to disregard a car burglar alarm, assuming that the owner has set it off accidentally. Provided he keeps his "cool", the thief has only to cut the wires to the horn or siren and drive away.

One of the worst thieves, as far as the car owner is concerned, is the "joyrider". This is the person who grabs your lovingly cared for Ford, Holden, Porsche, etc and takes it for a "spin around the block" to see for himself just how fast it will go. If the owner is lucky, the car will be found intact a day or so later, usually minus the radio-cassette player and any other valuable accessories that may have been fitted.

But even this can have a sting in the tail, with the real damage to the car often unseen. After all, the thief doesn't care two hoots about your property. The engine could well have been overheated or had the inside revved out of it. Or the car could have been used to show off innumerable "wheelies" to the detriment of the tyres and suspension.

Often, of course, the car will not be

recovered or will be damaged beyond repair. Many cars are stolen by professional thieves to be stripped and used for spare parts. But whatever the circumstances, car theft causes the owner a great deal of expense and inconvenience.

Ignition killer


In order to protect your car against the above situations we have devised a rather cunning little circuit. We've christened it the "Ignition Killer".

It works like this: imagine a thief has just broken into your car. He starts the engine and begins to drive off. Just as he does, the engine dies. He immediately cranks the engine and a few seconds later it starts. Again he begins to drive off and again the engine dies. In desperation he tries a third time only to have the engine die again.


The above sequence of events should automatically deter any joyriders and many so-called professional thieves as well. After all, it is difficult to get any joy out of the car that only moves a few metres at a time. In this situation, most thieves will simply assume that the car has an engine problem and will abandon it for easier "game".

The simple circuit that creates this mayhem is simply an astable oscillator based on the ubiquitous 555 timer IC. The output of the 555 oscillator is connected to a relay which in turn has its normally open contacts wired in parallel with the car's points or coil switching transistor (see Fig. 1).

A few seconds after the car is started,

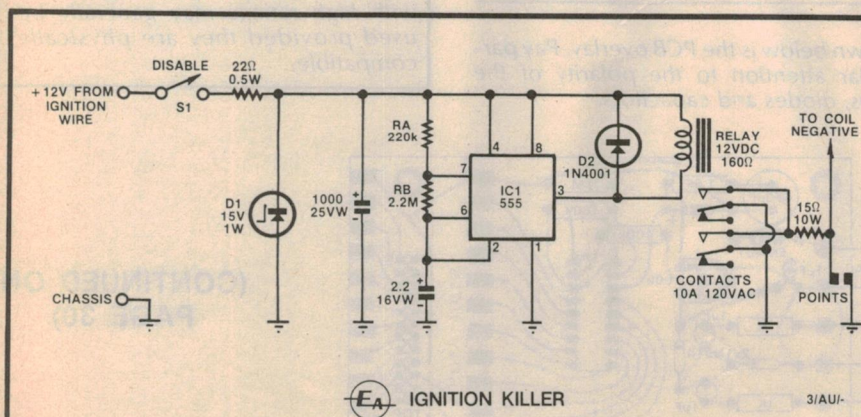

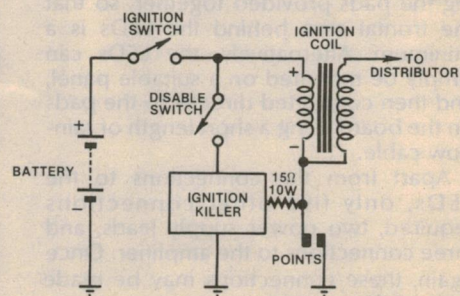
The circuit consists of a 555 timer IC driving a relay.



The Ignition Killer is simply connected in parallel with the points (or the coil switching transistor).

★ OR BUILD YOUR OWN TEST GEAR AND \$AVE \$AVE \$AVE!


LCD Panel Meter

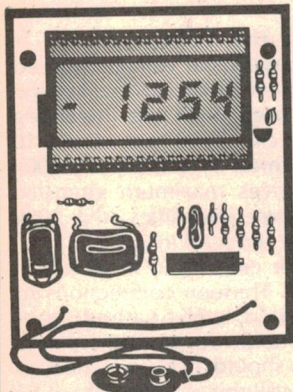

Here's great value! A versatile, accurate liquid crystal display panel meter ideal for building in to virtually any project to display virtually what ever you want! Very comprehensive instructions are supplied: it can be 'tailor made' to suit your particular requirements. Draws less than a milliamp, runs from plus or minus five to fifteen volts: that's versatility!
Cat K-3450

\$34⁵⁰

Everyone needs a VARIABLE POWER SUPPLY

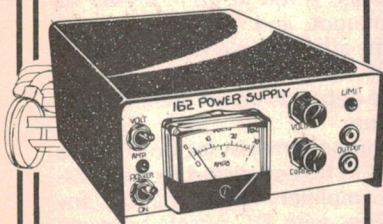


30 volts at 1 amp!

Yes - you need a variable supply if you're involved in any way in electronics: hobbyist, experimenter, amateur, technician, lab worker...

This superb supply features an up-to-date circuit, and has full metering plus overload protection. As described in ETI.
Cat K-3475

\$59⁰⁰

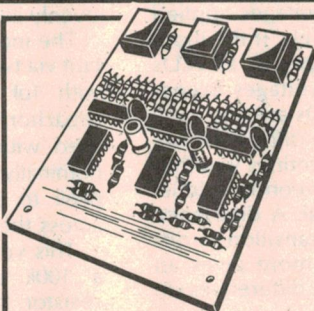

It's the circuitry that counts...

3 DIGIT COUNTER MODULE

What versatility: now you can build a counter to count just about anything! Designed for maximum flexibility, suits a huge range of inputs and triggers - and counts at up to 2MHz! Very wide power supply range too: 5 to 15 volts.

Fully comprehensive instruction manual included.
Cat K-3451

\$19⁹⁵

STOP! Don't throw away good bits!



Check them with this

RLC BRIDGE

Now you can save a fortune by using those components you'd normally throw out! Check them with this RLC bridge: it measures resistance, capacitance and inductance easily and simply! Snazzy looking case & panel, too: your friends will think you purchased this one! Check out these ranges:

10 ohms to 10 Megohms
10pF to 10uF

A must for the serious hobbyist!
Cat K-3468

ONLY \$37⁵⁰

A BUILD-IT-YOURSELF BARGAIN FOR THE SERVICEMAN




TV PATTERN GENERATOR

Crosshatch, dot and blank raster - all from a project with just 7 IC's! And it's small enough to keep in the tool box just in case - battery eliminator (9V) runs it perfectly. **EXCLUSIVE:** We include the video modulator in our kit: why pay more?
Cat K-3472

\$29⁹⁵

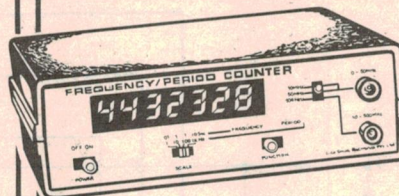PLUG-PACK BATTERY ELIMINATOR TO SUIT: Cat M-9525 @ \$10.95



Build your own DIGITAL FREQUENCY COUNTER

An absolute MUST for the serious hobbyist and professional involved in electronics: a digital frequency counter. This superb kit is the result of years of experience with earlier DFM kits: this one is the ultimate! With professional design and finish, it offers specifications you'd expect on commercial units costing hundreds of dollars more, such as:

- 3 Frequency ranges 0-10, 0-50 and (with optional pre-scaler) 10-500MHz
- 4 gating times: .01, .1, 1 and 10 seconds
- High input sensitivity: 10mV to 30MHz, 100mV to 500MHz at 1M input impedance.
- Huge, bright, high efficiency LED display.
- High accuracy: better than plus/minus .005%!

And it's very easy to build, with virtually no PC board wiring - and switches are all integrated with front panel. It really is easy with our step-by-step instructions!

Cat K-3439

**INCLUDING
DELUXE
CASE**

\$125

500MHz pre-scaler

Increases the basic range of the counter to 500MHz. Ideal for UHF work - very easy to fit into existing PCB.

Cat K-3432

\$34⁵⁰

**DICK SMITH
ELECTRONICS**

PTY LTD

You'll need some Test Gear too!!




Talking Multimeter!

Not just a multimeter: it's got an audible continuity checker built in. Really handy for checking cables, wiring, etc. 20,000 ohms per volt sensitivity, 19 ranges. Cat Q-1022

ALL FOR JUST

\$24⁹⁵

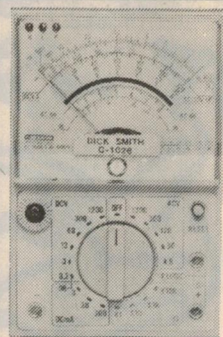

Multimeter & Logic Tester

Or try this one: it checks high, low & pulse logic states. 20 ranges - 20,000 ohms per volt sensitivity - and it has a shielded movement so it's ideal for RF circuit checking too. Cat Q-1026

SUPER LOW PRICE


\$34⁵⁰



Our top analogue meter: Test bench in a case!

Very high sensitivity (100,000 ohms per volt) multimeter with all the ranges you'd ever want, PLUS much, much more: it checks transistor leakage and gain (NPN & PNP) PLUS diodes. PLUS has two capacitance ranges. What a beauty! Cat Q-1140


\$76⁵⁰

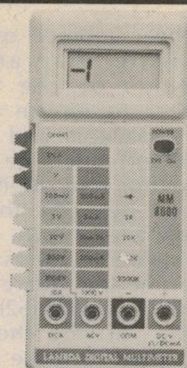

Want to go digital? Try this one!

Top value LCD digital has push button range selection, goes to 10A DC and has diode check facility too! And look at the low, low price! Cat Q-1444

VALUE AT JUST \$59⁵⁰

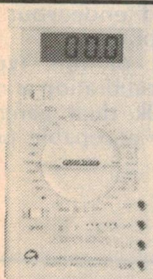

Check Capacitors Too!

Our most popular digital: and no wonder! 10 megohm input impedance, five ranges of capacitance, two ranges of conductance, diode check... PLUS all the usual multimeter functions (including 10A AC & DC!) with superb accuracy! A professional model at a hobbyists price! Cat Q-1460

WOW!!! ONLY \$99




The very latest... LCD multimeter AND transistor checker

What a multimeter! LCD display, up to 10A AC & DC, high input sensitivity... PLUS it checks transistors too! PLUS diodes. PLUS it has an audible continuity checker! What more could you want? Capacitance check! Yes, it's got that too (up to 20uF!). Cat Q-1500

\$149⁹⁵

Get yourself a CRO!

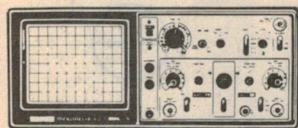

You'll never believe how much use a CRO can be until you own one. But don't go for a half baked five meg job: get the big gun: famous brand Hitachi goes to 20MHz, dual trace - and is small enough to go where you go.

● 20MHz bandwidth ● 5mV/div vertical ● Dual trace. Cat Q-1243

\$699

PROBES TO SUIT

Set x1/x10 probes with BNC sockets, multiple tips.




Cat Q-1245

\$29⁹⁵

BUILDING PROJECTS WITH METERS? Look at our great range of panel meters!

Standard range

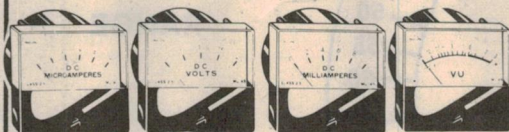Standard range includes typical useful scales, ideal for building into projects. Obviously, if we haven't the one you want, you can series or shunt them to virtually anything! Size 58 x 52mm, scale size 58 x 31mm.



0-1mA (200 ohms) Cat Q-2010
0-20V DC (1k ohms/V) Cat Q-2040
0-50uA (3500 ohms) Cat Q-2020
-20 to +3VU (1.228V/0dB) Cat Q-2050


ALL ONE LOW, LOW PRICE: \$9⁹⁵
(10 up only \$8.95 ea)

Large Panel Meters

Want even more? Check these out: 100 x 82mm overall, scale size 100 x 50mm.

0-1mA (200 ohms) Cat Q-2060

0-100uA (3500 ohms) Cat Q-2070

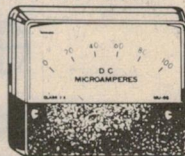

\$13²⁵
(10 up \$11.95)

Moving Iron Types

AC or DC - it's all the same to moving iron meters! Rugged, accurate - in two handy scales. Size approx 55mm wide, 58mm high.


0-10A (AC & DC) \$9⁵⁰ Cat Q-2090

0-20V (AC & DC) (10 up \$7.25 ea) Cat Q-2080

Level Meters


On the level, this lot. Choose the type you require - or add a series multiplier or parallel shunt to suit your particular circuit.

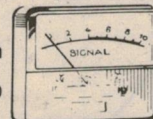Signal Strength 250uA FSD scale labelled 1-10 Cat Q-2100




\$5⁵⁵

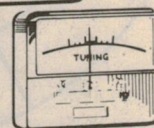Tuning Centre Zero Sensitivity is 250uA half FSD (in either direction). Cat Q-2095



\$5⁵⁵

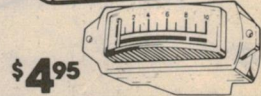Edge Level Meter Scale size 32 x 10mm, it's ideal for a fine level adjustment meter, audio or battery level, etc. Cat Q-2110



\$4⁹⁵

available in due course. The battery is clamped to one end of the case with a small piece of scrap aluminium, while the PCB is simply screwed to the bottom of the case using additional nuts as spacers.

Use the combined overlay diagram and wiring diagram to aid in placements of the components. Remember to ensure that the electrolytic capacitors and transistors are oriented correctly. The output coupling capacitor and attenuator resistors are wired between the front panel components as shown.

Use shielded cable as shown to connect the sine and square wave signals to the function switch (S2). The shield of the cable carrying the square wave signal is used to make the earth connection to the COM terminal. Remember to earth the front panel itself to this point also.

Use rainbow cable for the remaining connections to the front panel, and to the power input socket and the battery terminals. Keep these leads as far as possible away from the output terminals.

Once construction is complete, operation can be checked using some sort of audio level indicator. A CRO is ideal, with an audio millivoltmeter the next best thing. If necessary, an audio amplifier can be pressed into service, so that you can listen to the output.

Check operation over all frequencies, and in both sine and square wave positions. Do not forget to check for

If you make your own printed circuit boards, then this full sized reproduction can be used as a drawing guide.

correct operation using both the internal battery and the external plugpack.


Calibration of the completed unit is quite simple. If you have access to a frequency meter, simply set the dial at the correct point while the oscillator is producing about a 3kHz tone.

You can then check accuracy on the remaining ranges, padding the appropriate capacitors if necessary. The actual scale calibrations were deter-


mined experimentally, and were made using a potentiometer supplied by Dick Smith Electronics, marked "JP-7G" and "B10k". For maximum calibration accuracy, readers should endeavour to use the same type of pot.

On an instrument of this type, however, accuracy of calibration is not essential, and any 10k dual ganged linear pot should give acceptable performance.

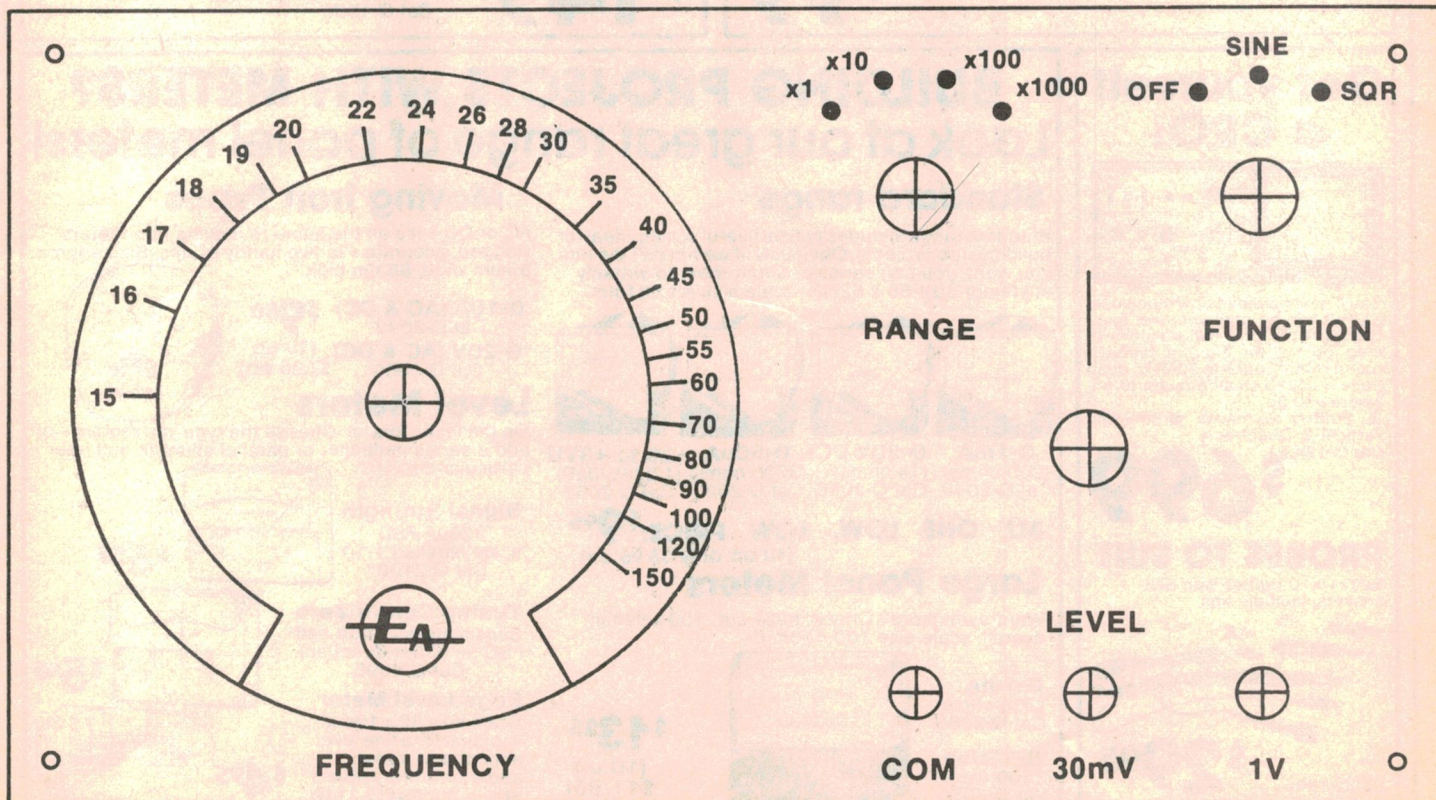This full sized reproduction of the front panel can be used directly, or copied.




Sine/square wave Oscillator

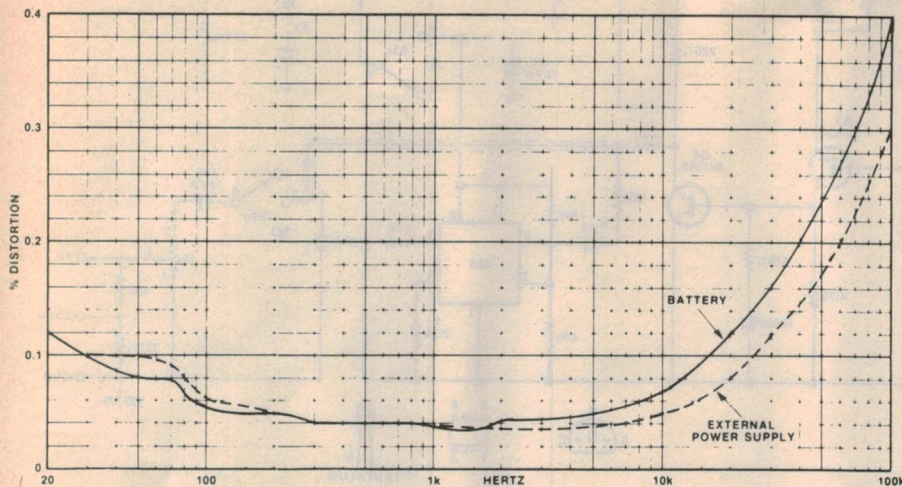

ABOVE: Graph showing how the distortion of the prototype varies with the oscillator frequency.

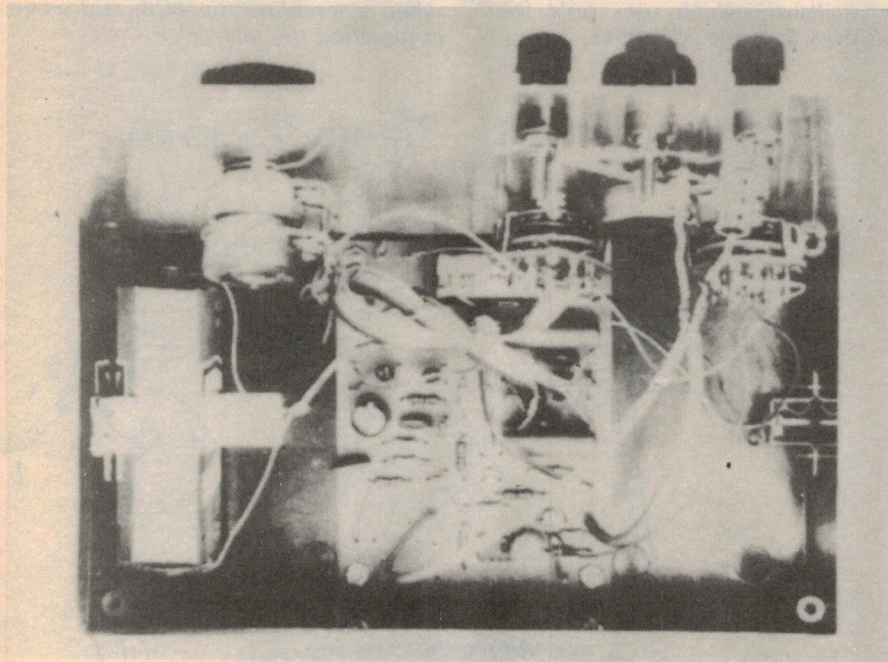BELOW: The internal layout of the prototype can be seen in this picture. Note the battery clamp.



ed, and two inputs are biased at approximately 1.5V by the 220k and 47k resistors. The 2.2k resistor connected to pin five is used to lower the input thresholds to 2V and 1V, so that an approximately even duty cycle square wave is obtained.

Switch S2a is used to select either the sine or square wave signal, with the latter being attenuated to a 1V RMS level by the 3.3k resistor in series with pin 3. A coupling capacitor is provided, with a 1k potentiometer used as an output level control. To facilitate the generation of millivolt-level signals, a fixed divider is provided across the output terminals, to give a nominal signal of 30 mV maximum.

Filtering of the supply line is provided

by a 1000uF capacitor. A 100uF capacitor is used to remove glitches from the supply line to the 555, and a 100 ohm resistor inserted in the negative lead of the plugpack input reduces the effects of mains ripple to insignificant levels.

Construction of the unit is quite simple, and should be within the capabilities of even inexperienced constructors. Most of the components are mounted on a single printed circuit board, measuring 101 x 76mm and coded 78a06.

Commence construction by fitting all the hardware to the case. The front panel of the prototype was made from photosensitive aluminium, but we hope that commercial panels will be

PARTS LIST

SEMICONDUCTORS

- 2 BC549 or similar NPN transistors
- 2 BC559 or similar PNP transistors
- 1 555 timer IC

CAPACITORS

- 1 1000uF 16VW axial lead electrolytic
- 5 100uF 16VW radial lead electrolytics
- 1 2.2uF tantalum
- 2 1uF polyester
- 2 0.1uF polyester
- 2 0.01uF polyester
- 2 0.001uF polyester
- 1 470pF polystyrene or ceramic
- 1 100pF polystyrene or ceramic

RESISTORS


- 1 x 220k, 1 x 47k, 1 x 18k, 1 x 15k, 2 x 10k, 1 x 4.7k, 1 x 3.3k, 1 x 2.2k, 2 x 1.8k, 3 x 1k, 2 x 470 ohm, 1 x 330 ohm, 2 x 220 ohm, 3 x 100 ohm, 1 x 33 ohm.
- 1 dual 10k linear potentiometer
- 1 1k linear potentiometer
- 1 RA 53 thermistor


MISCELLANEOUS

- 1 2 pole 4 position rotary switch
- 1 3 pole 3 position rotary switch
- 1 case, 197 x 60 x 112mm
- 4 knobs
- 3 terminals, 2 red, 1 black.
- 4 rubber feet
- 1 Eveready 2362 or similar battery and suitable connecting clips
- 1 front panel (see text)
- 1 A&R PS309 or similar 9V plugpack
- 1 2.1mm DC input jack socket and metric screws to suit
- 1 printed circuit board, coded 78a06, 101 x 76mm
- Rainbow cable, shielded cable, printed circuit board pins, machine screws and nuts, scrap aluminium, perspex, solder

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used provided they are physically compatible.

Fig. 1: This circuit shows the basic principles of the oscillator, whose frequency is determined by the RC network.

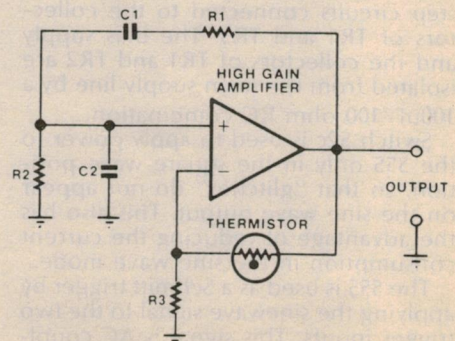

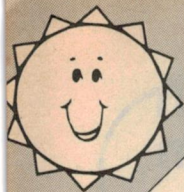

—It runs from a 9V supply! Wien bridge—

Sine and Square Wave Oscillator

This new audio oscillator is simple to construct, covers frequencies from 15Hz to 150kHz in four overlapping ranges, and runs from an external power supply or an inbuilt battery. In the important midband region, distortion of the prototype was less than 0.05 per cent. Both sine and square wave outputs are available.

by DAVID EDWARDS

One of the most useful pieces of equipment on an experimenter's bench, apart from the ubiquitous multimeter, is usually some form of audio oscillator. In the past, we have presented a number of designs for such instruments, including designs both simple and complicated.

The unit described in this article is fairly simple, but still designed for serious work. Performance wise, it is quite respectable, with a nominal maximum output of 1V variable down to zero with a potentiometer and a preset divider. It has quite low distortion figures. As you can see in the accompanying graph, between 20Hz and 20kHz distortion is less than 0.1 per cent, with a minimum distortion centred about 1kHz of about 0.04 per cent. Yet at the same time it is low in cost.

Only four low cost transistors are required for the basic oscillator, along with a thermistor (negative temperature coefficient resistor). A 555 timer is used as a Schmitt trigger to

provide a square wave output. The unit has been purposely designed to run from a 9V supply rail, allowing the use of a single 9V battery, or one of the now commonly available "plugpack" power supplies.

Use of a plugpack, rather than an in-built mains supply, is not only cheaper but avoids the problems of magnetic induction from the transformer field into sensitive portions of the circuit. In addition, a single plugpack can be used to power several units (not at the same time of course), leading to a further reduction in cost.

The new instrument has been designed as a companion for the RLC Bridge described in the March 1978 issue. As you can see in the photographs, the unit is mounted in a plastic "zipper" box, with a black front panel having white lettering.

Turning now to Fig. 1, we can discuss the operation of the basic Wien bridge oscillator circuit. A frequency selective network is used to apply positive feed-

back to a high gain amplifier. This network is formed by R1, C1, R2 and C2.

At a particular frequency, this network has a "pseudo-resonance", where a signal applied to R1 at the output of the amplifier is transmitted back to the amplifier input without any phaseshift, and with a minimum of attenuation. In fact, if R1 is made equal to R2, and if C1 is made equal to C2, this frequency is given by the reciprocal of $2\pi R_1 C_1$, and the feedback transmission loss falls to a minimum of 3.0.


For a feedback amplifier to produce sustained and steady oscillations, there must be positive feedback with zero phase shift at a particular frequency, while at the same time the overall loop gain must be unity. We can achieve these conditions in the present case by applying negative feedback to give the amplifier a gain of 3.0.

This is the purpose of the network formed by R3 and the thermistor. The thermistor serves a second purpose in this case though, and that is to stabilise the amplitude of the oscillations. If the thermistor was replaced by a fixed resistor equal in value to 2R3, the circuit would oscillate, but the oscillations would continue to increase in amplitude until clipping occurred.

This is obviously undesirable. The thermistor acts to prevent this however, because as the output signal rises the power dissipated in the thermistor increases, and its temperature increases. This causes the resistance of the thermistor to reduce, (it has a negative temperature coefficient), so that the amount of negative feedback is increased, and hence the gain is reduced.

The thermistor also ensures reliable starting of the oscillator, because when there is no oscillation, there is minimal power dissipation in the thermistor, so that the gain of the amplifier is quite high. As the signal level then increases, the thermistor acts to stabilise the amplitude. With the thermistor specified, and the value of R3 used, the

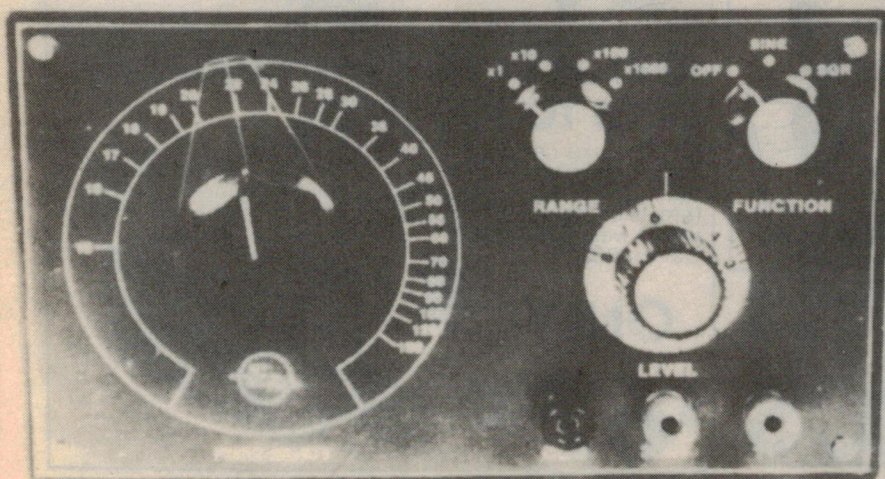Use this photograph of the completed unit as your guide in the choice of knobs. Make a pointer for the frequency dial with a piece of perspex or clear plastic.



Want to build a kit you can really get your teeth into? Try one of these value-packed kits from the Dick Smith Electronics range....


HOW ABOUT A LIGHTSHOW!!!

Build these two fantastic kits and turn your parties into a blast!

MUSICOLOR IV

Not just a colour organ - it's a chaser too! The very latest in sound triggered light - inbuilt microphone included -

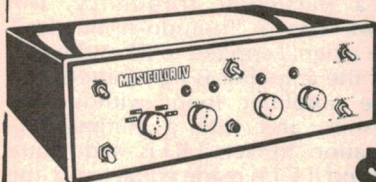PLUS you get the fantastic effects of automatic chaser patterns, reversals, the lot! Simple to use - save \$\$\$ on commercial units! Cat K-3143




\$109

OR A STROBE

A must for parties - and the perfect 'pigeon pair' for the Musicolor IV! Brilliant Xenon flash lamp controllable from one to twenty flashes per second: stops action, freezes figures!

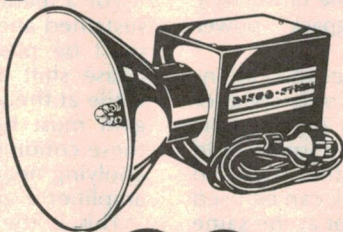And our strobe kit has been designed with safety in mind - perspex cover for flashtube, for example. And there is space on the PCB for a second tube circuit to be added for even greater light output! Cat. K-3152



\$39⁹⁵

SAVE ON MOTOR SPEED CONTROLLER


Get the most from your electric drill, saw, etc. Controls universal (brush-type) motors from near full speed down to virtually zero RPM, while maintaining torque.

Ideal for drilling sheet metal (or teeth) ... controlling food processors with limited speed (eg too fast and even faster!) ... electric saws ... and many other hand tools and appliances.

Uses opto-coupled triac trigger for isolation and safety. Cat K-3081

WAS \$22.50

NOW ONLY \$19⁵⁰

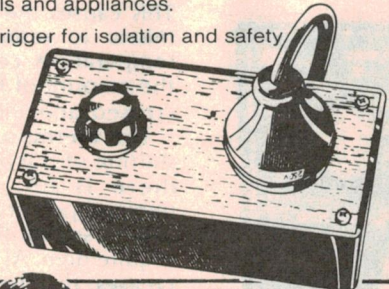

DICK SMITH ELECTRONICS




PTY LTD



TRANSISTOR ASSISTED IGNITION

Better performance ... lower running costs ... less tune-ups ... that's what thousands of people have found with transistor assisted ignitions. Our kit is easy to build, easy to fit (fits any conventionally carburetted, standard ignition (Kettering) vehicle - and that's about 90% of them!) Cat K-3301


ONLY \$37⁵⁰

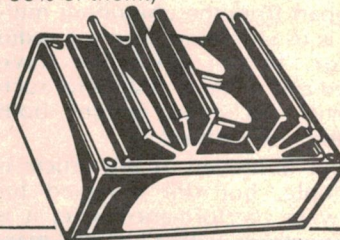

HOW ABOUT A LED TACHO FOR THE CAR?

Just like the General and Henry are fitting to their latest up-market models! Turn your down-market model into an up-market! LED tachometer shows engine speed at a glance: no meter lag, no working out figures. EASY! And it works with most cars (conventional ignition type). Cat K-3240


ONLY \$24⁵⁰

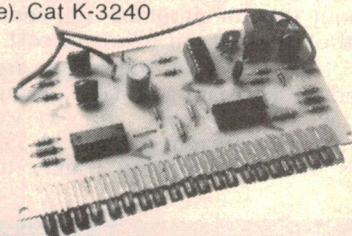

AND JUST IN CASE SOMEONE TRIES TO PINCH IT ...

Fit a deluxe car alarm. This kit from Electronics Australia magazine rates better than commercial alarms (according to the NRMA's specifications). It's almost impossible to beat (provision for inbuilt battery just in case they try!) - and it really works well. Cat K-3252

ONLY \$67⁵⁰

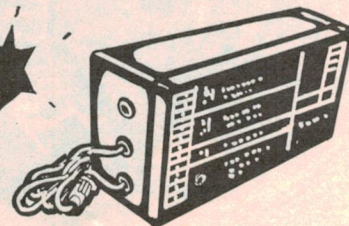

LOOKING FOR SOMETHING BIGGER AND BETTER?

DON'T RISK LOSING YOUR VCR!

Is your video next to go? Protect it with this superb alarm. Designed specifically to protect VCRs and other small appliances that might become hot property down at the pub! Pressure sensitive switches included. Cat K-3423



WAS \$54.95

ONLY **\$44⁹⁵**

WANT A SIREN?


Fantastic for everything from burglar alarms to playing cops and robbers! Ear-splitting sound with high efficiency piezo tweeter – yet draws very little current. PCB solders direct to tweeter. Cat K-3505



ONLY

\$19⁹⁵

WHAT A SUPPLY!

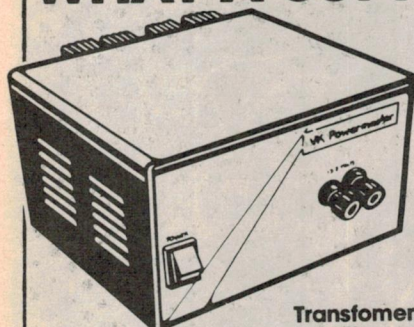

Capable of a massive 25A peak at 13.8V (depending on the transformer you choose) – the VK powermaster is the ideal bench supply for:

- High Power Transceivers
- Service Work
- Pool lights & pumps
- Etc Etc Etc

Basic kit (without transformer). Cat K-3448


Transformers to suit:

\$99

14A continuous (25A Pk) Cat M-2010 **\$49.95**
6A continuous (10A Pk) Cat M-2000 **\$24.95**

NOVELTY MUSIC GENERATOR

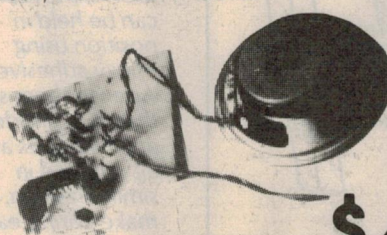Here's a great one for the kids! Neat little kit plays Greensleeves and Home on the Range – or gives a 'Ding Dong'. Make into a beaut doorbell – or put inside a toy. It's great, mate! Cat K-3512



ONLY

\$12⁹⁰

BUILD AN AMATEUR TRANSCEIVER

AT LAST! You can build an amateur transceiver AND save money over the commercial units AND have equal performance to the commercial units!

YES – the days of home brew are back: many hundreds of these kits have now been built and everyone has said 'Isn't it great to build something again!'

But it's even better when you can build it yourself and save!

UHF (70cm) Transceiver Kit Cat K-6300 **NOW INCLUDES REPEATER UPGRADE KIT – VALUE \$24.50 – FREE!**

ONLY \$199

VHF (2m) Transceiver Kit Cat K-6308 **Was fantastic value at**

\$199.00 ... THIS MONTH ONLY \$179

POWER SUPPLY TO SUIT. Built in same case – really looks the part. Cat K-6310

ONLY \$49⁵⁰




need for a separate flasher circuit.

Transistors Q1, Q2 and Q4 form a solid state on/off switch, and save money by eliminating the need for a conventional mechanical switch. The way in which this part of the circuit operates is quite simple: When the CLIMB button is initially pressed (ie circuit off), the voltage on the 470uF capacitor rises and turns on Q1 and Q2. These two transistors then provide forward bias to Q4, which turns on and supplies power to the UAA170 IC.

The game is turned off by deliberately pressing the CLIMB button while the LED display is off. This discharges the 470uF capacitor into the output of the CMOS oscillator cutting off forward bias to Q1 and Q2 and turning off Q4 to remove power from the UAA170. It will usually be necessary to press the CLIMB button two or three times in order to discharge the capacitor sufficiently for the game to turn off.

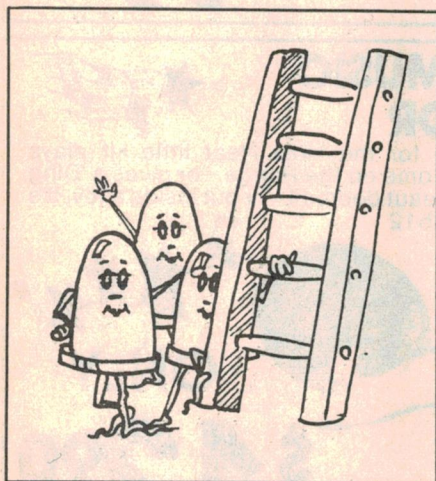Note that power is removed only from the UAA170 and the LED display. The 4011 IC is left permanently powered,



while the voltage divider networks on pins 12 and 13 of the UAA170 also draw current on a continuous basis. Even so, total current consumption in the off-state can be considered negligible and will have little effect on battery life.

We used eight 1.5V penlight cells to power the circuit, giving a nominal 12V supply. The batteries are mounted in an eight-way battery holder, as shown in one of the photographs. Average current drain of the circuit in the "on" state is about 28mA, giving an estimated battery life of 40 hours.

CONSTRUCTION

Construction of the game is quite simple, as all the major components, except the LEDs and the CLIMB switch, are mounted on a small PC board measuring 81 x 76mm and coded 80LL7.

Commence construction by wiring the PC board according to the circuit and component overlay diagrams. Fit the passive components (resistors and

capacitors) first, followed by the transistors and the UAA170 IC. Make sure that all polarised components are correctly oriented, and don't forget the six wire links.

The 4011 IC is a CMOS device and should be left till last. Take the usual precautions when soldering CMOS devices. Connect the soldering iron barrel to the earth track on the PC board, using a clip lead, and solder the supply pins (pins 7 & 14) first. These measures will prevent damage to the IC by static charges.

We mounted the game in a plastic utility box measuring 150 x 90 x 50mm and fitted with an aluminium lid. The box is used upside down, with a Scotchcal adhesive label glued to the plastic base to provide an attractive front panel.


Use either the Scotchcal panel or the actual size artwork reproduced with this article as a drilling template for the 16 LEDs. The LEDs are then pushed into the mounting holes and glued at the rear with epoxy adhesive. Arrange them so

that the anodes and cathodes are all oriented in similar fashion, to make wiring easier.


The wiring from the PCB to the LEDs and the switch is best done with rainbow cable, as this makes for easy identification of the different leads. Complete the interconnections between the LEDs first, using the circuit diagram as a guide, and then connect them to the PCB. The completed circuit board is fastened to the lid of the box using machine screws and nuts, together with the battery holder which is held in place by an aluminium clamp.

We attached four rubber feet to the bottom of the case to prevent scratches to table tops etc. Stick-on rubber feet are available from Dick Smith Electronics.

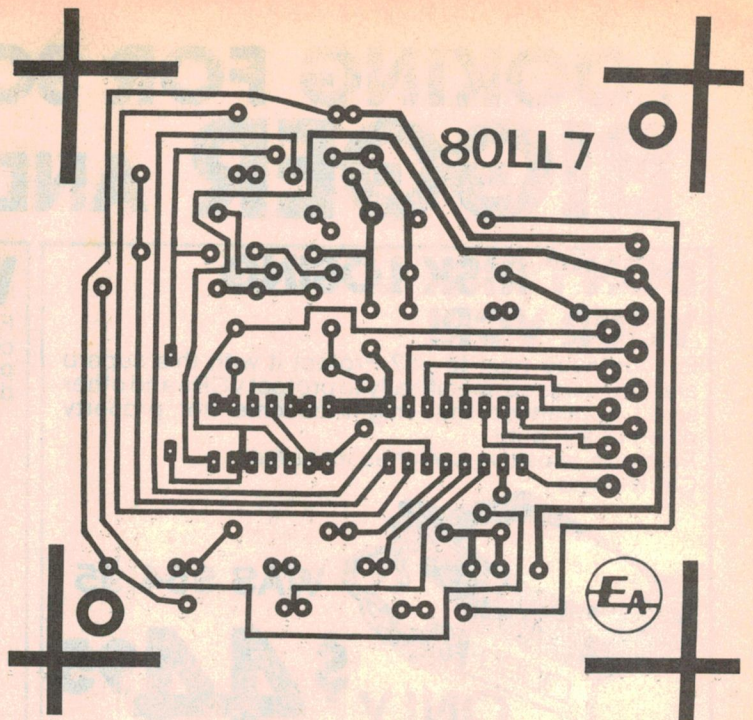Construction is then complete, and you can attempt to climb the ladder. If the LEDs do not come on in order, it is likely that the connections to them are in error. Any LEDs failing to emit will probably have anode and cathode transposed.



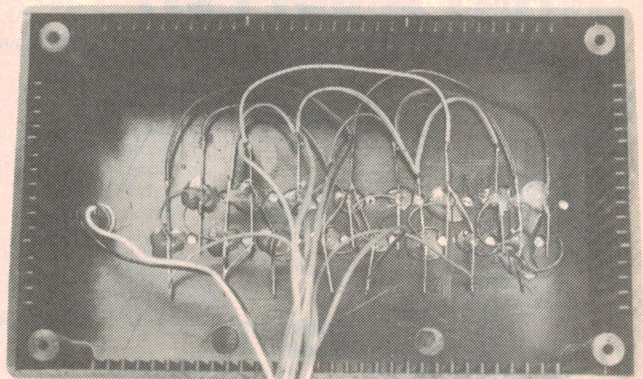ABOVE: actual size reproduction of the PC pattern.



RIGHT: the LEDs can be held in position using epoxy adhesive. Arrange them so that their anodes and cathodes are all oriented in similar fashion, to make wiring easier.

WHY DID WE CALL IT THE Z SERIES?

Because nothing can follow it.

The TEAC Z Series. Three cassette decks that are all the cassette deck anyone will ever need. Designed and built to provide absolutely the finest in cassette reproduction quality. In precision of performance. And in operational versatility. The transport and electronics are the pinnacle of TEAC technology, drawing on our know-how in producing superior open reel decks and professional equipment. Operational sophistication is unmatched. Any function worth having on a cassette deck is on the Z-7000. And the Z-6000 and Z-5000 are almost as impressive. In fact, you can tell just by looking that these decks are in a class by themselves. Bigger. Heavier. Without extraneous frills. Built for solid, stable, permanent excellence. The Z Series. Cassette deck performance from A to Z.

- Direct-drive capstan motor
- 3-head system
- dbx and Dolby B-C noise reduction
- Manual recording bias, level and EQ calibration system
- Heavy duty diecast chassis
- Electroload head loading system

- 3 direct-drive DC motors
- Direct-coupled playback EQ amplifier
- 3-head system
- dbx and Dolby B-C noise reduction
- dbx disc position
- Manual recording bias, level and EQ calibration system

- 3 direct-drive DC motors
- 3-head system
- dbx and Dolby B-C noise reduction
- dbx disc position
- Automatic recording bias, level and EQ calibration system
- Tape calibration memory
- Block Repeat

- Direct-coupled playback EQ amplifier
- Real-time tape counter
- Memory repeat/play/stop
- CPS (Computomatic Program Search)
- Rec mute with auto spacer
- Standard remote control unit

- Dual-capstan closed-loop transport system
- Real time tape counter
- Automatic tape select
- 30-segment FL peak level meters
- Memory repeat/play/stop
- CPS (Computomatic Program Search)

- Dual-capstan closed-loop transport system
- Real-time tape counter
- Automatic tape select
- Search To Cue, Search To Zero, Search To Record
- Spot Erase System
- CPS (Computomatic Program Search)



Z-5000



Z-6000




Z-7000

TEAC®

Where Art and Technology Meet

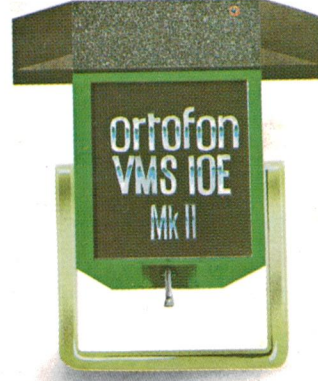TEAC Australia Pty., Ltd.: 115 Whiteman Street South Melbourne, Victoria 3205 Phone: 699-6000



Sound facts in detail.

Ortofon have always dedicated themselves to pursuing the world's finest sound reproduction.

So when they discovered that the existing moving magnetic systems missed much of the sound detail, they did something about it.

They designed, developed and patented a new cartridge principle that could pick up as much detail as possible, accurately, from the record groove.


(Of course, as one of the recognized world leaders in sound reproduction, Ortofon were well-qualified in this area.)

They called it the VMS Principle.


The VMS Principle (Variable Magnetic Shunt) utilizes a light tubular armature of magnetic conducting material.

This is attached to the cantilever and encircled by a powerful ring magnet. When the cantilever moves the armature closer to the ring magnet, the armature short-circuits part of the magnetic field, generating a voltage in the coils.

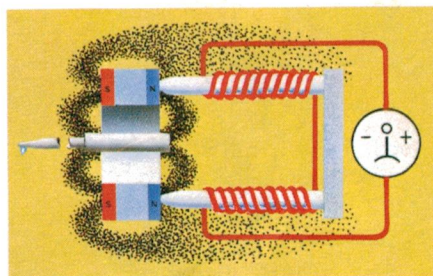
And the result is an increased high frequency tracking ability, low distortion and superb



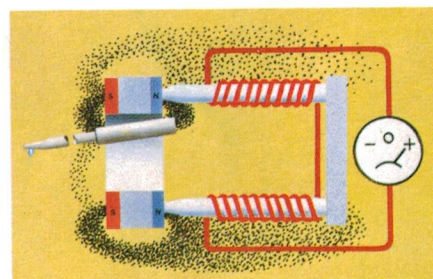Symmetrical flux fields with the armature in the central (neutral) position. These flux fields emanate from the magnet positioned in front of the pole pins. As the fields are in balance, there are no changes in flux around and inside the coils. Therefore, no voltage is generated.



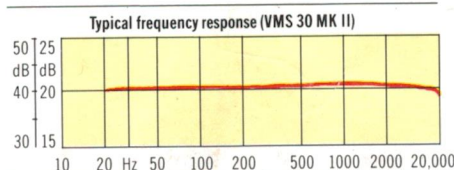When the cantilever moves, the armature is brought closer to the ring magnet and acts as a shunt, short-circuiting part of the magnetic field. As a result, the flux field in front of the pole pins varies, and a voltage is generated in the coils.



Technical data		VMS 30 MK II
Weight	5 g
Type of stylus	Fine Line
Equivalent stylus tip mass	0.45 mg
Frequency response	20-20,000 Hz
Output voltage at 1000 Hz per 5 cm/sec.	5 mV
Channel separation at 1000 Hz	27 dB
Channel balance at 1000 Hz	2 dB
Compliance static, vertical	28 µm/mN
Compliance dynamic, lateral (10 Hz)	22 µm/mN
Recommended tracking force	13 mN (1.3 g)
Tracking force range	10-16 mN (1.0-1.6 g)
Tracking ability at 315 Hz lateral	90 µm
Vertical tracking angle	20°
FIM distortion	1% (13 mN)
DC resistance	800 ohm
Inductance	600 mH
Recommended load resistance	47 kohm
Recommended load capacitance	400 pF

transient reproduction – right down to the very last detail.

As if that wasn't enough, the VMS also reduced sensitivity to hum pick-up and minimized distortion and non-linearity in the magnetic system.

Presumably, the cost of an Ortofon VMS Magnetic Cartridge would be high.

Surprisingly, it's not. In fact, it's especially affordable.

Check the facts on the VMS 10E MK II, 20E MK II and 30 MK II at your hi-fi or Ortofon dealer.

And while you're there, find out how to home-test your stereo equipment with the Ortofon Pick-up Test Record.

It's another sound fact in detail.

Distributed by Vanfi (Aust.) Pty. Ltd.
Melbourne: 297 City Road, South Melbourne, Vic. 3205.
Tel. 690 6200.

Sydney: 283 Alfred Street, North Sydney, N.S.W. 2060.
Tel. 929 0293.

ortofon
accuracy in sound